

# Announcements

①

Syllabus : chapters 10, 11, 12 + 16 — ①


② Tuesday 4:30 pm - 6:30 pm make up Quiz 1 + 2

③ Tentative Tuesday 11:00<sup>am</sup> - 12:30 pm

④ cheat sheet <sup>handwritten</sup> 2 A4 pages / calculator
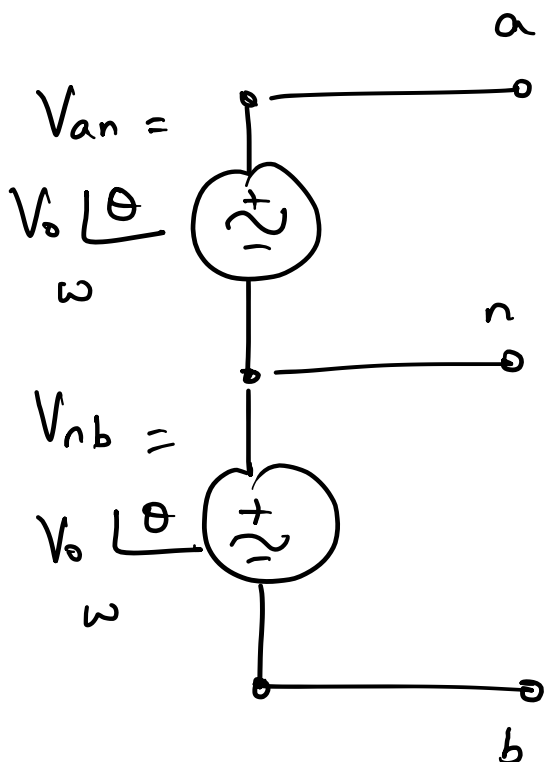
## Review

Single Phase Differential / Two phase /  
Single Phase Three wire



$$v_{an} = V_0 \cos(\omega t + \theta)$$


$$v_{bn} = V_0 \cos(\omega t + \theta - 180^\circ)$$

Balanced  
power  
supply

$$V_{bn} = -V_{nb} = V_0 \angle \theta - 180^\circ$$

$$V_{an} + V_{bn} = 0$$

(2)

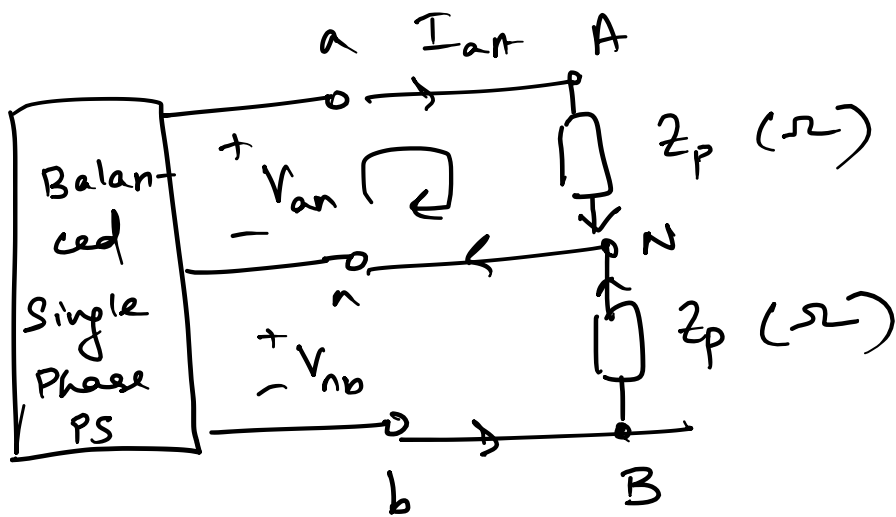


When you have balanced supply  $\equiv$  balanced load

$$P_{Nn} = 0 \text{ A}$$

$$|I_{aA}| = |I_{bB}|$$

(3)

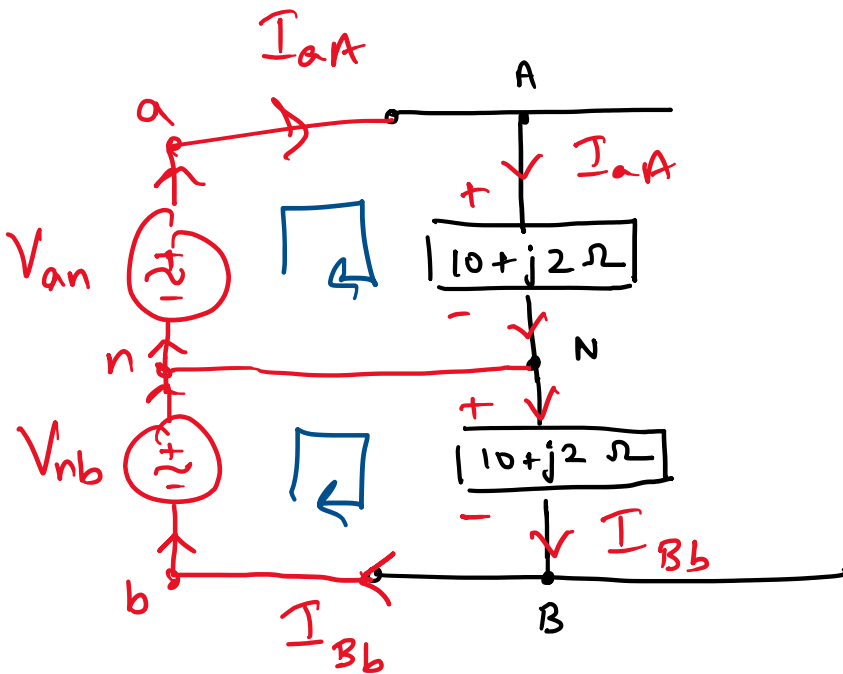4. Consider the balanced load represented in the figure, if it is connected to a three-wire balanced source operating at 50 Hz such that  $V_{an} = 115$  V, (a) Determine the power factor of the load if the capacitor is omitted; (b) Determine the value of capacitance  $C$  that will achieve a unity power factor for the total load.



$$\omega = 2\pi f = 2 \times \pi \times 50 = 100\pi \text{ rad/s}$$

$$V_{an} = 115 \angle \theta, \quad V_{nb} = 115 \angle \theta$$

$$+V_{an} - I_{aA} \times (10 + j2) = 0$$


$$I_{aA} = \frac{V_{an}}{10 + j2} = \frac{115 \angle \theta}{\sqrt{104} \angle 11.3^\circ}$$

$$\therefore I_{aA} = 11.27 \angle \theta - 11.3^\circ \text{ A}$$

$$pf = \cos(11.3^\circ) \quad \text{lagging}$$

(b)

④

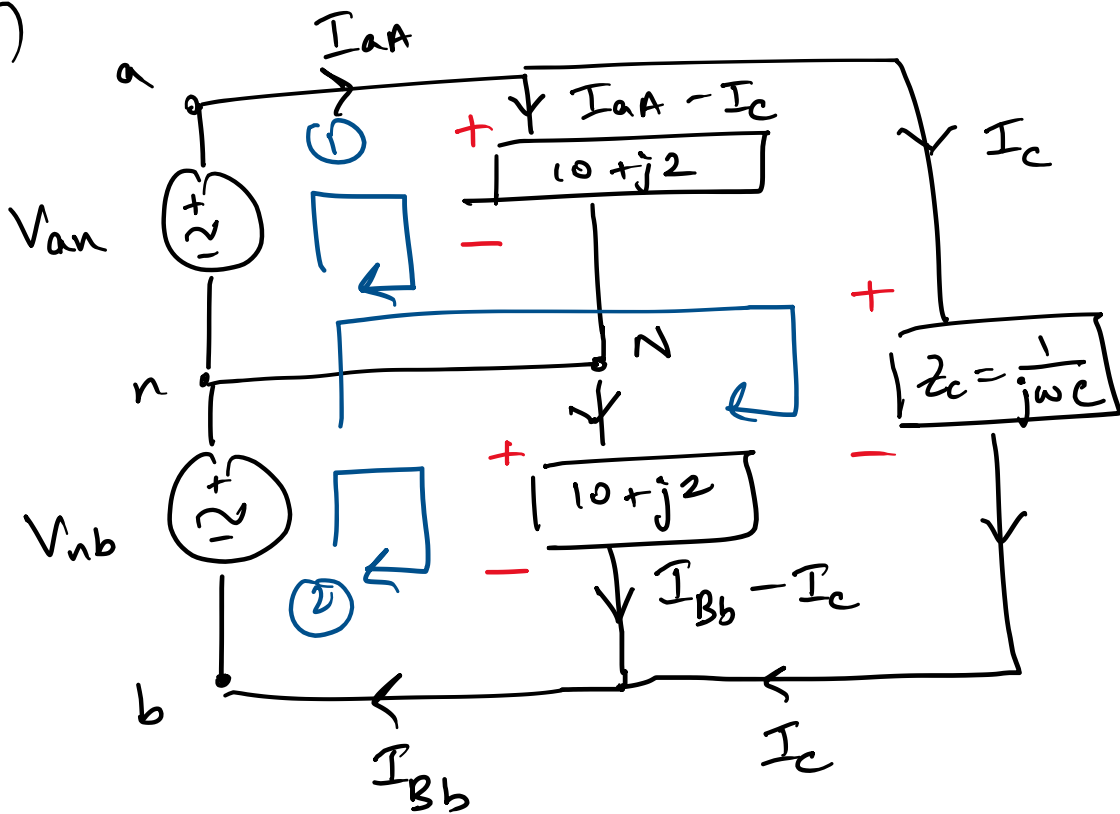Loop 1

$$+V_{an} - (I_{aA} - I_c) \times Z_p = 0$$

$$I_{aA} - I_c = \frac{V_{an}}{Z_p}$$

— ①

Loop 2

$$+V_{nb} - (I_{Bb} - I_c) \times Z_p = 0$$

$$I_{Bb} - I_c = \frac{V_{nb}}{Z_p}$$

— ②

Loop 3

$$V_{an} + V_{nb} = I_c \times Z_c$$

$$\Rightarrow I_c = \frac{V_{ab}}{Z_c}$$

— ③

(5)

$$Pf = 1 = \cos(\theta - \phi) =$$

$$\phi = \theta$$

$$Pf = 1 = \frac{\operatorname{Re}\{S\}}{\|S\|} \rightarrow \text{when } \operatorname{Im}\{S\} = 0$$

$S$  = complex power of load

$$= \frac{1}{2} \times V_{an} (I_{aA} - I_c)^* + \frac{1}{2} V_{nb} (I_{Bb} - I_c)^* + \frac{1}{2} V_{ab} (I_c)^*$$

$$= \frac{1}{2} V_{an} \times \left( \frac{V_{an}}{z_p} \right)^* + \frac{1}{2} V_{nb} \times \left( \frac{V_{nb}}{z_p} \right)^* + \frac{1}{2} V_{ab} \times \left( \frac{V_{ab}}{z_c} \right)^*$$

↑  
loop 1
↑  
loop 2
↑  
loop 3

$$= \frac{1}{2} \frac{|V_{an}|^2}{z_p^*} + \frac{1}{2} \frac{|V_{nb}|^2}{z_p^*} + \frac{1}{2} \frac{|V_{ab}|^2}{z_c^*}$$

$$= \frac{|V_{an}|^2}{z_p^*} \times \frac{z_p}{z_p} + \frac{1}{2} \frac{|V_{ab}|^2}{z_c^*} \times \frac{z_c}{z_c}$$

$$= \frac{|V_{an}|^2}{|z_p|^2} \times z_p + \frac{1}{2} \frac{|V_{ab}|^2}{|z_c|^2} \times z_c \quad (6)$$

$$= \frac{(115)^2}{104} \times (10 + j2) + \frac{1}{2} \times \frac{(230)^2}{\left(\frac{1}{\omega^2 C^2}\right)} \times \frac{1}{j\omega C}$$

$$= \frac{(115)^2}{104} (10 + j2) + \frac{1}{2} \times \frac{(230)^2}{\omega^2 C^2} \times -j\omega C$$

$$\text{Im}\{S\} = 0$$



$$\frac{115^2}{104} \times j2 + j\omega C \times \frac{1}{2} \times (230)^2 = 0$$

$$\Rightarrow \frac{\omega C}{2} \times (230)^2 = \frac{2 \times (115)^2}{104}$$

$$\Rightarrow C = \frac{2 \times 2 \times (115)^2}{\omega \times (230)^2 \times 104} = 30 \mu\text{F}$$

# Three Phase Power Supply

(7)

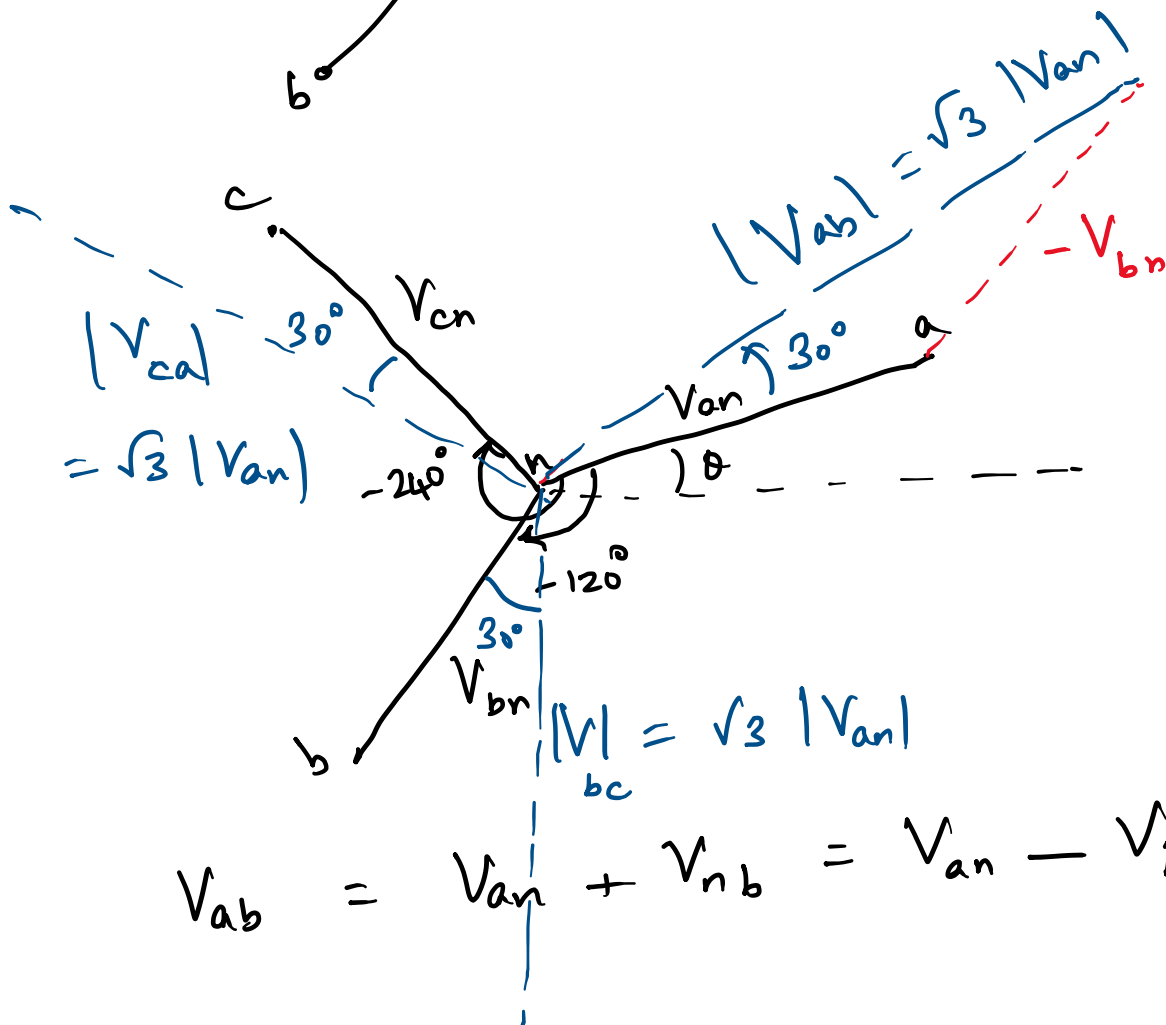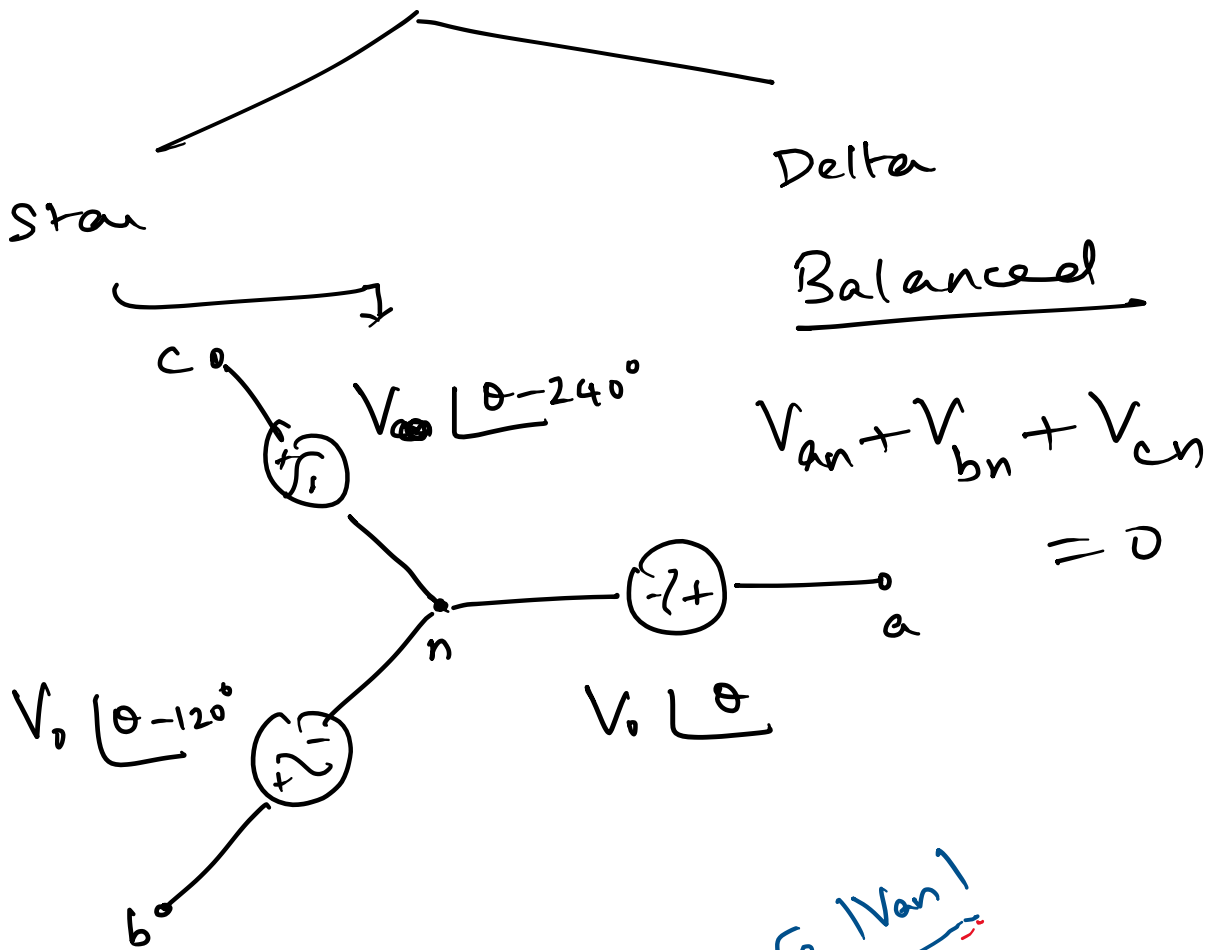

$$\rightarrow f = 50 \text{ Hz}$$

$$V_{an} = 230 \text{ V} \angle 30^\circ \text{ rms}$$

⑧  
} Balanced  
} 3 phase  
} supply

phase voltages in time domain  
line voltages in time domain

Ans.

$$\omega = 2\pi f = 100\pi \text{ rad/s}$$

$$\begin{aligned} V_{an}(t) &= 230\sqrt{2} \cos(100\pi t + 30^\circ) \text{ V} \\ V_{bn}(t) &= 230\sqrt{2} \cos(100\pi t - 90^\circ) \text{ V} \\ V_{cn}(t) &= 230\sqrt{2} \cos(100\pi t - 210^\circ) \text{ V} \end{aligned}$$

} phase voltages

$$\begin{aligned} V_{ab} &= \sqrt{3} |V_{an}| \angle \theta + 30^\circ \\ &= \sqrt{3} \times 230 \times \sqrt{2} \angle 30^\circ + 30^\circ \end{aligned}$$



$$\begin{aligned} V_{ab}(t) &= 230\sqrt{6} \cos(100\pi t + 60^\circ) \text{ V} \\ V_{bc}(t) &= 230\sqrt{6} \cos(100\pi t - 60^\circ) \text{ V} \\ V_{ca}(t) &= 230\sqrt{6} \cos(100\pi t - 180^\circ) \text{ V} \end{aligned}$$

} line voltages




# Three Phase Load

9

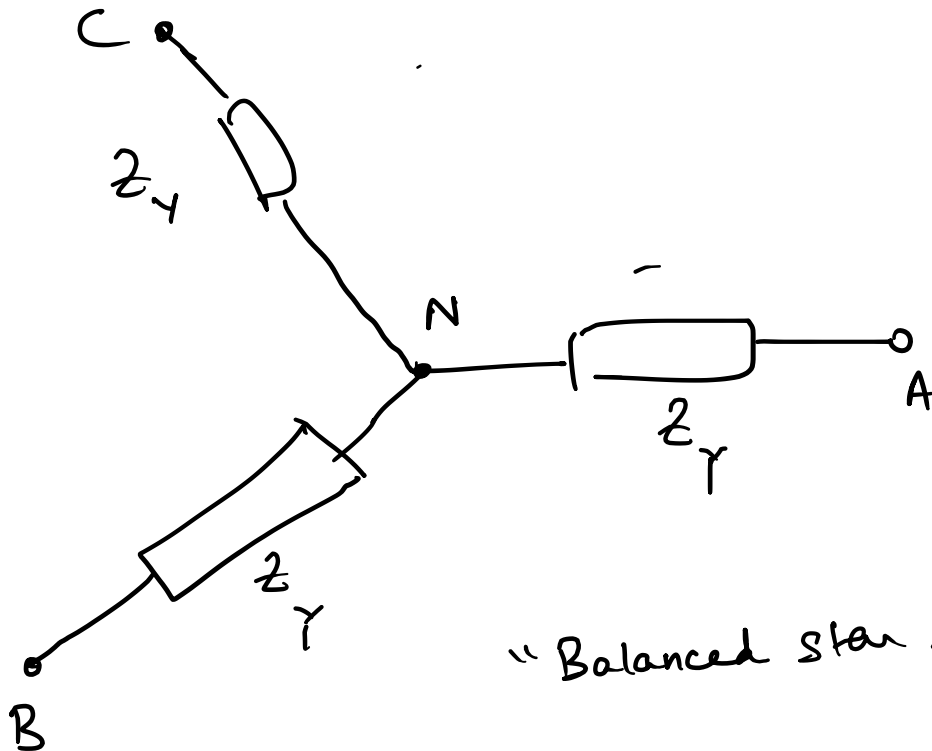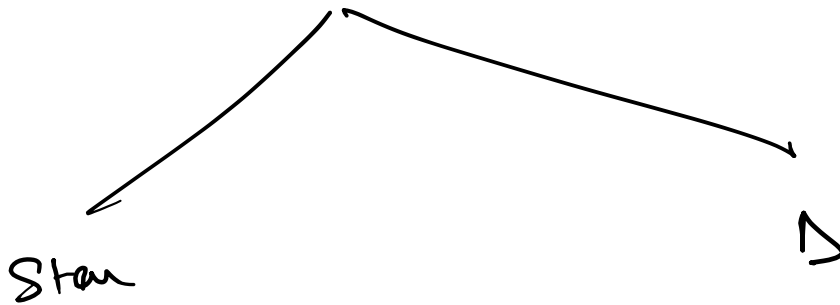

"Balanced star load"

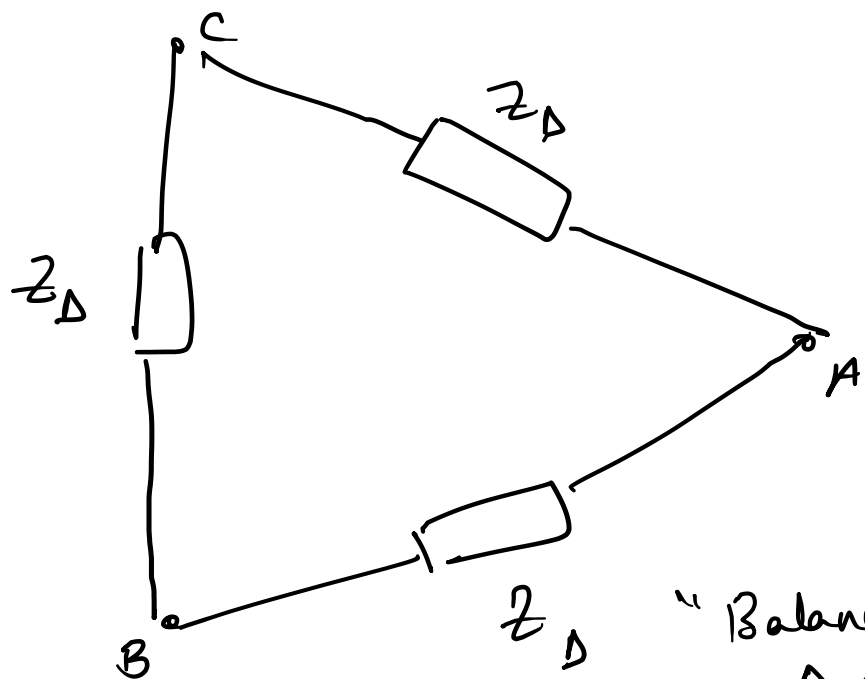

"Balanced  $\Delta$  load"