

Tutorial 2

Q Calculate the average power delivered by current $4 - j2$ A

$$Z = \frac{1.5 \angle -19^\circ}{2 + j} \text{ k}\Omega$$

solⁿ

$$Z = \frac{1.5 \angle -19^\circ}{(2 + j)} \rightarrow \text{convert to polar form}$$

$$Z = \frac{1.5 \angle -19^\circ}{2.24 \angle 26.57^\circ} = 0.66 \angle -45.57^\circ \text{ k}\Omega$$

$$V = Z \cdot I$$
$$= 669.66 \angle -45.57^\circ \cdot (4 - j2)$$

~~$= 669.66 \angle -45.57^\circ \cdot 4.47 \angle -26.57^\circ$~~

$$= 2993.3 \angle -72.14^\circ \text{ V}$$

$$V = 2993.3 \angle -72.14^\circ \text{ V}$$


$$\langle P_{avg} \rangle = \frac{V_o I_o}{2} \cos(\theta - \phi) \text{ Watts}$$

$$= \frac{2993.3 \times 4.47}{2} \cos(-72.14 - (-26.57))$$

$$= 6690 \cos(-45.57^\circ)$$

$$= 4.68 \text{ kW}$$

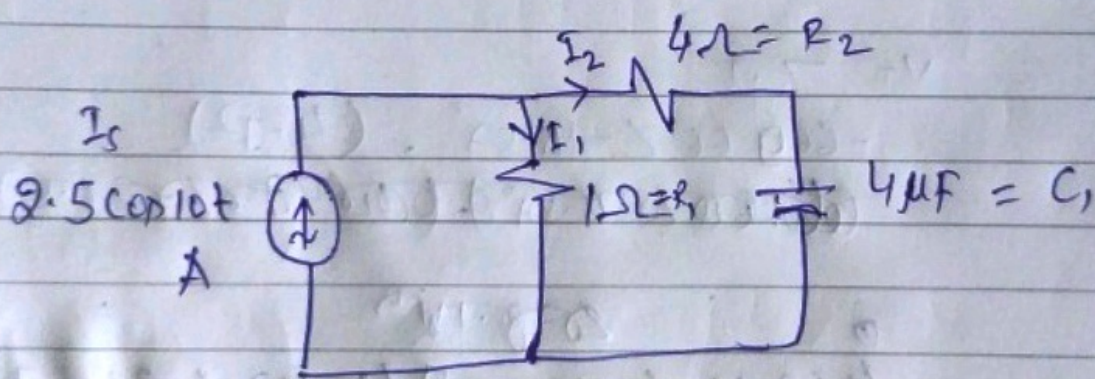Q Assuming no transients are present, calculate the power absorbed by each element at $t = 0, 10, \text{ and } 20 \text{ ms}$



Solⁿ obtain frequency equivalent circuit

$$I_s = 2.5 \angle 0^\circ \text{ A}; R_1 = 1 \Omega; C_1 = \frac{1}{j(10)(4 \times 10^{-6})} = -j25 \text{ k}\Omega$$

$$\omega = 10 \text{ rad/sec} \quad R_2 = 4 \Omega$$

$$\begin{aligned}
 \underline{I}_1 &= \frac{1}{R_2 + j\omega C_1} \cdot \underline{I}_S \\
 &= \frac{4 + \frac{1}{j \times 10 \times 4 \times 10^{-6}}}{1 + 4 + \frac{1}{j \times 10 \times 4 \times 10^{-6}}} \cdot 2.5 \angle 0^\circ \\
 &= \frac{25.02 \angle -90^\circ}{25.02 \angle -89.98^\circ} \cdot (2.5 \angle 0^\circ)
 \end{aligned}$$

$$\underline{I}_1 \approx 2.5 \angle 0^\circ \text{ A}$$

$$\underline{I}_{4\Omega} \approx 0 \text{ A}$$

$$\begin{aligned}
 P_{R_1}(t) &= \cancel{I_1^2(t)} \cdot R_1, W_{\text{eff}} = (2.5 \cos 10(t))^2 \cdot 1 \\
 &= 6.25 \cos^2 10(t) \\
 &= 6.25 \frac{(1 + \cos 20(t))}{2} \\
 &= 3.125 (1 + \cos 20(t))
 \end{aligned}$$

$$\text{at } t=0 \Rightarrow 6.25 \text{ W}$$

$$\text{at } t \Rightarrow 10 \Rightarrow 3.125 (1 + \cos(20 \times 10 \times 10^{-3} \times \frac{180^\circ}{\pi})) = 6.19 \text{ W}$$

$$t = 20 \text{ ms} = 6 \text{ W}$$

$$\# P_{R_2}(t) \approx 0 \text{ for all } t$$

$$P_{C_1}(t) \approx 0 \text{ for all } t$$

Across Current Source :-

at $t = 0$

$$P_s(t) \Rightarrow - \frac{(2.5 \angle 0^\circ)}{i(t)} \times \frac{2.5 \angle 0^\circ}{V_s(t) = i(t) \cdot R_1}$$

or

$$\Rightarrow - 6.25 \text{ W}$$

Negative sign: Because the source delivers the power and thus:-

power consumed = - power delivered.

at $t = 10 \text{ msec}$


$$P_s(10 \text{ ms}) = - 6.19 \text{ W}$$

at $t = 20 \text{ ms}$

$$P_s(20 \text{ ms}) = - 6 \text{ W}$$


Q Determine the individual contribution of each source to the voltage $v_1(t)$

Repeat $\omega = 30 \text{ rad/sec}$

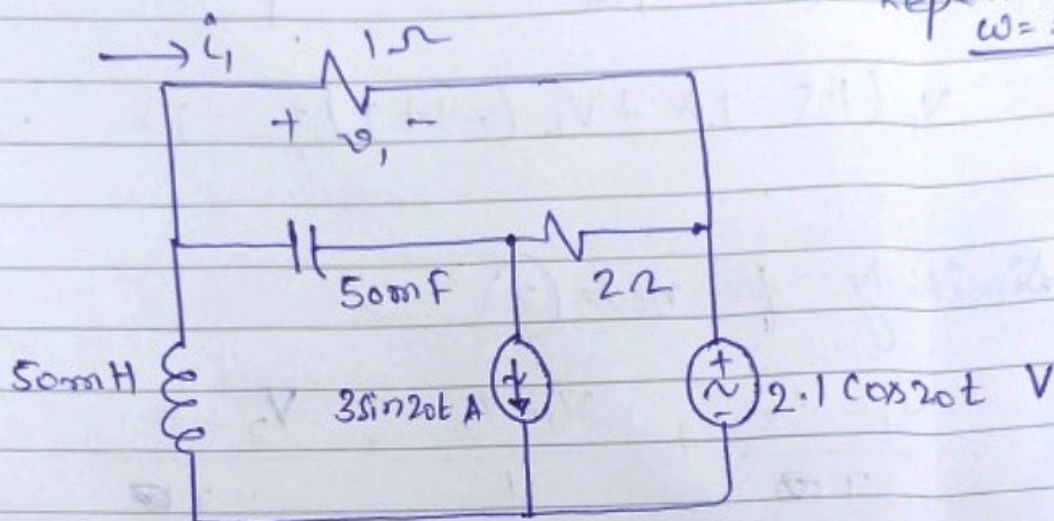

Solⁿ: Let consider current source only and draw equivalent frequency domain

$\omega = 20 \text{ rad/sec}$

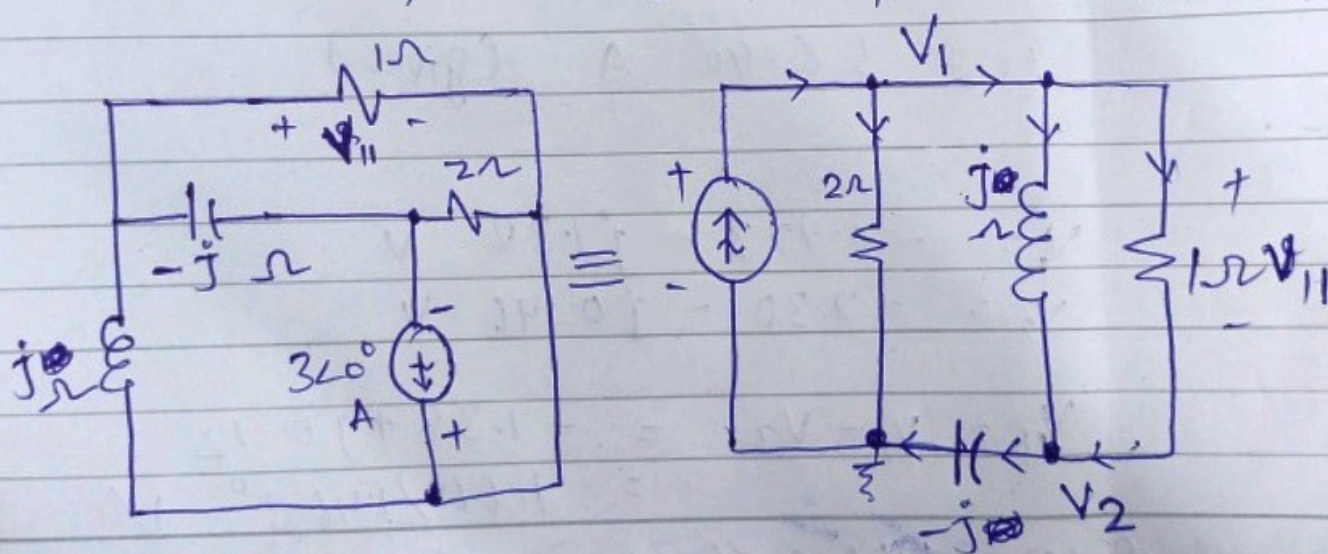

at Node (1)

$$I_s = \frac{V_1}{2} + \frac{V_1 - V_2}{j} + \frac{V_1 - V_2}{1}$$

$$V_1 (1.5 - j) + V_2 (-1 + j) = -j3 \quad \text{--- (1)}$$

Similarly for node (2)

$$\frac{V_1 - V_2}{j} + \frac{V_1 - V_2}{1} = \frac{V_2 - 0}{-j}$$

$$V_1 (-j + 1) + V_2 (+j - 1 - j) = 0$$

$$V_1 (1 - j) - V_2 = 0 \quad \text{--- (2)}$$

$$I_s = 3 \angle -90^\circ \text{ A (given)}$$


$$V_1 = -0.923 - j1.38 \text{ V}$$

$$V_2 = -2.30 - j0.46 \text{ V}$$

$$\begin{aligned} V_{11} = V_1 - V_2 &= -1.38 + j0.92 \\ &= 1.66 \angle 146.3^\circ \text{ V} \end{aligned}$$

$$v_{11}(t) = 1.66 \cos(20t + 146.3^\circ) \text{ V}$$

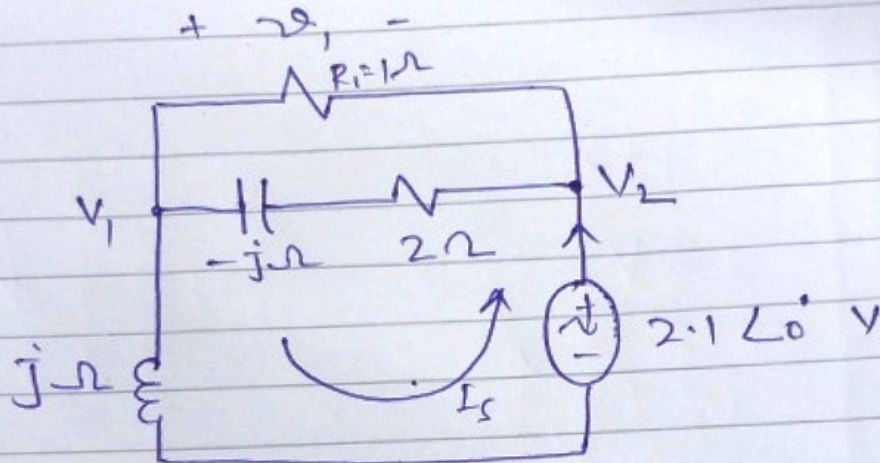Now let us consider voltage source only :-



$$I_s = \frac{V_s}{Z} = \frac{2.1}{\frac{2-j}{3-j} + j} = 1.13 - j1.45 \text{ A}$$

$$= 1.84 \angle -52.07^\circ \text{ A}$$

$$V_1 = I_s \cdot j \Rightarrow (1.84 \angle -52.07^\circ) \cdot (1 \angle 90^\circ)$$

$$V_1 = 1.84 \angle 37.93^\circ \text{ Volt}$$

$$V_2 = V_1 - V_s$$

$$= 1.84 \angle 37.93^\circ - 2.1 \angle 0^\circ$$

$$= 1.3 \angle 119.8^\circ \text{ V}$$