

Lecture - 3
Chapter 16 from Text book

①

Frequency Response

→ Laplace variable $s = j\omega$ (Note)



~~$s = j\omega$~~



$s = j\omega$

→ Transfer function = $\frac{\text{Output response}}{\text{Input response}} = H(s)$

case 1:

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} \quad (V/V)$$

case 2:

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} \quad (\Omega)$$

case 3

$$H(s) = \frac{I_{out}(s)}{V_{in}(s)} \quad (\Omega^{-1})$$

case 4

$$H(s) = \frac{I_{out}(s)}{I_{in}(s)} \quad (A/A)$$

linear scale

$$[H(s)]$$

2

$$1. [H(s)] = 20 \log_{10} \left| \frac{V_{out}(s)}{V_{in}(s)} \right| \quad \text{dB}$$

$$2. [H(s)] = 20 \log_{10} \left| \frac{V_{out}(s)}{I_{in}(s)} \right| \quad \text{dB}\Omega$$

$$3. [H(s)] = 20 \log_{10} \left| \frac{I_{out}(s)}{I_{in}(s)} \right| \quad \text{dB}$$

$$4. [H(s)] = 20 \log_{10} \left| \frac{I_{out}(s)}{V_{in}(s)} \right| \quad \text{dB}\Omega^{-1}$$

$$\rightarrow H(s) = 3 + j4 \rightarrow [H(s)] \quad \text{dB}$$

$$H(s) = 25 + j100 \rightarrow [H(s)]$$


$$|H(s)| = \sqrt{3^2 + 4^2} = 5$$

$$\log_{10} 5 = 0.69$$

$$20 \log_{10} 5 = 20 \times 0.69 = 13.8 \text{ dB}$$

→ Find the transfer function of the following ckt

3

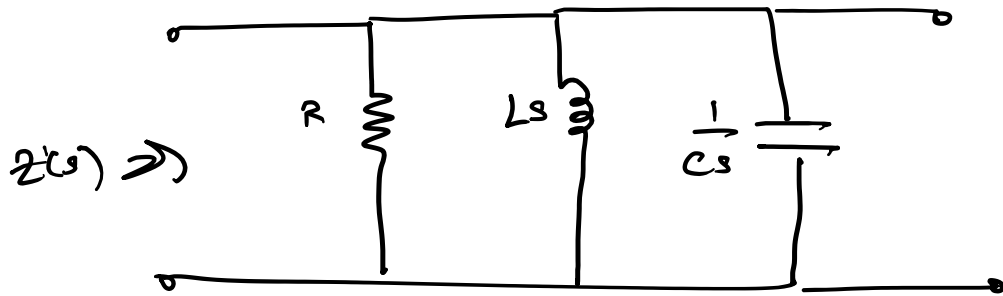

$$H(s) = \frac{V_{out}(s)}{I_{in}(s)} = \frac{1}{Y(s)} = \frac{1}{\frac{1}{R} + \frac{1}{Ls} + cs}$$



$$= \frac{1}{Ls + R + RLCs^2}$$

$$= \frac{RLS}{RLCs^2 + Ls + R} \times \frac{\frac{1}{RLC}}{\frac{1}{RLC}} = \frac{s/c}{s^2 + \frac{s}{RC} + \frac{1}{LC}} \quad (s-)$$

Frequency Response of ckt

$$H(s) = \frac{s/c}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

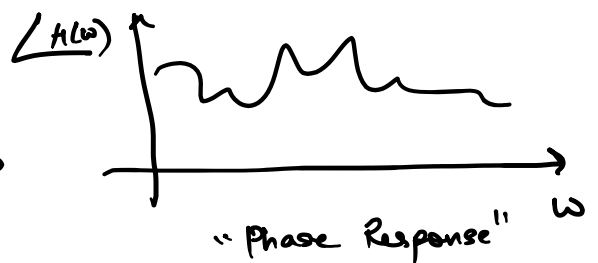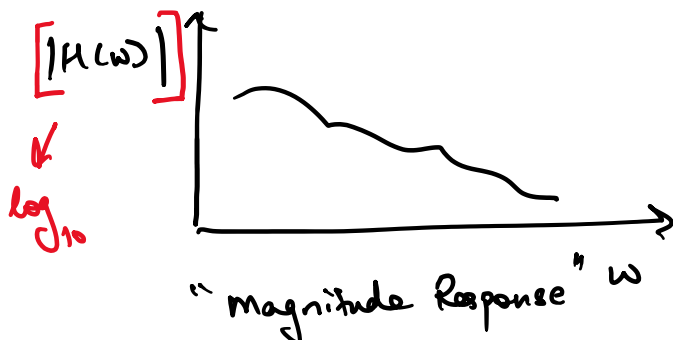
$$H(\omega) = \frac{j\omega/c}{(j\omega)^2 + \frac{j\omega}{RC} + \frac{1}{LC}} \rightarrow \text{Complex function in frequency domain}$$




$$H(\omega) = \frac{j\omega/c}{\left(\frac{1}{Lc} - \omega^2\right) + j\frac{\omega}{Rc}}$$


$$|H(\omega)| = \frac{\omega/c}{\sqrt{\left(\frac{1}{Lc} - \omega^2\right)^2 + \left(\frac{\omega}{Rc}\right)^2}}$$

$$\begin{aligned} & \textcircled{4} \\ & x = a + jb \\ & |x| = \sqrt{a^2 + b^2} \\ & \angle x = \tan^{-1}\left(\frac{b}{a}\right) \end{aligned}$$

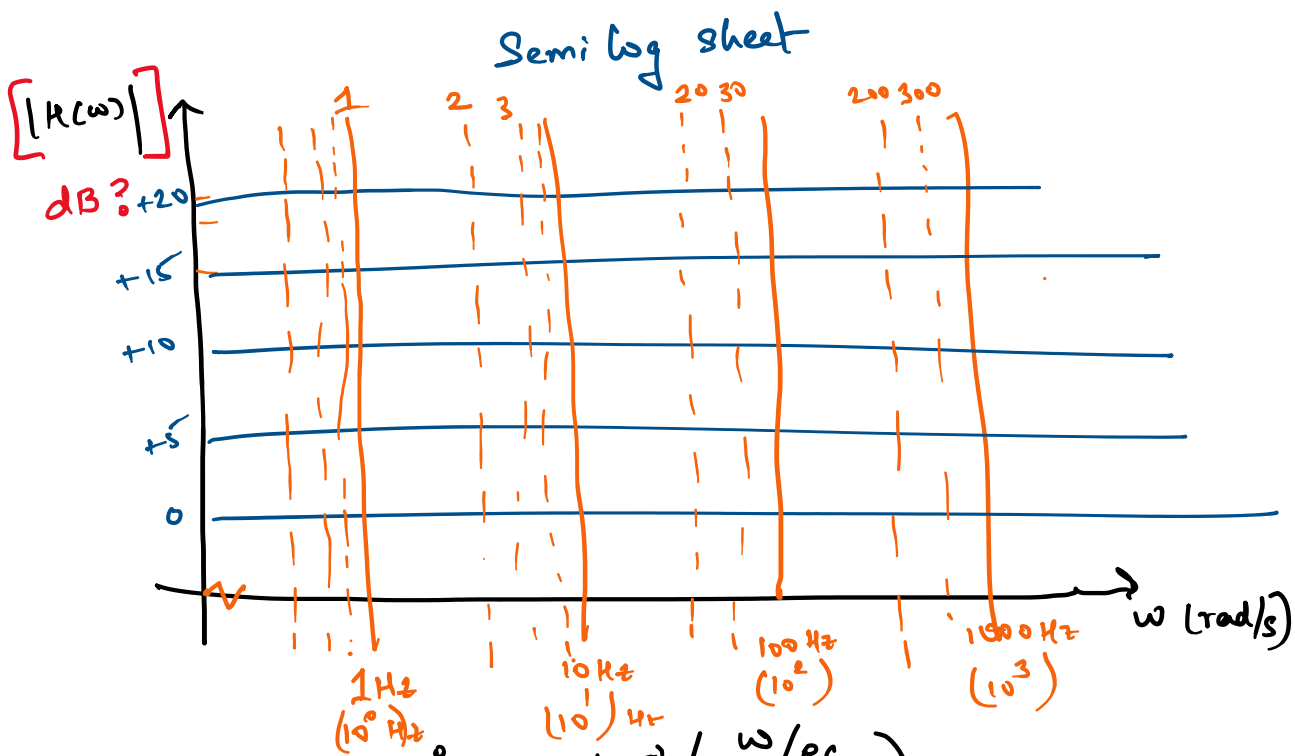
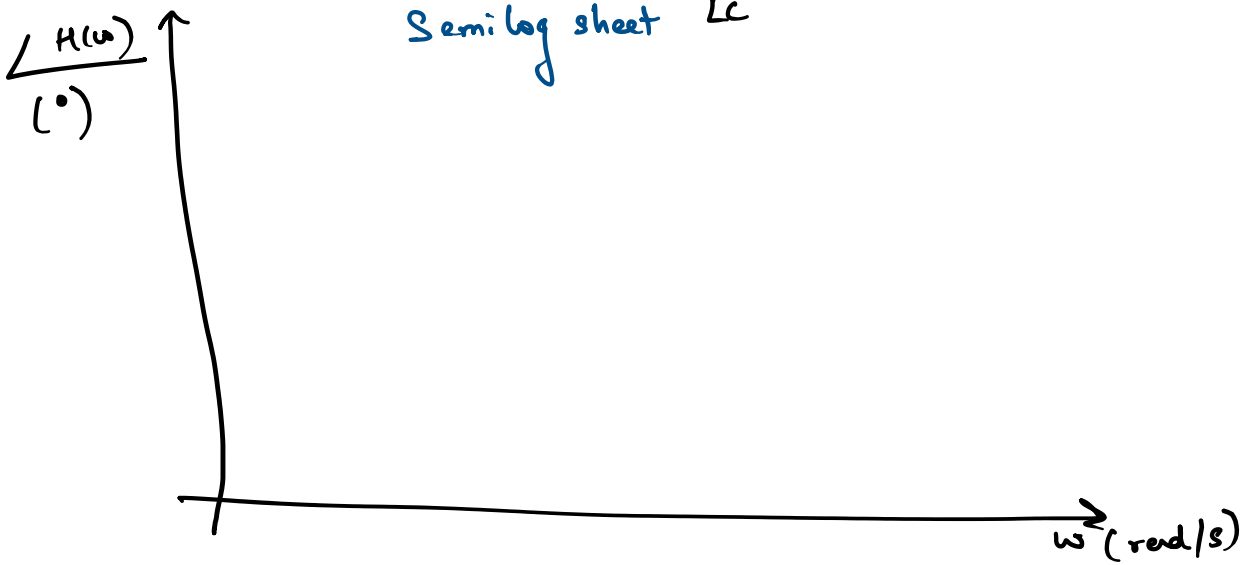
$$\angle H(\omega) = 90^\circ - \tan^{-1}\left(\frac{\omega/Rc}{\frac{1}{Lc} - \omega^2}\right)$$



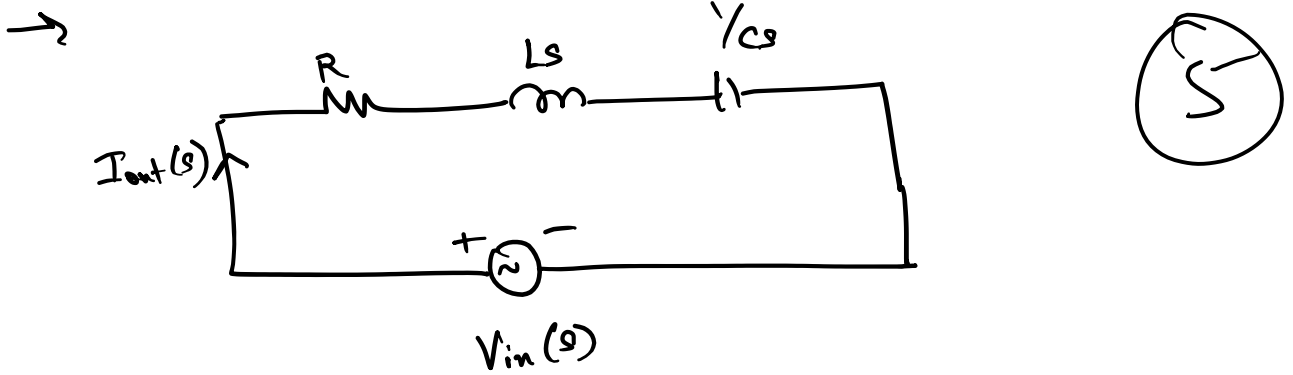

$$\begin{aligned}
 H(s) &= \frac{I_{out}(s)}{V_{in}(s)} = \frac{1}{Z(s)} = \frac{1}{R + Ls + \frac{1}{Cs}} \\
 &= \frac{Cs}{RCS + Lcs^2 + 1} \times \frac{\frac{1}{Lc}}{\frac{1}{Lc}} = \frac{s/L}{s^2 + s\frac{R}{L} + \frac{1}{Lc}}
 \end{aligned}$$

→ Draw magnitude + phase response of (6)

$$H(s) = \frac{1}{1 + s/a}$$

$a = \text{real constant}$

(i) $s = j\omega$

$$H(j\omega) = \frac{1}{1 + j(\omega/a)}$$

(iii) $|H(\omega)| = \frac{1}{\sqrt{1 + (\frac{\omega}{a})^2}}, \quad \angle H(\omega) = 0^\circ - \tan^{-1}(\frac{\omega}{a})$

$$[|H(\omega)|] = 20 \log_{10} \left(\frac{1}{\sqrt{1 + \omega^2/a^2}} \right)$$

	ω	$ H(\omega) $	$[H(\omega)]$	$\angle H(\omega)$
↑ 5 decades ↓	$\omega = a/100$	1	0	$\sim 0^\circ$
	$\omega = a/10$	1	0	-5.7°
	$\omega = a$	$1/\sqrt{2}$	-3	-45°
	$\omega = 10a$	0.1	-20	-85°
	$\omega = 100a$	0.01	-40	-90°

1. $\omega = a/100$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega/a)^2}} = \frac{1}{\sqrt{1 + (\frac{a/100}{a})^2}} = \frac{1}{\sqrt{1 + (\frac{1}{100})^2}}$$

$$= \frac{1}{\sqrt{1 + 0.0001}} \approx 1$$

$$[|H(\omega)|] = 20 \log_{10}(1) = 20 \log_{10}(10^0) = 0$$

$$\angle H(\omega) = -\tan^{-1}\left(\frac{\omega}{a}\right) = -\tan^{-1}\left(\frac{a/100}{a}\right) = \textcircled{7}$$

$$= -\tan^{-1}\left(\frac{1}{100}\right) = -0.573^\circ$$

2. $\omega = a/10$

8

$$|H(\omega)| = \left| \frac{1}{\sqrt{1 + \left(\frac{\omega}{a}\right)^2}} \right| = \frac{1}{\sqrt{1 + \left(\frac{1}{10}\right)^2}} \approx 1$$

$$[|H(\omega)|] = 20 \log_{10}(1) = 0$$

$$\angle H(\omega) = -\tan^{-1}\left(\frac{1}{10}\right) = -5.7^\circ$$

3. $\omega = a \rightarrow -3 \text{ dB frequency}$

$$|H(\omega)| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

$$[|H(\omega)|] = 20 \log_{10}(0.707) = -3$$

$$\angle H(\omega) = -\tan^{-1}\left(\frac{\omega}{a}\right) = -\tan^{-1}(1) = -45^\circ$$

4. $\omega = 10a$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (10)^2}} \approx \frac{1}{10} = 0.1$$

$$[|H(\omega)|] = 20 \log_{10}(10^{-1}) = -20$$

$$\angle H(\omega) = -\tan^{-1}(10) = -85^\circ$$


5. $\omega = 100a$

Please work it out

Bode Plot

Magnitude Response

⑨

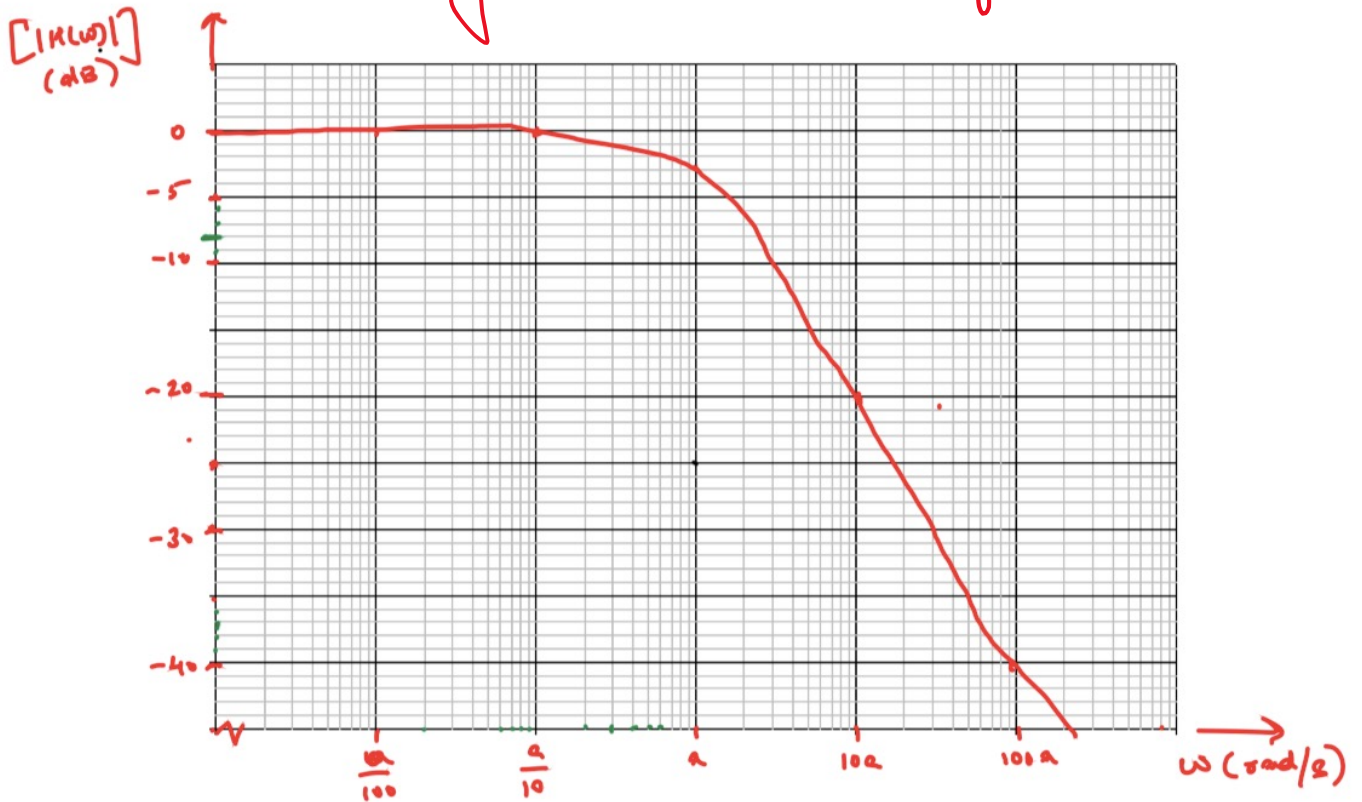

Phase Response

