
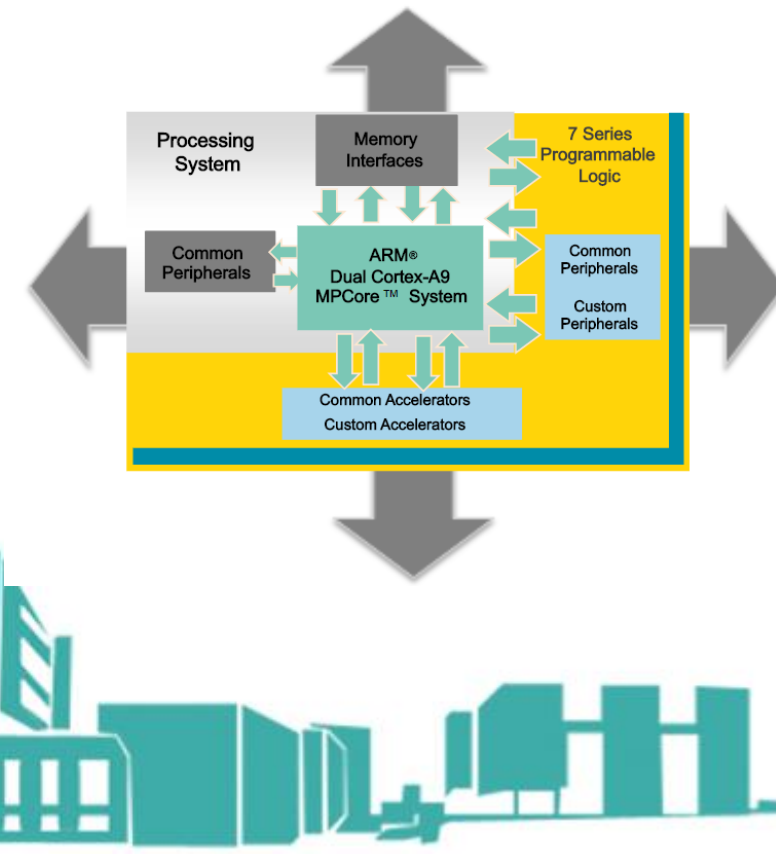


 


ECE 270: Embedded Logic Design



LUT

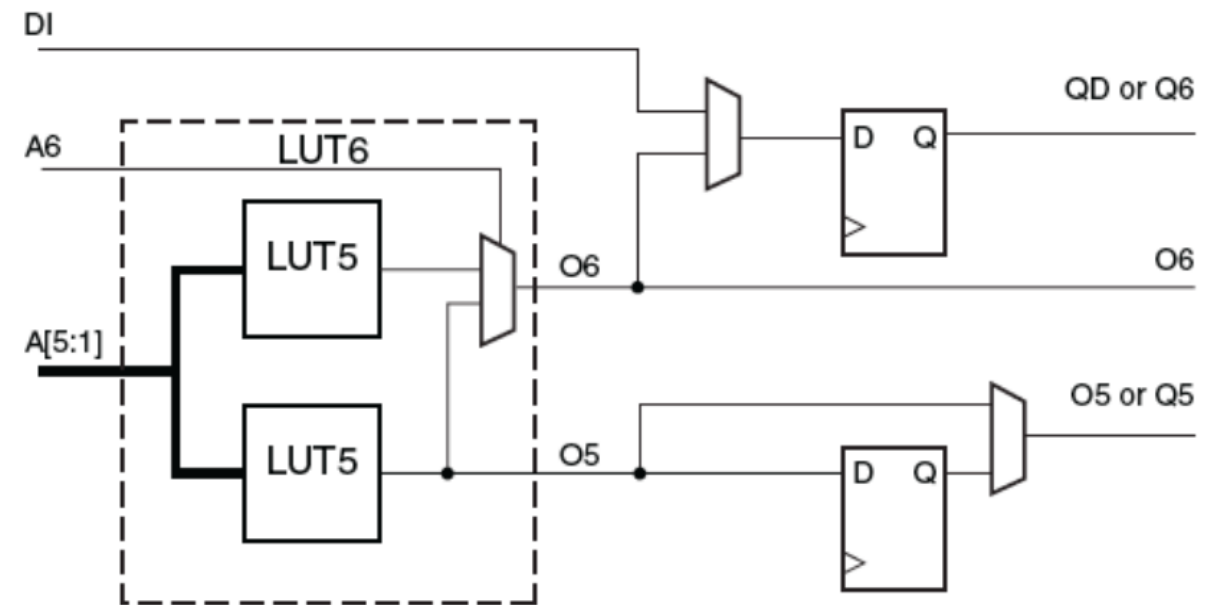
- There are six independent inputs (A inputs - A1 to A6) and two independent outputs (O5 and O6)



3-Input LUT for Logic

- Any single arbitrarily defined 3-input Boolean function
- A 3-input function uses: A1-A3 inputs and O3 output
- Two arbitrarily defined 2-input Boolean functions, as long as these two functions share common inputs
- Two 2-input or less functions use: A1–A2 inputs, A3 driven High, O2 and O3 outputs
- Two arbitrarily defined Boolean functions of 1 input

6-Input LUT for Logic

 

- Any arbitrarily defined six-input Boolean function
- A six-input function uses: A1-A6 inputs and O6 output
- Two arbitrarily defined five-input Boolean functions, as long as these two functions share common inputs
- Two five-input or less functions use: A1–A5 inputs, A6 driven High, O5 and O6 outputs
- Two arbitrarily defined Boolean functions of 3 and 2 inputs or less

What is Memory?

LUT as Memory

- Only in **SLICEM**
- Multiple LUTs in a SLICEM can be combined in various ways to store large amount of data
- **Synchronous** write operation, **WEN** must be high
- **Asynchronous or synchronous read** (using **flip-flop** in the same slice)

LUT as Memory

- **Single port:** Common address port for synch write and asynch read i.e. read and write addresses share the same address bus

LUT as Memory


- **Dual port:** One port for synch write and asynch read, one port for asynch read

LUT as Memory

- **Quad port:** One port for synchronous write and asynchronous read and three ports for asynchronous reads

LUT as Memory

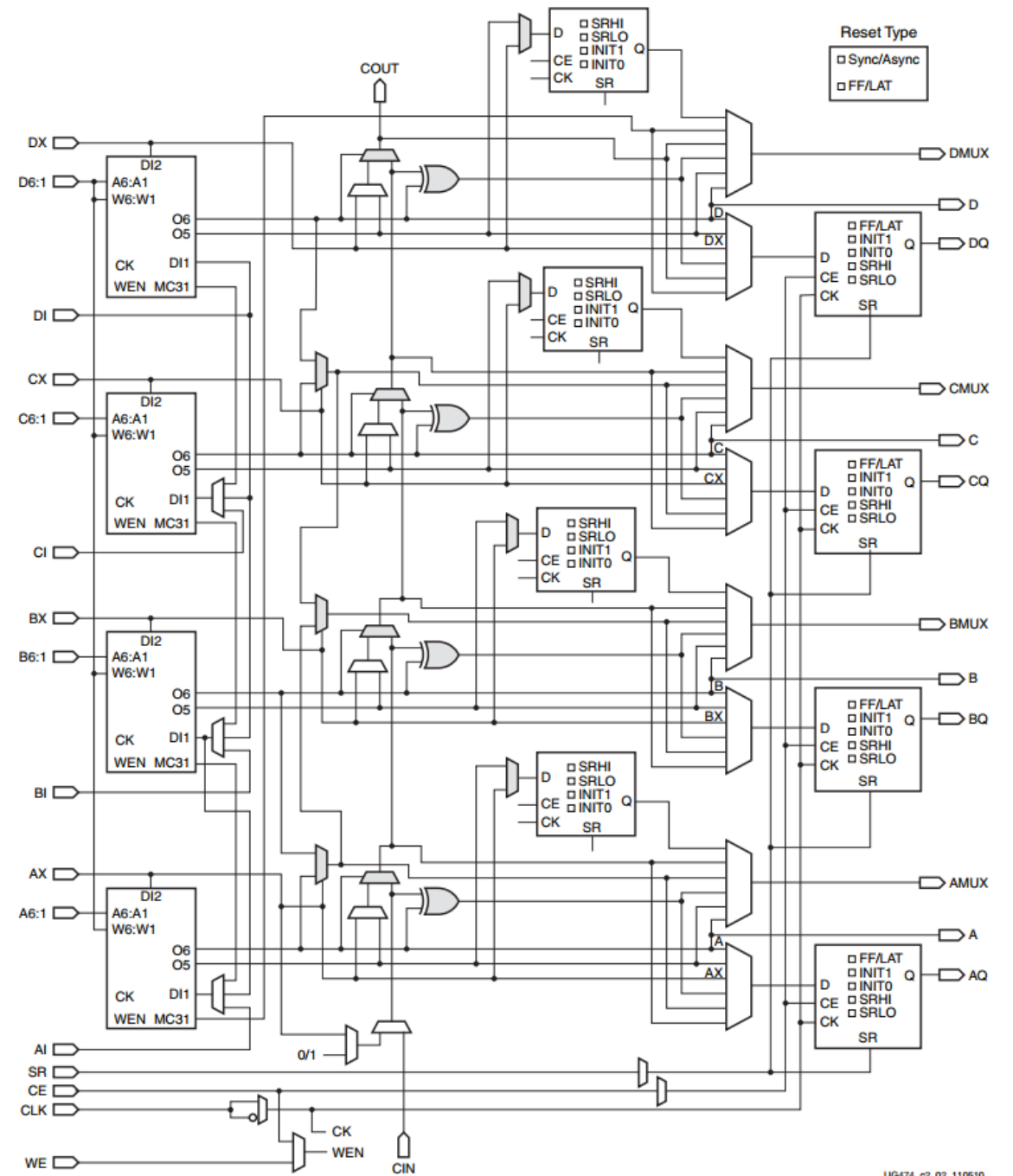
- **Simple dual port:** One port for synchronous write (no data out/read port from the write port) and one port for asynchronous reads



LUT as Memory: 64X1 Single Port

LUT as Memory: 64X1 Single Port

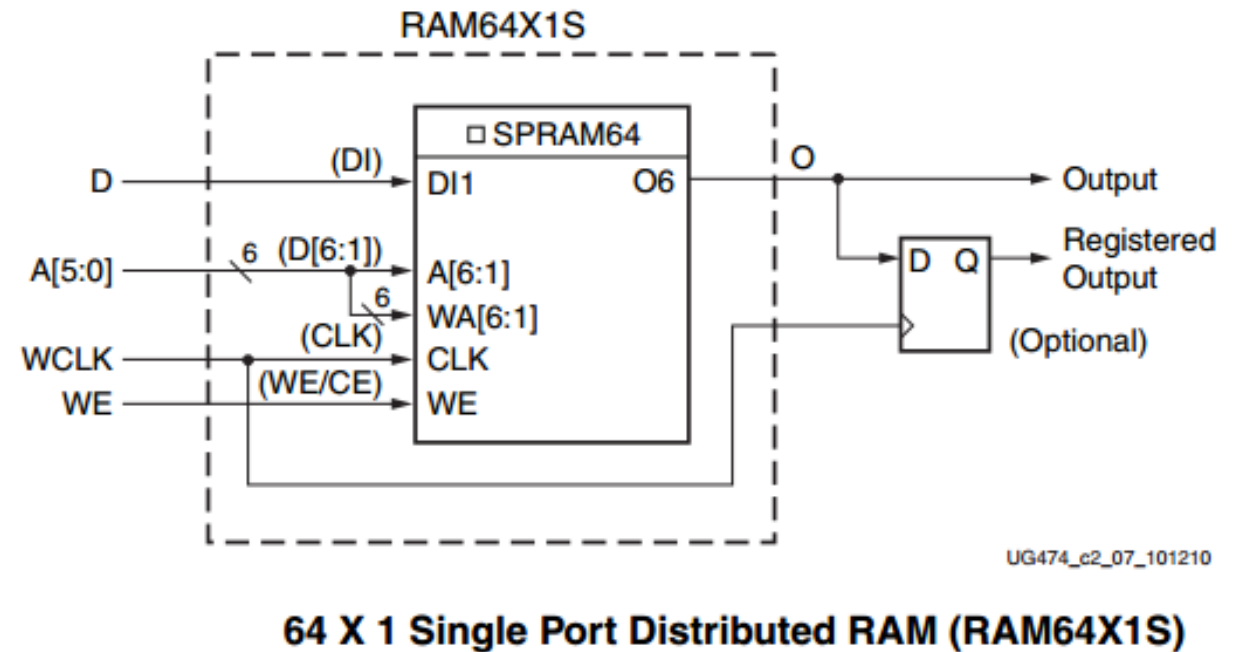
- **Single port:** Common address port for synch write and asynch read
- One SLICEM can have **FOUR 64 x 1-bit memories** as long as they share the **same clock, write enable, and shared read and write port address inputs**
- This configuration equates to a 64 x 4-bit single-port distributed RAM.
- What about O5 output?



LUT as Memory: 64X1 Dual Port

LUT as Memory: 64X1 Dual Port

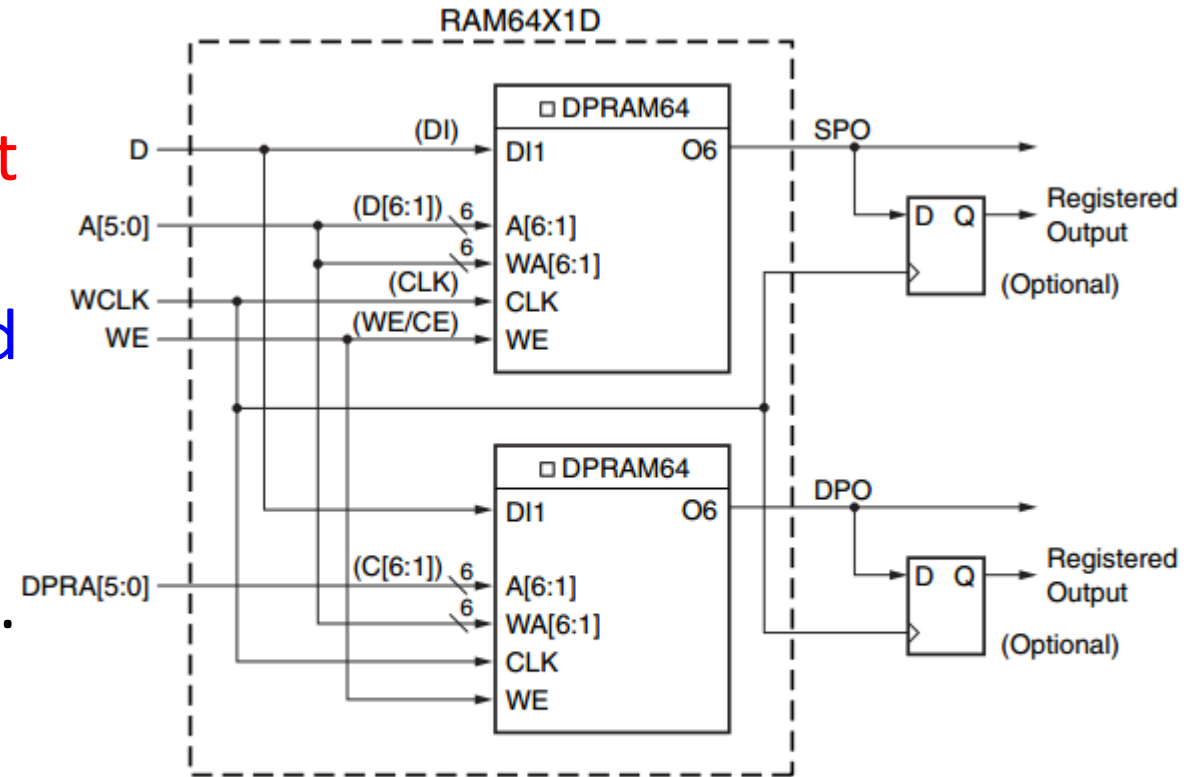- One SLICEM can have **TWO 64 x 1-bit memories** as long as they **share the same clock, write enable, and shared read and write port address inputs**
- This configuration equates to a **64 x 2-bit dual-port distributed RAM**.




64 X 1 Dual Port Distributed RAM (RAM64X1D)


LUT as Memory

- **Synchronous Write Operation**

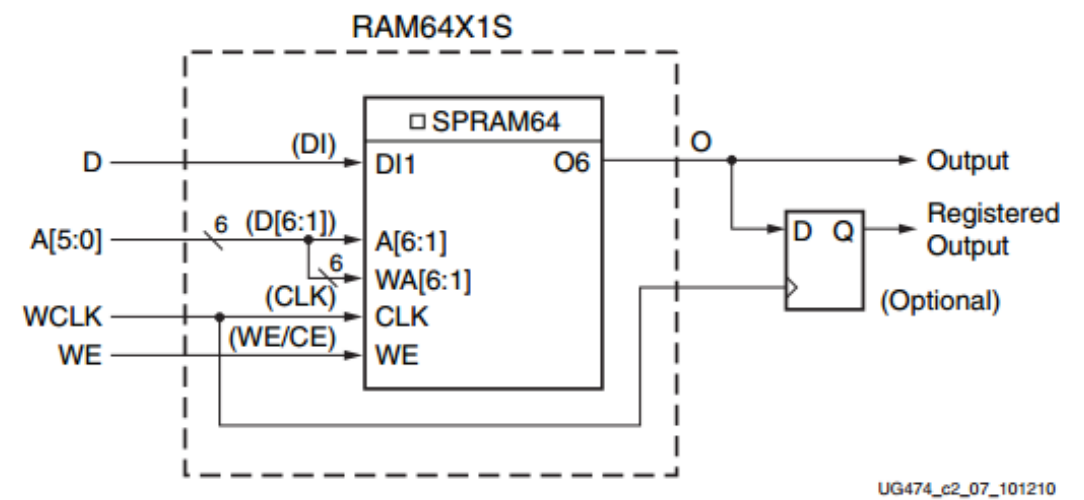The synchronous write operation is a single clock-edge operation with an active-High write-enable (WE) feature. When WE is High, the input (D) is loaded into the memory location at address A.



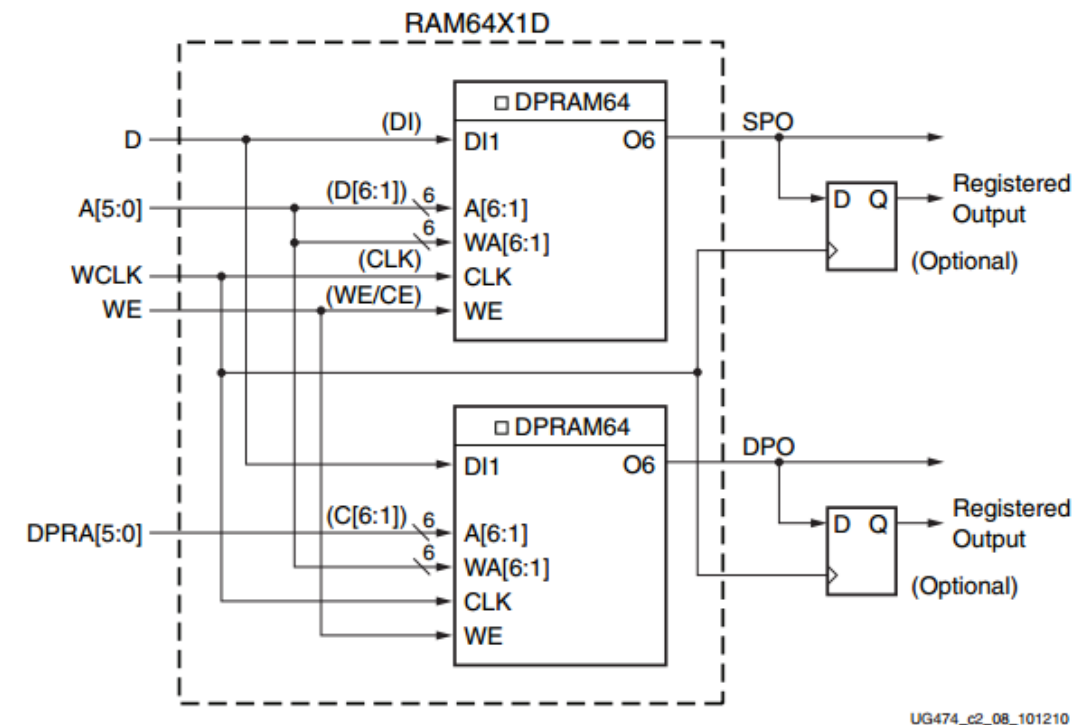64 X 1 Single Port Distributed RAM (RAM64X1S)




64 X 1 Dual Port Distributed RAM (RAM64X1D)

LUT as Memory


- **Asynchronous Read Operation**

The output (or **output SPO of dual-port mode**) is determined by the **address A** for the **single-port mode** or **address DPRA** determines the **DPO** output of **dual-port mode**.

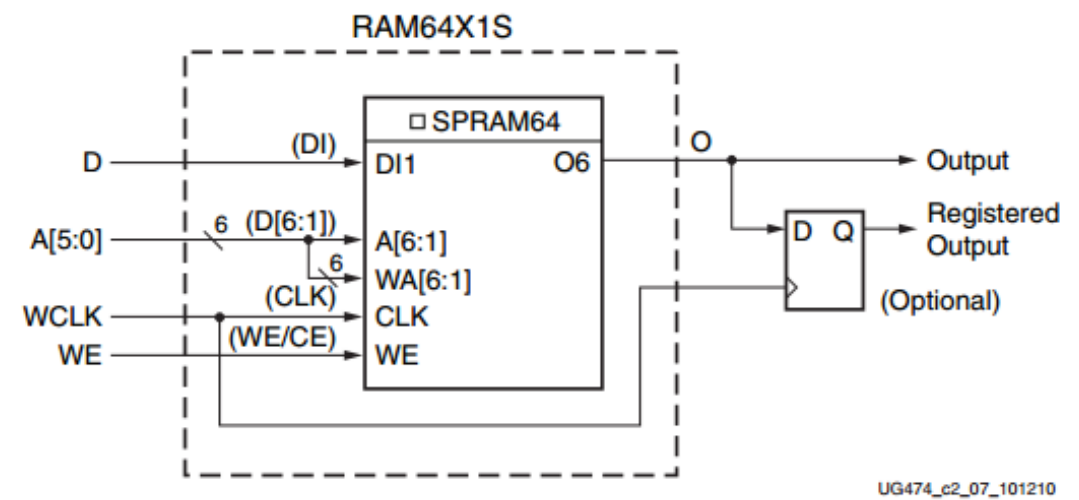- Each time a new address is applied to the address pins, the data value in the memory location of that address is available on the output.
- This operation is **asynchronous** and **independent** of the clock signal.




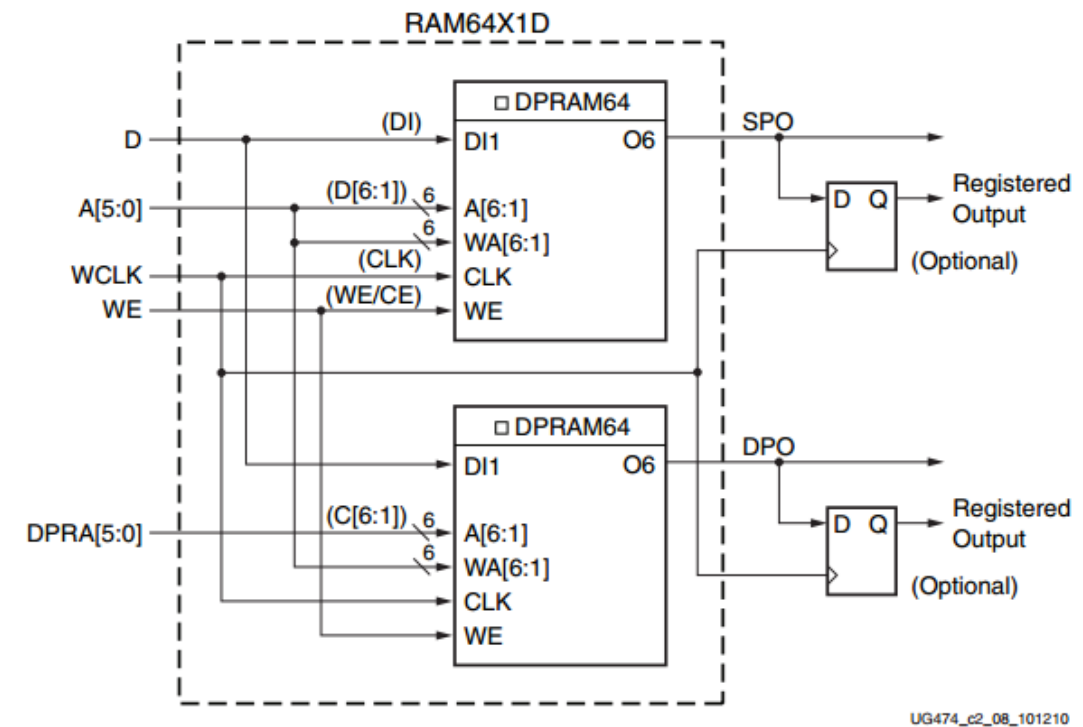64 X 1 Single Port Distributed RAM (RAM64X1S)




64 X 1 Dual Port Distributed RAM (RAM64X1D)

LUT as Memory: 64X1 Dual Port

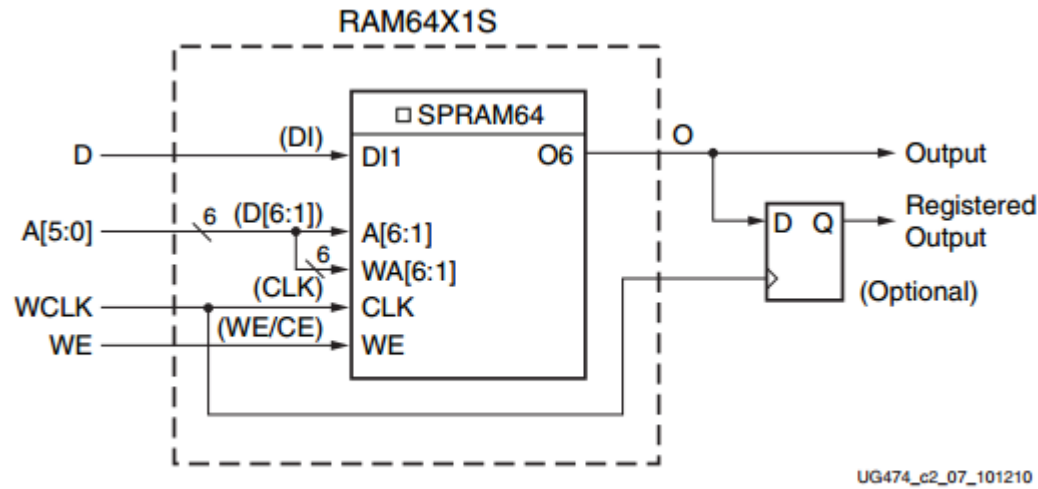

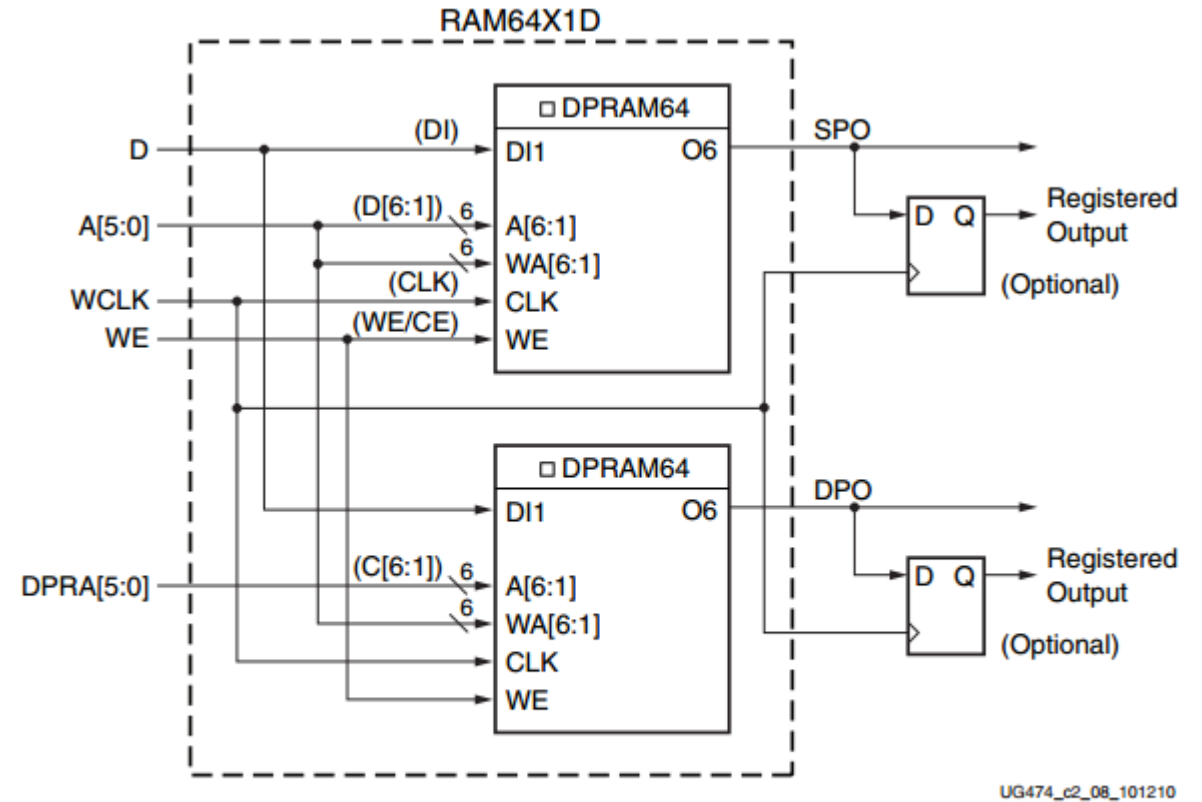64 X 1 Single Port Distributed RAM (RAM64X1S)



64 X 1 Dual Port Distributed RAM (RAM64X1D)