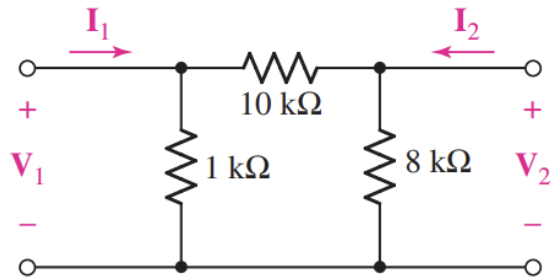


Tutorial 12

Q.1.


Obtain a complete set of y parameters which describe the two-port shown in Fig. 17.40.



■ FIGURE 17.40

Q.2.

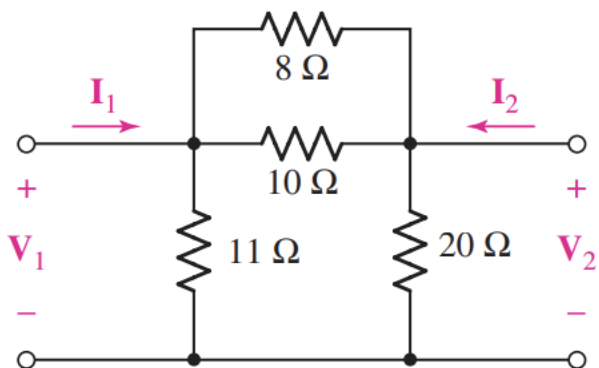
(a) Determine the short-circuit admittance parameters which completely describe the two-port network of Fig. 17.41. (b) If $V_1 = 3\text{ V}$ and $V_2 = -2\text{ V}$, use your answer in part (a) to compute I_1 and I_2 .



■ FIGURE 17.41

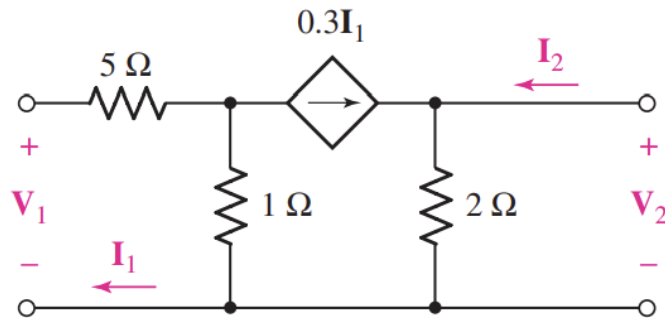Q.3.

Employ an appropriate method to obtain \mathbf{y} for the network of Fig. 17.47.



■ **FIGURE 17.47**

Q.4.


Convert the following \mathbf{z} parameters to \mathbf{y} parameters, or vice versa, as appropriate:

$$\mathbf{z} = \begin{bmatrix} 2 & 3 \\ 5 & 1 \end{bmatrix} \Omega \quad \mathbf{z} = \begin{bmatrix} 1000 & 470 \\ 2500 & 900 \end{bmatrix} \Omega$$

$$\mathbf{y} = \begin{bmatrix} 0.001 & 0.005 \\ 0.006 & 0.03 \end{bmatrix} \text{S} \quad \mathbf{y} = \begin{bmatrix} 1 & 2 \\ -1 & 3 \end{bmatrix} \text{S}$$

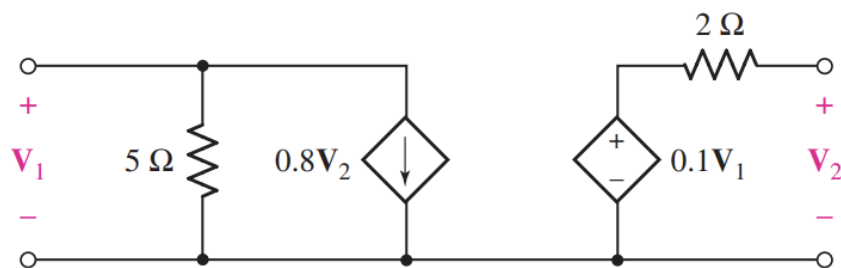Q.5.


Determine the impedance parameters for the two-port exhibited in Fig. 17.58.



■ **FIGURE 17.58**

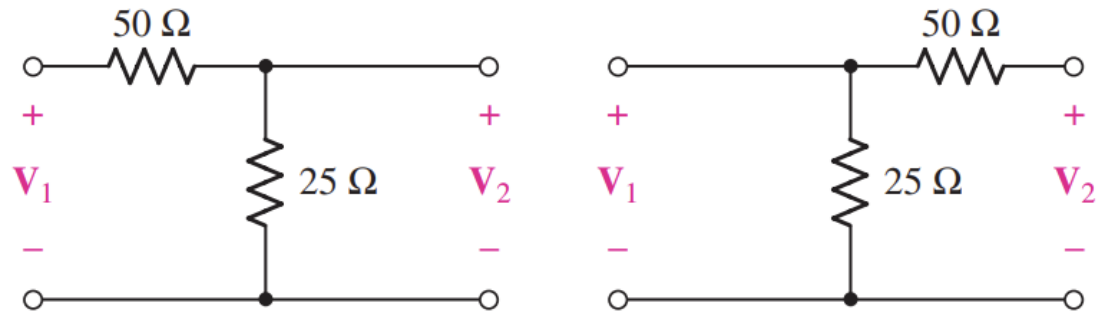Q.6.

Obtain the **h** parameters of the two-ports of Fig. 17.61.



■ **FIGURE 17.61**