

# ELD Lab 5


## Design of Digital Clock

# Objective

- Design digital clock with Second and Minute Display using behavioral modelling
- Verify the circuit using virtual input and output (VIO) and Integrated Logic Analyzer.
- **Lab Homework:** Design the counter with output sequence as 4-> 6 -> 8 -> 4 -> 6 -> 8 .....

Lab

# Proposed Approach (Extension of Lab 3)

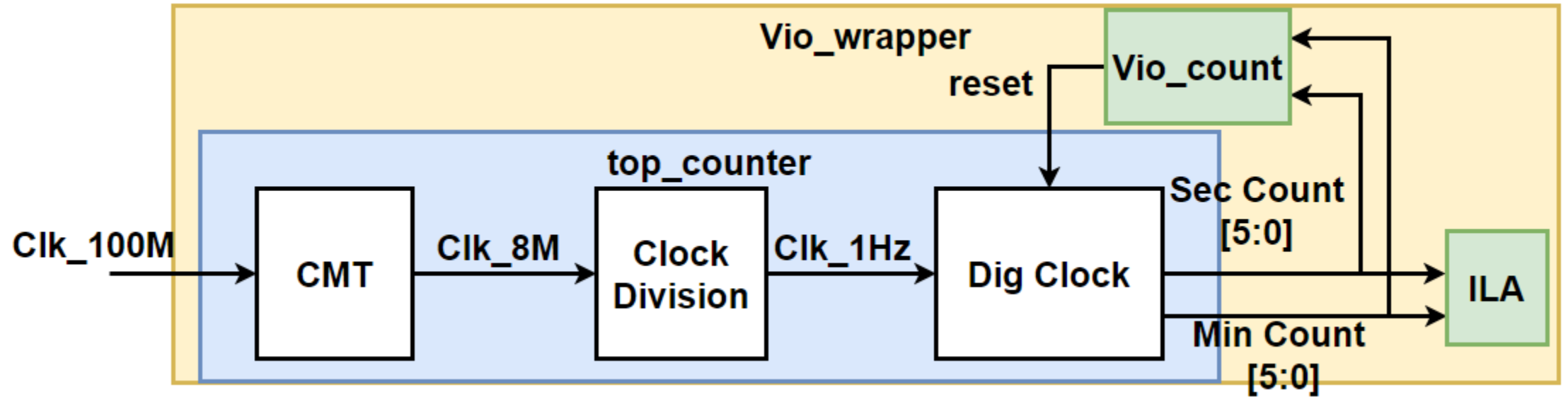


# Digital Clock

```
module Dig_clock(  
    input Clk_1Hz,  
    input reset,  
    output [5:0] Sec_Count,  
    output [5:0] Min_Count  
);
```

```
    reg [5:0] Sec_Count_next;  
    reg [5:0] Sec_Count_reg=0;  
    always@(posedge Clk_1Hz or posedge reset)  
    begin  
        if(reset)  
            Sec_Count_reg <= 0;  
        else  
            Sec_Count_reg <= Sec_Count_next;  
    end  
    always@(*)  
    begin  
        if(Sec_Count_reg == 59)  
            Sec_Count_next = 0;  
        else  
            Sec_Count_next = Sec_Count_reg + 1;  
    end
```

```
    reg [5:0] Min_Count_next;  
    reg [5:0] Min_Count_reg=0;  
    always@(posedge Clk_1Hz or posedge reset)  
    begin  
        if(reset)  
            Min_Count_reg <= 0;  
        else  
            Min_Count_reg <= Min_Count_next;  
    end  
    always@(*)  
    begin  
        if(Sec_Count_reg == 59)  
            if(Min_Count_reg == 59)  
                Min_Count_next = 0;  
            else  
                Min_Count_next = Min_Count_reg + 1;  
        else  
            Min_Count_next = Min_Count_reg;  
    end  
    assign Sec_Count = Sec_Count_reg;  
    assign Min_Count = Min_Count_reg;
```

# ILA

 

Component Name ILA\_count

To configure more than 64 probe ports use Vivado Tcl

**General Options** **Probe\_Ports(0..2)**

Probe Port	Probe Width [1..4096]	Num
PROBE0	1	1
PROBE1	6	1
PROBE2	6	1

Component Name **ILA\_count**

To configure more than 64 probe ports use Vivado Tcl Console

**General Options** **Probe\_Ports(0..2)**

**Monitor Type**

☒ Native ☐ AXI

**Number of Probes** 3 [1...1024]

Sample Data Depth 1024

☒ Same Number of Comparators for All Probe Ports

Number of Comparators 1

☐ Trigger Out Port

☐ Trigger In Port

Input Pipe Stages 0

# Demo

hw_vio_1				
<div><div></div><div></div><div></div><div></div><div></div></div>				
Name	Value	Activity	Direction	VIO
<div><div></div>reset</div>	[B] 0		Output	hw_vio_1
> <div><div></div>Min_Count[5:0]</div>	[U] 0		Input	hw_vio_1
> <div><div></div>Sec_Count[5:0]</div>	[U] 3	<div></div>	Input	hw_vio_1

