

Tutorial 5

Q.1. Use the Bode approach to sketch the magnitude of each of the following

(a)

$$\frac{4}{s^3 + 7s^2 + 12s}$$


(b)

$$\frac{s + 300}{s(5s + 8)}$$

Q.2.

For the circuit shown in Fig. 16.1, let $R = 1 \text{ k}\Omega$, $C = 22 \text{ mF}$, and $L = 12 \text{ mH}$.

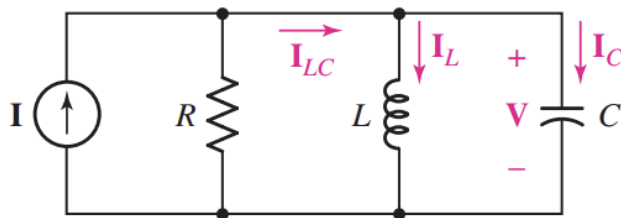(a) Calculate α , ω_0 , ζ , f_0 , and ω_d for the circuit. (b) If $\mathbf{I} = 1\angle 0^\circ \text{ A}$, plot \mathbf{V} , \mathbf{I}_{LC} , \mathbf{I}_L , and \mathbf{I}_C as a function of frequency, and verify that \mathbf{I} and \mathbf{V} are in phase at ω_0 . (c) What is the relationship of \mathbf{I}_L to \mathbf{I}_C at ω_0 ?



Q.3.


A parallel RLC network is constructed with a 5 mH inductor, and the remaining component values are chosen such that $Q_0 = 6.5$ and $\omega_0 = 1000 \text{ rad/s}$. Determine the approximate value of the input impedance magnitude for operation at (a) 500 rad/s ; (b) 750 rad/s ; (c) 900 rad/s ; (d) 1100 rad/s . (e) Plot your estimates along with the exact result using a linear frequency (rad/s) axis.

Q.4.

With regard to the series RLC circuit described in Exercise 15, adjust the resistor value such that Q_0 is reduced to 5, and (a) estimate the angle of the impedance at 90 krad/s , 100 krad/s , and 110 krad/s . (b) Determine the percent error in the estimated values, compared to the exact expression.

Q.5.

For the network represented in Fig. 16.55, determine the resonant frequency and the corresponding value of $|Z_{in}|$.

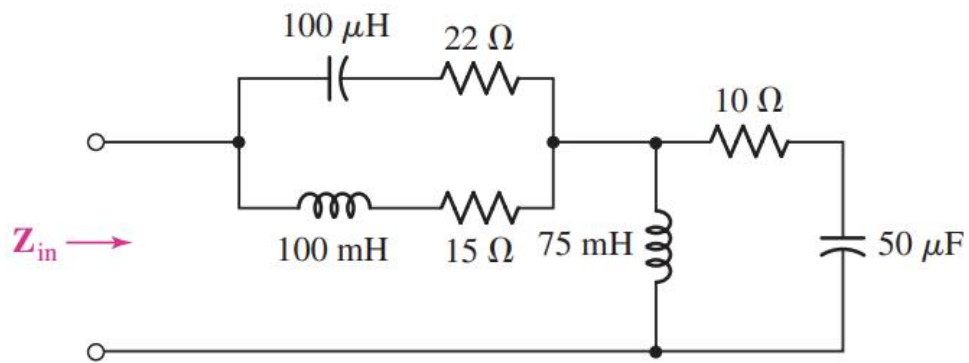

■ **FIGURE 16.55**