
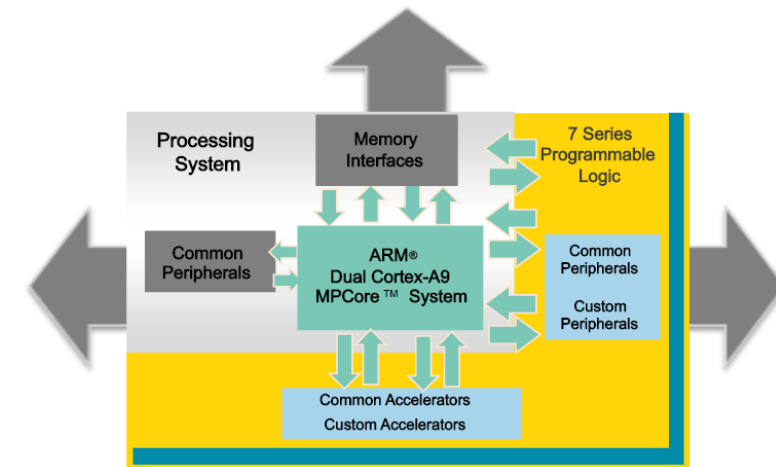


 

# ECE 270: Embedded Logic Design




# Evolution of Programmable Logic Device (PLD)


# PLD

- **Programmable logic devices (PLD):** Devices whose **internal architecture is predetermined** by manufacturer but which are created in such a way that they can be **configured in the field** to perform variety of functions
- How to make device field programmable?

# PLD

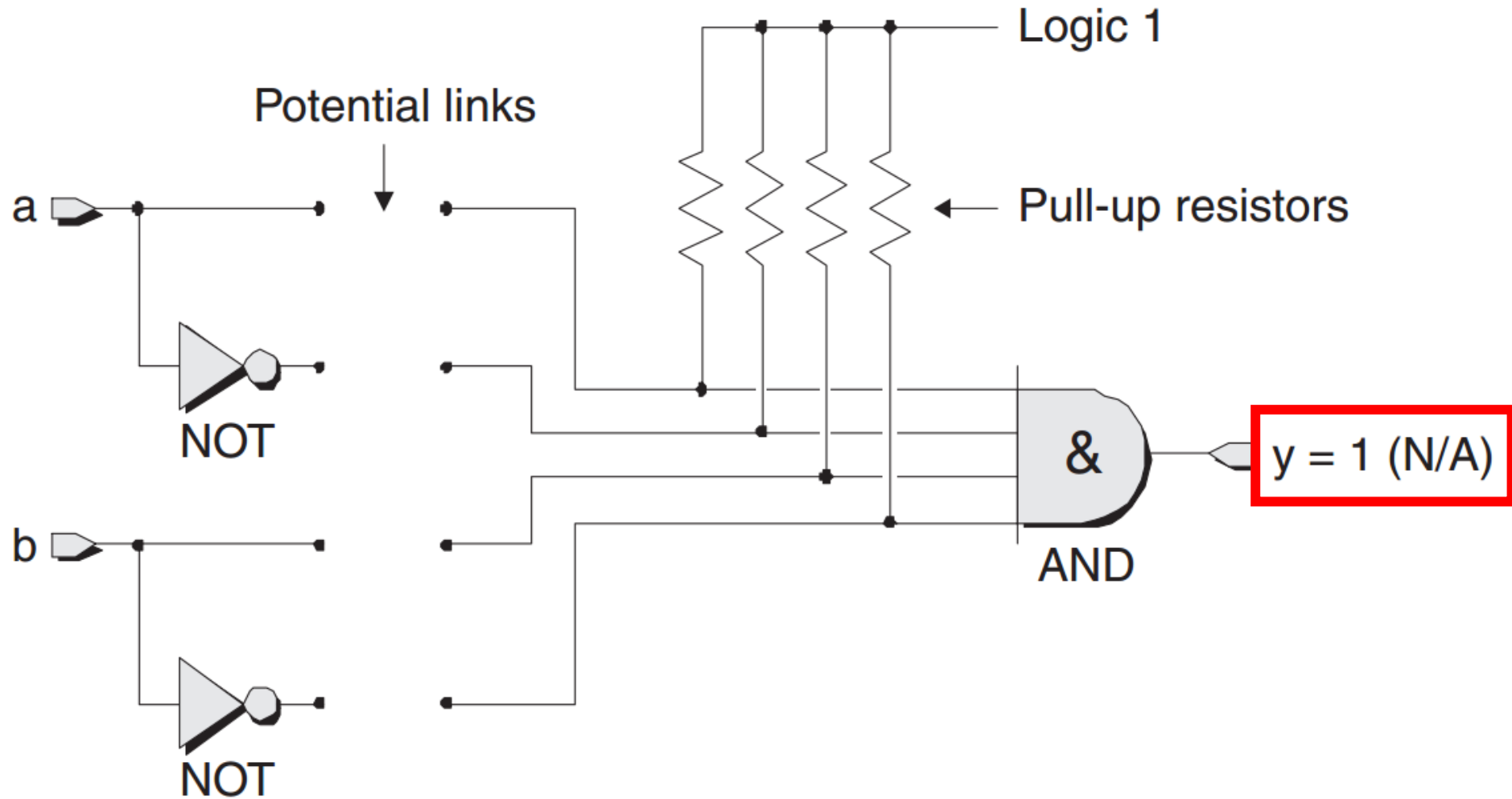


# PLD (Fusible Link Technology)

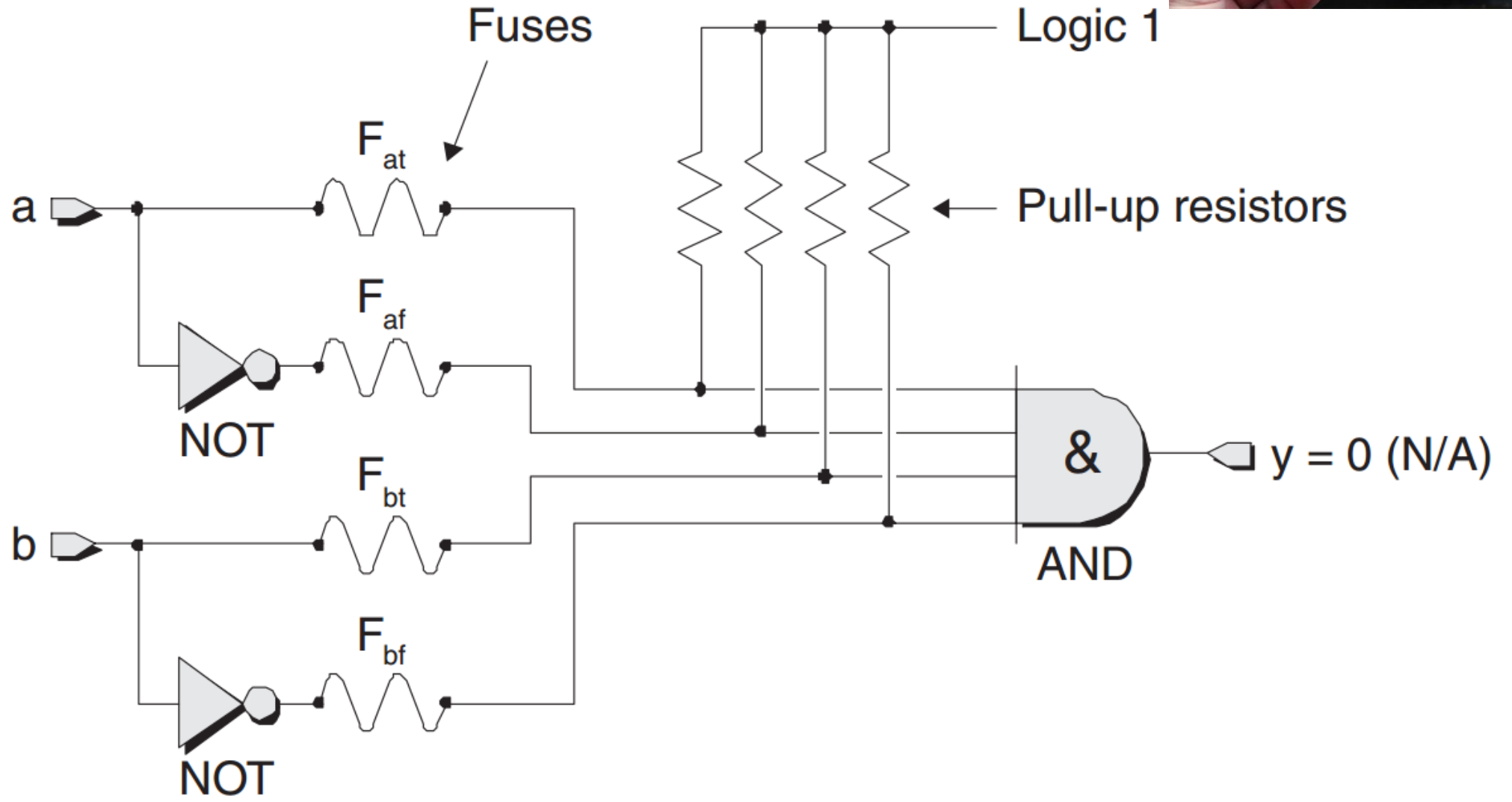

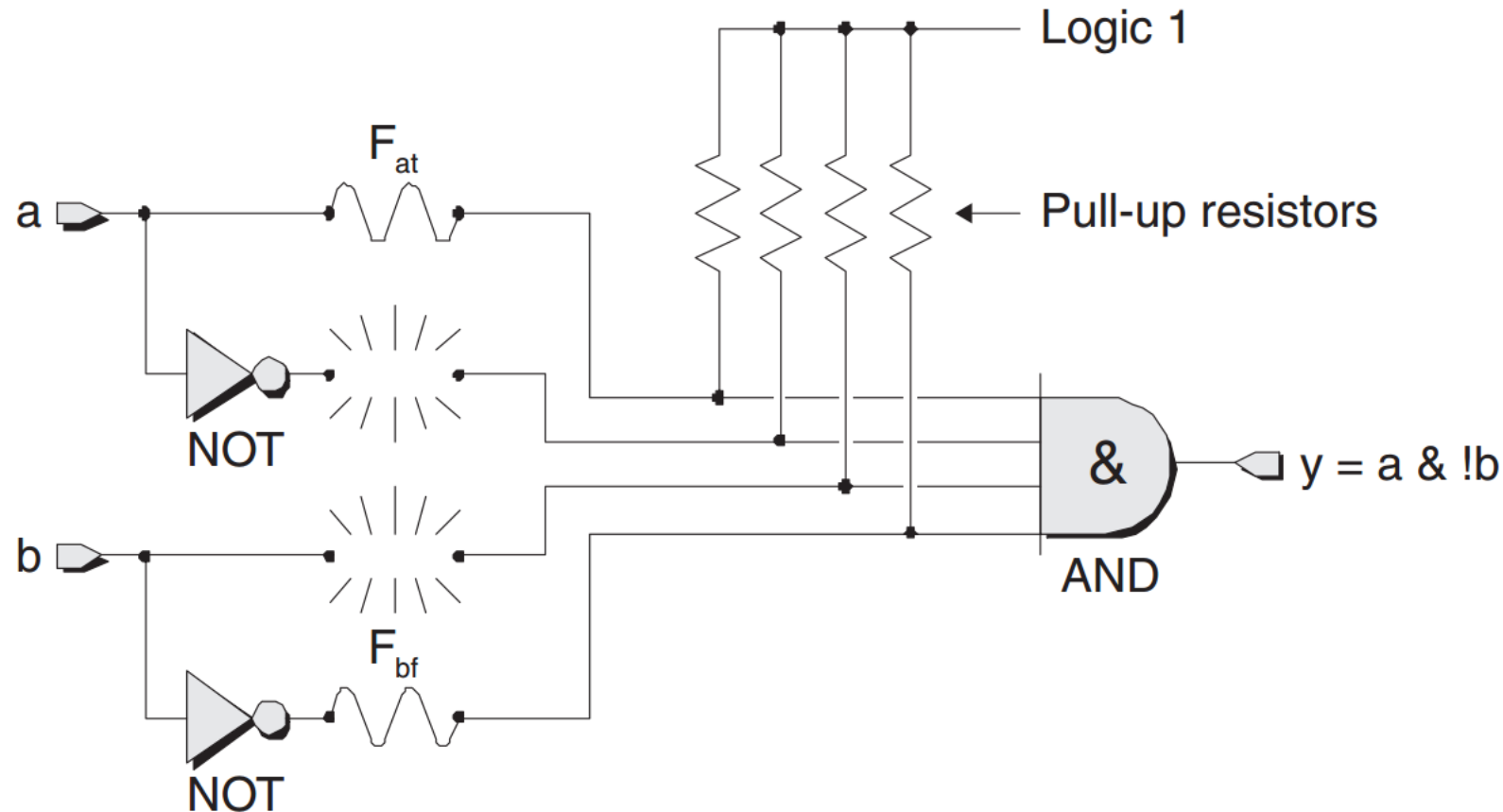
# PLD

- Programming the device/blowing the fuses/burning the device
- One time programmable
- Antifuse technology



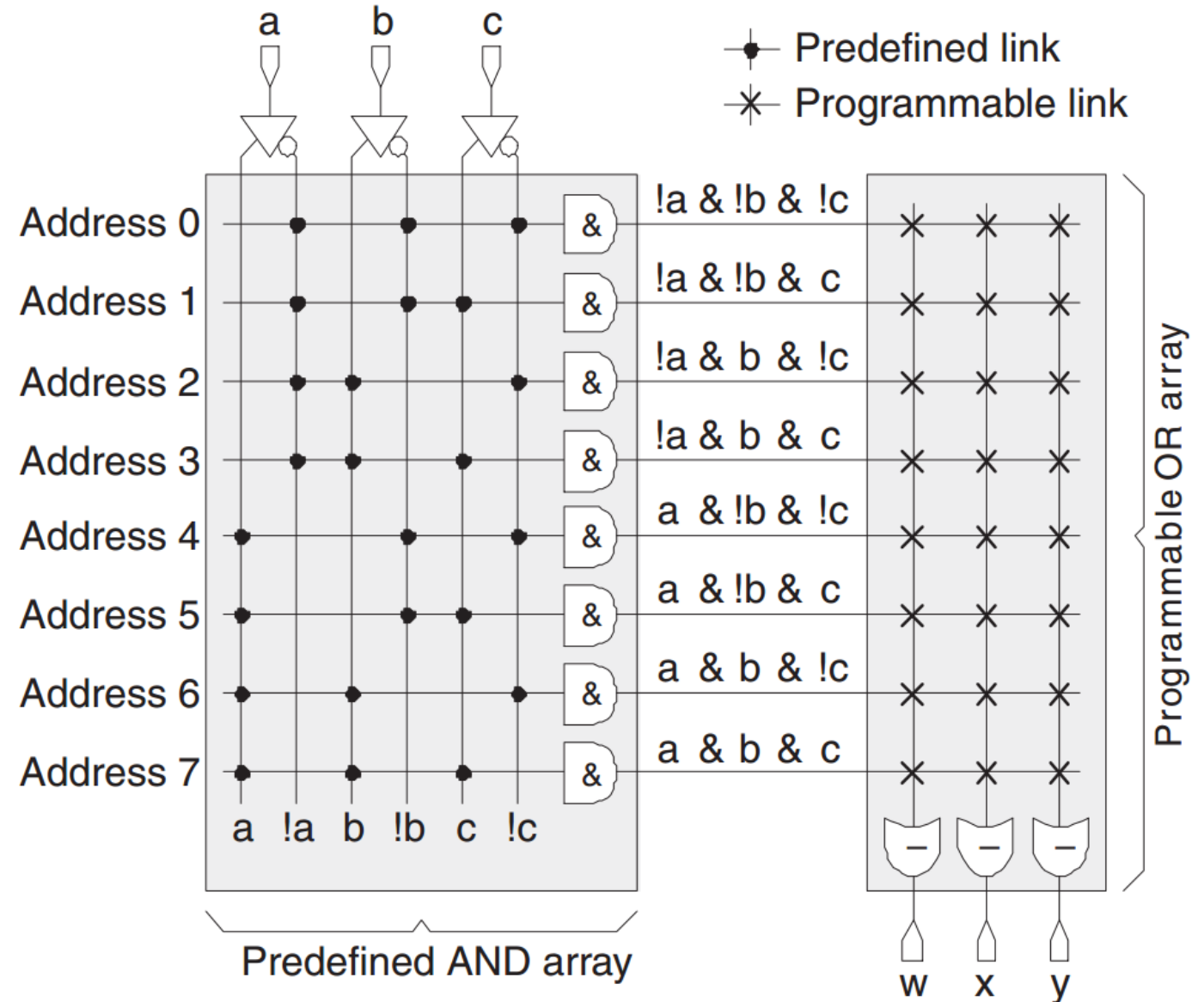
# PLD


- PROM: Programmable read only memory (1970)



# PROM

 


a	b	c	w	x	y
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	0	0

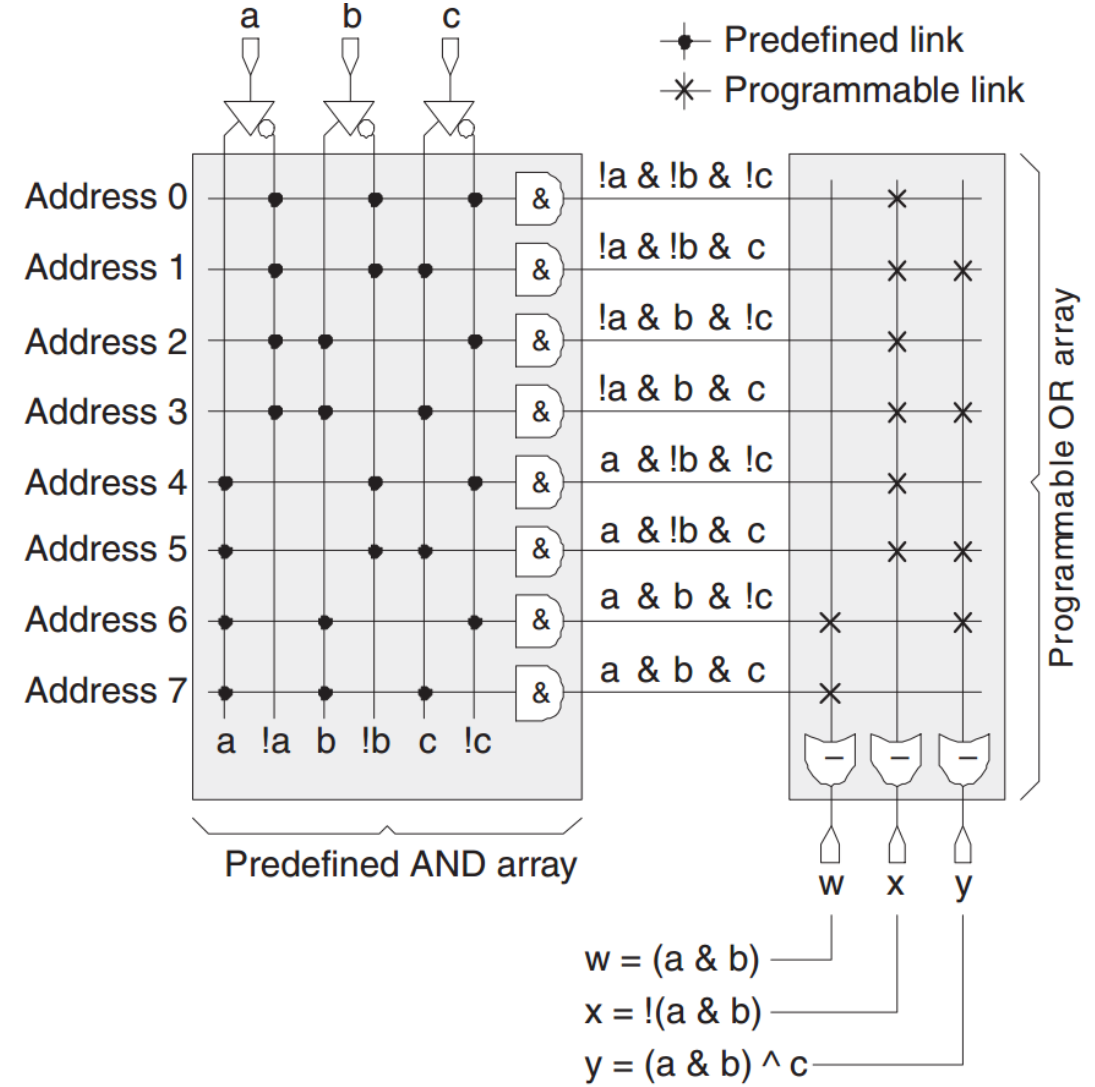


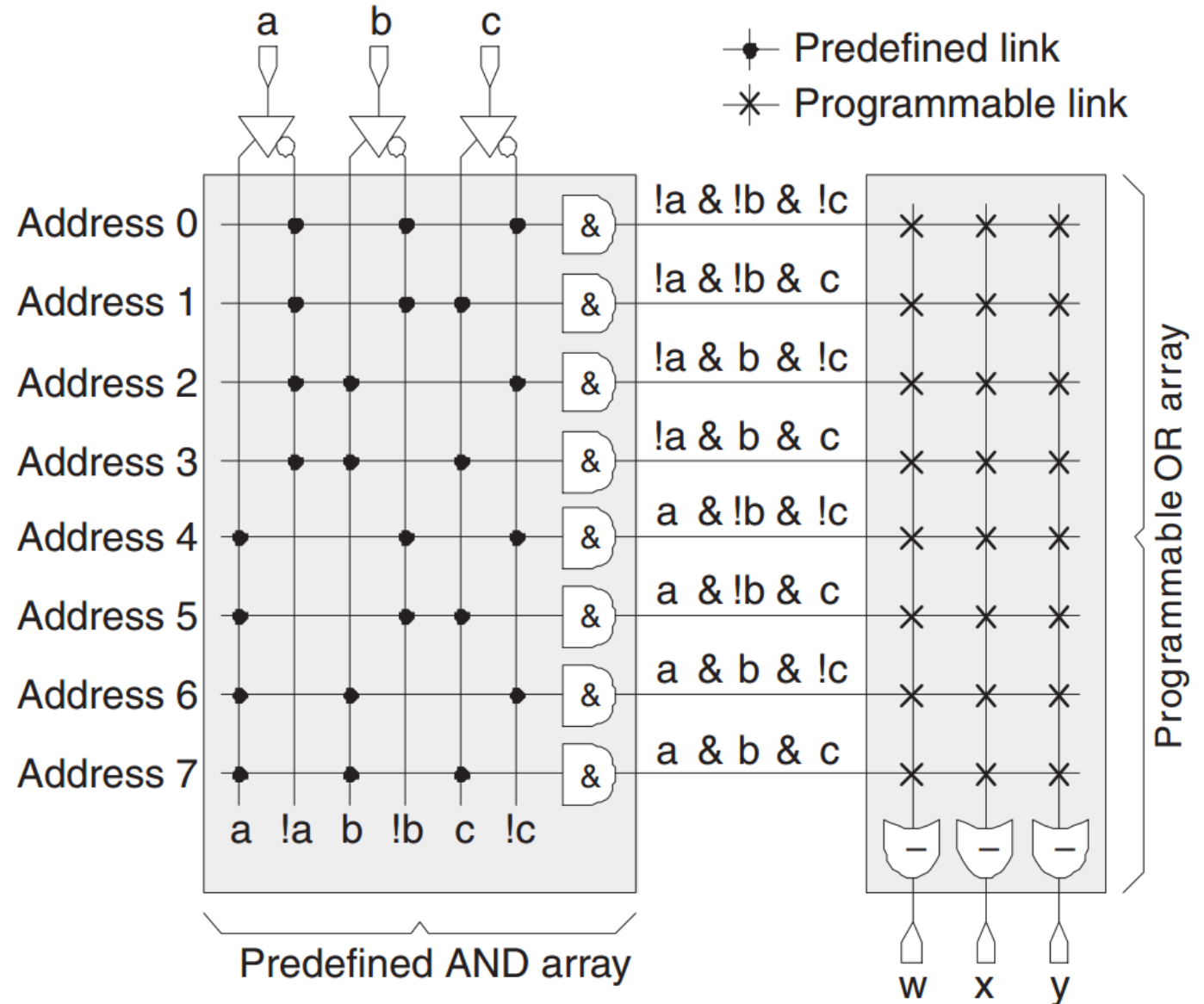
# PLD


- PROM: Programmable read only memory (1970)
- One time programmable
- Single PROM instead of multiple chips: smaller, lighter, cheaper and less prone to errors (fewer soldier joints), easy to identify errors or correct errors



# PLD


- PROM: Programmable read only memory (1970)
- Designed for use as memories to store computer programs and constant data values.
- Also useful for implementation simple logical function such as LUT and state machines
- EPROM (Intel 1971): Erasable PROM: Can be erased (UV rays) and re-programmed... smaller in size than fusible link devices
- Expensive and long erasure time (few minutes)
- Erasing process becomes complex as transistor density increases
- EEPROM: Electrically EPROM (larger than EPROM)

# PLA: Programmable Logic Arrays (1975)

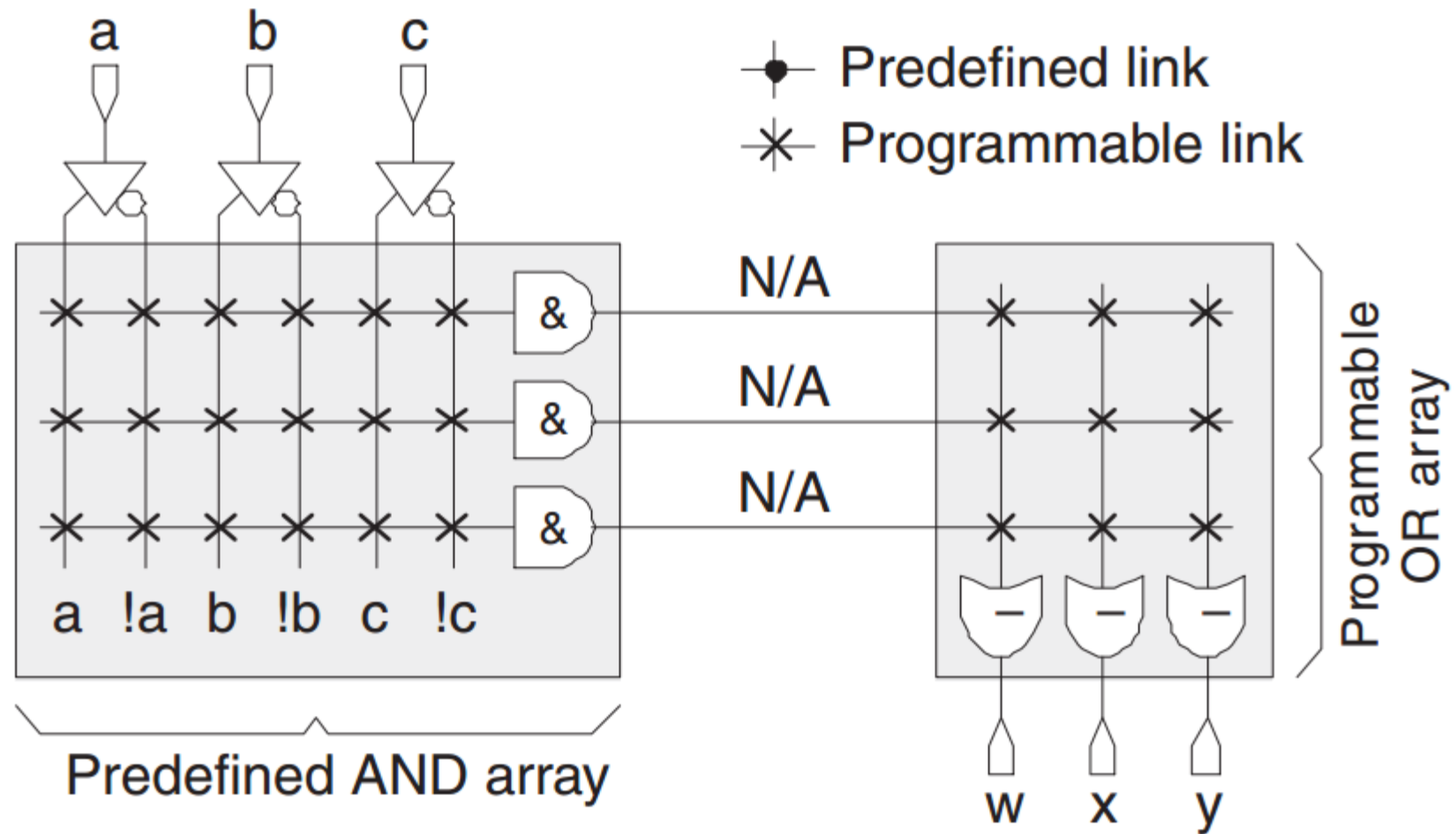

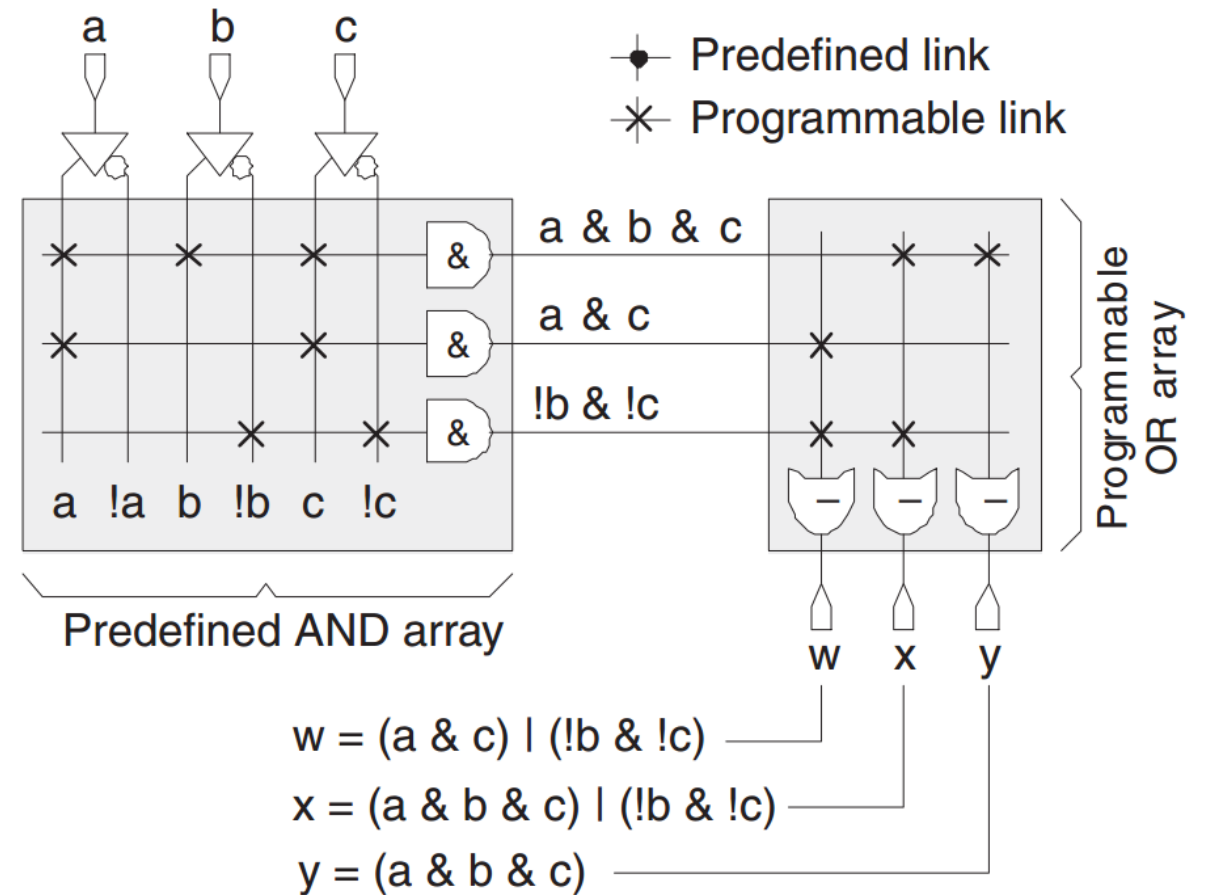
# PLA: Programmable Logic Arrays (PLA)

- Not very popular because SOP was the most popular approach for representation of digital circuits
- Variations: AND-NOR, NAND-OR and so on...
- Slower than PROM: signal takes long time to pass through programmable link than predefined link





 
# PAL: Programmable Array Logic (PAL)

- Faster than PLA
- Limited applications due to fewer number of AND terms



 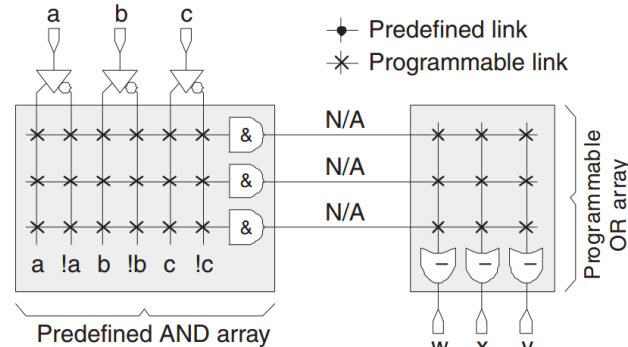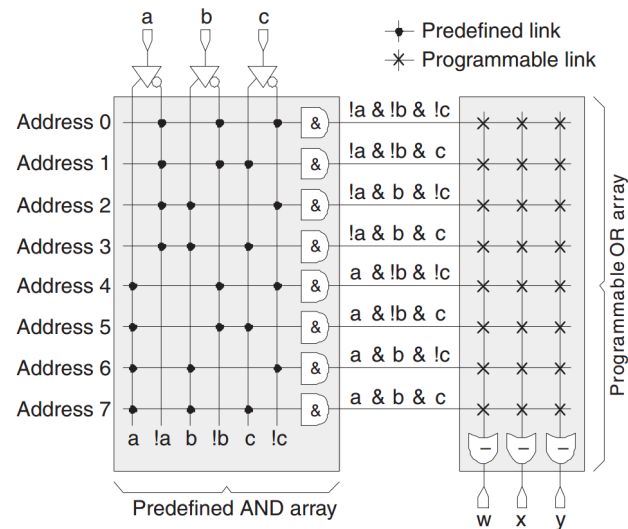
# PLD

- **Programmable logic devices (PLD):** Devices whose internal architecture is predetermined by manufacturer but which are created in such a way that they can be configured in the field to perform variety of functions




 
# PAL: Complex PLDs (CPLD) 1984

- Need for **bigger** (functional capability), **smaller** (size), **faster** and **cheaper** technology
- MegaPAL: interconnection of four PALs -> **high power consumption**
- 1984: Altera introduced **CPLD** using **CMOS** (high density, low power) and **EPROM/EEPROM** (programmability)
- Can implement complex functions, smaller size, cheaper and faster


  
# PAL: Complex PLDs



- **Novelty: Central interconnect**
- In addition to programming SPLD (PAL), connections can also be programmed using **programmable interconnect matrix**
- This leads to increase in the complexity of software tools





  
# Programming CPLDs

- Text file generation for programming (remember fuses) -> Device programmer
- Deep knowledge of architecture and file format used by device programmer
- Prone to error, time consuming process and difficult to locate error
- Lead to development of HDL (functional description to text file for device programmer)




 
# Why FPGAs?

- **CPLD:** Based on **EEPROM** and hence, **non-volatile**
- Signals from a Logic Block can be connected to **only the neighbouring Logic blocks** (In FPGAs, they can travel great distances through the interconnect)
- **Can not support large designs** like ASIC




# FPGA Architecture


# FPGA (1984)

  

# FPGA (1984)

 


Required function

 


Truth table

a	b	c	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


Programmed LUT

 

# LUT

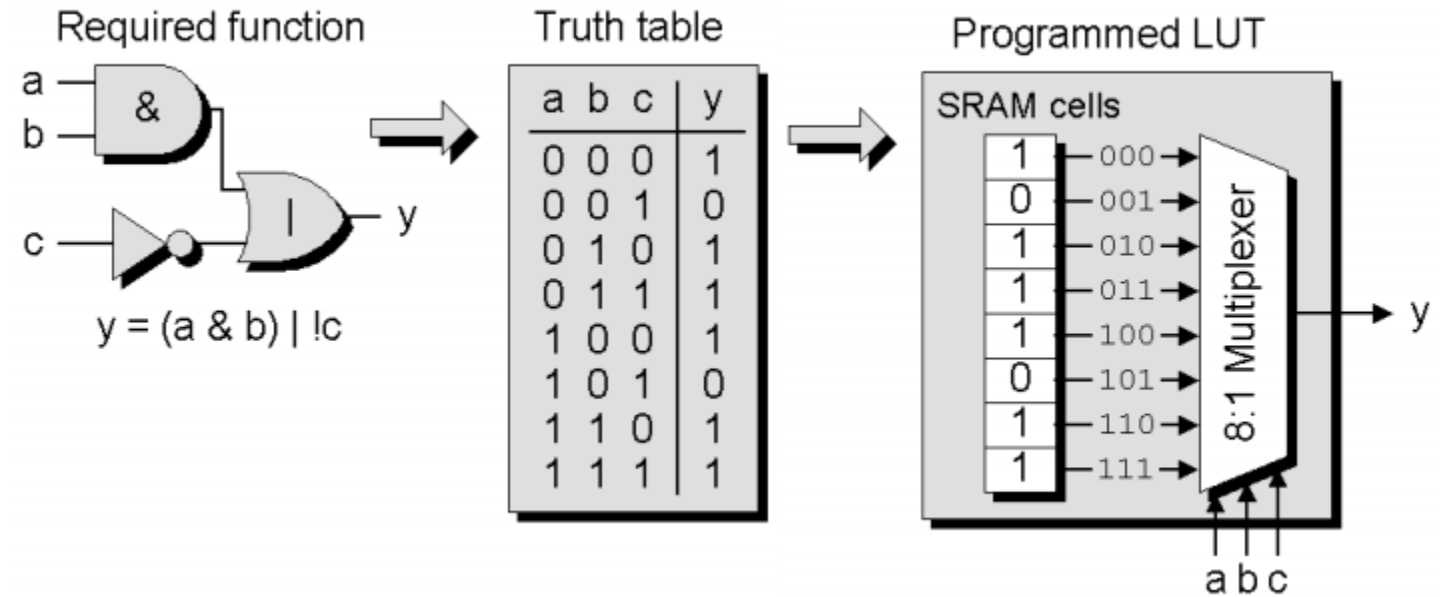


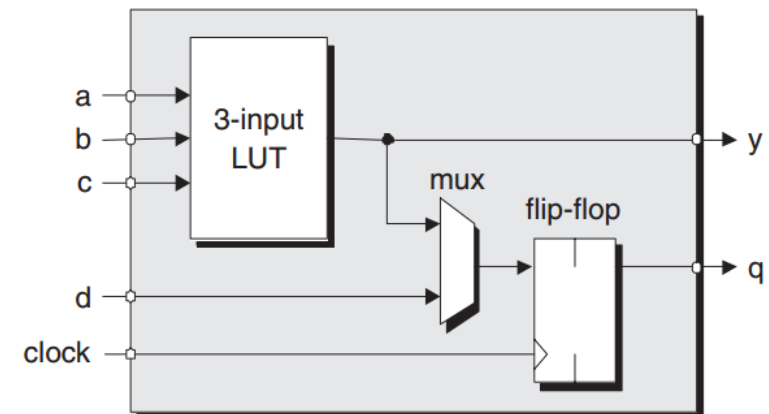- What is the difference between  $y$  and  $q$  outputs?


 
# Memory

**DRAM** (dynamic RAM, needs 'refresh' ~ 500 times/sec, 1 FETransistor)




- **DRAM: Dynamic RAM**
- A DRAM chip consists of a number of memory cells which can each hold 1-bit of data, stored in a capacitor.
- Due to the fact that **capacitors leak electric charge**, the state of the bit of information held by each memory cell will **eventually fade** unless the charge of the **capacitor is periodically refreshed** by the memory controller.
- The **memory controller** does this by reading the state of each memory cell and then writing the state back again.
- This is where **dynamic RAM** gets its name.

# Memory

- **SRAM: Static RAM**
- Whereas each bit of memory in DRAM is stored in a capacitor, SRAM uses **latches** to store the data.
- More space than DRAM and expensive
- No refreshing and hence, faster than DRAM
- Used in high-speed, low-capacity memory chips (L1 Cache)

**SRAM** (static RAM, no 'refresh' required, 6 FETransistors)


CMOS = complementary metal oxide silicon

 


 
# FPGA

- Islands of PLD surrounded by sea of programmable interconnects
- Based on CMOS and SRAM (EPROM or EEPROM in CPLD)
- FPGA Logic Blocks are implemented as LUTs (Look Up Tables) which are RAM based, while CPLDs implement sum-of-product style logic
- SRAM is mature technology and hence, efficient
- Easy and fast to program
- Less delay in data communication from one logic block to another



# FPGA

Feature	SRAM	Antifuse	E2PROM / FLASH
Technology node	State-of-the-art	One or more generations behind	One or more generations behind
Reprogrammable	Yes (in system)	No	Yes (in-system or offline)
Reprogramming speed (inc. erasing)	Fast	----	3x slower than SRAM
Volatile (must be programmed on power-up)	Yes	No	No (but can be if required)
Requires external configuration file	Yes	No	No
Good for prototyping	Yes (very good)	No	Yes (reasonable)
Instant-on	No	Yes	Yes
IP Security	Acceptable (especially when using bitstream encryption)	Very Good	Very Good
Size of configuration cell	Large (six transistors)	Very small	Medium-small (two transistors)
Power consumption	Medium	Low	Medium
Rad Hard	No	Yes	Not really