

# Review

①

## Bode plot using asymptotic curves

$$H(s) = \frac{100s}{s^2 + 420s + 8000}$$


$$= \frac{100s}{(s + 20)(s + 400)}$$

$$= \frac{100s}{20 \left(1 + \frac{s}{20}\right) \times 400 \left(1 + \frac{s}{400}\right)}$$

$$= \frac{\frac{100}{20 \times 400} \times s}{\left(1 + \frac{s}{20}\right) \left(1 + \frac{s}{400}\right)} = \frac{\frac{1}{80} \times s}{\left(1 + \frac{s}{20}\right) \left(1 + \frac{s}{400}\right)}$$

$$H(s) = \frac{1}{80} \times s \times \frac{1}{\left(1 + \frac{s}{20}\right)} \times \frac{1}{\left(1 + \frac{s}{400}\right)}$$

$$[H(s)] = \left[\frac{1}{80}\right] + [s] + \left[\frac{1}{1 + \frac{s}{20}}\right] + \left[\frac{1}{1 + \frac{s}{400}}\right]$$




$$[s] = [20 \log_{10} |\omega|] = 20 \log_{10} |\omega| \quad (2)$$

$\omega$	$ s $	$[s]$
0.01	0.01	$20 \log_{10}(0.01) = -40$ $20 \log_{10}(10^{-2})$
0.1	0.1	$20 \log_{10}(0.1) = -20$
1	1	$20 \log_{10}(10^0) = 0$
10	10	$20 \log_{10}(10^1) = +20$
100	100	$20 \log_{10}(10^2) = 40$
1000		


↑

Plot of  $[s]$
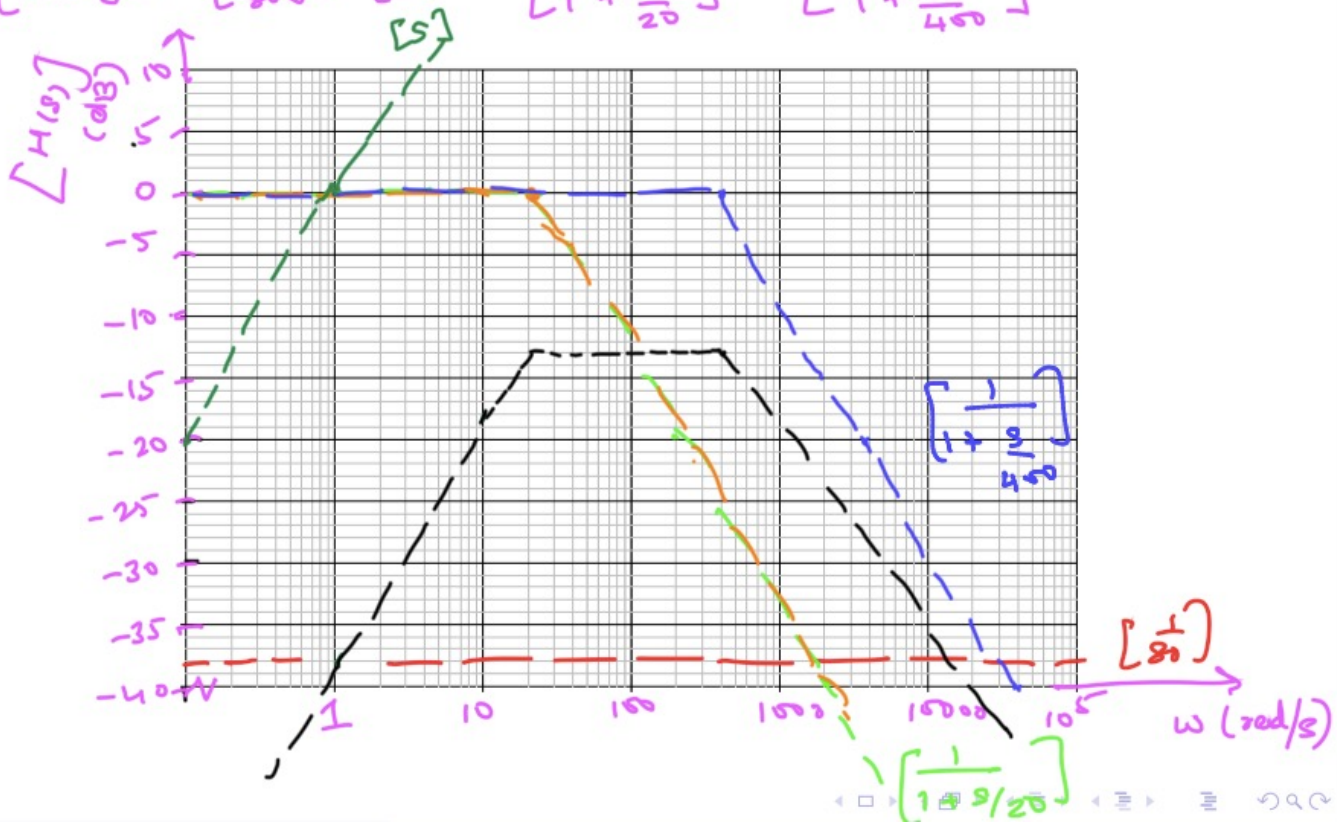
$$[H(s)] = \left[ \frac{1}{s^2} \right] + [s] + \left[ \frac{1}{1 + \frac{s}{20}} \right] + \left[ \frac{1}{1 + \frac{s}{400}} \right]$$



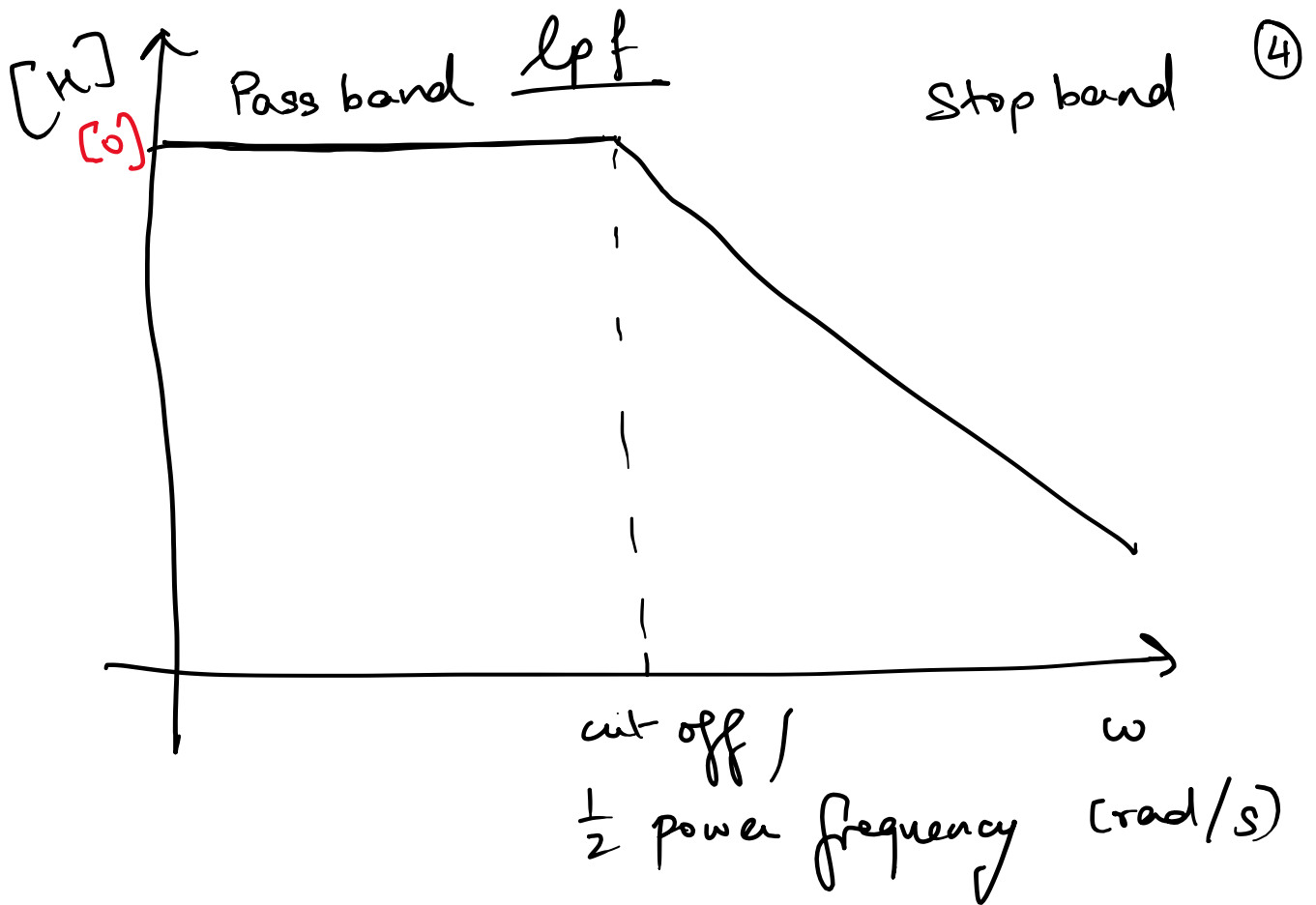Passive 2<sup>nd</sup> order band pass filter



$$H(s) = \frac{k}{s^n + a_{n-1}s^{n-1} + \dots + a_0}$$

active/passive  $n^{\text{th}}$  order lpf

↓  
number of poles / number of memory elements

$$\frac{1}{1 + s/p_1}$$


→

-20 dB/decade

$$\frac{1}{(1 + s/p_1)^2}$$

→

-40 dB/decade

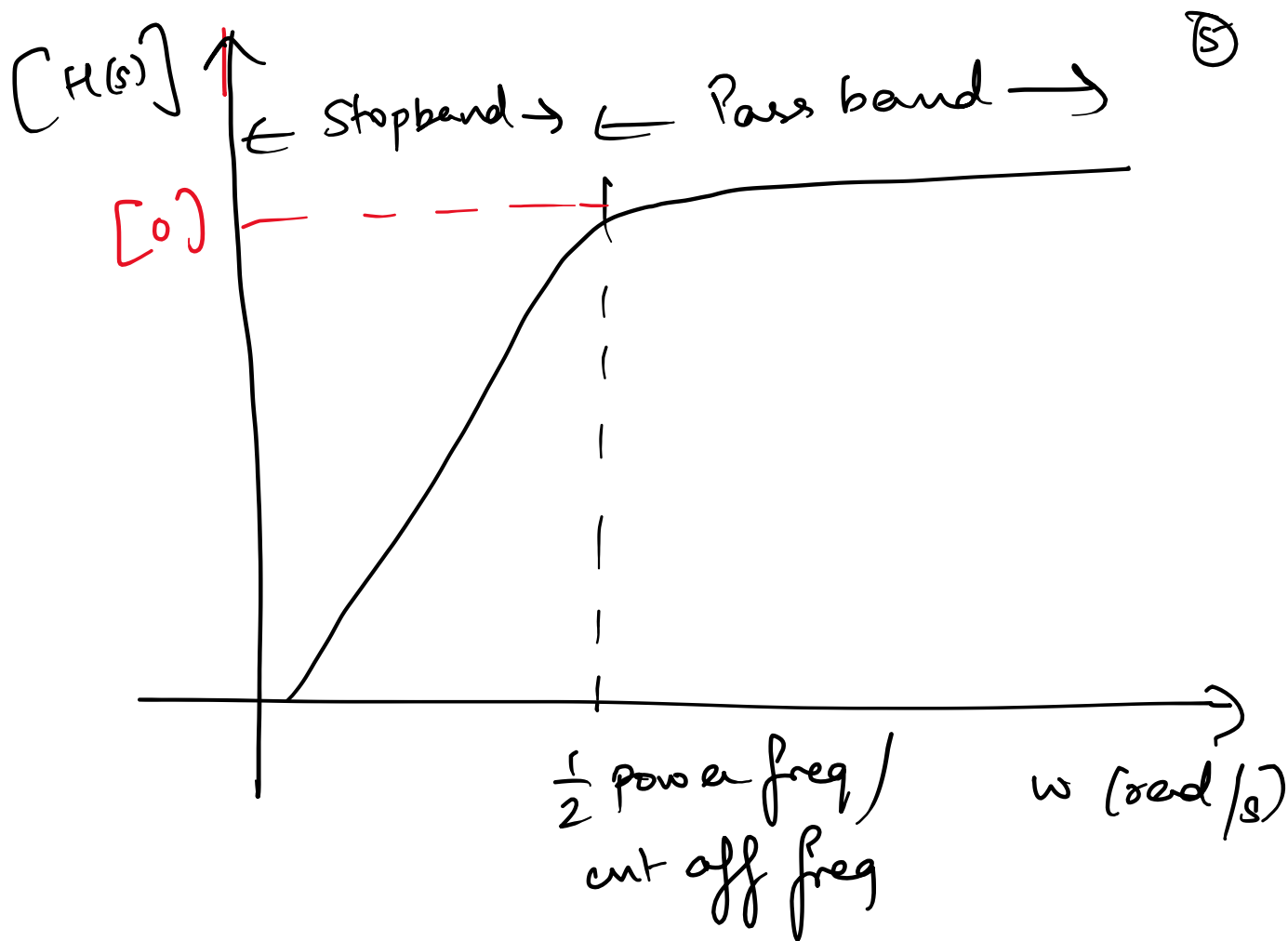


$$H(s) = \frac{K s^n}{s^n + a_{n-1} s^{n-1} + \dots + a_0}$$

→  $\frac{s}{s+a}$

active | passive  $n^{\text{th}}$  order hpf

# Band Pass filter

⑥

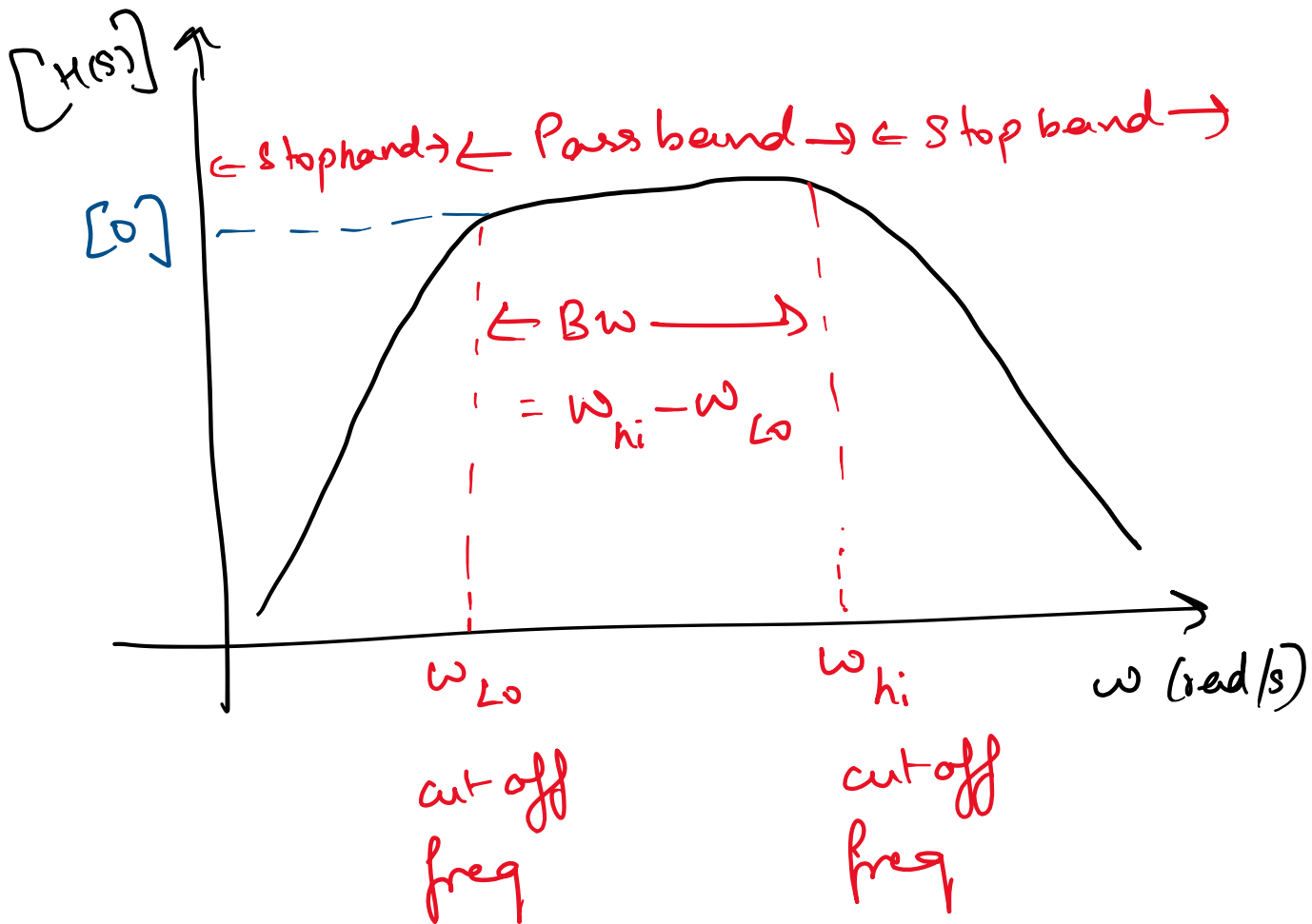


$$H(s) = \frac{k s^{n/2}}{s^n + a_{n-1} s^{n-1} + \dots + a_0}$$

min  $n = 2$  ( $n$  always even)  
active/passive  $n^{\text{th}}$  order bpf

$[H(\omega)]$


All pass filter


(7)

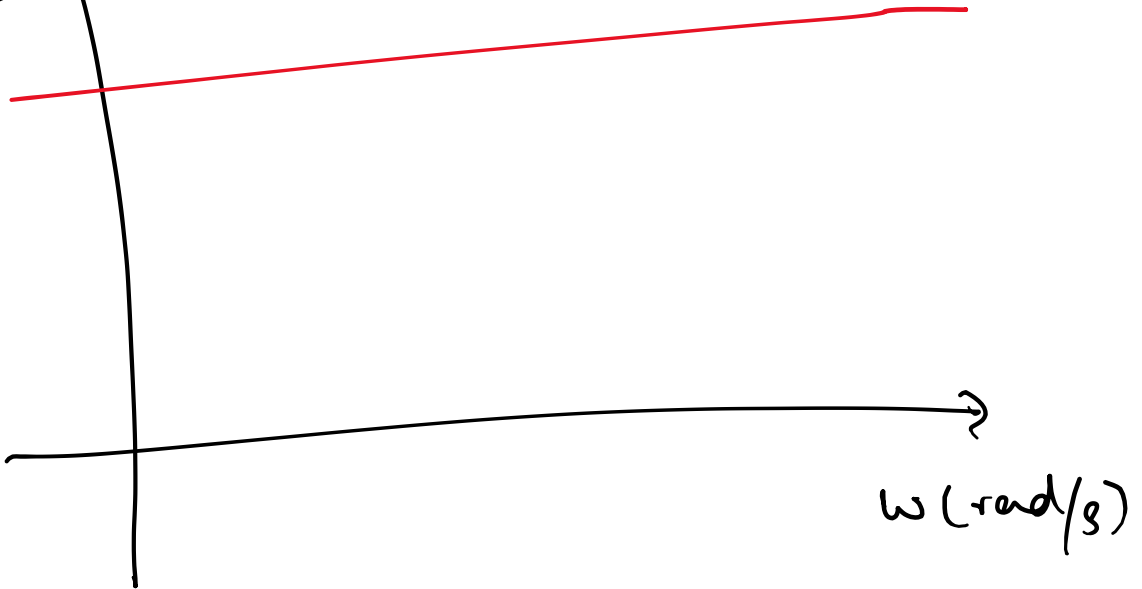

Band stop filter

$[H(\omega)]$

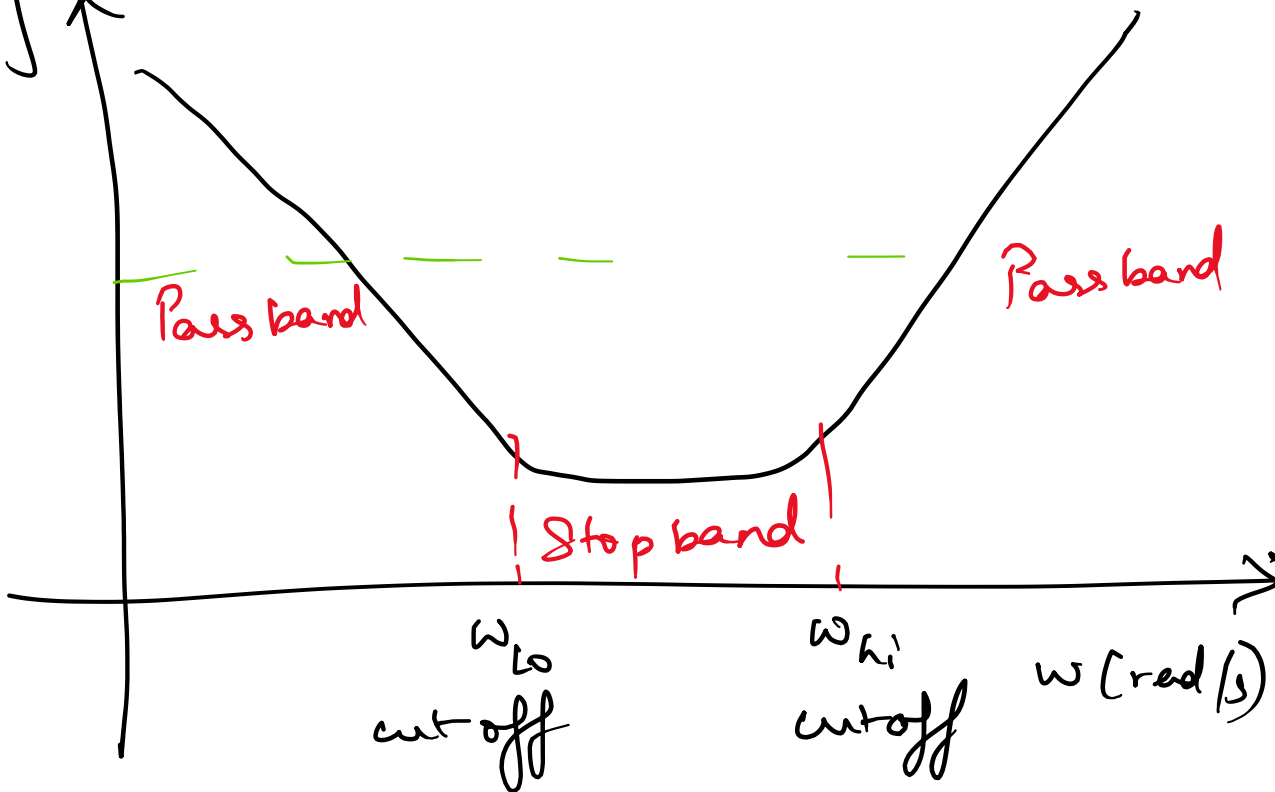


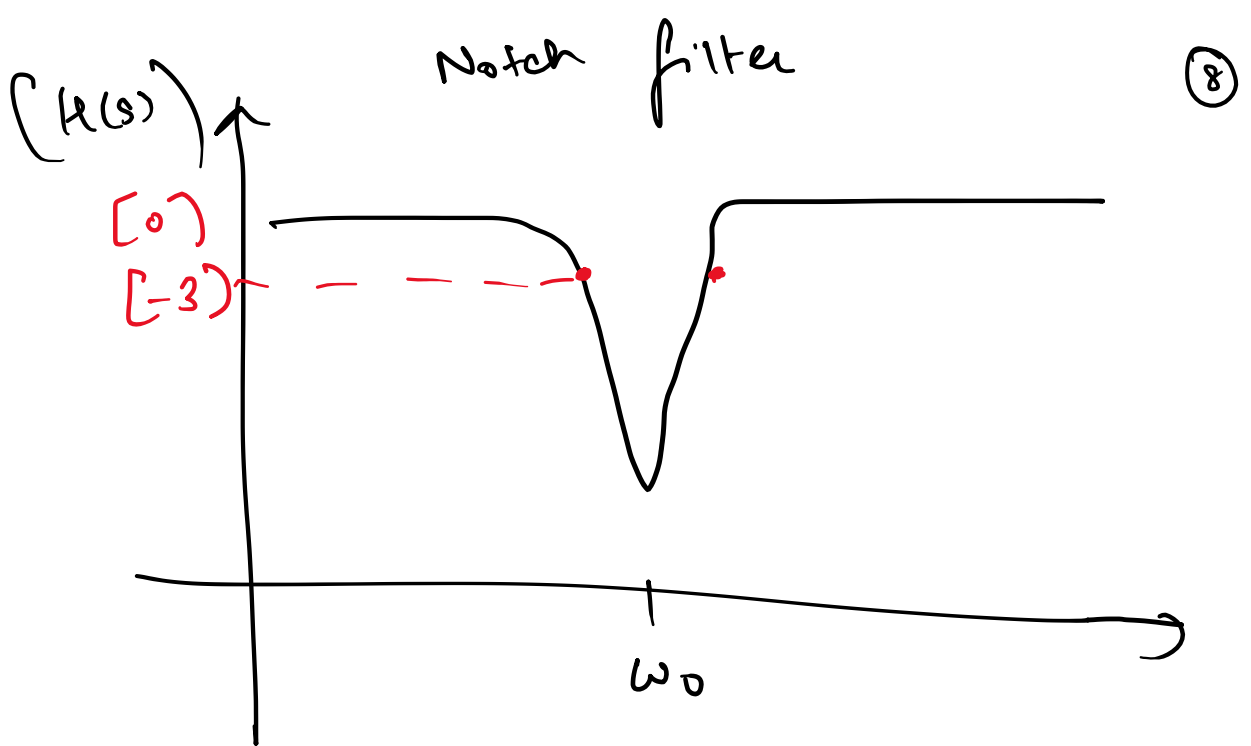

$$H(s) = \frac{k (s^2 + \omega_0^2)^{n/2}}{s^n + a_{n-1}s^{n-1} + \dots + a_0}$$



Parallel

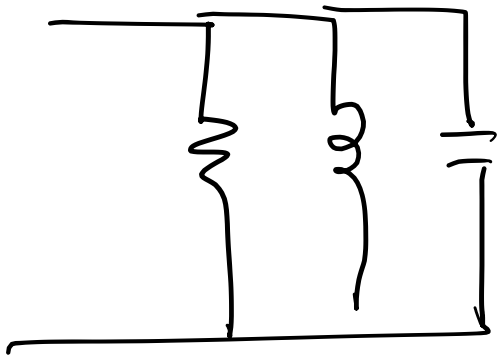


$$Y(\omega) = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

$$Y(\omega) = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

Series

④

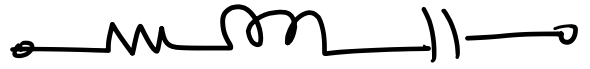

$$Z(\omega) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Resonant frequency

②  $\text{Im}\{Z\}$  or

$$\text{Im}\{Y\} = 0$$

$$\omega_0 C - \frac{1}{\omega_0 L} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 L = \frac{1}{\omega_0 C}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

16

$$Q = 2\pi \frac{\text{max energy stored in a ckt}}{\text{energy dissipated in T}}$$

$$Q = \omega_0 RC$$

$$Q = \frac{\omega_0 L}{R}$$

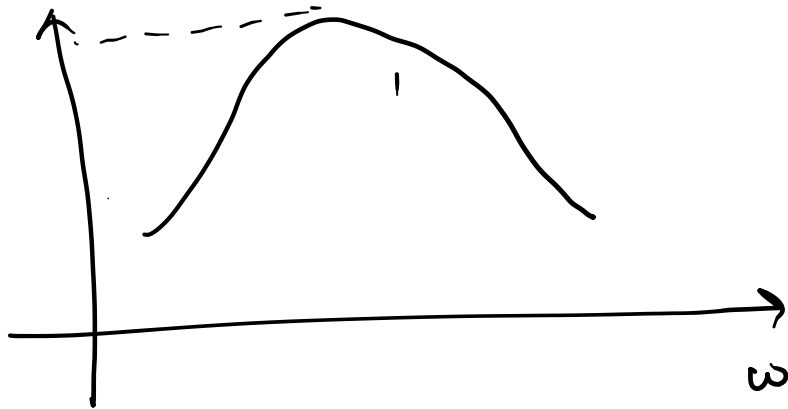

$$Q = \frac{BW}{\omega_0} = \frac{\omega_{hi} - \omega_{lo}}{\omega_0} \quad (\text{no unit})$$

High Q circuit is  $Q \geq 5$

(11)

- A parallel RLC circuit is built using  $L = 50\text{mH}$ ,  $C = 33\text{mF}$ . If  $Q_0 = 10$ , determine the value of  $R$ , and bandwidth.

$$L = 50 \times 10^{-3} \text{ H}$$

$$C = 33 \times 10^{-3} \text{ F}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50 \times 33 \times 10^{-6}}} = 24.62 \text{ rad/s}$$

$$Q = \omega_0 RC$$

$$\Rightarrow R = \frac{Q}{\omega_0 \times C} = 12.31 \Omega$$

$$\text{Bandwidth} = Q \times \omega_0 = 246.18 \text{ rad/s}$$

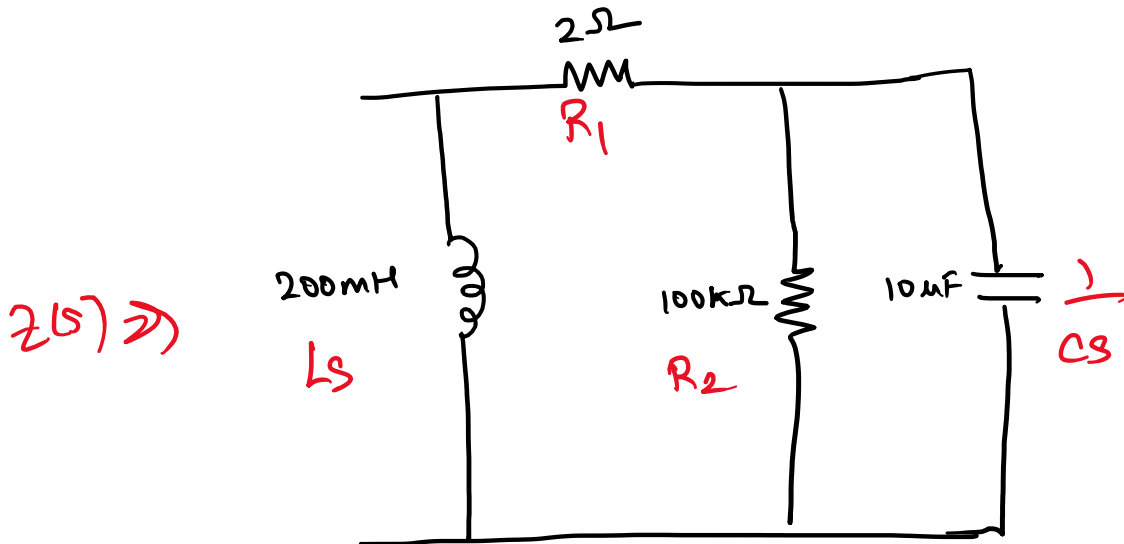- What is the input admittance of the network?  
Determine the resonant frequency and the bandwidth of the network.



$$Z(s) = \left\{ \left[ \frac{1}{Cs} \parallel R_2 \right] + R_1 \right\} \parallel L_s$$

$$= \left\{ \frac{\frac{R_2}{Cs} + R_1}{R_2 + \frac{1}{Cs}} \right\} \parallel L_s$$

$$= \left\{ \frac{R_2}{1 + R_2 Cs} + R_1 \right\} \parallel L_s$$

$$= \frac{R_1 + R_2 + R_1 R_2 Cs}{1 + R_2 Cs} \parallel L_s$$

(13)

$$Y(s) = \frac{1}{Ls} + \frac{1 + R_2Cs}{R_1 + R_2 + R_1R_2Cs}$$

$$= \frac{R_1 + R_2 + R_1R_2Cs + Ls + R_2LCs^2}{(R_1 + R_2 + R_1R_2Cs)Ls}$$

Solve it numerically

- Find the bandwidth of the each of the response curves.

