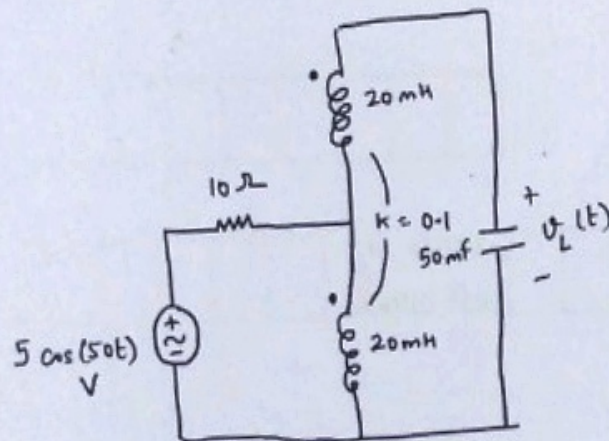



Jai Mangal

Quiz 3 (30 marks)


1. (15 marks) For the following circuit, write the mesh equations (in phasor domain) and steps required to compute the load voltage V_L . Detailed calculations can be omitted since they are not required.



2. (15 marks) In the following circuit, find the time averaged power delivered to the load.

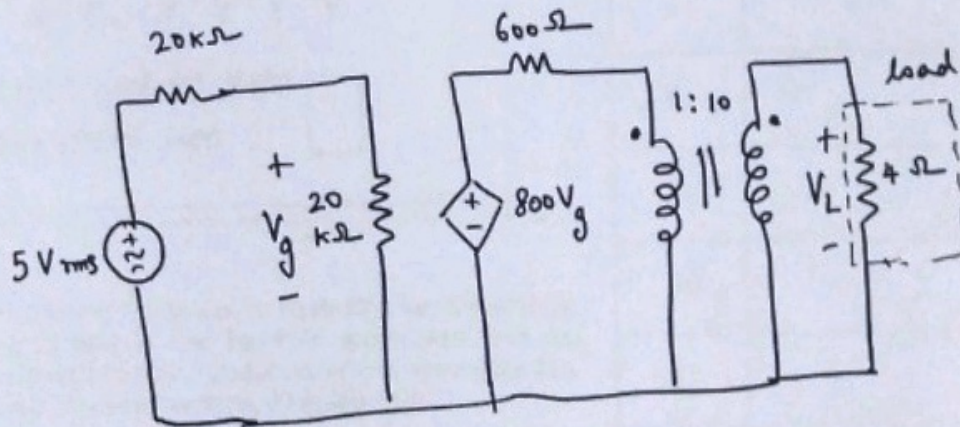

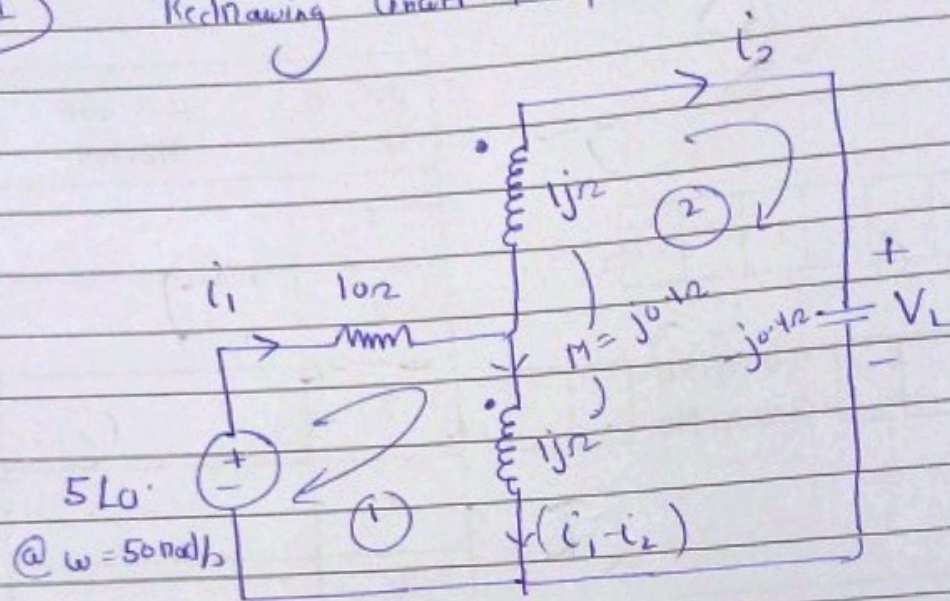Soln 1) Redrawing circuit in phasor domain:-



$$\Rightarrow X_L = j\omega L$$

$$X_{20mH} = j \times 50 \times 20 \times 10^{-3} = j1\Omega$$

$$\Rightarrow X_C = \frac{1}{j\omega C} = -j/\omega C = \frac{-j}{50 \times 50 \times 10^{-3}} = -j0.4\Omega$$

$$k = M / \sqrt{L_1 L_2}$$

$$M = k \sqrt{L_1 L_2} = 0.1 \times \sqrt{20 \times 20 \times 10^{-6}}$$

$$= 0.1 \times \sqrt{400 \times 10^{-6}}$$

$$= 0.1 \times \sqrt{4 \times 10^{-4}}$$

$$= 0.1 \times 2 \times 10^{-2}$$

$$= 2 \times 10^{-3} = 2mH$$

$$X_{2mH} = j\omega M = j \times 50 \times 2 \times 10^{-3} = j0.1\Omega$$

Let current in loop ① is i_1 and in loop ② is i_2 :-

⇒ Mesh equation for loop ① :-

$$510 - 10(i_1) - 1j(i_1 - i_2) + j0.1(i_2) = 0 \quad \text{--- (1)}$$

③

⇒ Mesh equation for loop ② :-

$$-(-j0.4)(i_2) + 1j(i_1 - i_2) - j0.1(i_2) - 1j(i_2) + j0.1(i_1 - i_2) = 0$$

③


--- (2)

By solving equation ① and ②, we can find i_1 and i_2 .

$$V_L = i_2 \times (-j0.4\Omega) \quad \text{--- (3)} = V_L/0 \quad \text{③}$$

Now, from putting the value of i_2 in ③, we can find V_L and convert it into time domain.
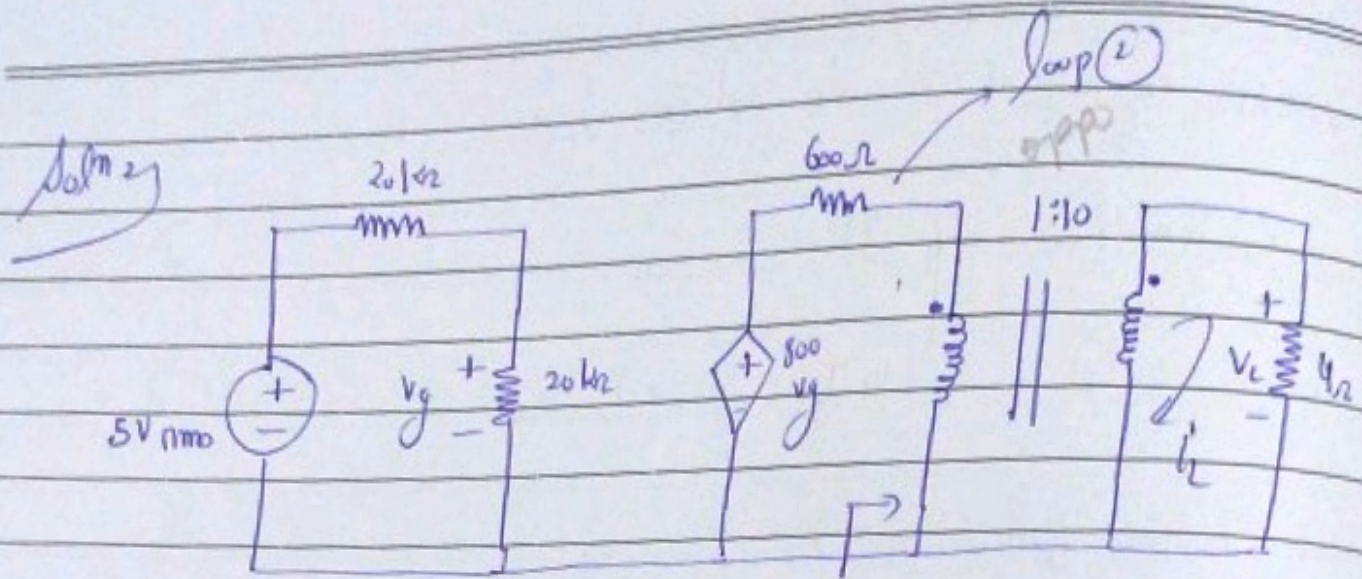
$$V_L(t) = V_L \cos(50t + 0) \quad \text{V} \quad \text{--- B}$$




$$V_g = \frac{5 \times 20k}{20k + 20k} \quad (\because a = 10)$$

$$\Rightarrow \frac{5 \times 20k}{40k} = 5/2 = 2.50 \text{ rms}$$

$$Z_{in} = Z_L / a^2 = 4 / 10^2 = 4 / 100 = 0.04 \Omega$$

Redrawing loop 2:-

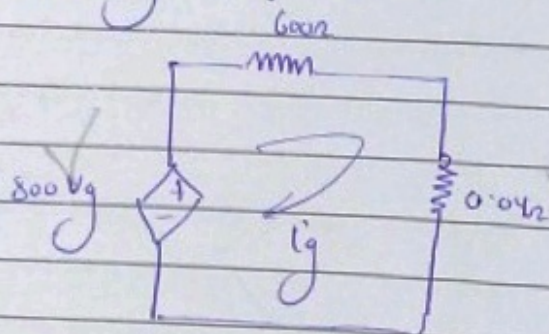

$$800 \times V_g = 800 \times 2.5 = 2000 \text{ V rms}$$

$$i_g = \frac{2000}{600 + 0.04} = \frac{2000}{600.04} = 3.33 \text{ A rms}$$

$$\frac{i_L}{i_g} = \frac{1}{a} \quad (\because M \text{ is opposite})$$

$$\Rightarrow \frac{i_L}{3.33} = \frac{1}{10} \quad (3)$$

$$\Rightarrow i_L = 0.33 \text{ A rms}$$

$$P_{\text{load}} = (i_L)^2 \times 4\Omega$$

$$= (0.33)^2 \times 4\Omega$$

$$= 0.4356 \text{ W} \quad \text{---} \quad (3)$$

↪ time averaged power