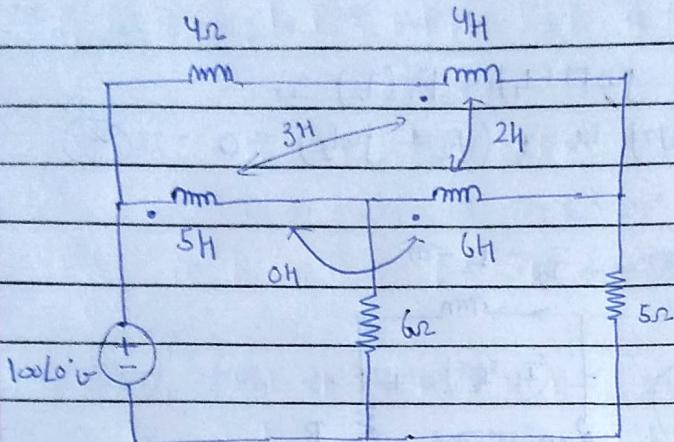


Tutorial 8

Date: / /

Page No.



(a) Write equations in terms of $\dot{I}_1(j\omega)$, $\dot{I}_2(j\omega)$, $\dot{I}_3(j\omega)$:-

$$X_C = 1/j\omega C \Omega$$

$$X_L = j\omega L \Omega$$

Now, Reactance of the 5H inductor is,

$$X_{5H} = j5\omega$$

Reactance of the 4H inductor is,

$$X_{4H} = j4\omega$$

Reactance of the 6H inductor is,

$$X_{6H} = j6\omega$$

Reactance of the 3H mutual inductance is,

$$X_{3H} = j3\omega$$


Reactance of the 2H mutual inductance is,

$$X_{2H} = j2\omega$$

Reactance of the 0H mutual inductance is,

$$X_{0H} = 0$$

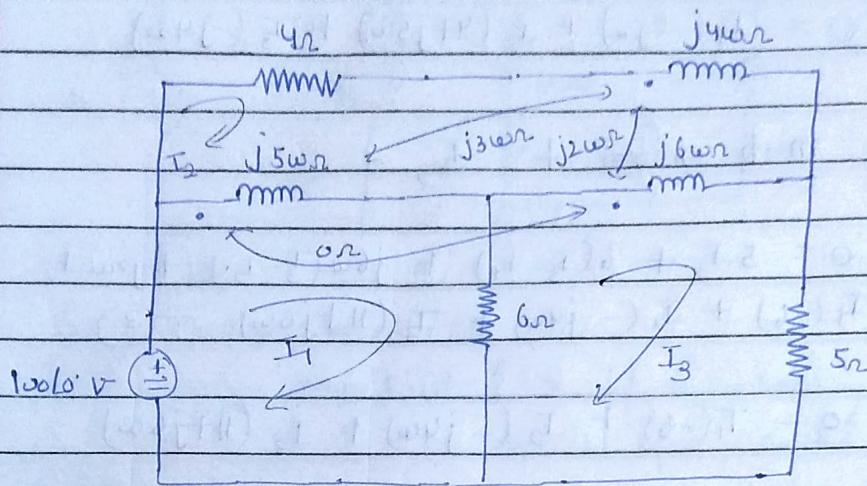→ Redrawing the circuit in the phasor domain:



From figure, the currents $I_1 - I_2$, I_2 and $I_3 - I_2$ are all entering the dotted terminal of their coils, so the mutual inductance is added to the self-inductance when these current directions are used.

→ Using mesh analysis at I_1 :

$$\begin{aligned} 100L_0 &= j5\omega(I_1 - I_2) + j3\omega I_2 + 6(I_1 - I_3) \\ &= I_1(6 + j5\omega) + I_2(-j2\omega) + I_3(-6) \quad (1) \end{aligned}$$

$$\Rightarrow 100 = I_1(6 + j5\omega) + I_2(-j2\omega) - 6I_3$$

→ Using mesh analysis at I_2 :

$$0 = 4I_2 + j4\omega I_2 + j2\omega(I_3 - I_2) + j3\omega(I_1 - I_2) - (j6\omega(I_3 - I_2) + j5\omega(I_1 - I_2))$$

$$\Rightarrow I_1(j3\omega - j5\omega) + I_2(4 + j4\omega - j2\omega - j3\omega + j6\omega - j2\omega + j5\omega - j3\omega) + I_3(j2\omega - j6\omega)$$

$$= I_1(-j2\omega) + I_2(4+j5\omega) + I_3(-j4\omega) \quad (2)$$

$$0 = I_1(-2j\omega) + I_2(4+j5\omega) + I_3(-j4\omega)$$

→ Using mesh analysis at I_3 ,

$$\begin{aligned} 0 &= 5I_3 + 6(I_3 - I_1) + j6\omega(I_3 - I_2) + j2\omega I_2 \\ \Rightarrow I_1(-6) + I_2(-j4\omega) + I_3(11+j6\omega) &= (3) \end{aligned}$$

$$0 = I_1(-6) + I_2(-j4\omega) + I_3(11+j6\omega)$$

(b) Now, to find $I_3(j\omega)$ substitute in (1), (2) and (3) by
 $\omega = 2 \text{ rad/s}$,

First, substitute in (1).

$$\begin{aligned} I_{00} &= I_1(6+j5x_2) + I_2(-j2x_2) + I_3(-6) \\ &= I_1(6+j10) + I_2(-j4) + I_3(-6) \quad (4) \end{aligned}$$

Substitute in (2),

$$\begin{aligned} 0 &= I_1(-j2x_2) + I_2(4+j5x_2) + I_3(-j4x_2) \\ \Rightarrow I_1(-j4) + I_2(4+j10) + I_3(-j8) &= (5) \end{aligned}$$

Substitute in (3),


$$\begin{aligned} 0 &= I_1(-6) + I_2(-j4x_2) + I_3(11+j6x_2) \\ &= I_1(-6) + I_2(-j8) + I_3(11+j12) \quad (6) \end{aligned}$$

By solving (4), (5), (6) for I_1 , I_2 and I_3 ,

$$I_3 = 3.52 - j3.5$$

$$= 4.3 \angle -54.3^\circ \text{ A} \quad \underline{\text{A}}$$

Δm
2
(ii)

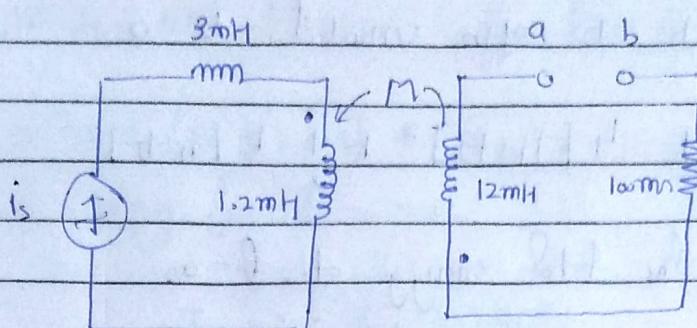

$$k = 0.75$$

$$L_s = 5 \text{ Cg Root mA}$$

Total energy stored at $t=0$ and $t=5\text{ms}$.

a-b is open circuited


$$k = \frac{M}{\sqrt{4L_s}}$$

$$\text{now, } M = k\sqrt{4L_s}$$

$$= 0.75 \sqrt{1.2 \times 10^{-3} \times 12 \times 10^{-3}}$$

$$= 7.85 \times 10^{-3} \text{ H}$$

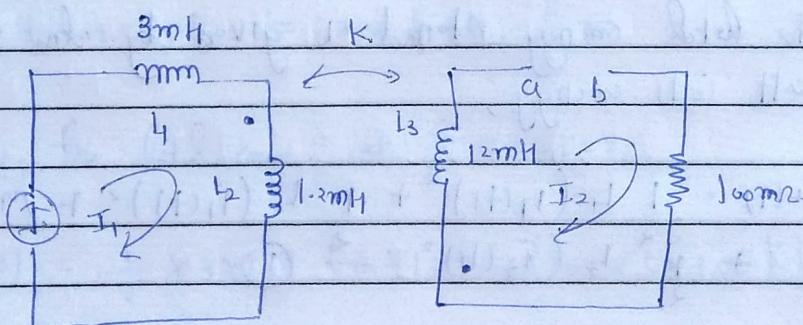From figure, the two currents i_1 and i_2 are entering the dotted terminals of their coils, so the mutual energy is added to self inductance energy.



⇒ The total energy stored is given by the summation of all coils energy :-

$$w(t) = \frac{1}{2} L_1 [i_1(t)]^2 + \frac{1}{2} L_2 [i_2(t)]^2 + M[i_1(t)][i_2(t)]$$

$$+ \frac{1}{2} L_3 [i_3(t)]^2$$

Since A-B is open circuit, $I_2 = 0$

$$W(t) = \frac{1}{2} L_1 (i_1(t))^2 + \frac{1}{2} L_2 (i_2(t))^2$$

Calculating the total energy at $\theta = 0^\circ$.

$$\begin{aligned} w(0 \text{ ms}) &= \frac{1}{2} \times 3 \times 10^{-3} [5 \times 10^{-3} C_0 (200 \times 0)]^2 + \\ &\quad \frac{1}{2} \times 1.2 \times 10^{-3} [5 \times 10^{-3} C_0 (200 \times 0)]^2 \\ &= 52.5 \text{nJ } A \end{aligned}$$

\Rightarrow Calculating the total energy at $\theta = 5 \times 10^{-3} \text{ rad}$

$$\begin{aligned} w(5 \text{ ms}) &= \frac{1}{2} \times 3 \times 10^{-3} [5 \times 10^{-3} C_0 (200 \times 5 \times 10^{-3})]^2 + \\ &\quad \frac{1}{2} \times 1.2 \times 10^{-3} [5 \times 10^{-3} C_0 (200 \times 5 \times 10^{-3})]^2 \\ &= 15.32 \times 10^{-9} \text{ J } B \\ &= (15.32 \text{nJ }) \circ B \end{aligned}$$

(b) \rightarrow The total energy stored is given by the summation of all coil energy;

$$\begin{aligned} w(t) &= \frac{1}{2} L_1 (i_1(t))^2 + \frac{1}{2} L_2 (i_2(t))^2 + M (i_1(t) i_2(t)) \\ &\quad + \frac{1}{2} L_3 (i_3(t))^2 \xrightarrow{\text{eqn 1}} \end{aligned}$$

since, A-B is short circuited, the value of i_2 needed to be determined using mesh analysis at 5.

$$\begin{aligned} 0 &= j 12 \times 10^{-3} w I_2 + 100 \times 10^{-3} I_2 + j \cdot 2.85 \times 10^{-3} w I_1 \\ &= I_2 (j 12 \times 10^{-3} \times 200 + 100 \times 10^{-3}) + I_1 (2.85 \times 10^{-3} \times 200) \\ &= I_2 (j 2.4 + 0.1) + I_1 (j 0.57) \end{aligned}$$

$$\Rightarrow \text{But } I_1 = 5 \times 10^{-3} \cos(200t) \text{ for } t=0, I_1 = 5 \times 10^{-3}$$

$$0 = I_2 (j2.4 + 0.1) + 5 \times 10^{-3} \times (j0.5)$$

now, solving for I_2 :

$$I_2 = \frac{-j2.85 \times 10^{-3}}{0.1 + j2.4}$$

$$= 1.1865 \times 10^{-3} / -177.6^\circ A$$

$$\Rightarrow i_2(+)=1.1865 \cos(200t - 177.6^\circ) A$$

→ Substitute by the values of i_1 and i_2 in (1) to calculate the total energy stored.

→ now, calculating the total energy at $t=0$.

$$\omega(0m) = \frac{1}{2} \times 3 \times 10^{-3} (5 \times 10^{-3})^2 + \frac{1}{2} \times 1.2 \times 10^{-3} (5 \times 10^{-3})^2$$

$$+ 3.85 \times 10^{-3} (5 \times 10^{-3}) (1.1865 \times 10^{-3} \cos(0 - 177.6^\circ))$$

$$+ \frac{1}{2} \times 1.2 \times 10^{-3} (1.1865 \times 10^{-3} (0 - 177.6^\circ))^2$$

$$= 4.404 \times 10^{-8} J = 44.04 mJ \quad B$$

→ Calculating the total energy at $t = 5 \times 10^{-3} s$,

$$\omega(5m) = \frac{1}{2} \times 3 \times 10^{-3} (5 \times 10^{-3} \cos(200 \times 5 \times 10^{-3}))^2$$

$$+ \frac{1}{2} \times 1.2 \times 10^{-3} (5 \times 10^{-3} \cos(200 \times 5 \times 10^{-3}))^2$$

$$+ 3.85 \times 10^{-3} [5 \times 10^{-3}] [1.1865 \times 10^{-3} \cos(200 \times 5 \times 10^{-3} - 177.6^\circ)]$$

$$+ \frac{1}{2} \times 1.2 \times 10^{-3} (1.1865 \times 10^{-3} \cos(200 \times 5 \times 10^{-3} - 177.6^\circ))^2$$

$$= 8.995 mJ \quad C$$

Sol(3) $Z_{in} = Z_{11} + \frac{\omega^2 M^2}{Z_2} \quad \text{--- (1)}$

and,

$$\begin{aligned} Z_{11} &= R_1 + jL_1\omega \\ &= (10 + j2 \times 10^6 \times 10) \\ &= 10 + j20 \times 10^{-6} \Omega \quad \text{--- (2)} \end{aligned}$$

and,

$$\begin{aligned} Z_{22} &= R_2 + j\omega L_2 + Z_L \\ &= 1 + j1 \times 10^6 \times 10 + Z_L \\ &= 1 + j10^5 + Z_L \quad \text{--- (3)} \end{aligned}$$

→ Substitute by (2) and (3) in (1) and find value of ω and M to get the expression for the input impedance in terms of Z_L .

$$Z_{in}(Z_L) = 10 + j20 \times 10^{-6} + \frac{10^2 (500 \times 10^{-9})^2}{1 + j10^5 + Z_L}$$

→ now, calculating Z_{in} when $Z_L = 1\Omega$

$$\begin{aligned} Z_{in}(1\Omega) &= 10 + j20 \times 10^{-6} + \frac{10^2 (500 \times 10^{-9})^2}{1 + j10^5 + 1} \\ &= 10 + j2 \times 10^{-5} \Omega \quad \text{B} \end{aligned}$$

(b) Z_{in} when, $Z_L = j\Omega$

$$\begin{aligned} Z_{in}(j\Omega) &= 10 + j20 \times 10^{-6} + \frac{10^2 (500 \times 10^{-9})^2}{1 + j10^5 + j} \\ &= 10 + j1.999 \times 10^{-5} \Omega \quad \text{B} \end{aligned}$$

(c) Z_{in} when, $Z_L = -j\Omega$

$$Z_{in}(-j\omega) = I_0 + j2 \times 10^6 + \frac{I_0^2 (500 \times 10^9)^2}{1 + j10^5 + (j)}$$

$$= 10 + j2 \times 10^5 \Omega \quad \text{Ans}$$

(d) Z_{in} when $Z_L = 5L33 \Omega$

$$Z_{in}(5L33) = I_0 + j2 \times 10^6 + \frac{I_0^2 (500 \times 10^9)^2}{1 + j10^5 + 5L33}$$

$$= 10 + j1.999 \times 10^5 \Omega \quad \text{Ans}$$