

Initial Condition of C

(1)


$$\mathcal{L}\{i_c(t)\} = \mathcal{L}\left\{\frac{dV_c}{dt}\right\}$$

$$\Rightarrow I_c(s) = C \left[s V_c(s) - V_c(0^-) \right]$$


$$sC V_c(s) = I_c(s) + C V_c(0^-) \quad \frac{1}{s} sC$$

$$\Rightarrow V_c(s) = \frac{I_c(s)}{sC} + \frac{V_c(0^-)}{s}$$

Voltage source


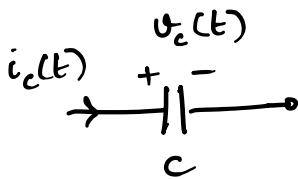


\equiv

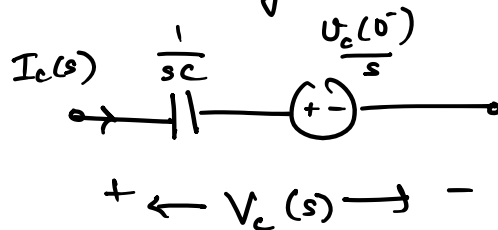

Redo the previous problem

$$V_c(0^-) = 1 \text{ V}$$

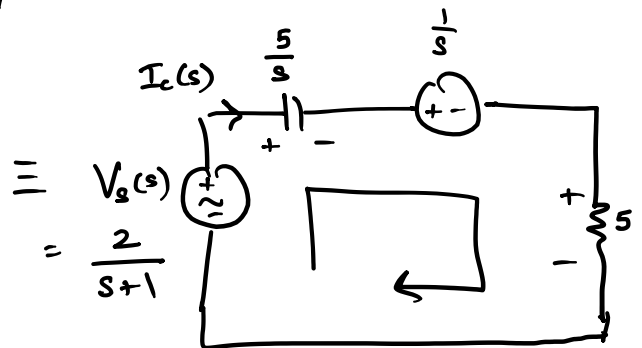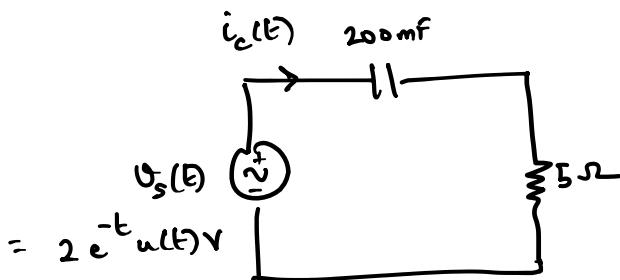

$$+V_s(s) - I_c(s) \times \frac{5}{s} - \frac{1}{s} - I_c(s) \times 5 = 0$$

$$\Rightarrow I_c(s) \left(\frac{5}{s} + 5 \right) = \frac{2}{s+1} - \frac{1}{s}$$

$$\Rightarrow I_c(s) \times 5 \left(\frac{1+s}{s} \right) = \frac{2}{s+1} - \frac{1}{s}$$

$$\Rightarrow I_c(s) = \frac{2/5 s}{(s+1)^2} - \frac{1/5}{(s+1)} = \frac{\frac{2}{5}(s+1-1)}{(s+1)^2} - \frac{1/5}{s+1}$$

$$\Rightarrow \mathcal{I}_c(s) = \frac{2/s}{s+1} - \frac{2/s}{(s+1)^2} - \frac{1/s}{(s+1)}$$


(2)

$$= \frac{1/s}{s+1} - \frac{2/s}{(s+1)^2}$$

$$\Rightarrow i_c(t) = \frac{1}{s} e^{-t} u(t) - \frac{2}{s} t e^{-t} u(t) \quad A$$


③

→

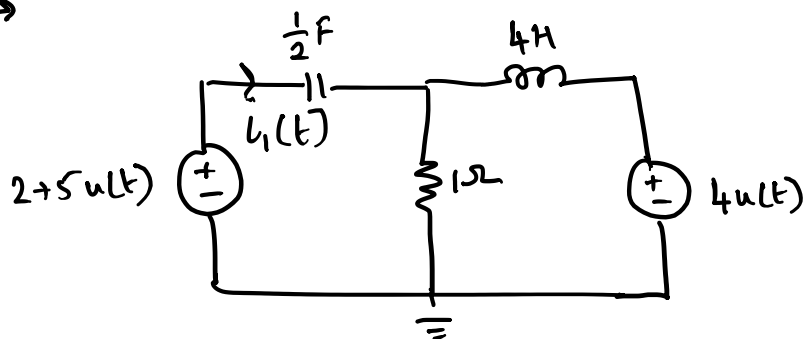

Yes there are initial conditions


At $t < 0$

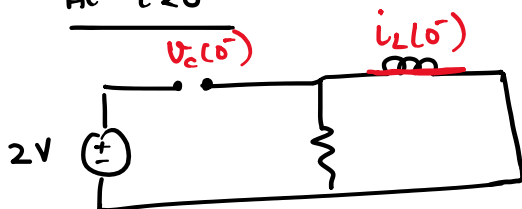

$$i_L(0^-) = 0 \text{ A}$$

$$V_C(0^-) = +2 \text{ V}$$

At $t > 0$

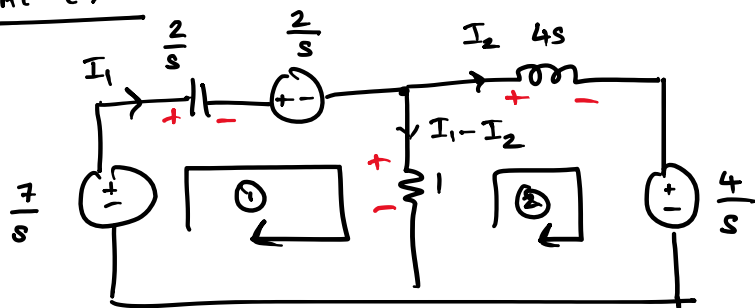

mesh (1)

$$+\frac{7}{s} - I_1 \times \frac{2}{s} - \frac{2}{s} - (I_1 - I_2)1 = 0$$

$$I_1 \left(\frac{2}{s} + 1 \right) + I_2 (-1) = \frac{5}{s} \quad \text{--- (1)}$$

mesh (2)

$$+1(I_1 - I_2) - 4s \times I_2 - \frac{4}{s} = 0$$

$$I_1(1) + I_2(-1 - 4s) = \frac{4}{s} \quad \text{--- (2)}$$

$$\textcircled{1} \times (4s+1) : \left[I_1 \left(\frac{2}{s} + 1 \right) - I_2 = \frac{5}{s} \right] \times (4s+1)$$

$$I_2(1) - I_2(4s+1) = \frac{4}{s}$$

(4)

$$I_1 \left(\frac{2}{s} + 1 \right) (4s+1) - I_2 (4s+1) = \frac{5}{s} (4s+1)$$

$$\ominus I_1 (1) \oplus I_2 (4s+1) = \ominus \frac{4}{s}$$

$$I_1 \left[\left(\frac{2}{s} + 1 \right) (4s+1) - 1 \right] = \frac{5}{s} (4s+1) - \frac{4}{s}$$

$$\Rightarrow I_1 \left(8 + 4s + \frac{2}{s} + 1 - 1 \right) = 20 + \frac{1}{s}$$

$$\Rightarrow I_1 = \frac{20 + \frac{1}{s}}{4s + \frac{2}{s} + 8} = \frac{20s + 1}{4s^2 + 8s + 2}$$

$$I_1 = \frac{20 \left(s + \frac{1}{20} \right)}{4 \left(s^2 + 2s + \frac{1}{2} \right)} = \frac{5 \left(s + \frac{1}{20} \right)}{s^2 + 2s + \frac{1}{2}}$$

Roots of $s^2 + 2s + \frac{1}{2} = 0$

$$s = \frac{-2 \pm \sqrt{4 - 4 \times \frac{1}{2}}}{2} = \frac{-2 \pm \sqrt{2}}{2} = -1 \pm \frac{1}{\sqrt{2}}$$

$$\Rightarrow I_1(s) = \frac{5 \left(s + \frac{1}{20} \right)}{\left(s + 1 - \frac{1}{\sqrt{2}} \right) \left(s + 1 + \frac{1}{\sqrt{2}} \right)} = \frac{A}{\left(s + 1 - \frac{1}{\sqrt{2}} \right)} + \frac{B}{\left(s + 1 + \frac{1}{\sqrt{2}} \right)}$$

$$\Rightarrow 5 \left(s + \frac{1}{20} \right) = A \left(s + 1 + \frac{1}{\sqrt{2}} \right) + B \left(s + 1 - \frac{1}{\sqrt{2}} \right)$$

$$\text{Let } s = -1 - \frac{1}{\sqrt{2}}$$

$$\Rightarrow 5 \left(-1 - \frac{1}{\sqrt{2}} + \frac{1}{20} \right) = B \left(-1 - \frac{1}{\sqrt{2}} + 1 - \frac{1}{\sqrt{2}} \right) = -B \left(\frac{2}{\sqrt{2}} \right)$$

$$\Rightarrow B = -5.86$$

Compare coeff of s

$$5 = A + B \Rightarrow A = 5 - B = 10.86$$





$$\Rightarrow \underline{I}_1(s) = \frac{10.86}{s + 0.29} + \frac{-5.86}{s + 1.7}$$

⑤

$$\Rightarrow i_1(t) = 10.86 e^{-0.29t} u(t) - 5.86 e^{-1.7t} u(t) \text{ A}$$

Stability Criterion

(6)

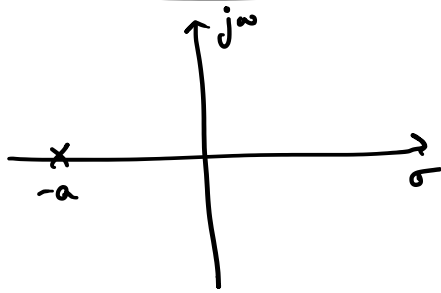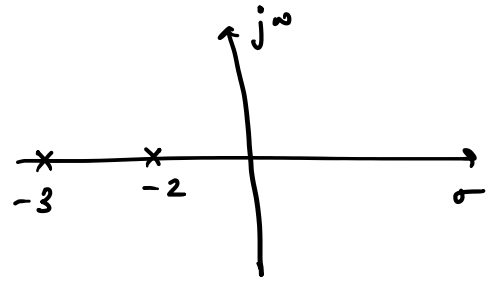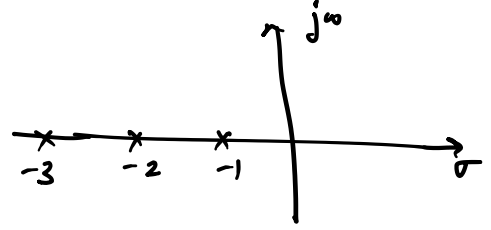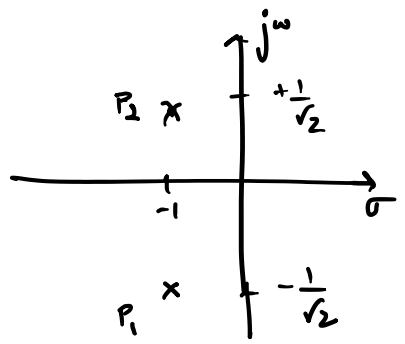$f(t)$	$F(s)$	Complex s plane
$e^{-at} u(t)$	$\frac{1}{s+a}$	
$3e^{-2t} u(t) + 4e^{-3t} u(t)$	$\frac{3}{s+2} + \frac{4}{s+3}$	<p>stable</p> 
	$\frac{8}{(s+1)(s+2)(s+3)}$	 <p>stable</p>
	$\frac{8}{(s+1+\frac{1}{\sqrt{2}}j)(s+1-\frac{1}{\sqrt{2}}j)}$	<p>Poles: $-1-\frac{1}{\sqrt{2}}$, $-1+\frac{1}{\sqrt{2}}$</p> <p>All left half plane so stable</p>
$Ae^{-t+\frac{1}{\sqrt{2}}jt} u(t) + Be^{-t+\frac{1}{\sqrt{2}}jt} u(t)$	$\frac{8}{(s+1+\frac{1}{\sqrt{2}}j)(s+1-\frac{1}{\sqrt{2}}j)}$	 <p>P_2 x $-1+\frac{1}{\sqrt{2}}j$</p> <p>P_1 x $-1-\frac{1}{\sqrt{2}}j$</p>

Summarize

7



$$F(s) = K \frac{(s-z_1)(s-z_2)\dots(s-z_n)}{(s-p_1)(s-p_2)\dots(s-p_m)}, \quad m \geq n$$

$z_1, z_2, z_3 \dots z_n \rightarrow$ complex frequencies called zeros

$p_1, p_2, \dots, p_m \rightarrow$ complex frequencies are called poles

$K =$ scaling constant

(1) If all poles lie on the left half s plane, then system is stable.

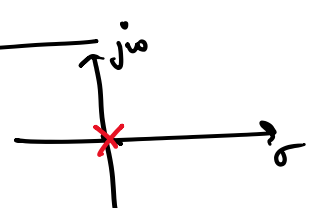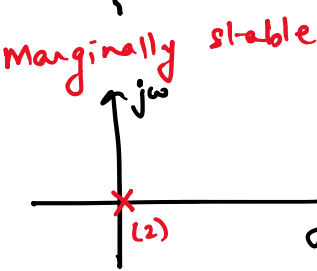$f(t)$	$F(s)$	
$u(t)$	$\frac{1}{s}$	
$t u(t)$	$\frac{1}{s^2}$	

M Marginally stable

Unstable

(2) 1st pole @ $s=0$ marginally stable but higher order/repeated poles are unstable


8

Complex s plane

$$f(t) \quad \cos(\omega_0 t) u(t)$$

$$F(s) = \frac{s}{s^2 + \omega_0^2}$$

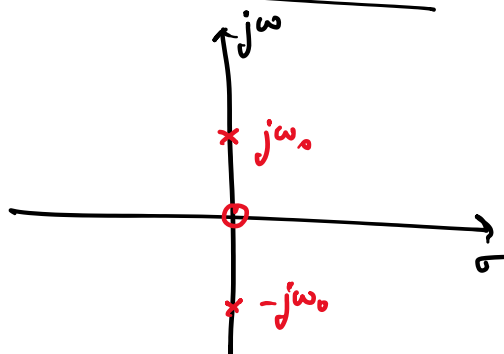
$$= \frac{s}{(s + j\omega_0)(s - j\omega_0)}$$



Marginally stable

$$\frac{t}{2\omega_0} \sin(\omega_0 t) u(t)$$
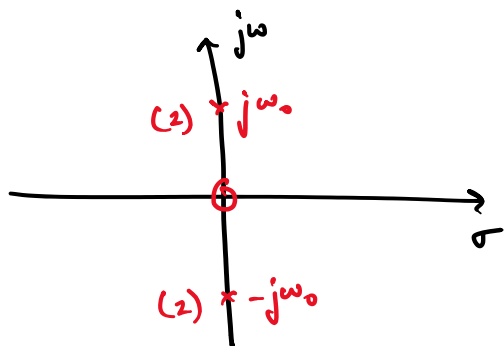
$$F(s) = \frac{s}{(s^2 + \omega_0^2)^2}$$




Unstable

$$t f(t) \quad \text{---} \quad -\frac{d}{ds} F(s)$$


- 1st order conjugate pair of poles is marginally stable but higher order repeated poles unstable

9

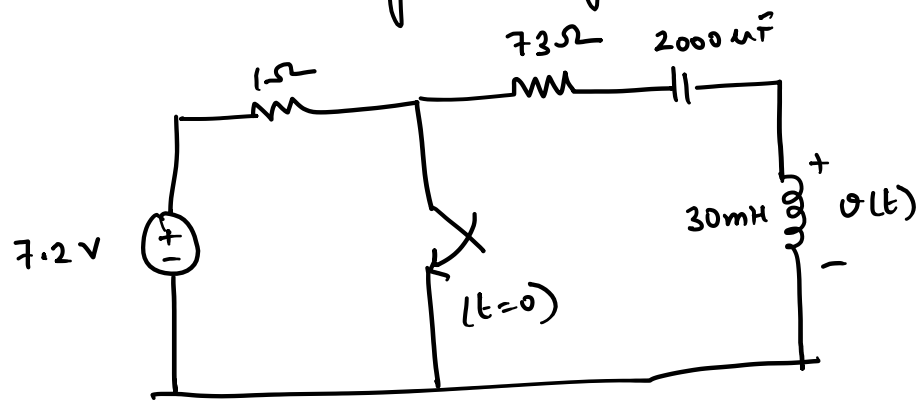→ Find $v(t \geq 0)$ for the following circuit




At $t < 0$

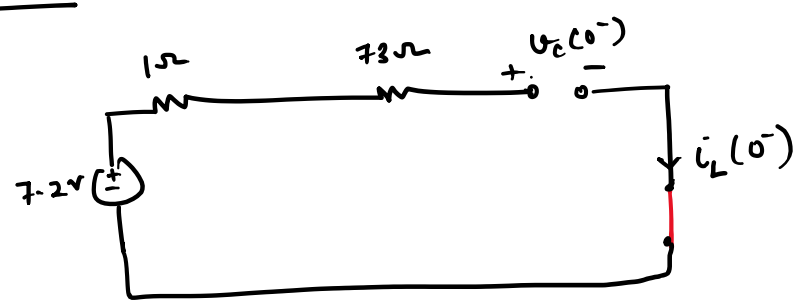

$$v_L(0^-) = 7.2V$$

$$i_L(0^-) = 0A$$

At $t \geq 0$

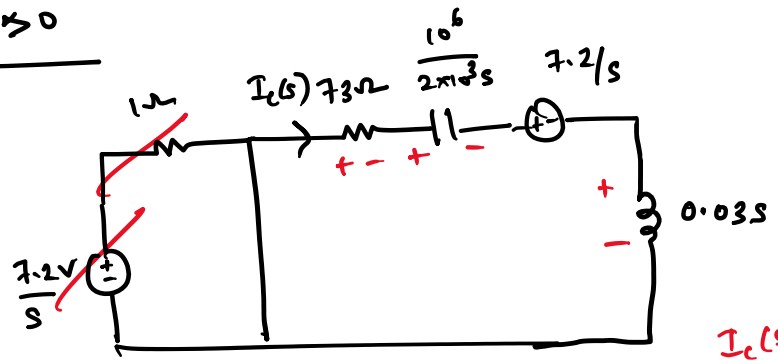

$$I_L(s) (-73 - \frac{500}{s} - 0.03s) - \frac{7.2}{s} = 0 \Rightarrow I_L(s) = \frac{-7.2/s}{73 + \frac{500}{s} + 0.03s}$$

$$I_L(s) = \frac{-7.2}{0.03s^2 + 73s + 500} = \frac{-7.2/0.03}{s^2 + \frac{73}{0.03}s + \frac{500}{0.03}}$$

$$= \frac{-240}{(s + 2426.1)(s + 6.9)} = \frac{A}{(s + 2426.1)} + \frac{B}{(s + 6.9)}$$

$$\Rightarrow -240 = A(s + 6.9) + B(s + 2426.1)$$

Put $s = -6.9$

(10)


$$\Rightarrow -240 = A(0) + B(-6.9 + 2426.1)$$

$$\Rightarrow B = -0.0989$$

Compare coeff of s^1

$$0 = A + B \Rightarrow A = -B = +0.0989$$
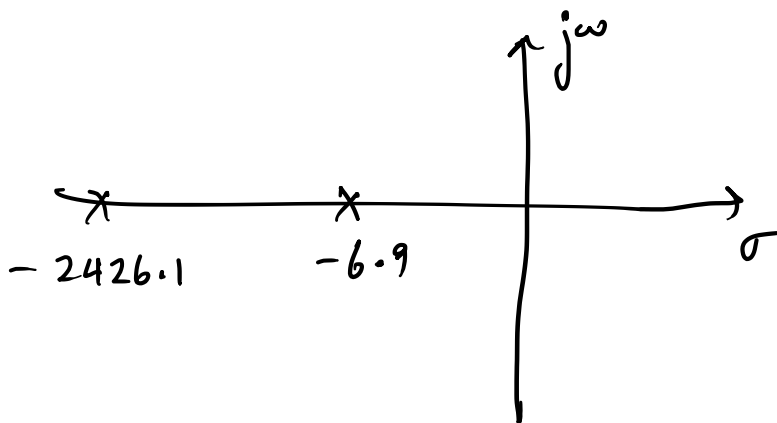
$$\Rightarrow I_c(s) = \frac{0.0989}{(s + 2426.1)} + \frac{-0.0989}{(s + 6.9)}$$



Poles are in the left half s plane.

So system is stable

$$i_c(t) = 0.0989 e^{-2426.1t} - 0.0989 e^{-6.9t} u(t) \text{ A.}$$