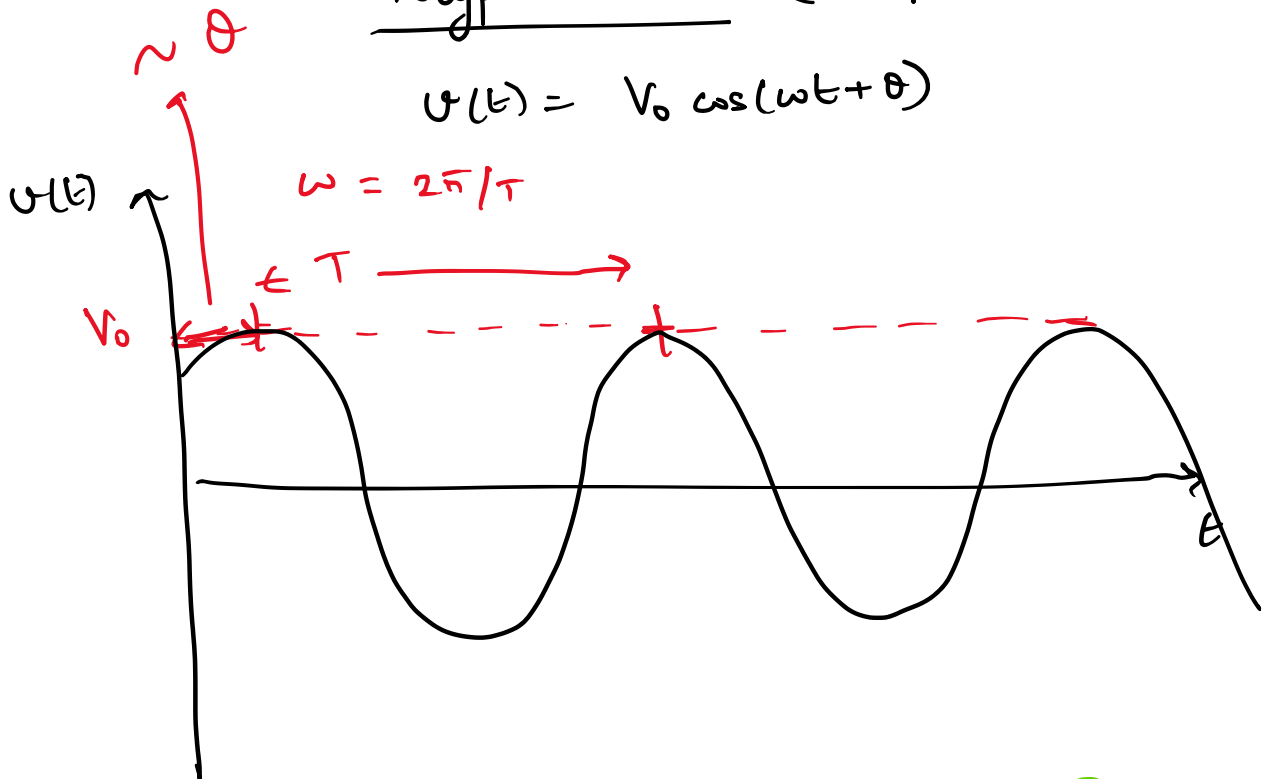


Polyphase Ckts (Chapter 12)

$$v(t) = V_0 \cos(\omega t + \theta)$$




$$v_{an}(t) = V_0 \cos(\omega t)$$

$$v_{bn}(t) = V_0 \cos(\omega t - 120^\circ)$$


$$v_{cn}(t) = V_0 \cos(\omega t - 240^\circ)$$

Fig 12.1

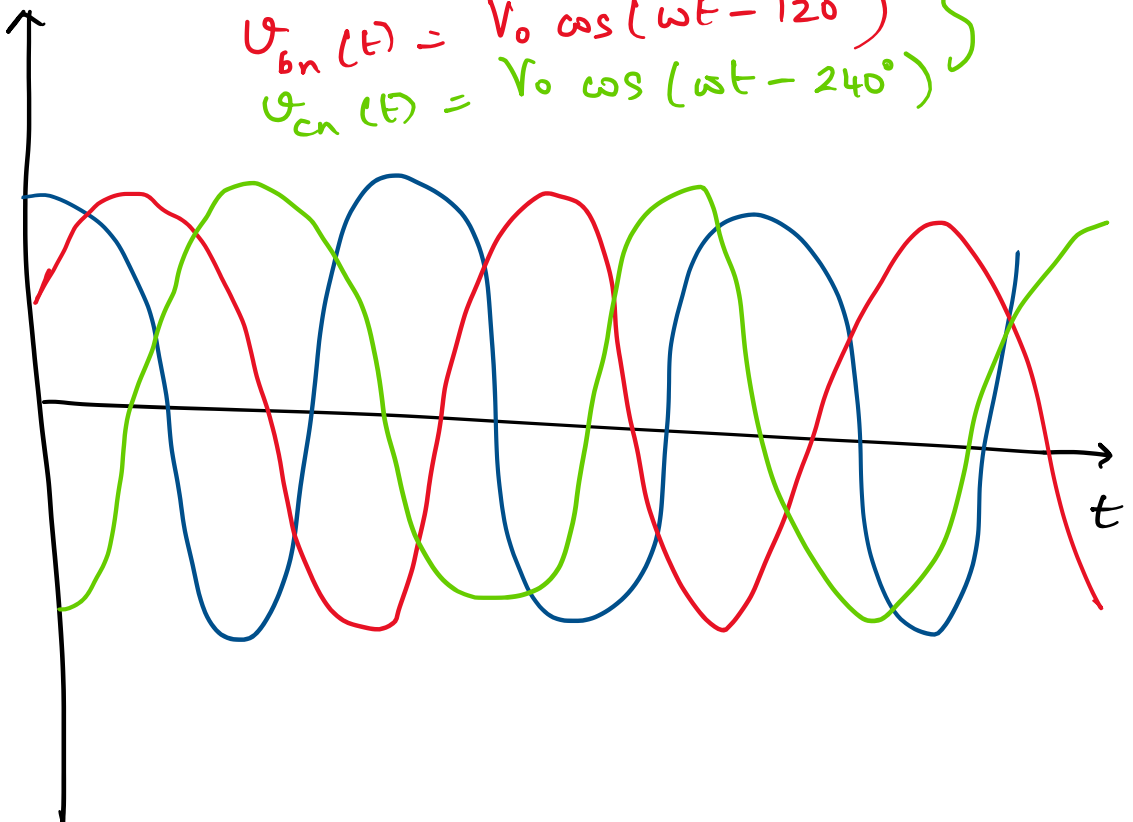


Time Domain	Phasor / Freq Domain ②
$V_{an}(t) = V_o \cos(\omega t + \theta)$	$V_{an} = V_o \angle \theta$
$V_{bn}(t) = V_o \cos(\omega t + \theta - 120^\circ)$	$V_{bn} = V_o \angle \theta - 120^\circ$
$V_{cn}(t) = V_o \cos(\omega t + \theta - 240^\circ)$	$V_{cn} = V_o \angle \theta - 240^\circ$

"Balanced Three-Phase Source"

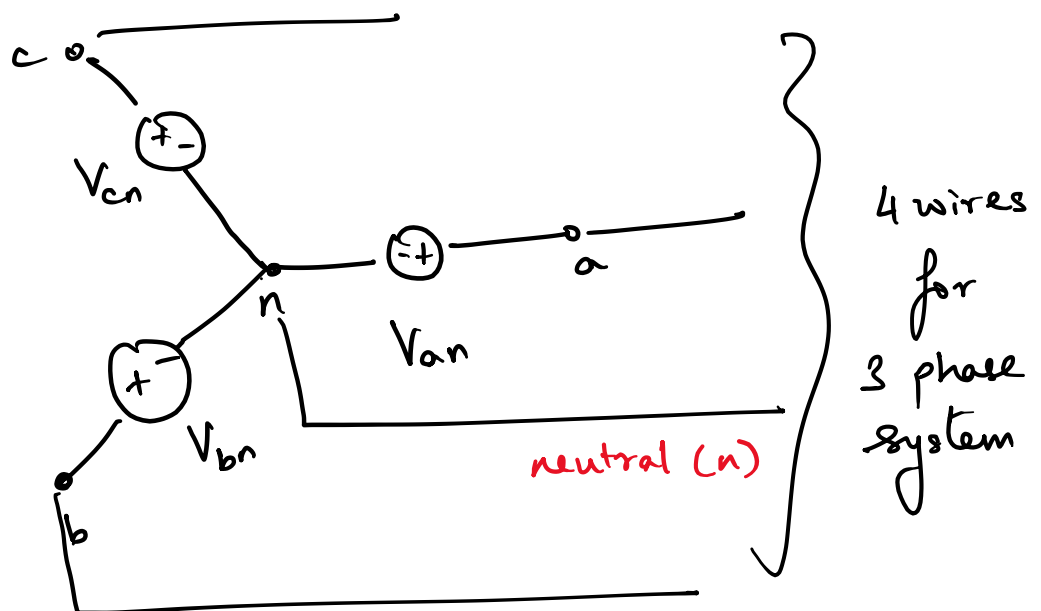

Three phase power generation

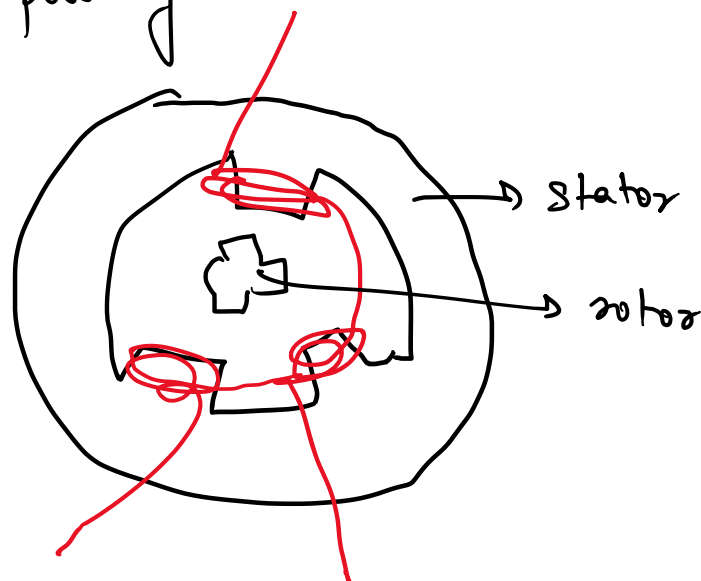

Time Domain

$$v_{an} = V_0 \cos(\omega t + \theta)$$

$$v_{bn} = V_0 \cos(\omega t + \theta - 180^\circ)$$


Frequency Domain (3)

$$V_{an} = V_0 \angle \theta$$


$$V_{bn} = V_0 \angle \theta - 180^\circ$$

$$= -V_{an}$$

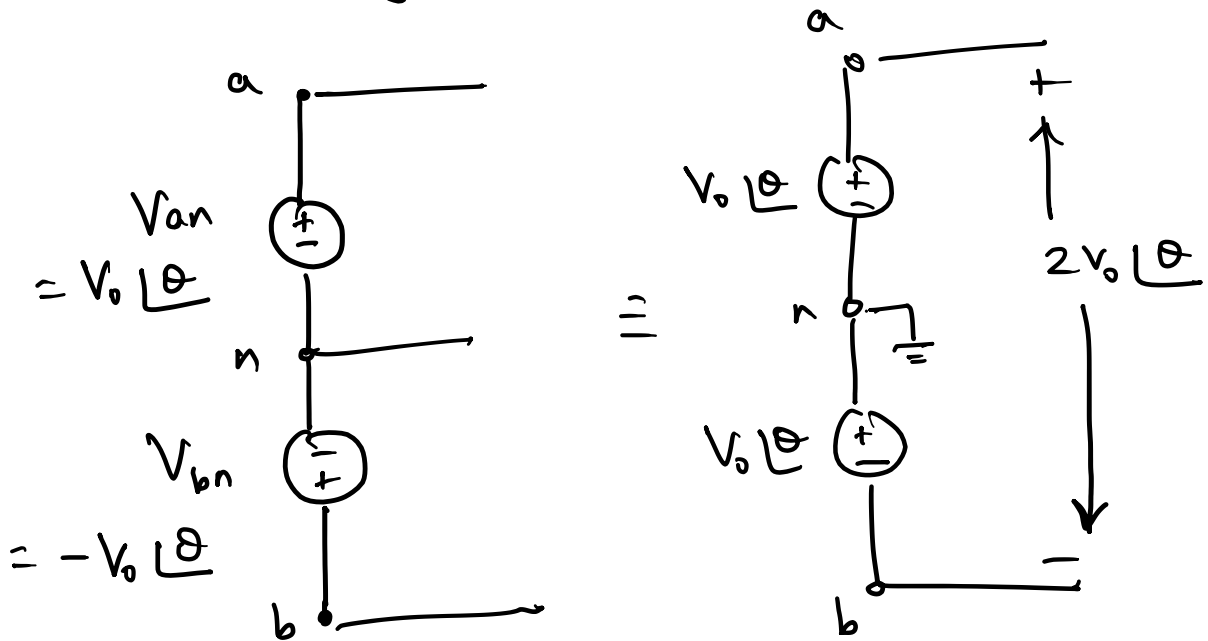Balanced Two Phase System or
Single Phase Differential System



Four Phase Supply

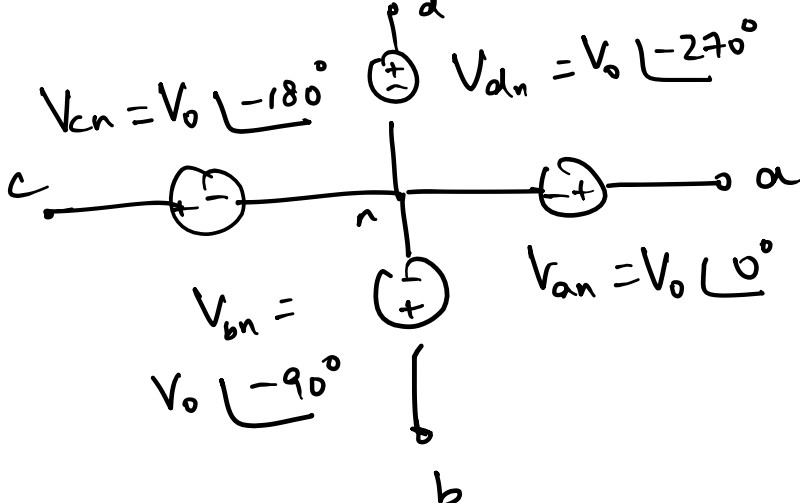


④

- Voltages associated with a circuit are given by $V_{12} = 9 \angle 30^\circ \text{ V}$, $V_{32} = 3 \angle 130^\circ \text{ V}$, and $V_{14} = 2 \angle 10^\circ \text{ V}$. Determine V_{21} , V_{13} , V_{34} and V_{24} .

$$V_{12} = 9 \angle 30^\circ$$

$$V_{21} = -V_{12} = 9 \angle 30^\circ - 180^\circ = 9 \angle -150^\circ$$

$$V_{13} = V_{12} + V_{23}$$

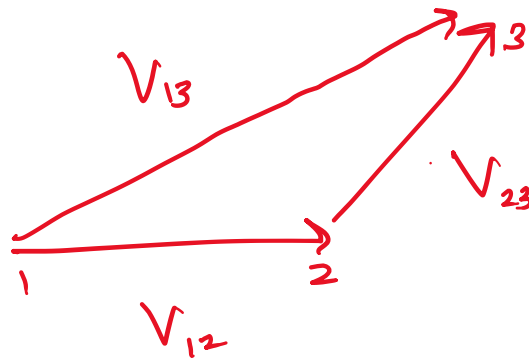

$$\Rightarrow V_{13} = V_{12} - V_{32} = 9 \angle 30^\circ - 3 \angle 130^\circ$$

$$\neq 6 \angle -100^\circ$$

(No subtraction in polar format)


$$= (9 \cos 30^\circ - 3 \cos 130^\circ) + j(9 \sin 30^\circ - 3 \sin 130^\circ)$$

$$= 9.7226 + j2.201 \text{ V}$$

$$V_{34} = V_{31} + V_{14} = -V_{13} + V_{14} = -9.7226 - j2.201 + 2 \angle 10^\circ = -7.75 - j1.85 \text{ V}$$

$$V_{24} = V_{21} + V_{14} = 9 \angle -150^\circ + 2 \angle 10^\circ = -5.82 - j4.15 \text{ V}$$

3. For the system represented below, the ohmic losses in the neutral wire are so small they can be neglected and it can be adequately modeled as a short circuit. (a) Calculate the power lost in the two lines as a result of their nonzero resistance. (b) Compute the average power delivered to the load. (c) Determine the power factor of the total load.

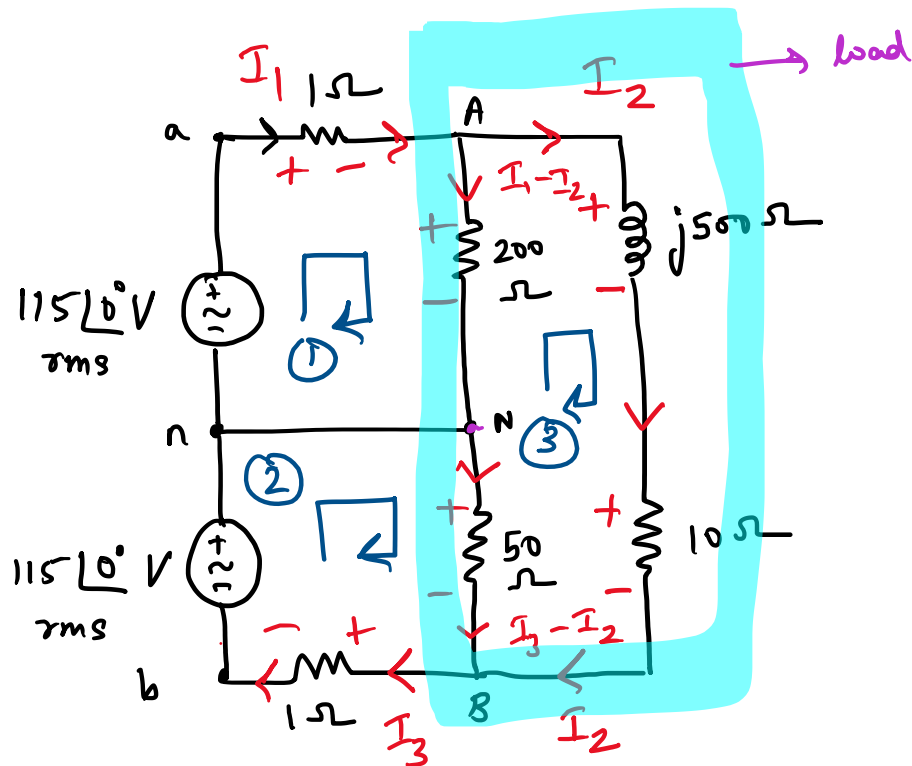

Loop 1

$$+115 - I_1 \times 1 - (I_1 - I_2) \times 200 = 0$$

$$\Rightarrow 201 I_1 - 200 I_2 + 0 \times I_3 = 115 \quad \text{--- (1)}$$

Loop 2

$$+115 - 50 \times (I_3 - I_2) - I_3 \times 1 = 0$$

$$0 \times I_1 + 50 I_2 - 51 I_3 = -115 \quad \text{--- (2)}$$

Loop 3

$$+(I_1 - I_2) \times 200 - I_2 \times (j50 + 10) + 50 \times (I_3 - I_2) = 0$$

$$I_1 (200) + I_2 (-260 - j500) + I_3 (50) = 0 \quad \text{--- (2)} \quad (6)$$

$$200 I_1 - 260 I_2 + 0 I_3 = 115$$

$$0 + 50 I_2 - 51 I_3 = -115$$

$$200 I_1 + (-260 - j500) I_2 + 50 I_3 = 0$$

$$I_1 = 0.7376 \angle -37.8^\circ \text{ A}, \quad I_2 = 0.454 \angle -88.6^\circ, \quad I_3 = 2.31 \angle -11.1^\circ \text{ A}$$

$$\begin{aligned} \text{(a) Power lost in line aA} &= \operatorname{Re} \left\{ \underbrace{I_1 \times R_w}_V \times \underbrace{I_1^*}_{I^*} \right\} \\ &= |I_1|^2 R_w \quad \text{(omitted } \frac{1}{2} \text{ due to rms)} \\ &= 0.5440 \quad \text{Watts} \end{aligned}$$

$$\begin{aligned} \text{(b) Power lost in line bB} &= \operatorname{Re} \left\{ I_3 \times R_w \times I_3^* \right\} \\ &= |I_3|^2 R_w = 5.3310 \text{ Watts} \end{aligned}$$

Time averaged

$$\text{(c) } \wedge \text{ Power lost in load} =$$

$$|I_1 - I_2|^2 \times 200 + |I_3 - I_2|^2 \times 50 + |I_2|^2 \times 10 \quad \text{Watts}$$

$$= 65.4573 + 254.185 + 2.0631$$

$$= 321.7055 \text{ Watts}$$