
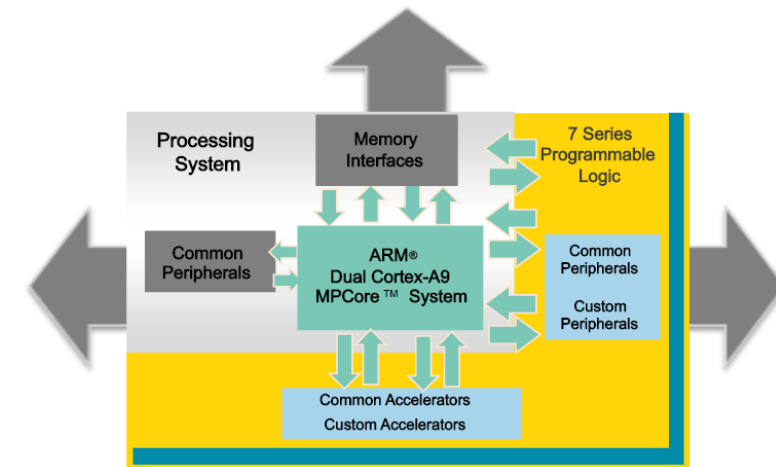



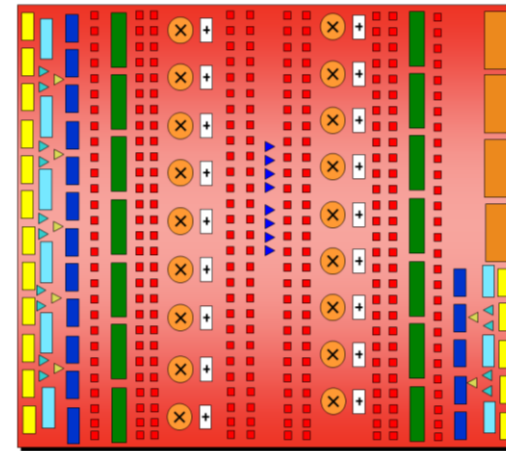


# ECE 270: Embedded Logic Design




# Pipelining

# FF Timing Constraints

  


# FF Timing Constraints

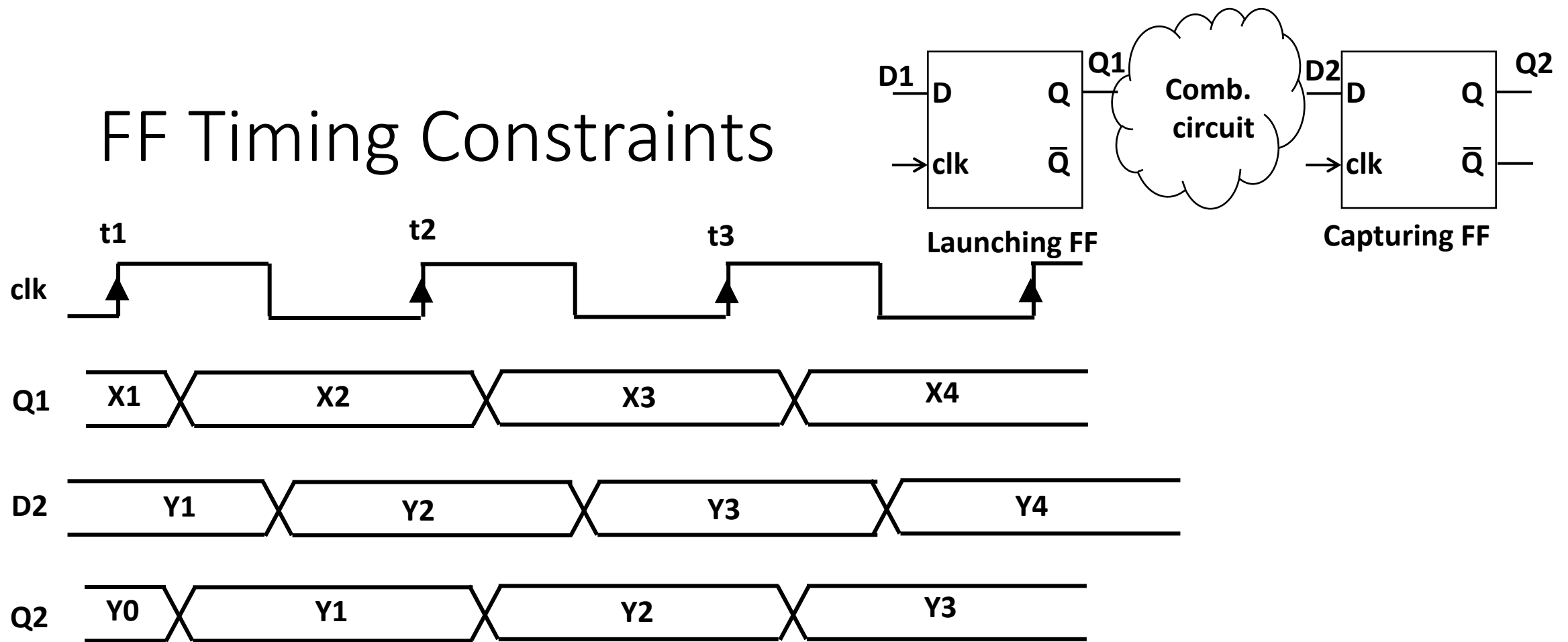


$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$

 - This is very important equation since it puts **limit on the minimum value of clock period** and hence, **maximum value of clock frequency**.
- Limit on maximum value of clock frequency means **limit on the speed at which the circuit can operates**.





- How to increase the clock frequency or reduce the clock period?
 
$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$


  
# Pipelining

- Now, **F** and **G** can be working on input  $X_{i+1}$  while **H** is performing its computations on  $X_i$ .
- This is **2-stage pipeline** i.e. if we have valid input  $X$  during clock cycle  $j$ ,  $P(X)$  is valid during clock cycle  $j+2$ .
- Assuming  $F$ ,  $G$  and  $H$  have propagation delay of 15, 20 and 25 ns, and ideal registers i.e. FFs, then



	<u>latency</u>	<u>throughput</u>
unpipelined	45	1/45
2-stage pipeline	50	1/25

# Pipelining (Summary)



- A **well-formed K-Stage Pipeline** (“K-pipeline”) circuit have exactly K registers **on every path** from an input to an output.
- A **COMBINATIONAL CIRCUIT** is thus a **0-stage pipeline**.
- Every pipeline stage, hence every K-Stage pipeline, has a register on its OUTPUT (not on its input).
- The CLOCK common to all registers must have a period sufficient to cover propagation delay of combinational circuit, clock-to-output delay of launching FF, setup time of capturing FF and clock skew.
- The **LATENCY** of a K-stage pipeline is K times the period of the system’s clock. The **THROUGHPUT** of a K-stage pipeline is the frequency of the clock.

$$T_{clk} \geq \cancel{T_{clk-out}} + T_{pmax} + \cancel{T_{setup}} + \cancel{T_{skew}}$$

$$T_{clk} \geq \cancel{T_{clk-out}} + T_{pmax} + \cancel{T_{setup}} + \cancel{T_{skew}}$$

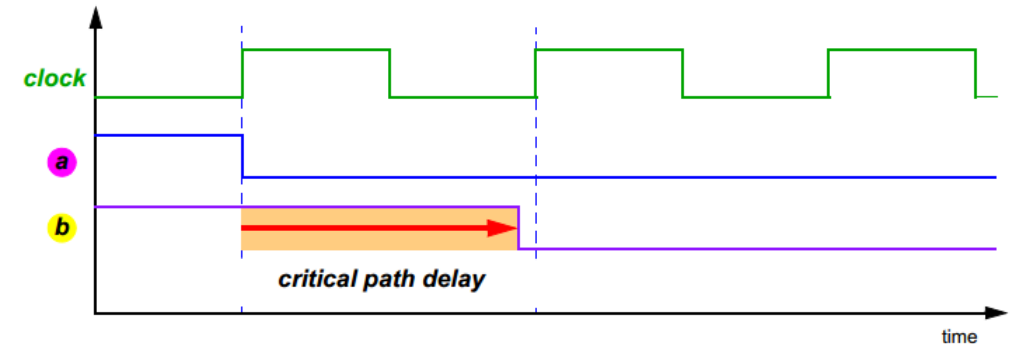 
# Critical Path Delay

- ❖ Signals experiences **logic and routing delays** through all logic paths, as they propagate from one clocked register (FF) to the next.
- ❖ **Critical path delay** is the delay along the critical path i.e. the longest combinatorial propagation delay through the circuit.
- ❖ Critical path delay must be shorter than one clock period in order to guarantee the correct operation of the circuit.






# Critical Path Delay

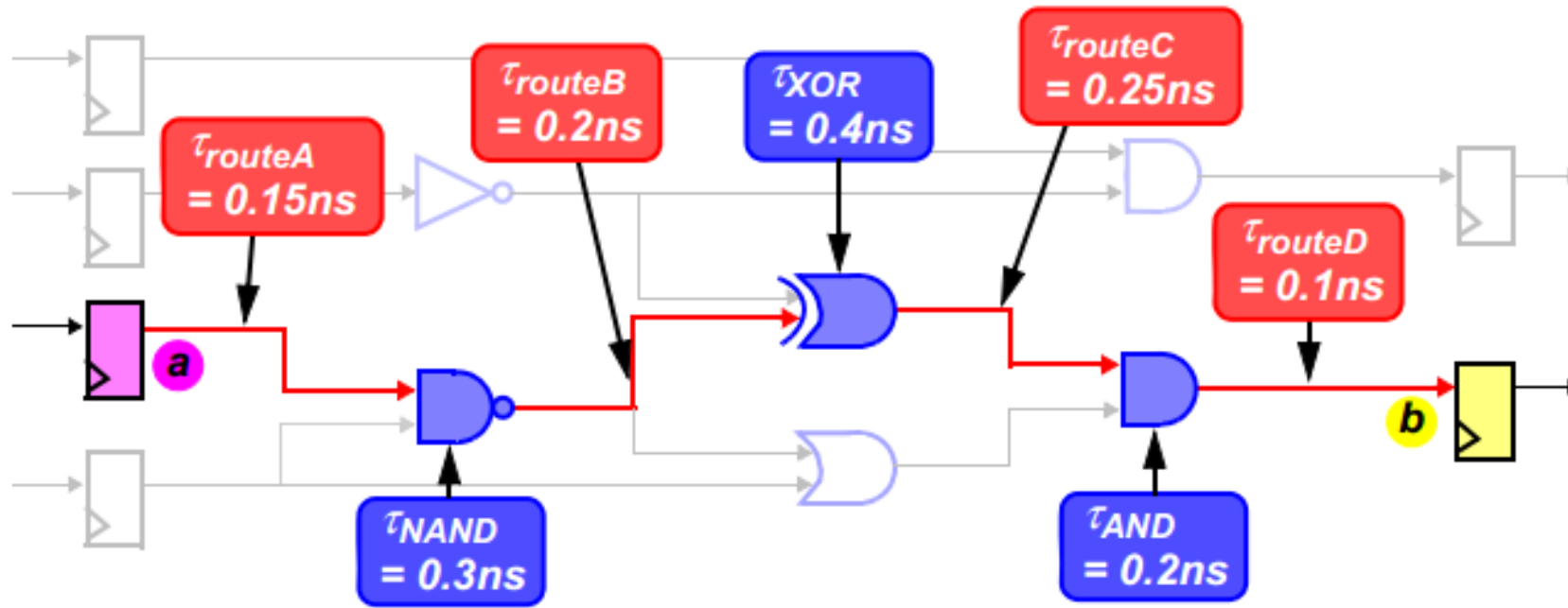

# Critical Path Delay

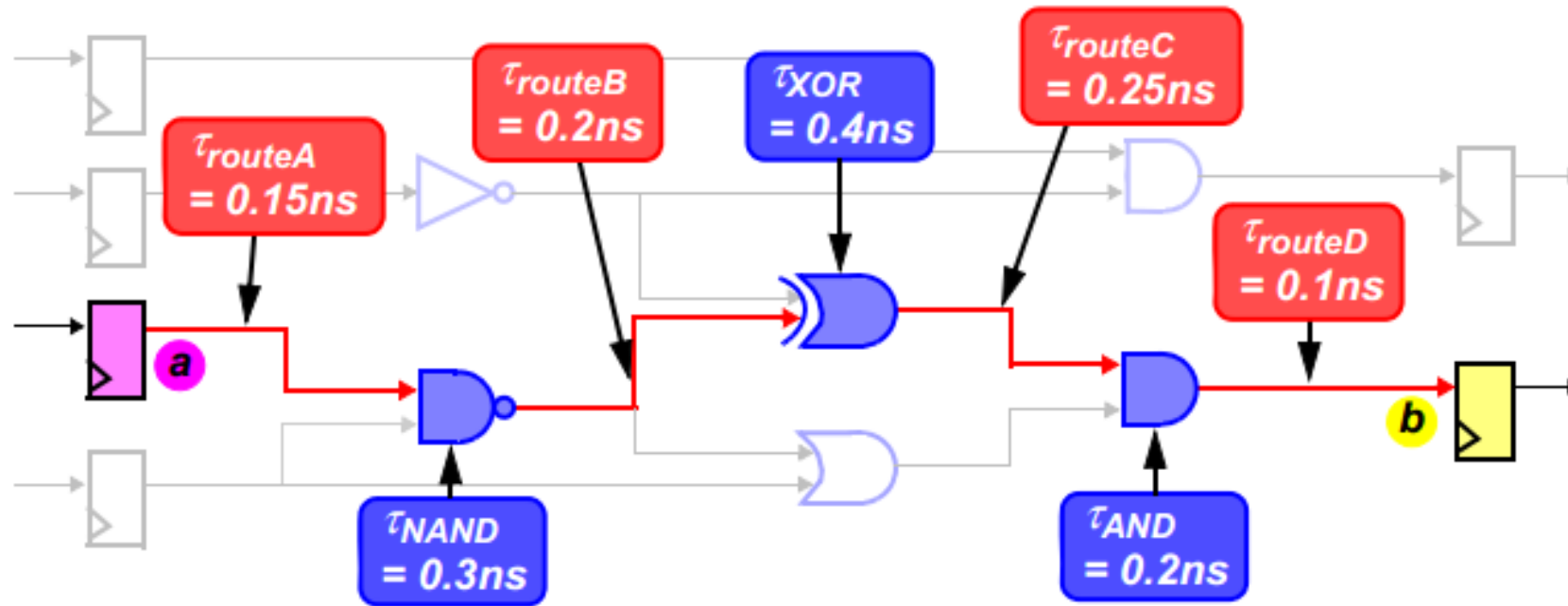

$$\tau_{CPD} = \underbrace{\tau_{NAND} + \tau_{XOR} + \tau_{AND}}_{\text{logic delays}} + \underbrace{\tau_{routeA} + \tau_{routeB} + \tau_{routeC} + \tau_{routeD}}_{\text{routing delays}}$$

$$\begin{aligned}\tau_{CPD} &= 0.3ns + 0.4ns + 0.2ns + 0.15ns + 0.2ns + 0.25ns + 0.1ns \\ &= 1.6ns\end{aligned}$$


# Maximum Clock Frequency

- ❖ Maximum clock frequency depends on critical path delay as given below

$$f_{clk_{max}} = \frac{1}{\tau_{CPD}} = \frac{1}{1.6ns} = 625MHz$$


- ❖ If the clock frequency applied is less than 625 MHz, then a signal leaving one register arrives at the next register within one clock period.

# Critical Path Delay

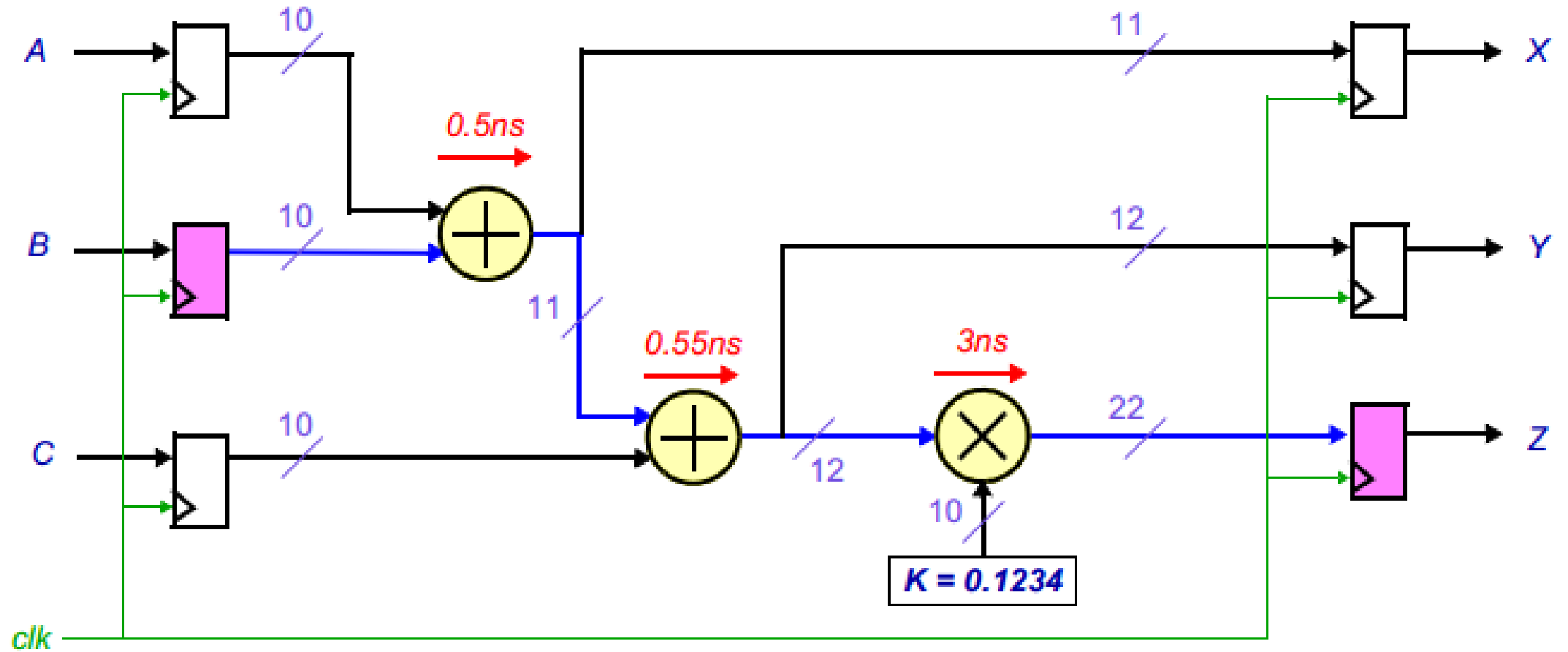

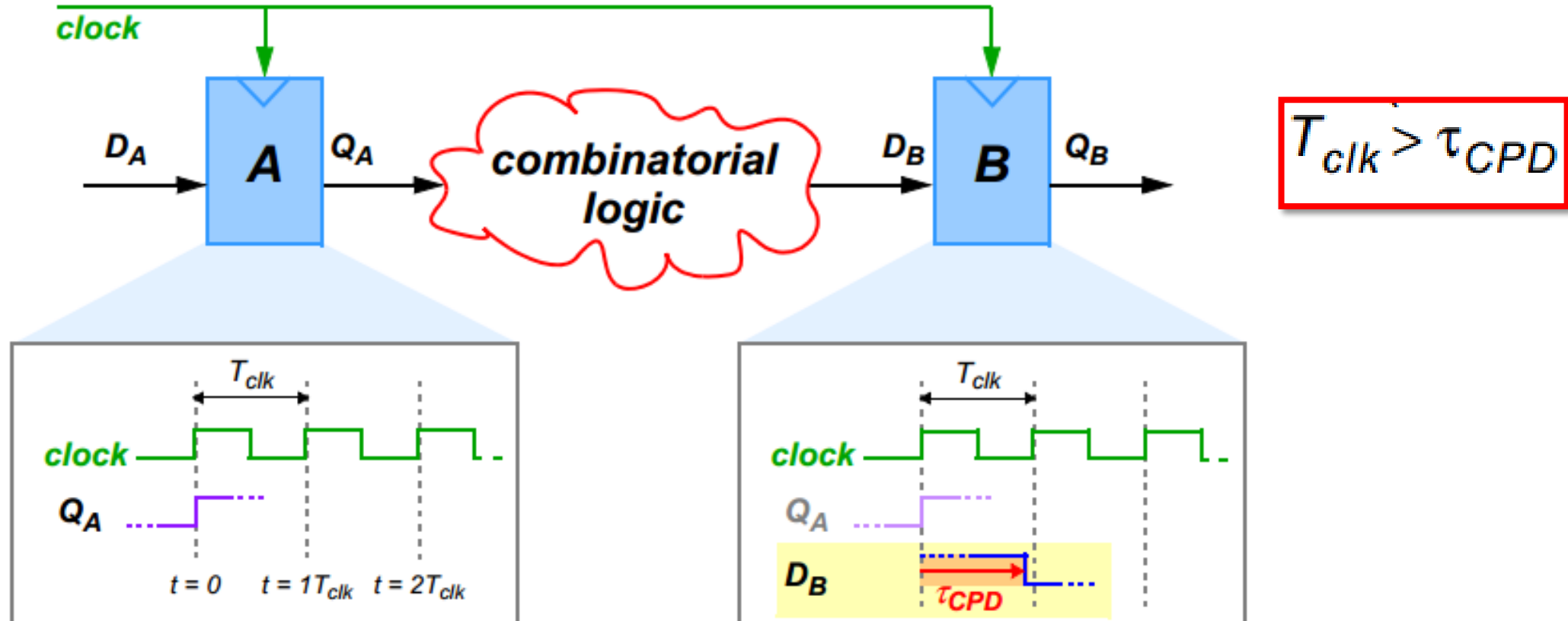
# Maximum Clock Frequency

- ❖ Maximum clock frequency should be as high as possible



 
# Pipelining

- ❖ Pipelining: Breaking of critical path by inserting additional registers



 
# Pipelining

- ❖ Pipelining: Breaking of critical path by inserting additional registers



- ❖ The effect of adding the additional pipeline register is to increase the maximum clock frequency by a factor of 2 **(Is it true?)**


# Pipelining

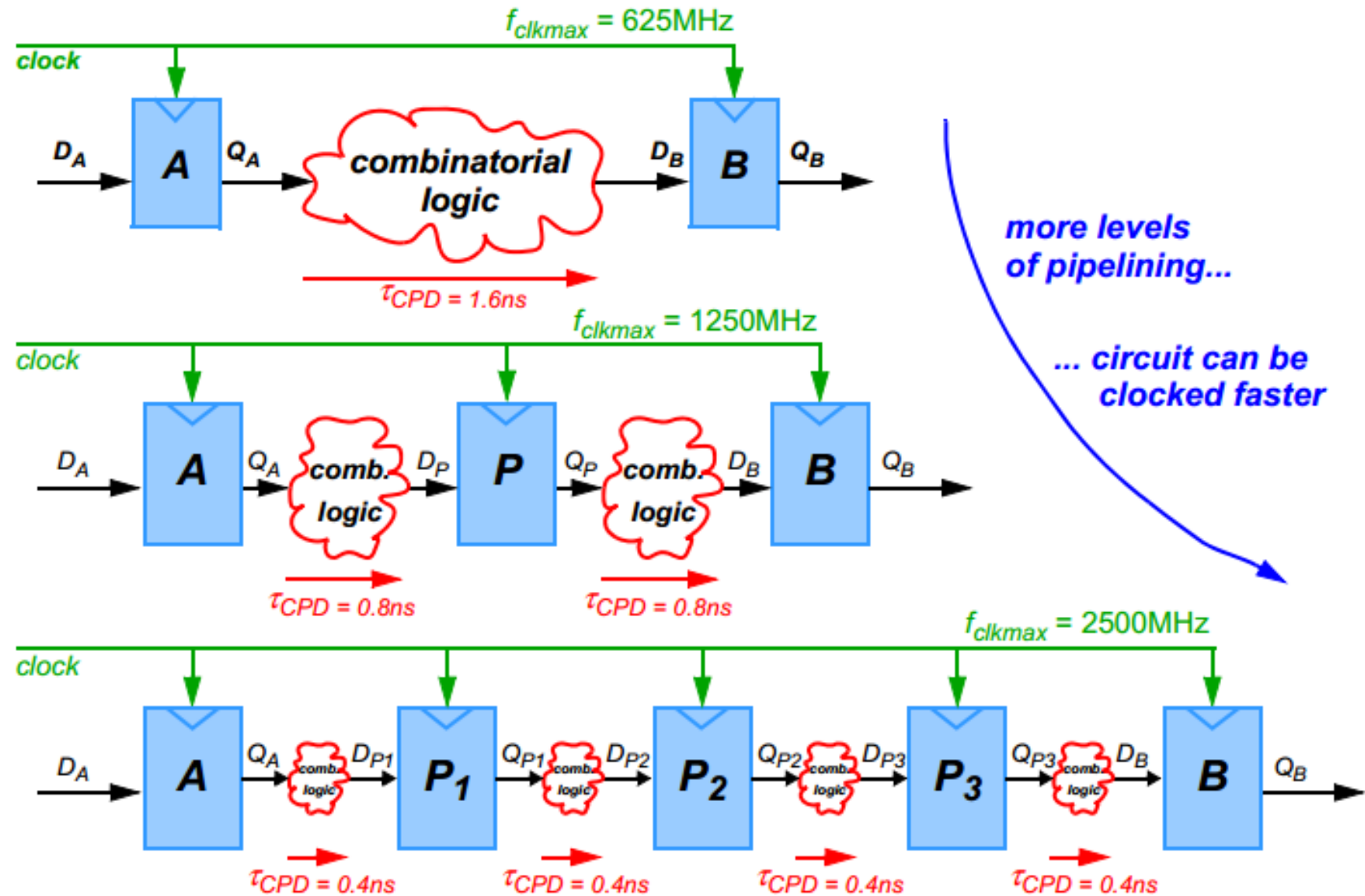


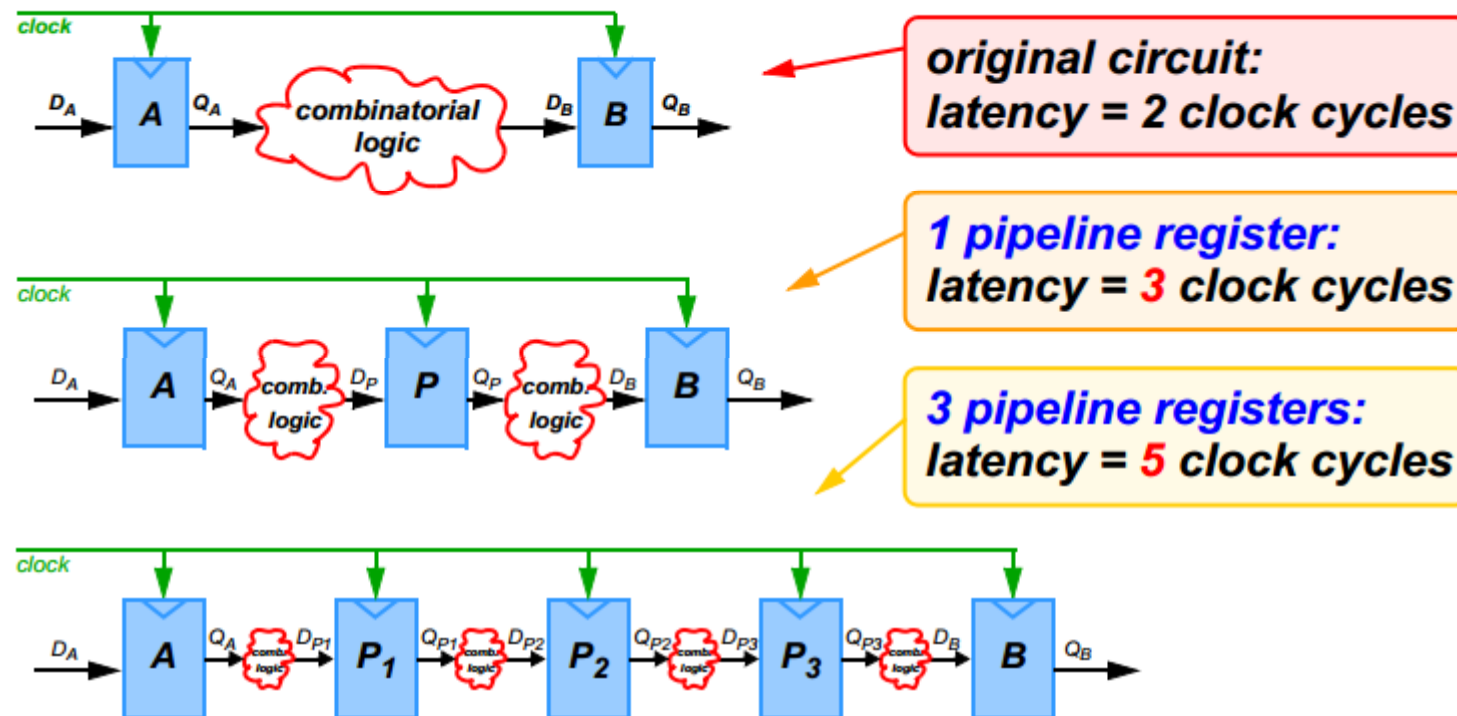
# Pipelining


- ❖ Inserting pipeline registers clearly has an effect on the latency of the circuit i.e. the number of clock cycles from input to output.
- ❖ For every pipeline register, the latency increases by 1 clock cycle



# Pipelining

```
module top_FA(  
    input clk,  
    input [2:0] A,  
    input [2:0] B,  
    output reg [3:0] Sum=0  
);  
  
    wire [1:0] Carry;  
  
    fa FA0(.A(A[0]), .B(B[0]), .C(1'b0), .Sum(Sum[0]), .Carry(Carry[0]));  
    fa FA1(.A(A[1]), .B(B[1]), .C(Carry[0]), .Sum(Sum[1]), .Carry(Carry[1]));  
    fa FA2(.A(A[2]), .B(B[2]), .C(Carry[1]), .Sum(Sum[2]), .Carry(Sum[3]))  
  
endmodule
```


# Pipelining

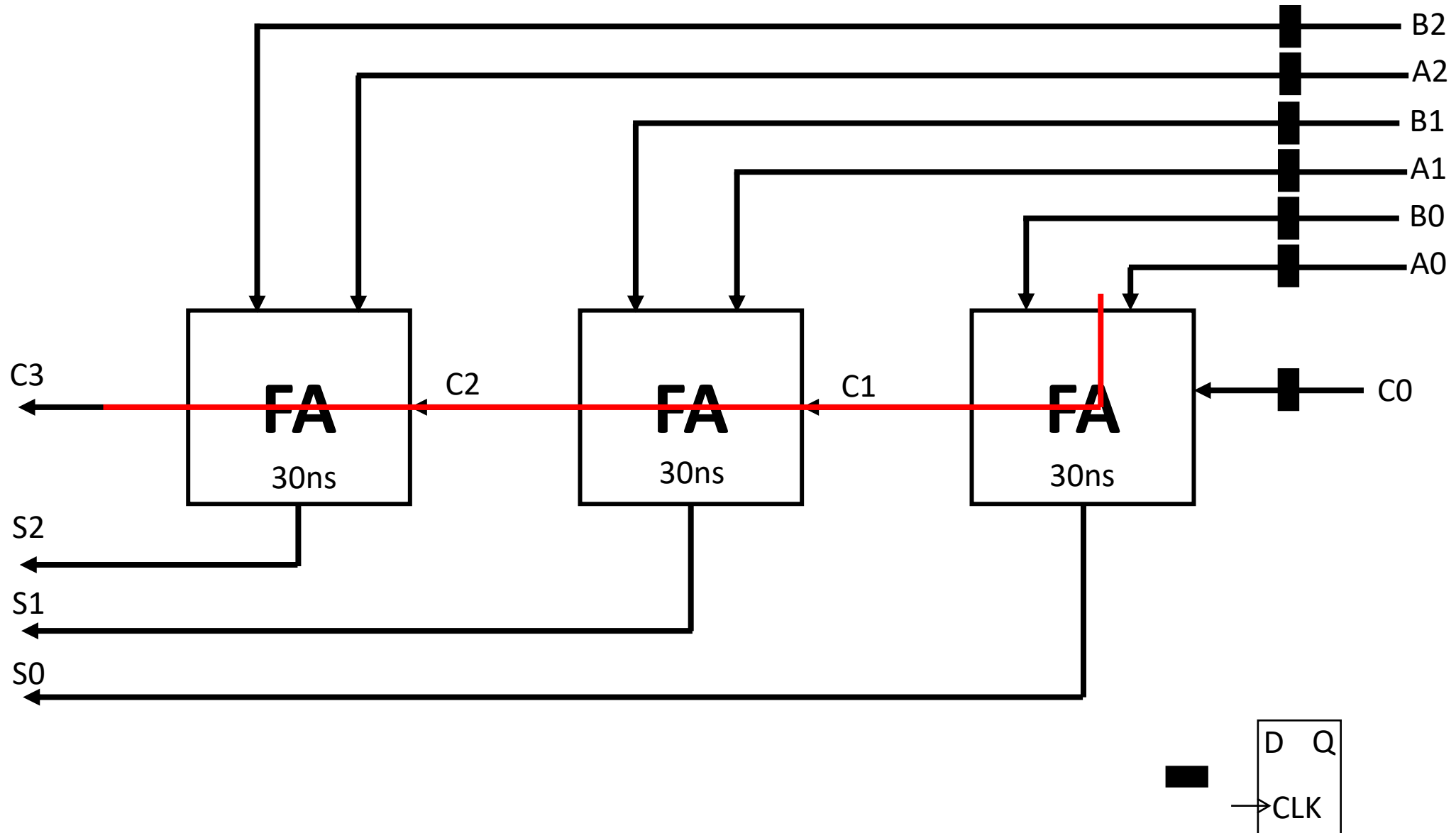


# Critical Path Delay

- ❖ Does arithmetic word lengths affect critical path delay???
- ❖ The last bit of result is not available until the calculation is complete and all the necessary carries have propagated from LSB to MSB.
- ❖ Hence, longer the arithmetic word length, longer is the critical path delay.


# Pipelining

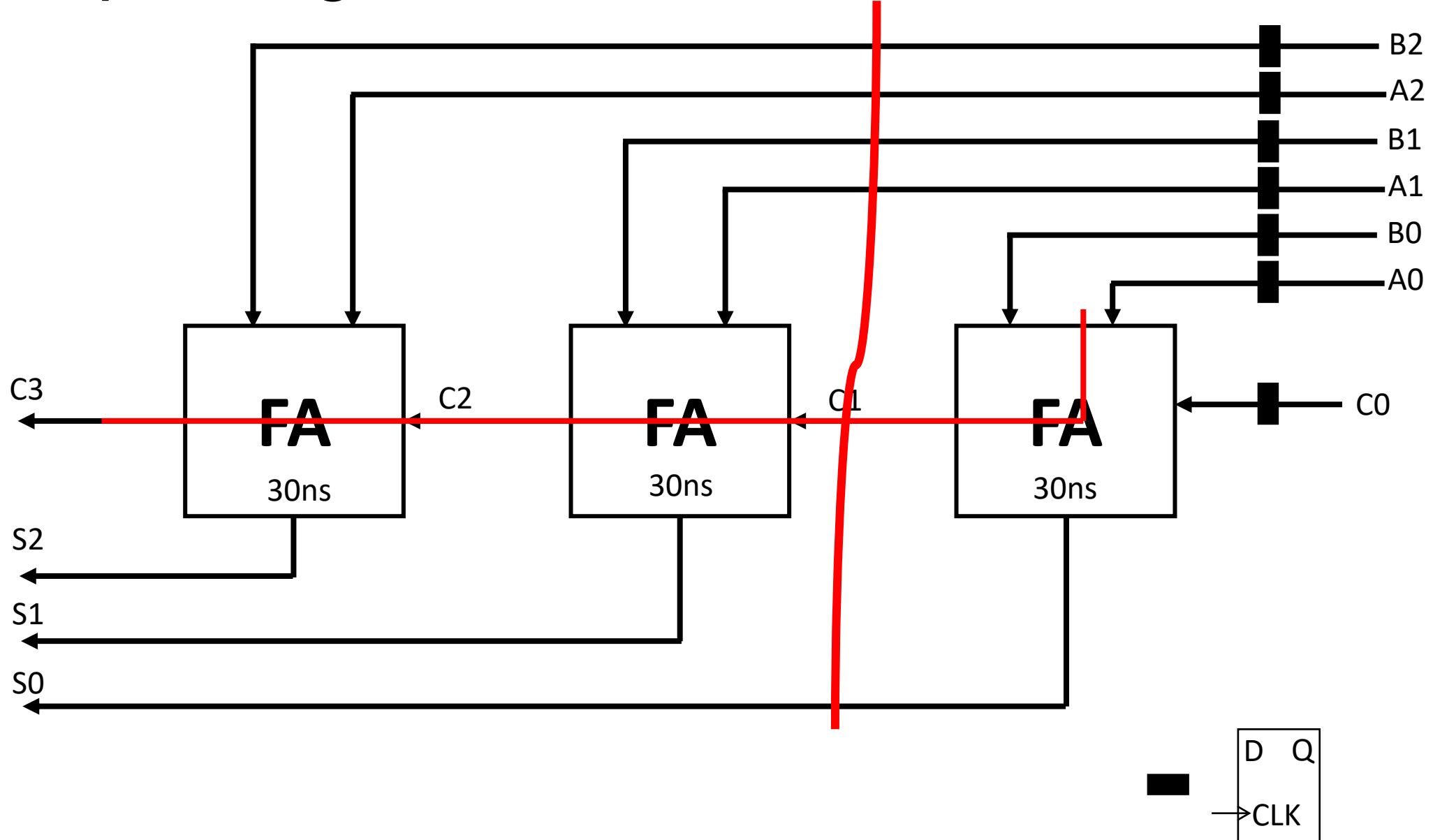


# Pipelining

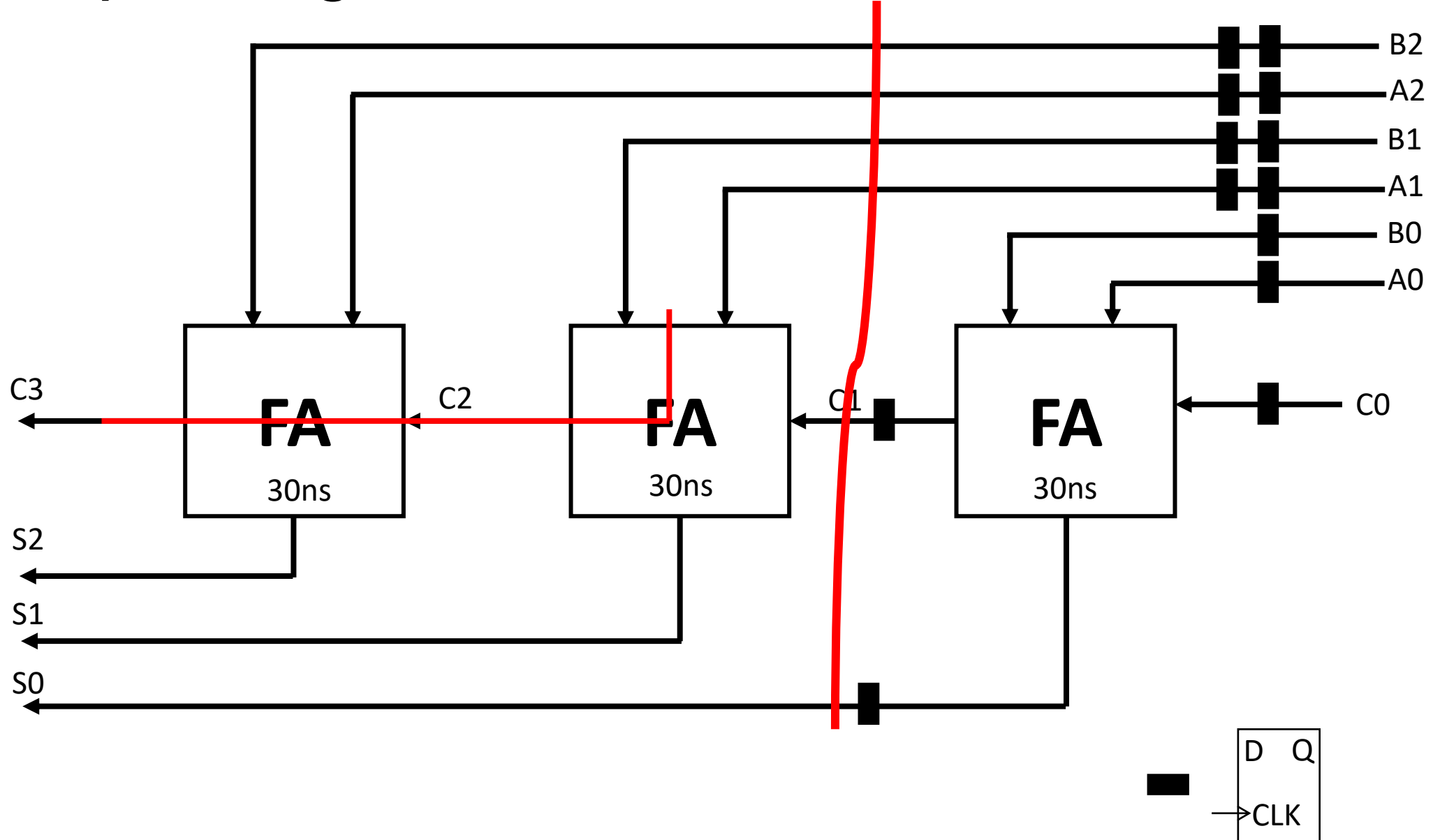

# Pipelining

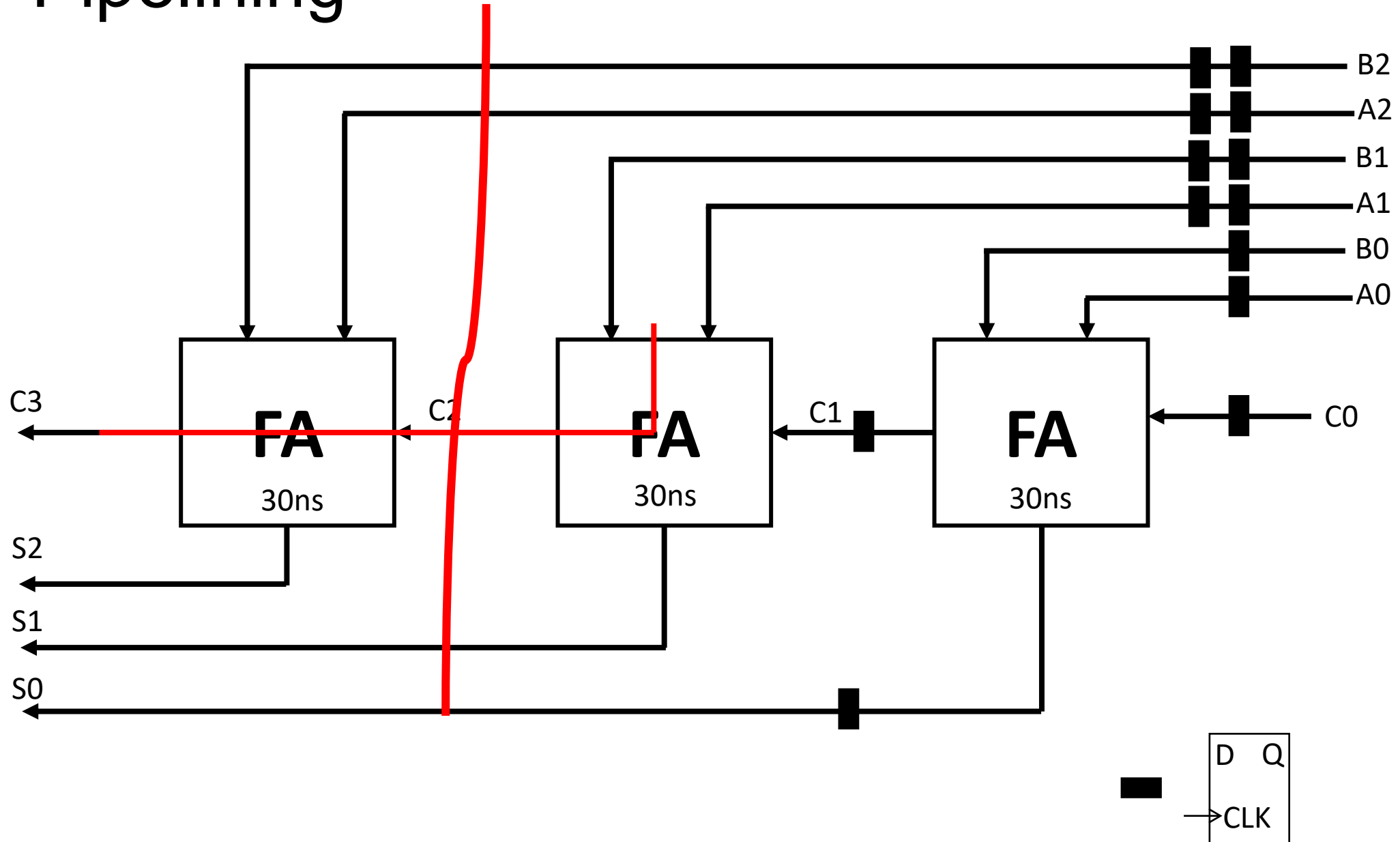


# Pipelining

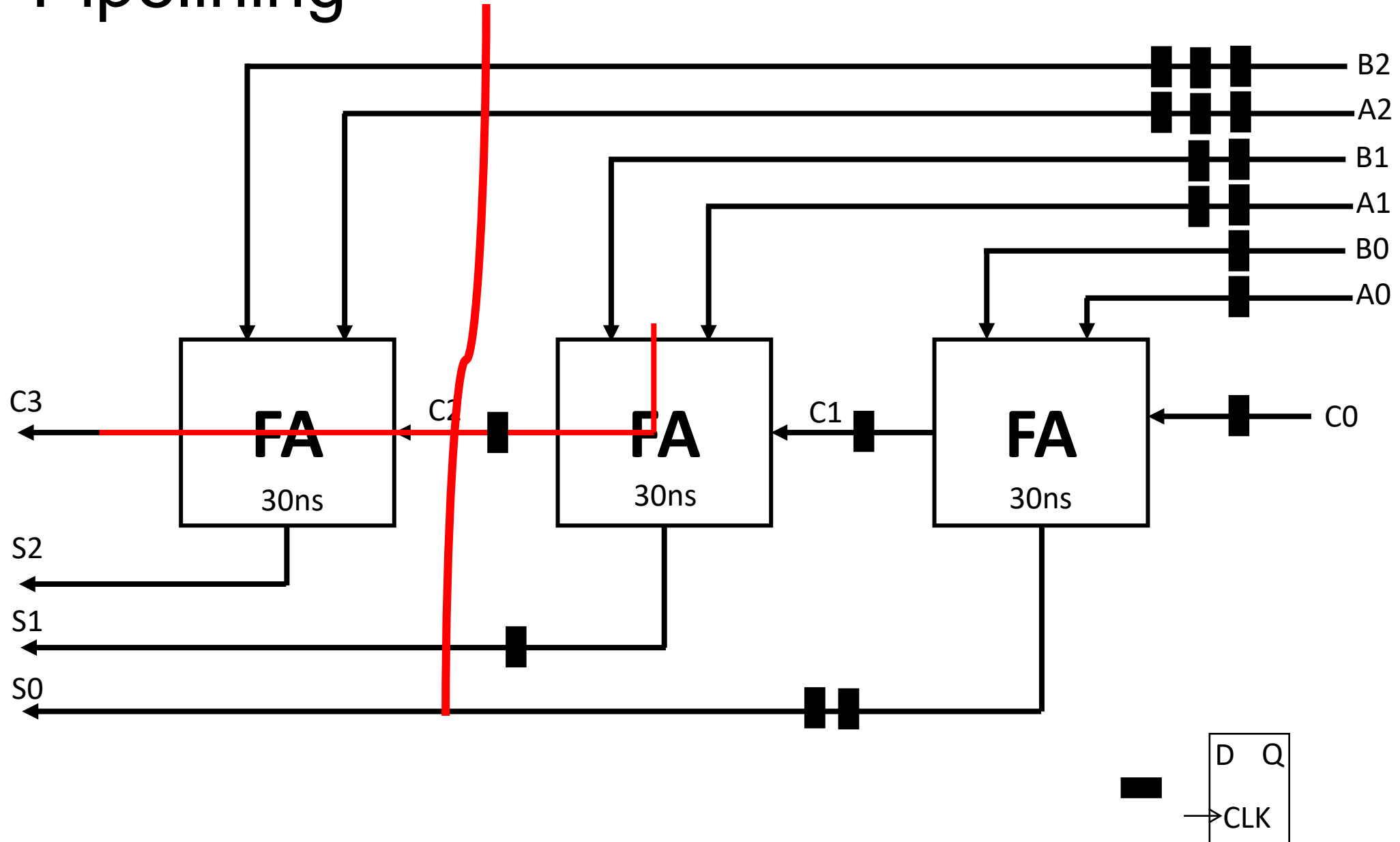





# Pipelining

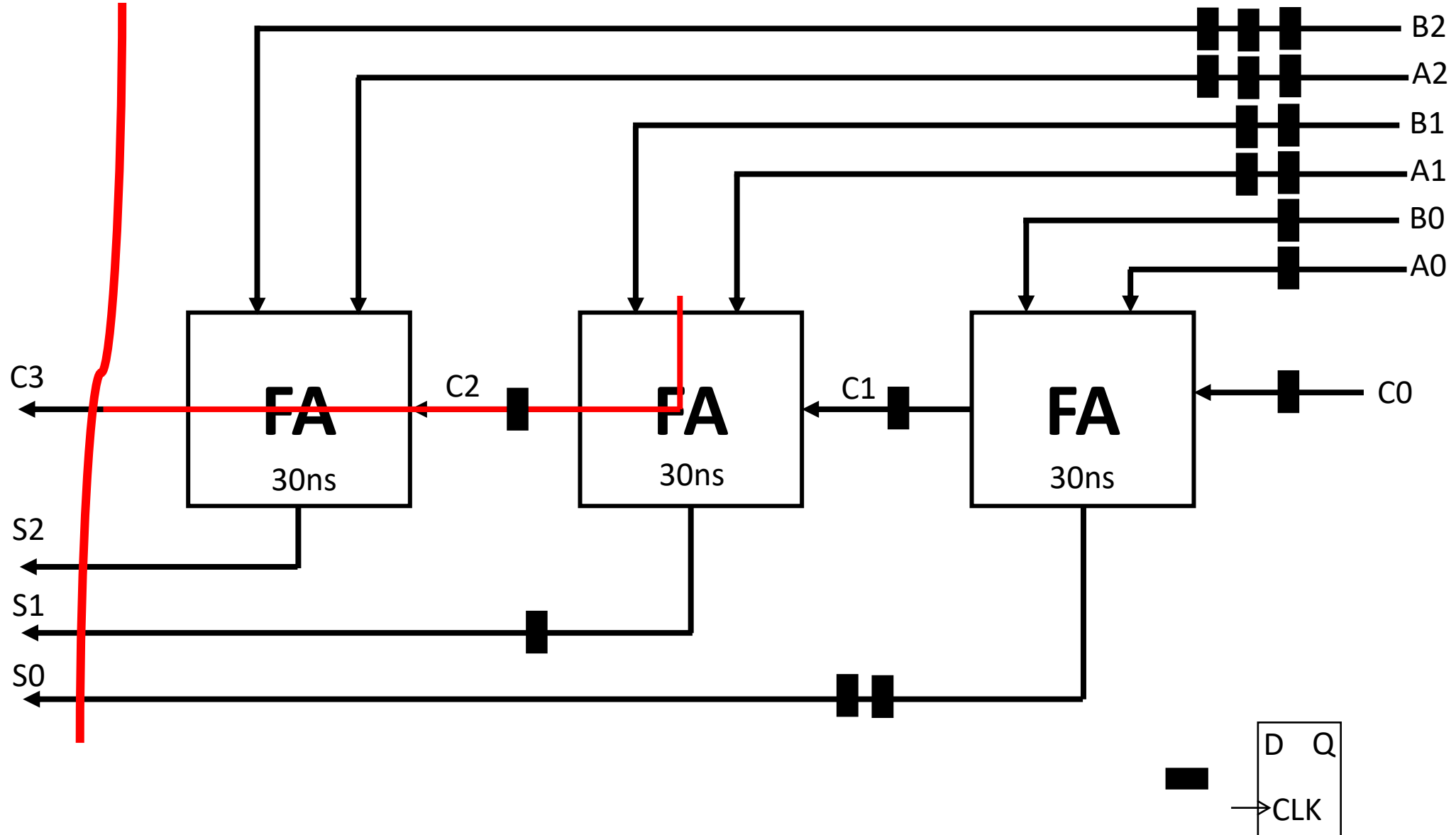

# Pipelining

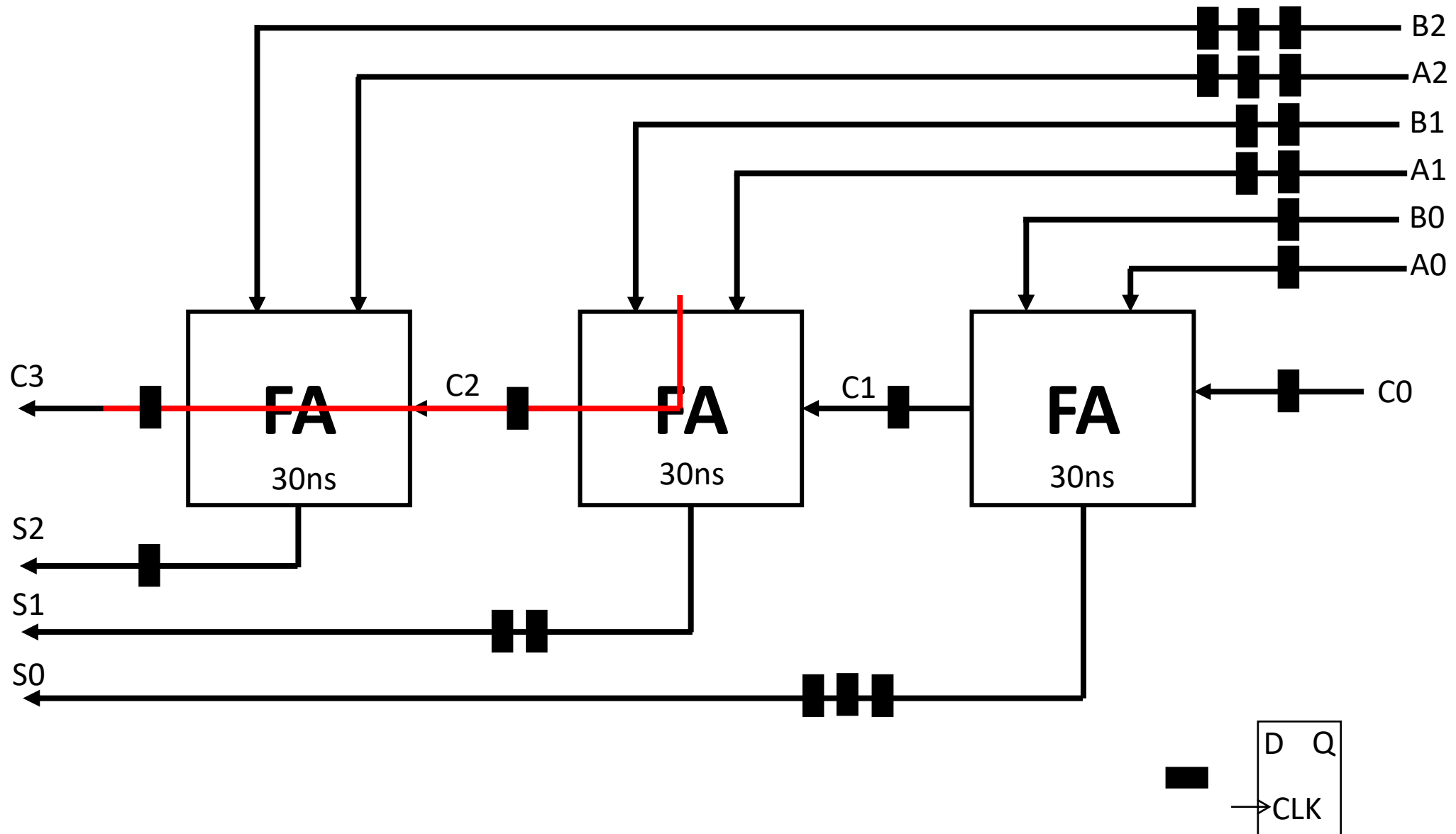

# Pipelining

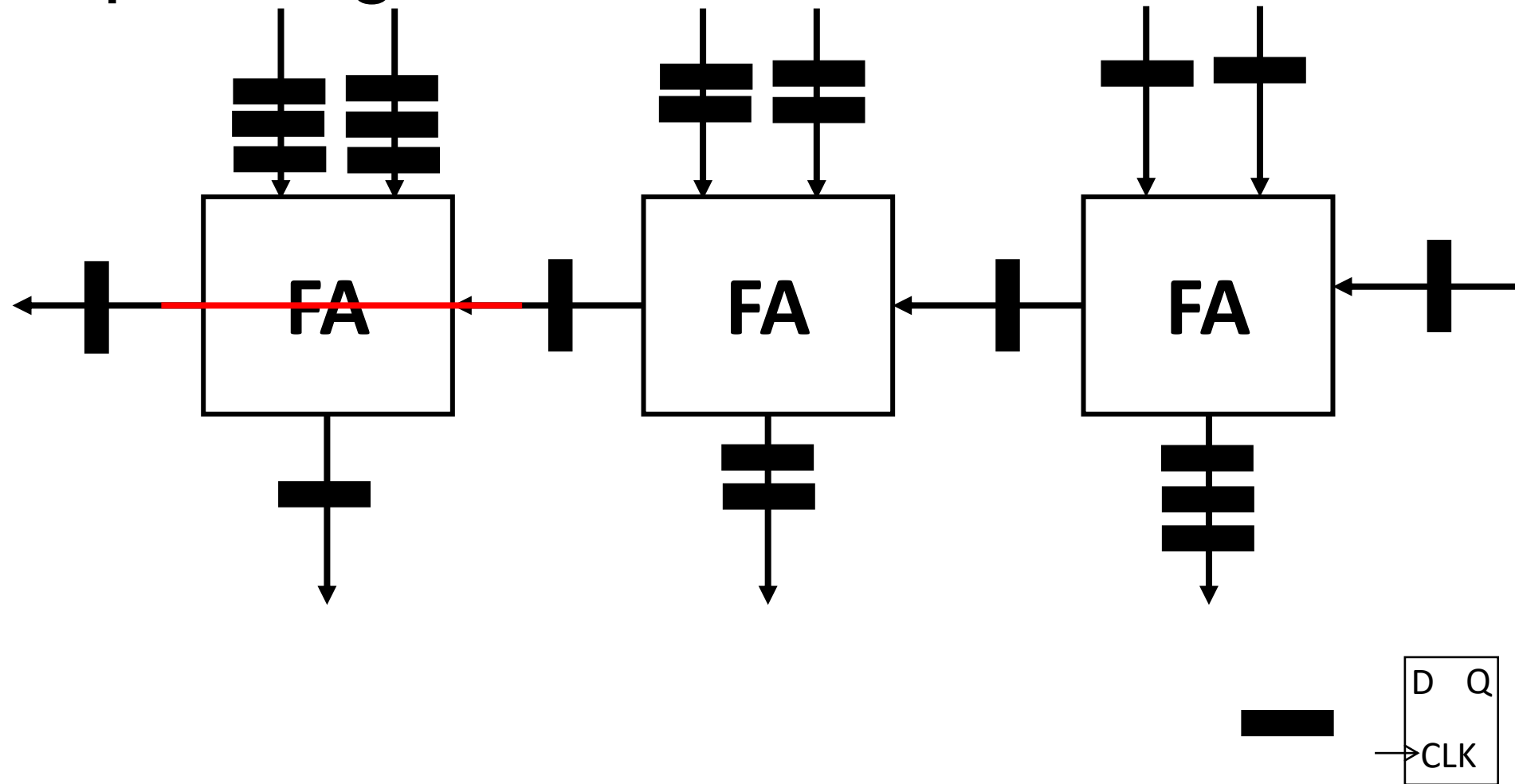

```

module top_pipeline(
  input clk,
  input [2:0] A,
  input [2:0] B,
  output reg [3:0] Sum=0
);
  always@(posedge clk)
  begin
    FF_A01 <= A[0];
    FF_B01 <= B[0];
  end

  always@(posedge clk)
  begin
    FF_A11 <= A[1];
    FF_B11 <= B[1];
  end

  always@(posedge clk)
  begin
    FF_A12 <= FF_A11;
    FF_B12 <= FF_B11;
  end

```

```

  always@(posedge clk)
  begin
    FF_A21 <= A[2];
    FF_B21 <= B[2];
  end

  always@(posedge clk)
  begin
    FF_A22 <= FF_A21;
    FF_B22 <= FF_B21;
  end

  always@(posedge clk)
  begin
    FF_A23 <= FF_A22;
    FF_B23 <= FF_B22;
  end

  always@(posedge clk)
  begin
    C_1reg <= C_1;
    C_2reg <= C_2;
  end

```

```

  always@(posedge clk)
  begin
    Sum[3] <= sum_3;
    Sum[2] <= sum_2;
    sum_11 <= sum_1;
    sum_01 <= sum_0;
  end

  always@(posedge clk)
  begin
    Sum[1] <= sum_11;
    sum_02 <= sum_01;
  end

  always@(posedge clk)
  begin
    Sum[0] <= sum_02;
  end

```

```



fa FA0(.A(FF_A01), .B(FF_B01), .C(1'b0), .Sum(sum_0), .Carry(C_1));
fa FA1(.A(FF_A12), .B(FF_B12), .C(C_1reg), .Sum(sum_1), .Carry(C_2));
fa FA2(.A(FF_A23), .B(FF_B23), .C(C_2reg), .Sum(sum_2), .Carry(sum_3));

```


# FIR Filter

## $N$ -weight Finite Impulse Response (FIR)

$$y(k) = \sum_{n=0}^{N-1} x(k-n)w_n$$

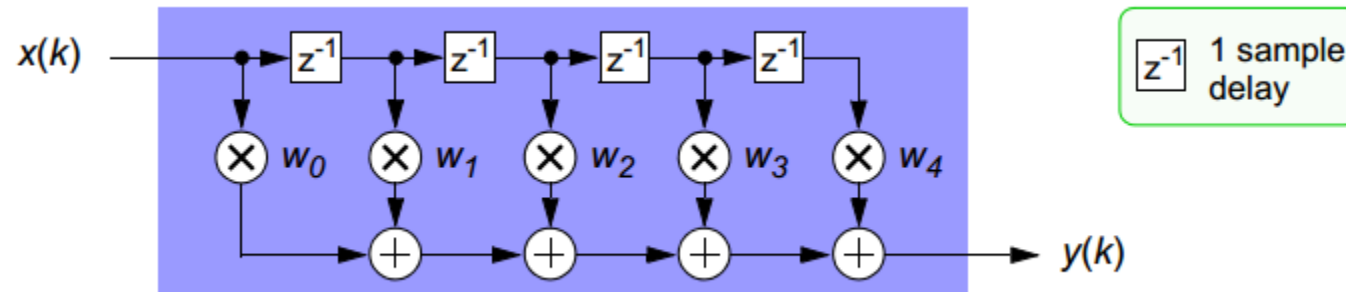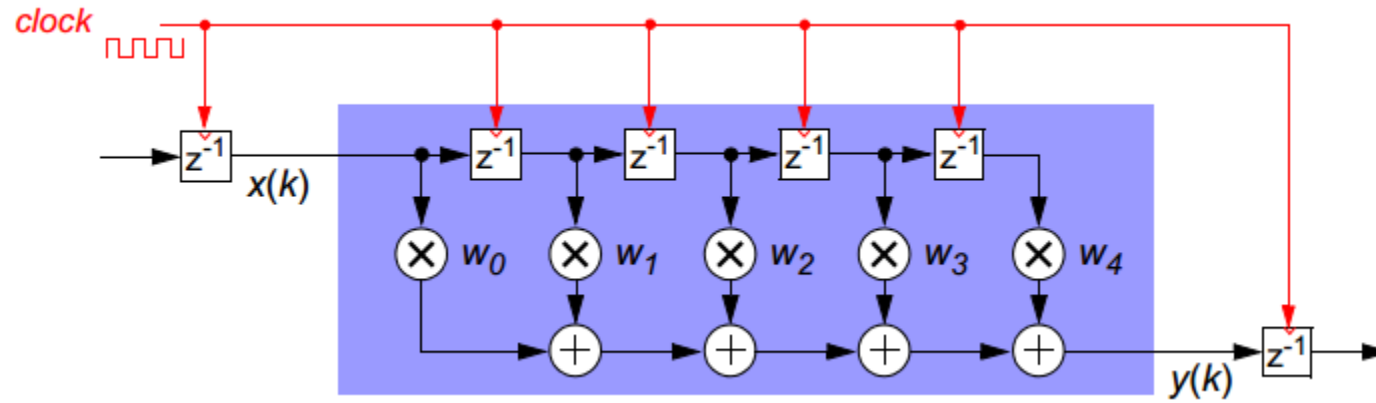

# FIR Filter

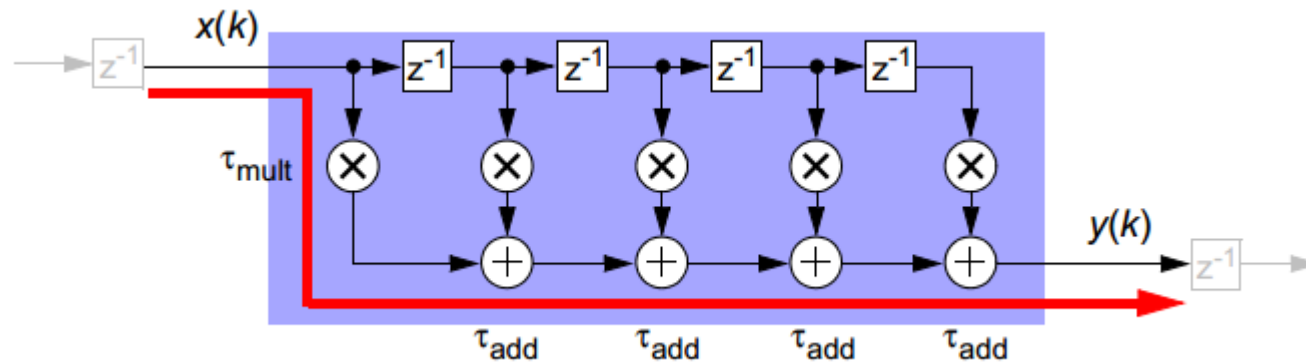

$$\text{critical path delay} = \tau_{\text{mult}} + 4\tau_{\text{add}}$$

$$f_{\text{clk(max)}} = \frac{1}{\tau_{\text{mult}} + 4\tau_{\text{add}}}$$

## N-weight Finite Impulse Response (FIR)

$$y(k) = \sum_{n=0}^{N-1} x(k-n)w_n$$

$$\tau_{\text{add}} = 0.1\text{ns} \quad \tau_{\text{mult}} = 1\text{ns}$$

$$f_{\text{clk}} = \frac{1}{1 + (4 \times 0.1)} \times 10^9 \approx 714\text{MHz}$$

$$f_{\text{clk}} = \frac{1}{1 + (9 \times 0.1)} \times 10^9 \approx 526\text{MHz}$$

*zero sample latency* between input and output

# How to Pipeline Architecture?