

# ELD Lab 4



## Design of Sequence Detector

# Objective


- Design 1011 sequence detector using behavioral modelling
- Verify the circuit using virtual input and output (VIO).
- **Lab Homework:** Change the sequence to 1111

# Finite State Machines


1101

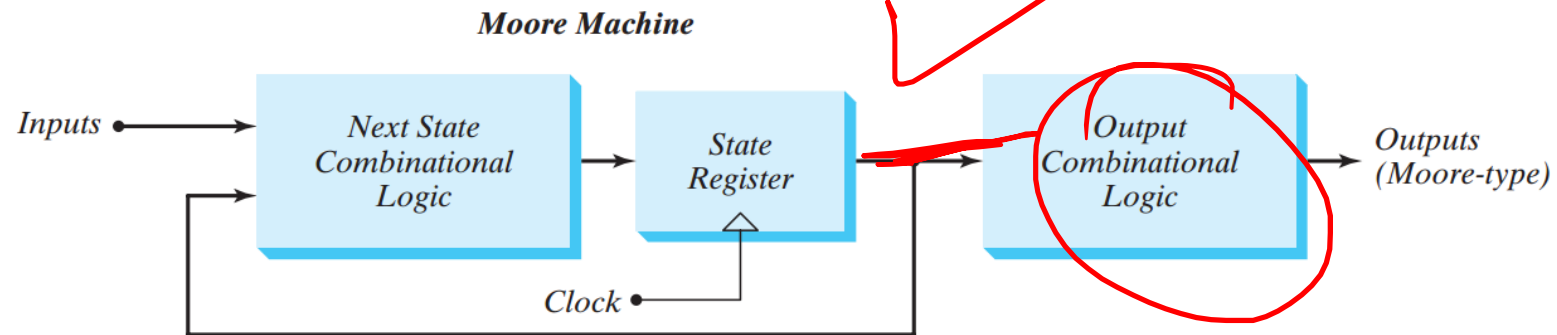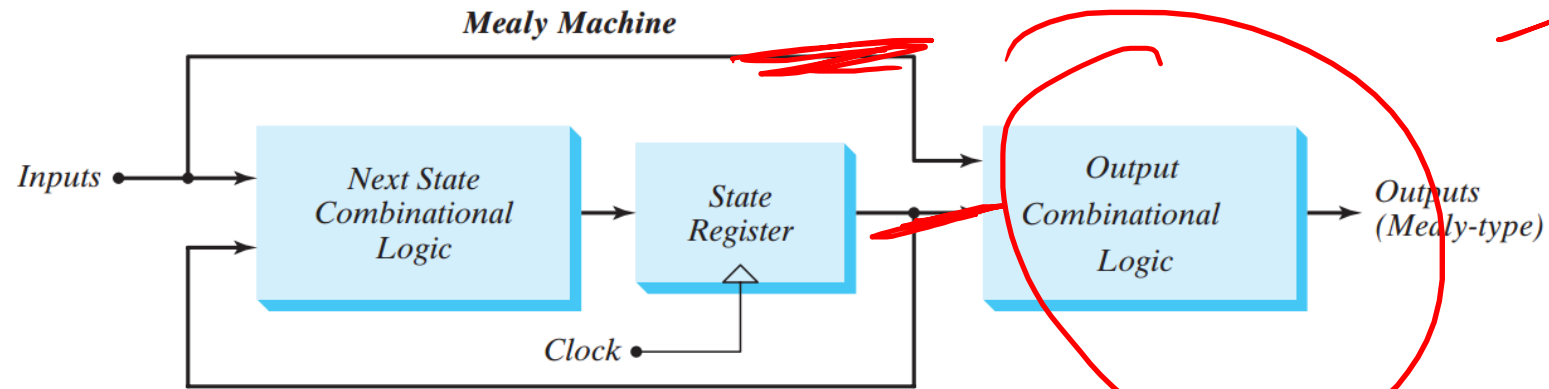

# FSM: Sequence Detector 1101 (Moore)

 


# FSM: Sequence Detector 1101 (Moore)

 

```
1 module FSM_moore_1101 (  
  input wire clk ,  
  input wire clr ,  
  input wire din ,  
  output reg dout  
);
```

```
2 reg[2:0] present_state, next_state;  
parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, // states  
          S3 = 3'b011, S4 = 3'b100;
```

# FSM: Sequence Detector 1101 (Moore)

 

3

```
// State registers
always @(posedge clk or posedge clr)
begin
    if (clr == 1)
        present_state <= S0;
    else
        present_state <= next_state;
end
```

5

```
always @(*)
begin
    if (present_state == S4)
        dout = 1;
    else
        dout = 0;
end
```

4


```
always @(*)
begin
    case (present_state)
    S0: if (din == 1)
        next_state = S1;
        else
        next_state = S0;
    S1: if (din == 1)
        next_state = S2;
        else
        next_state = S0;
    S2: if (din == 0)
        next_state = S3;
        else
        next_state = S2;
    S3: if (din == 1)
        next_state = S4;
        else
        next_state = S0;
    S4: if (din == 0)
        next_state = S0;
        else
        next_state = S2;
    default next_state = S0;
    endcase
end
```

Lab

# Proposed Approach



# FSM

 

```
module FSM_moore_1101(  
  input Clk_pb,  
  input Clear,  
  input Inp_1,  
  output reg Detect,  
  output [2:0] FSM_state  
);
```


```
parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011, S4 = 3'b100;  
reg [2:0] present_state = S0;  
reg [2:0] next_state;
```

```
always@(posedge Clk_pb or posedge Clear)  
begin  
  if (Clear)  
    present_state <= S0;  
  else  
    present_state <= next_state;  
end
```

```
always@(*)  
begin  
  if(present_state == S4)  
    Detect = 1;  
  else  
    Detect = 0;  
end  
assign FSM_state = present_state;
```

```
always@(*)  
begin  
  case(present_state)  
    S0: if(Inp_1 == 1)  
      next_state = S1;  
      else  
        next_state = S0;  
    S1: if(Inp_1 == 1)  
      next_state = S2;  
      else  
        next_state = S0;  
    S2: if(Inp_1 == 0)  
      next_state = S3;  
      else  
        next_state = S2;  
    S3: if(Inp_1 == 1)  
      next_state = S4;  
      else  
        next_state = S0;  
    S4: if(Inp_1 == 0)  
      next_state = S0;  
      else  
        next_state = S2;  
    default next_state = S0;  
  endcase  
end
```


# Detection of Push Button Press

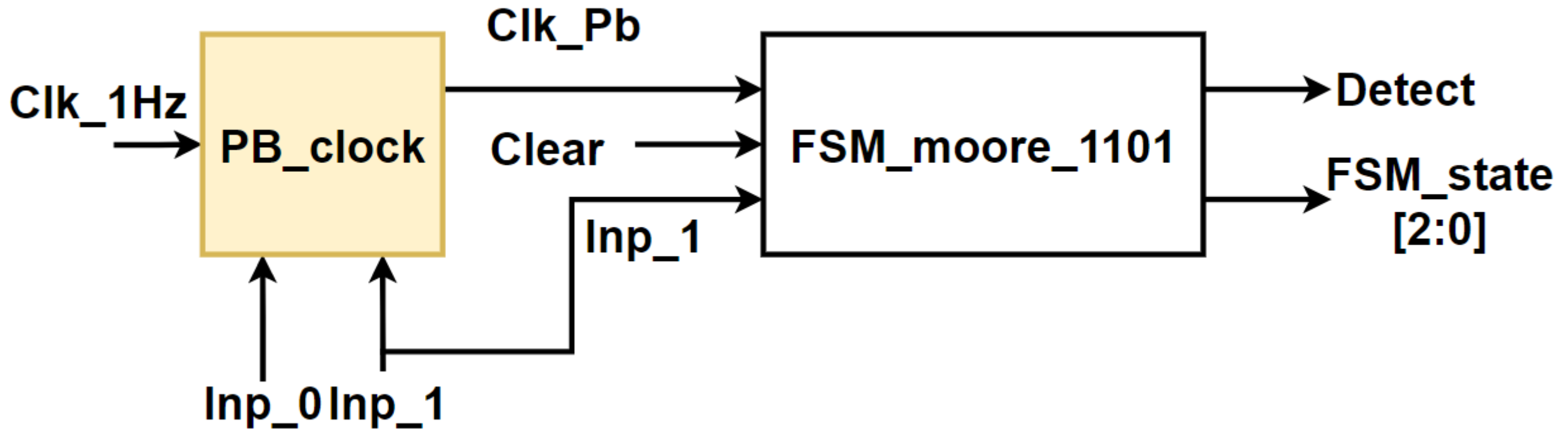


# Detection of Push Button Press

```
module PB_clock(  
    input Clk_1Hz,  
    input Inp_0,  
    input Inp_1,  
    output reg Clk_pb  
);  
wire Inp_pulse;  
assign Inp_pulse = Inp_0 | Inp_1;  
  
always@(posedge Clk_1Hz)  
    Clk_pb <= Inp_pulse;  
  
endmodule
```

# FSM with Clock Division

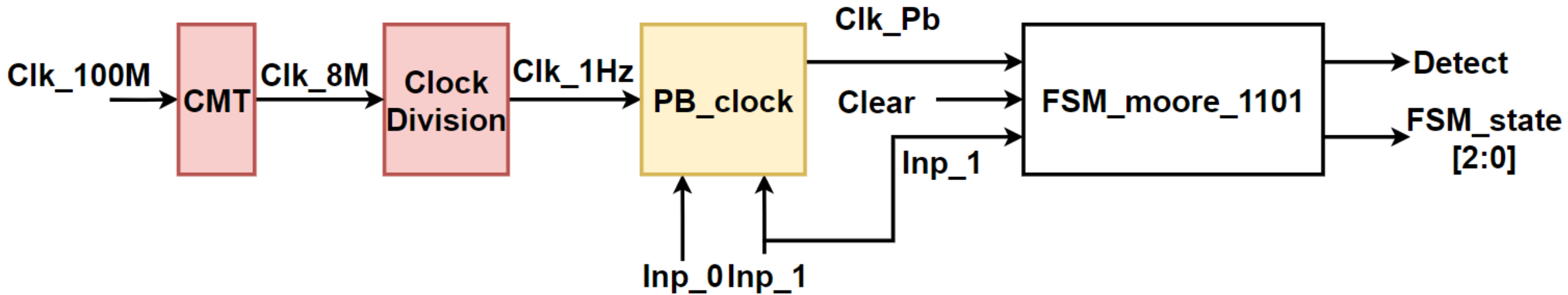


# VIO Wrapper

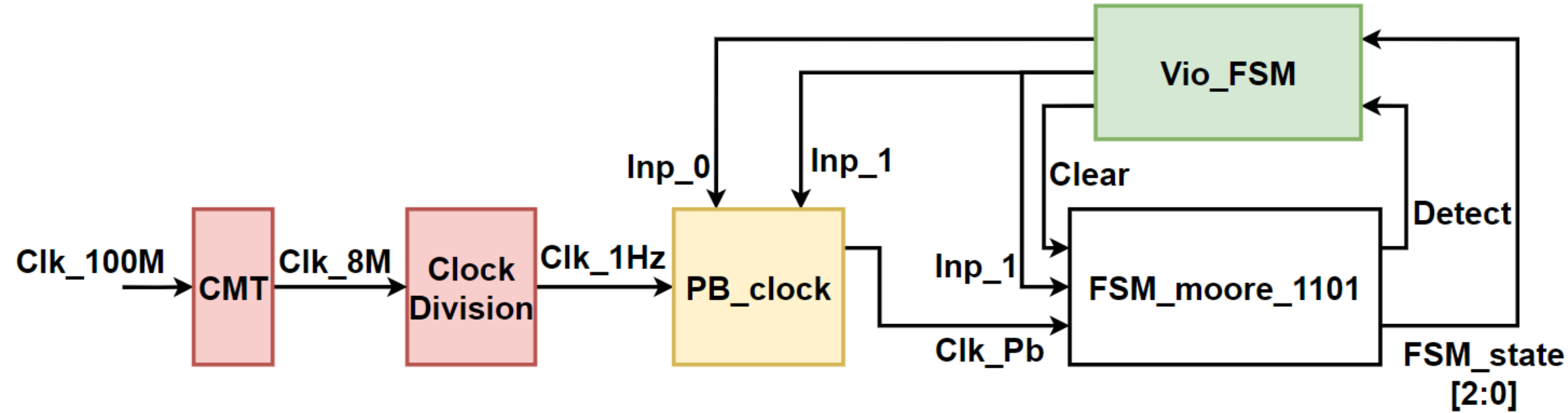
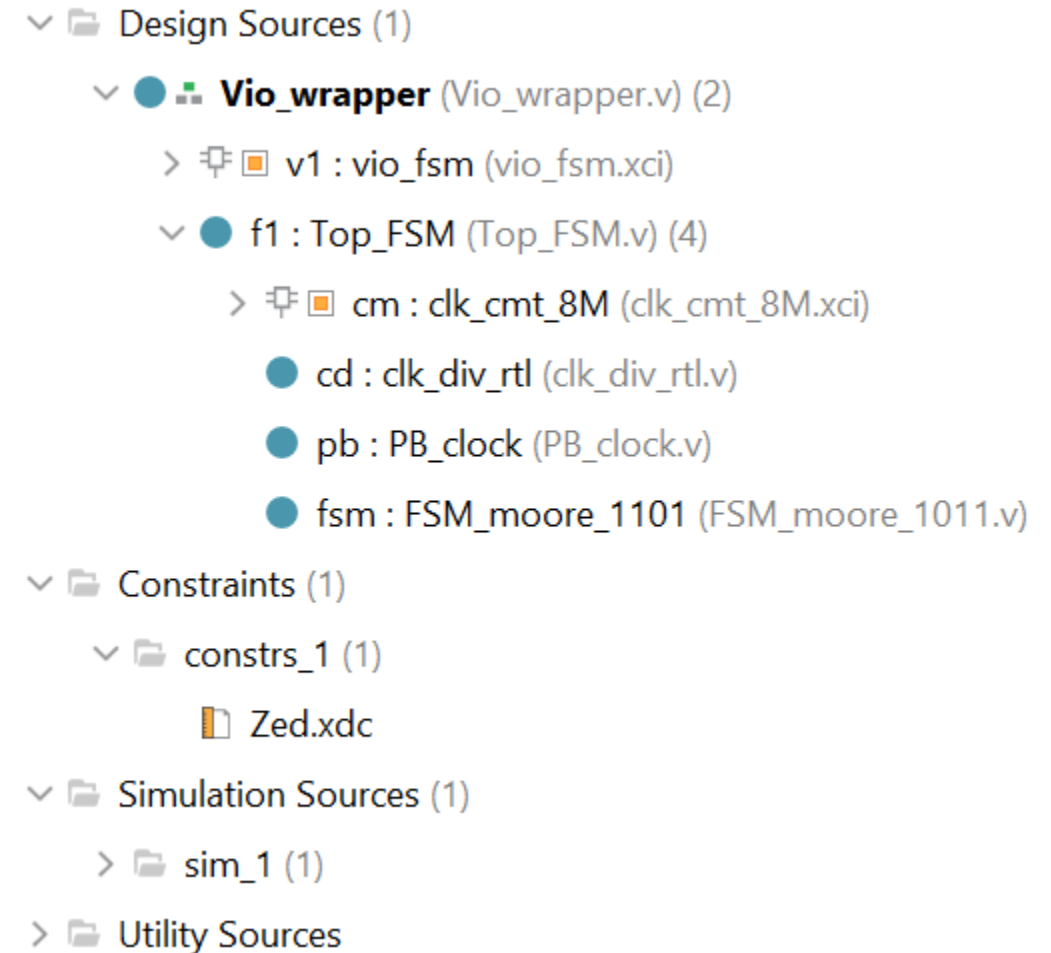
# Demo

- Add XDC file and generate bitstream
- Verify the functionality using VIO
- Use toggle button option in VIO



# Possible Extensions

- Moore/Mealy FSMs for any sequence
- Asynchronous/Synchronous active high/low Clear
- Change the FSM input clock to Clk\_xHz where x can be any positive integer
- Design a counter (2->4->8->2->4->8.....) using FSM
- FSM with two outputs: Detect and Error. Detect is set to 1 when sequence is correct and Error is set to 1 when sequence is wrong.