

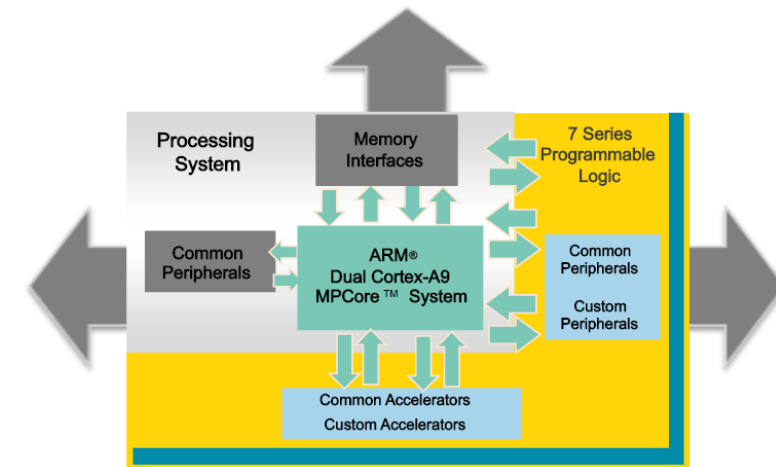


 


ECE 270: Embedded Logic Design

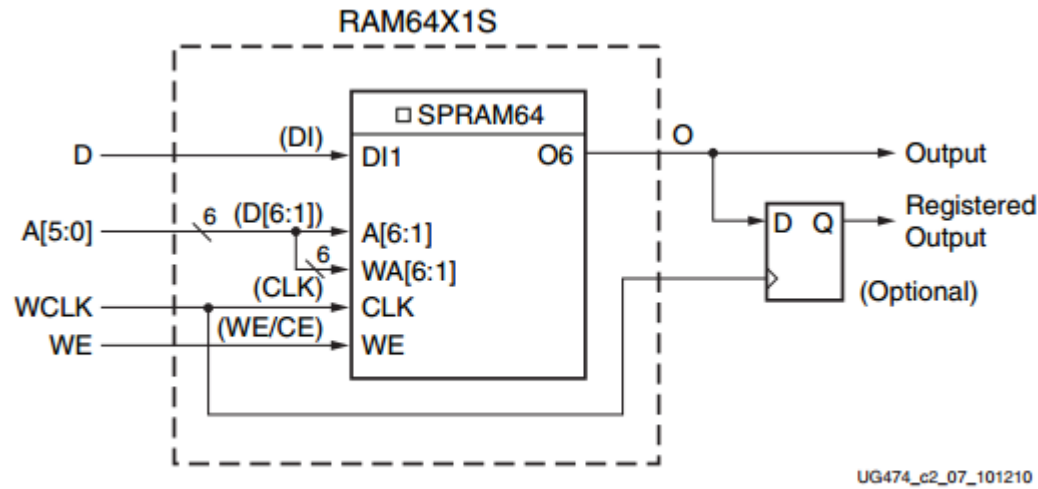

LUT as Memory: 64X1 Dual Port




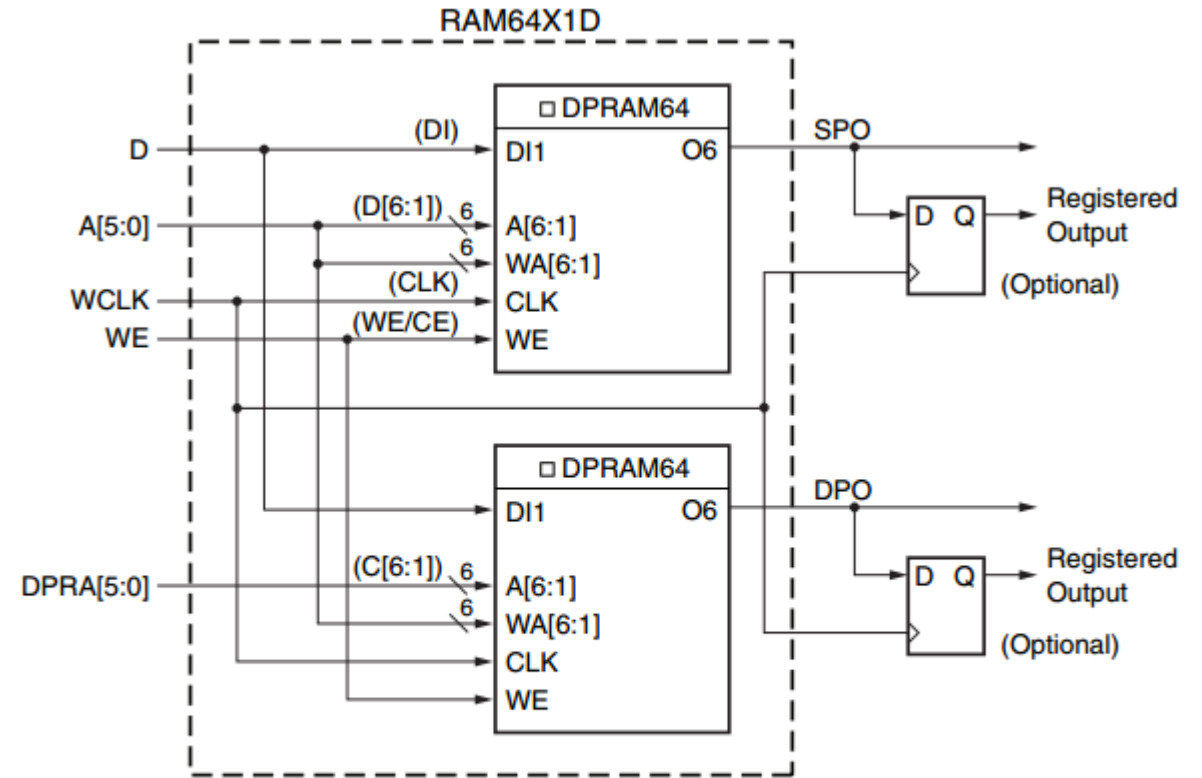64 X 1 Single Port Distributed RAM (RAM64X1S)



64 X 1 Dual Port Distributed RAM (RAM64X1D)


LUT as Memory: 64X1 Quad Port

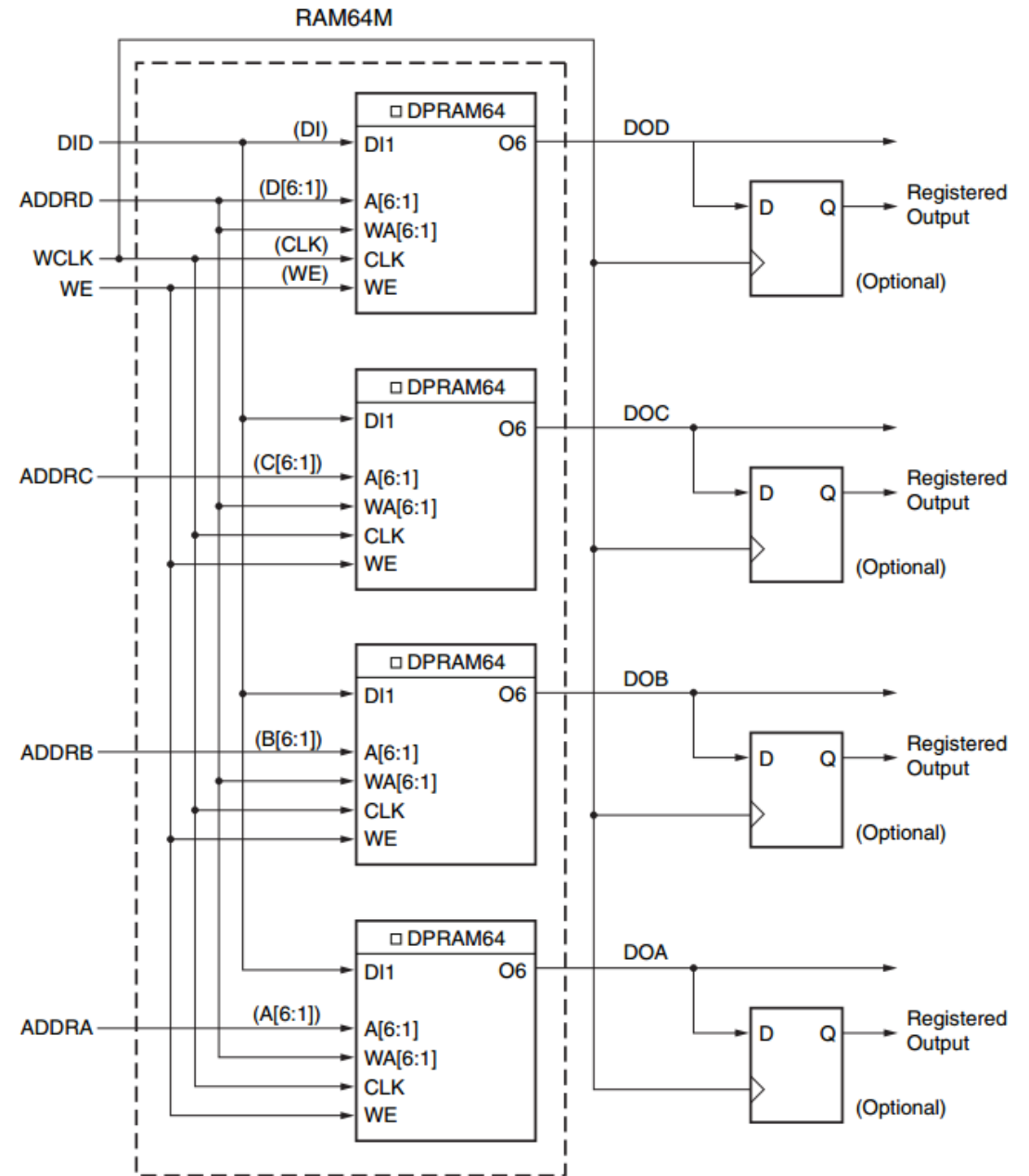

UG474_c2_09_070914

64 X 1 Quad Port Distributed RAM (RAM64M)

LUT as Memory: 64X3 Simple Dual Port

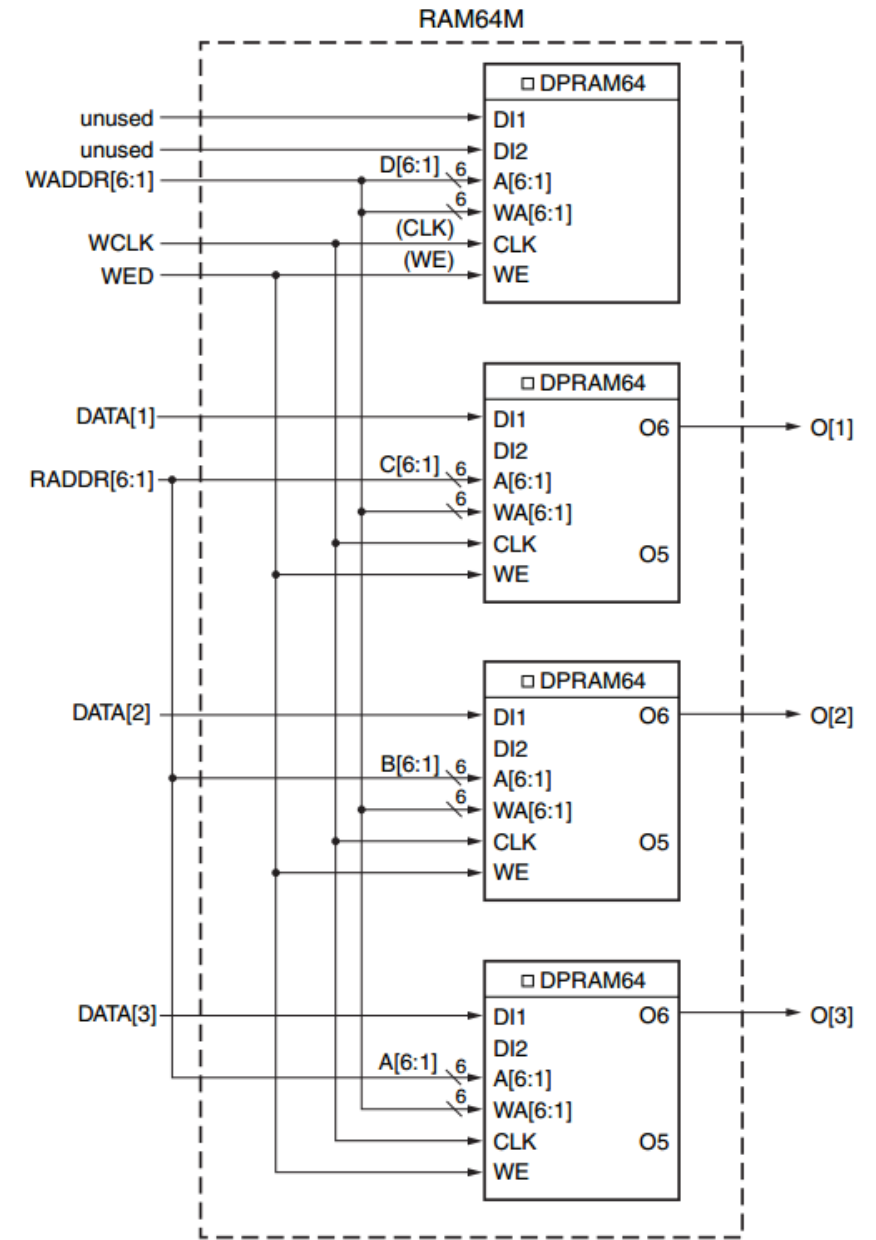


UG474_c2_10_070

64 X 3 Simple Dual Port Distributed RAM (RAM64I)


LUT as Memory: 128X1 Single Port

- Implementation of **distributed RAM configurations** with **depth greater than 64** requires the usage of **wide-function multiplexers (F7AMUX, F7BMUX, and F8MUX)**
- One SLICEM can have **TWO single port 128 x 1-bit memories** as long as they share **the same clock, write enable, and shared read and write port address inputs**
- This configuration equates to a **128 x 2-bit single-port distributed RAM**.

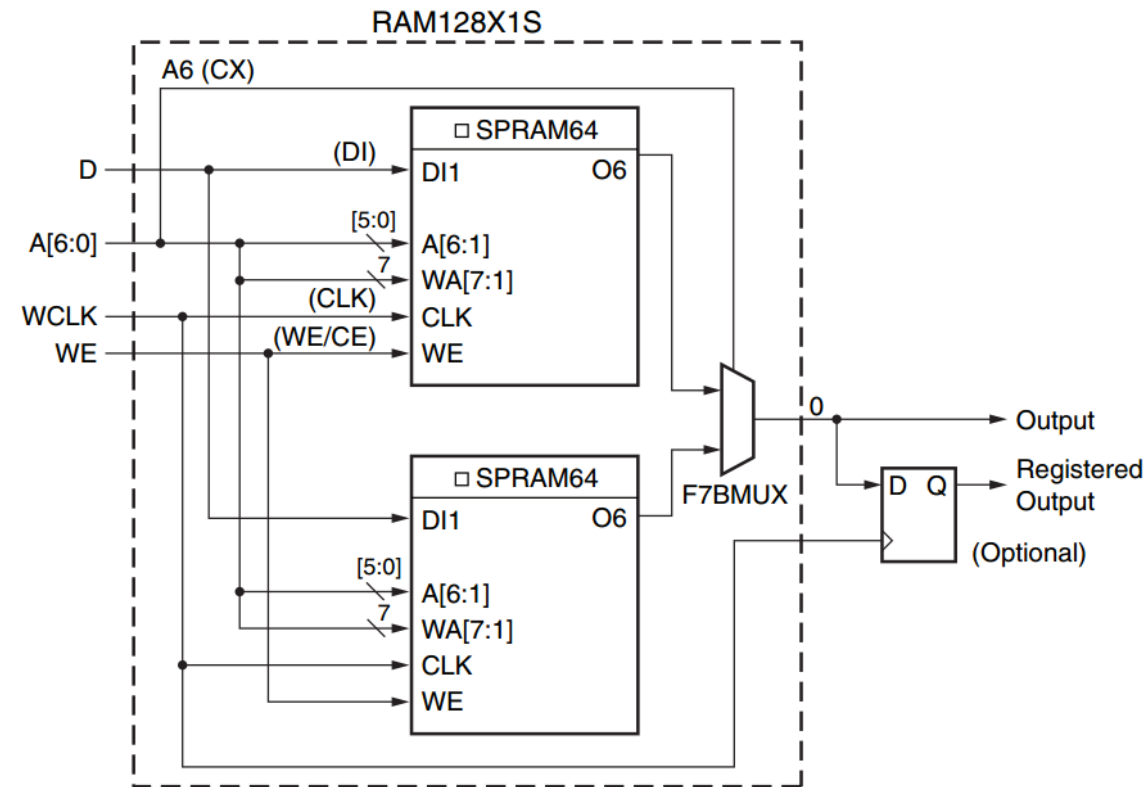


UG474_c2_11_101210

128 X 1 Single Port Distributed RAM (RAM128X1S)

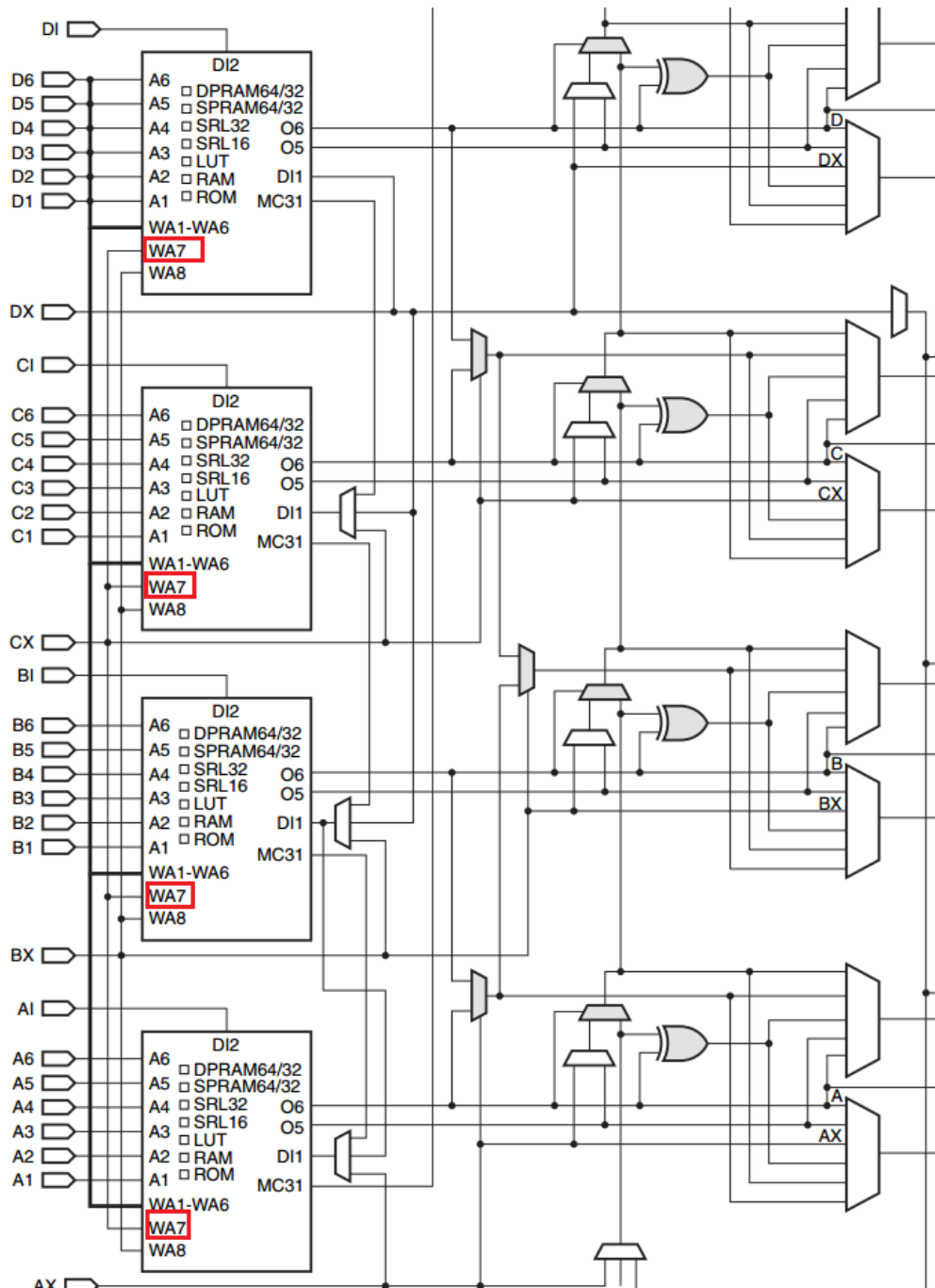

WA7: Enable for 7-input LUT

WA8: Enable for 8-input LUT

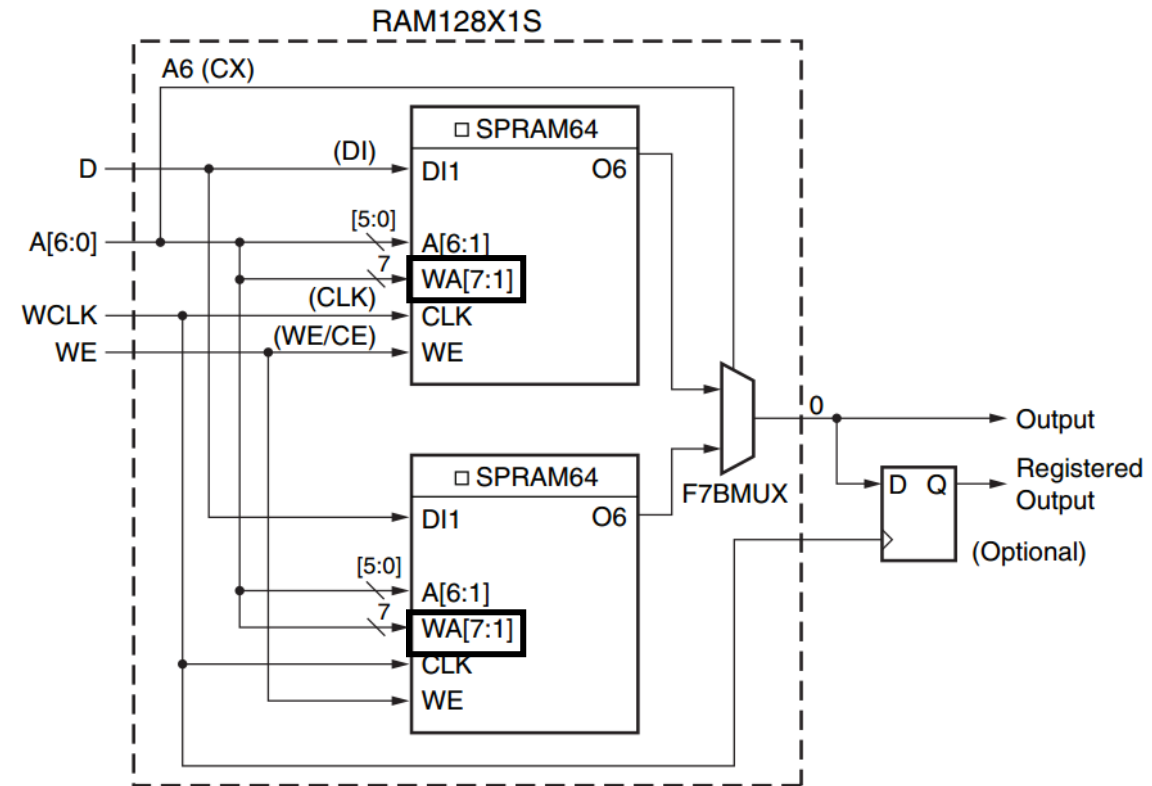


UG474_c2_11_101210

128 X 1 Single Port Distributed RAM (RAM128X1S)

LUT as Memory: 128X1 Dual Port


- 128X1 Quad Port?
- 128X2 Dual Port?

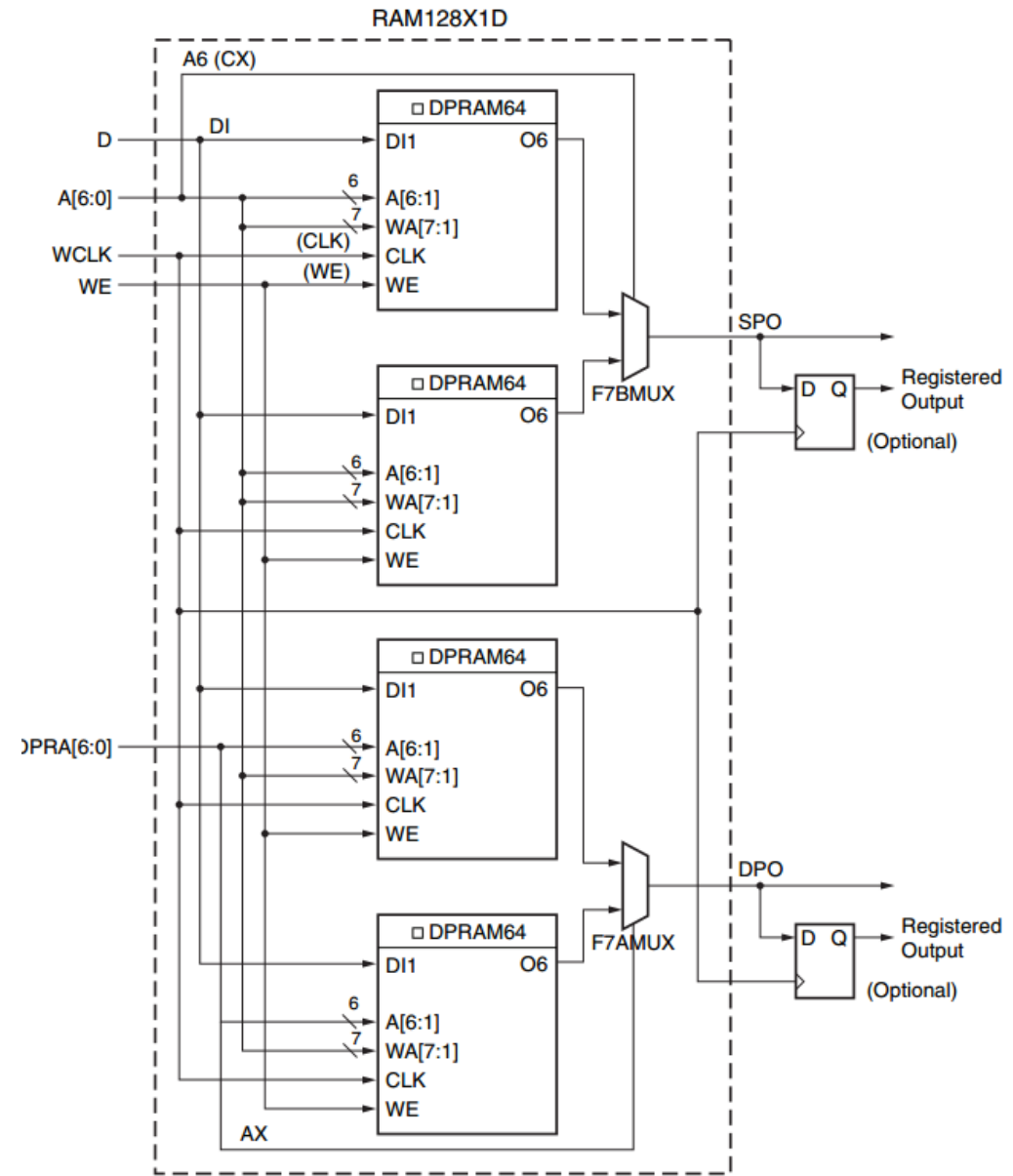

UG474_c2_12_101210


128 X 1 Dual Port Distributed RAM (RAM128X1D)

LUT as Memory: 256X1 Single Port

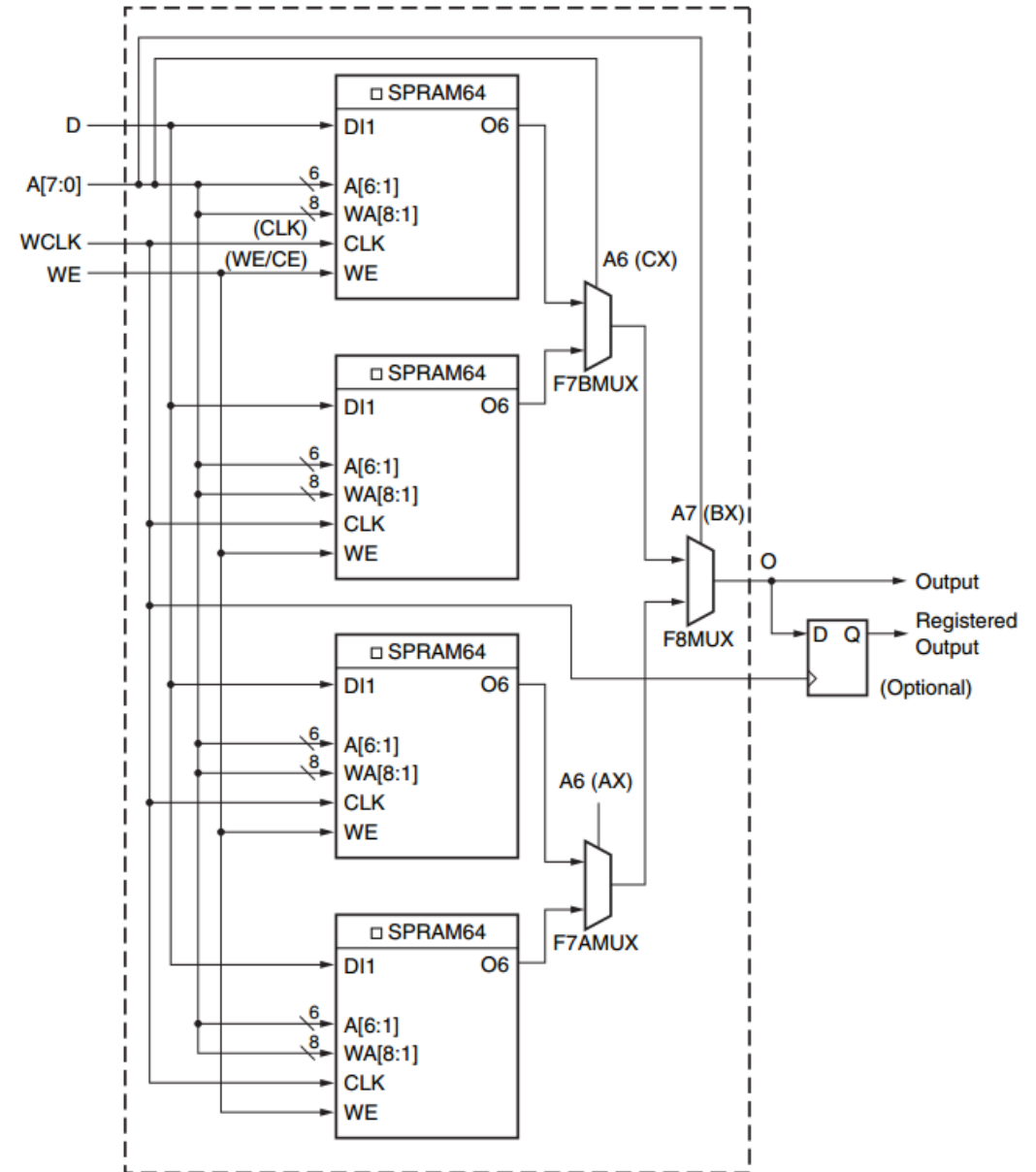

256 X 1 Single Port Distributed RAM (RAM256X1S)

LUT as Memory: 32X2 Quad Port

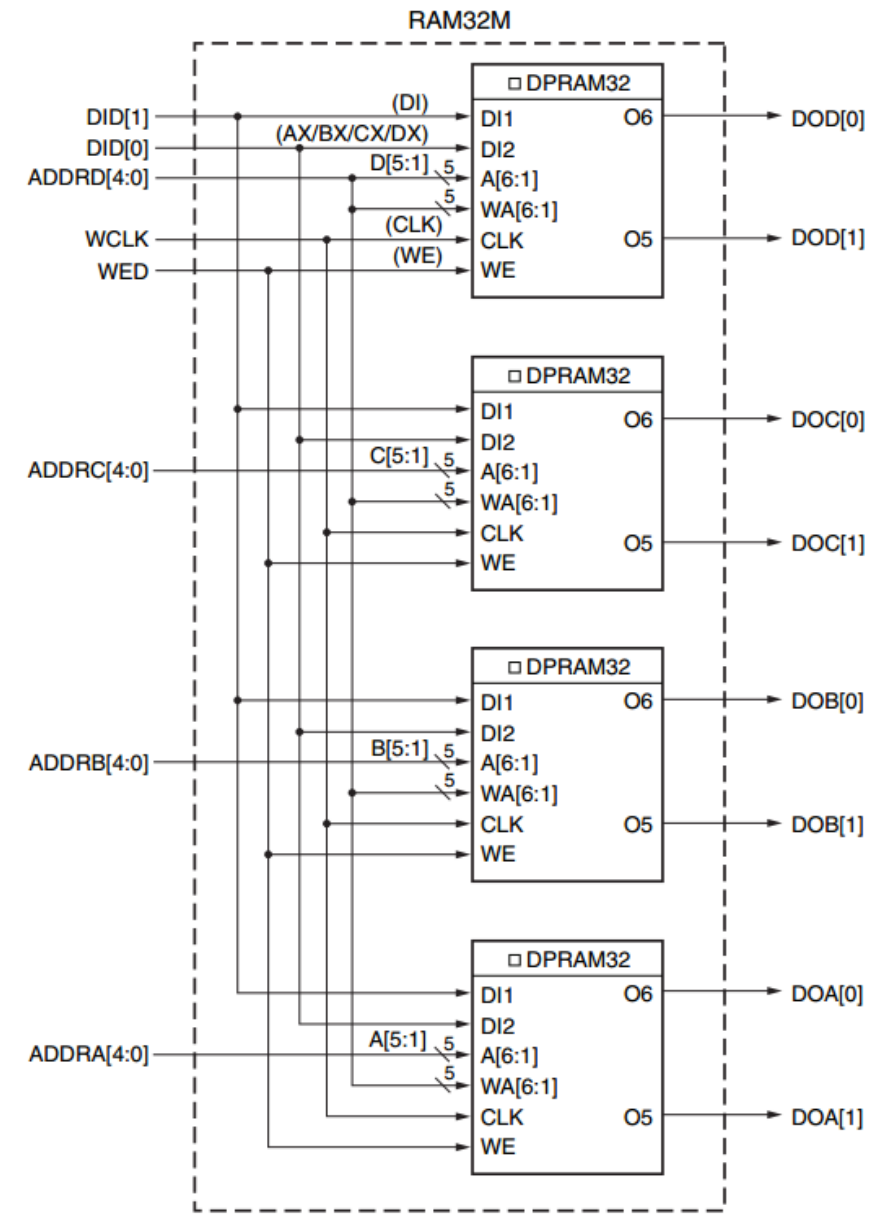


UG474_c2_06_070914

32 X 2 Quad Port Distributed RAM (RAM32M)

LUT as Memory:
32X8 Simple Dual Port

LUT as Memory: 32X6 Simple Dual Port

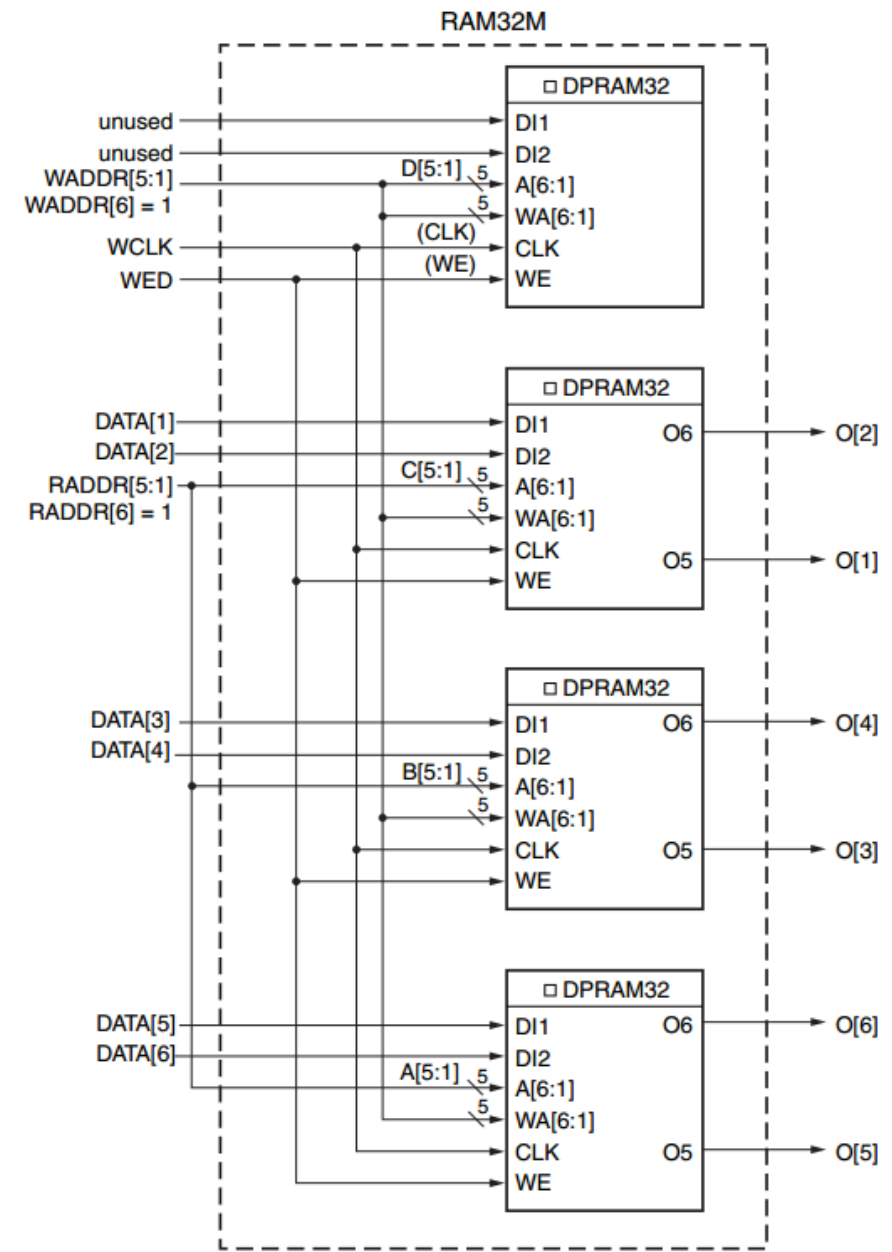

UG474_c2_06_07091

32 X 6 Simple Dual Port Distributed RAM (RAM32M)

LUT as Memory

RAM	Description	Primitive	Number of LUTs
32 x 1S	Single port	RAM32X1S	1
32 x 1D	Dual port	RAM32X1D	2
32 x 2Q	Quad port	RAM32M	4
32 x 6SDP	Simple dual port	RAM32M	4
64 x 1S	Single port	RAM64X1S	1
64 x 1D	Dual port	RAM64X1D	2
64 x 1Q	Quad port	RAM64M	4
64 x 3SDP	Simple dual port	RAM64M	4
128 x 1S	Single port	RAM128X1S	2
128 x 1D	Dual port	RAM128X1D	4
256 x 1S	Single port	RAM256X1S	4

Single Port	Dual Port	Simple Dual Port	Quad Port
32x2	32x2D	32x6SDP	32x2Q
32x4	32x4D	64x3SDP	64x1Q
32x6	64x1D		
32x8	64x2D		
64x1	128x1D		
64x2			
64x3			
64x4			
128x1			
128x2			
256x1			


Each Port Has Independent Address Inputs

LUT as SRL

Sequential Circuits


- 4-bit serial shift register:
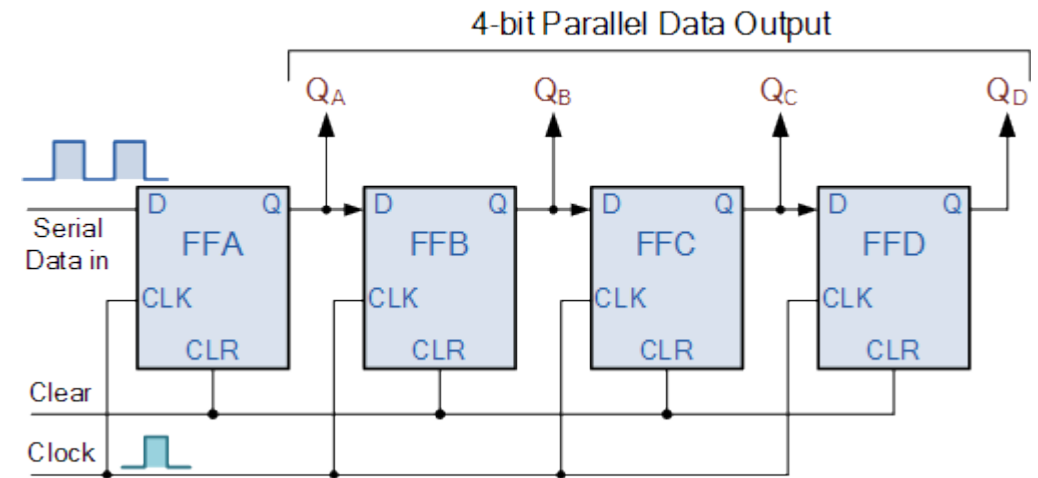
```
module ShiftReg(  
    input wire clk,  
    input wire clr,  
    input wire data_in,  
    output reg [3:0] Q  
);  
  
//      4-bit Shift Register  
always @(posedge clk or posedge clr)  
begin  
    if(clr == 1)  
        Q <= 0;  
    else  
        begin  
            Q[3] <= data_in;  
            Q[2:0] <= Q[3:1];  
        end  
    end  
end  
endmodule
```




Shift Register Using FFs

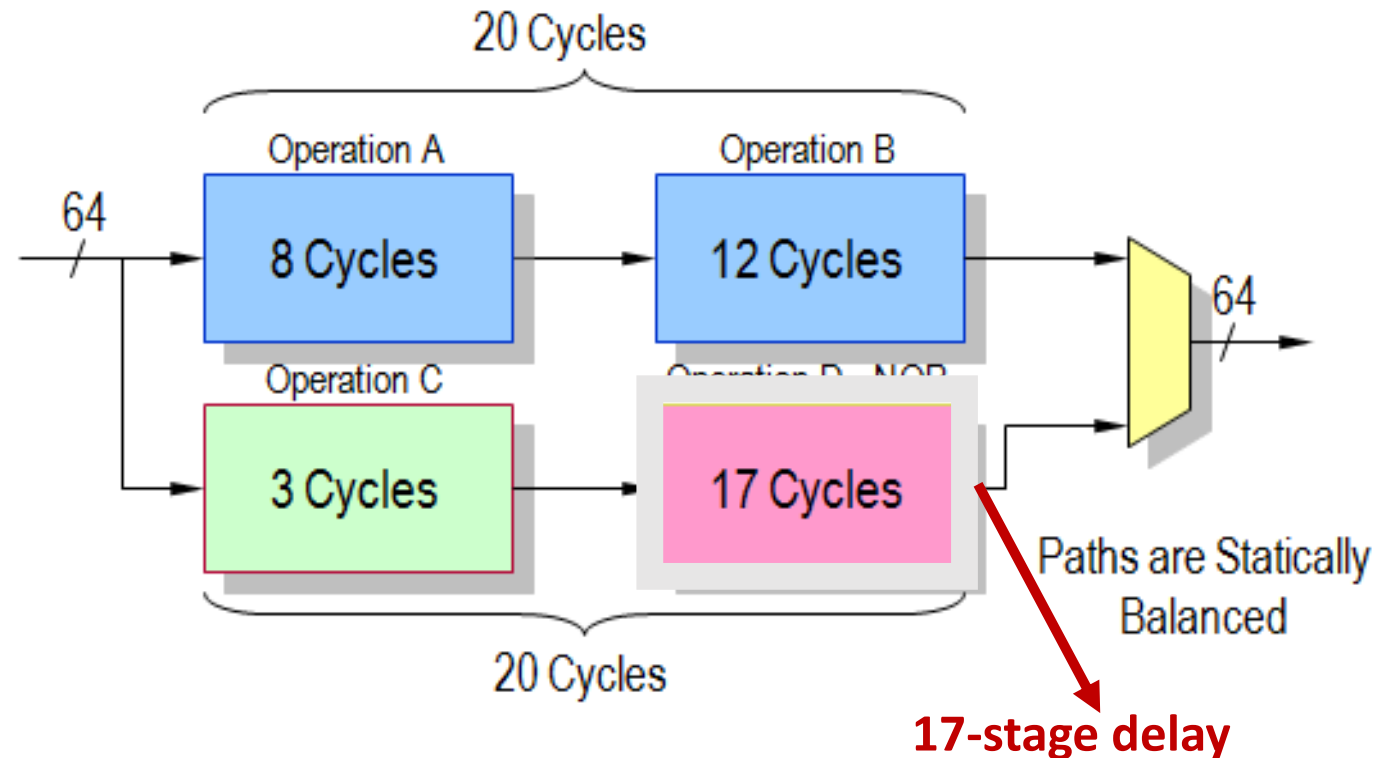
- Operation D - NOP must add 17 pipeline stages of 64 bits each
 - 1,088 flip-flops (hence 136 slices)



LUT as Shift Registers (only in SLICEM)

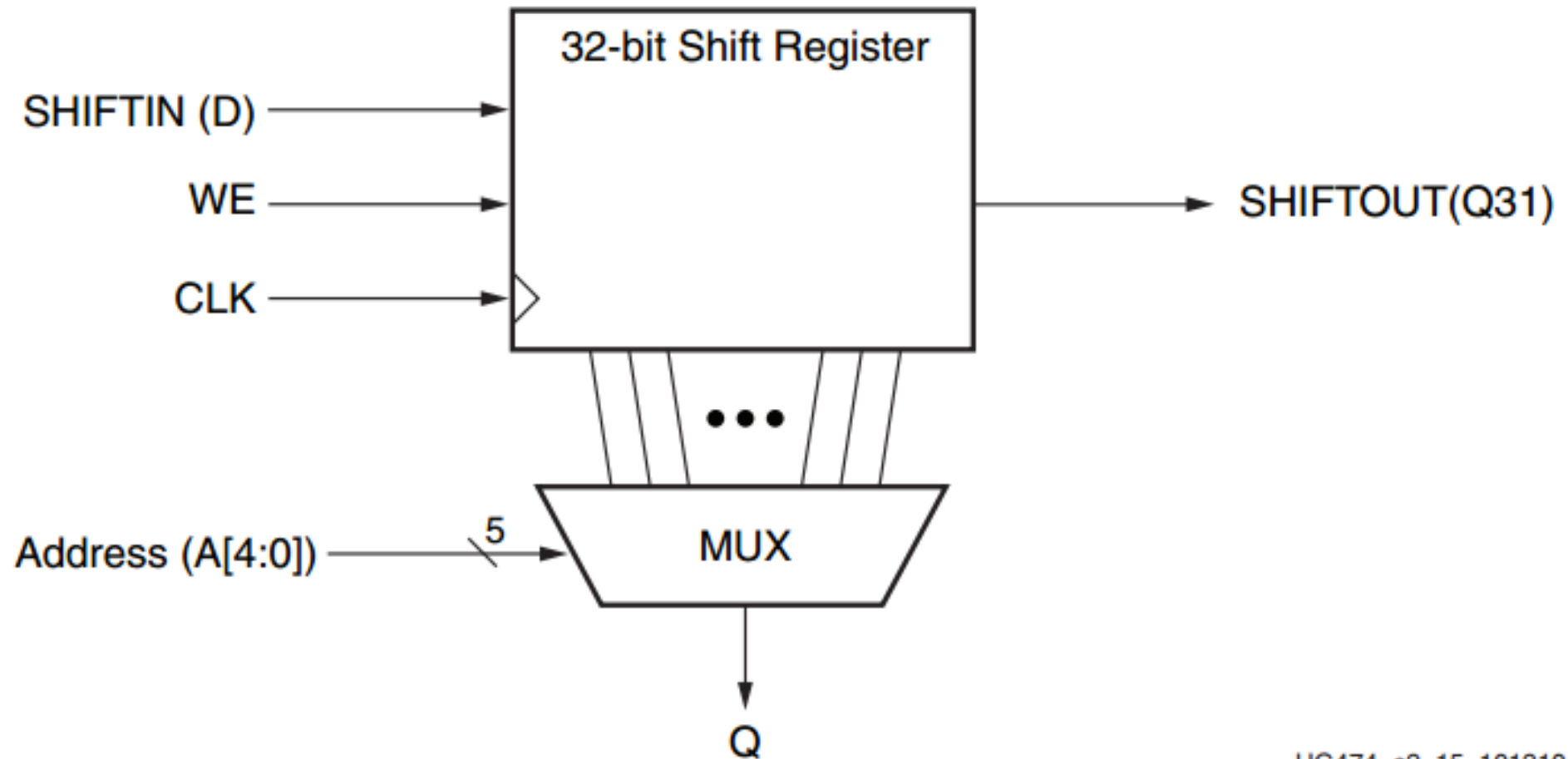


SLICEM

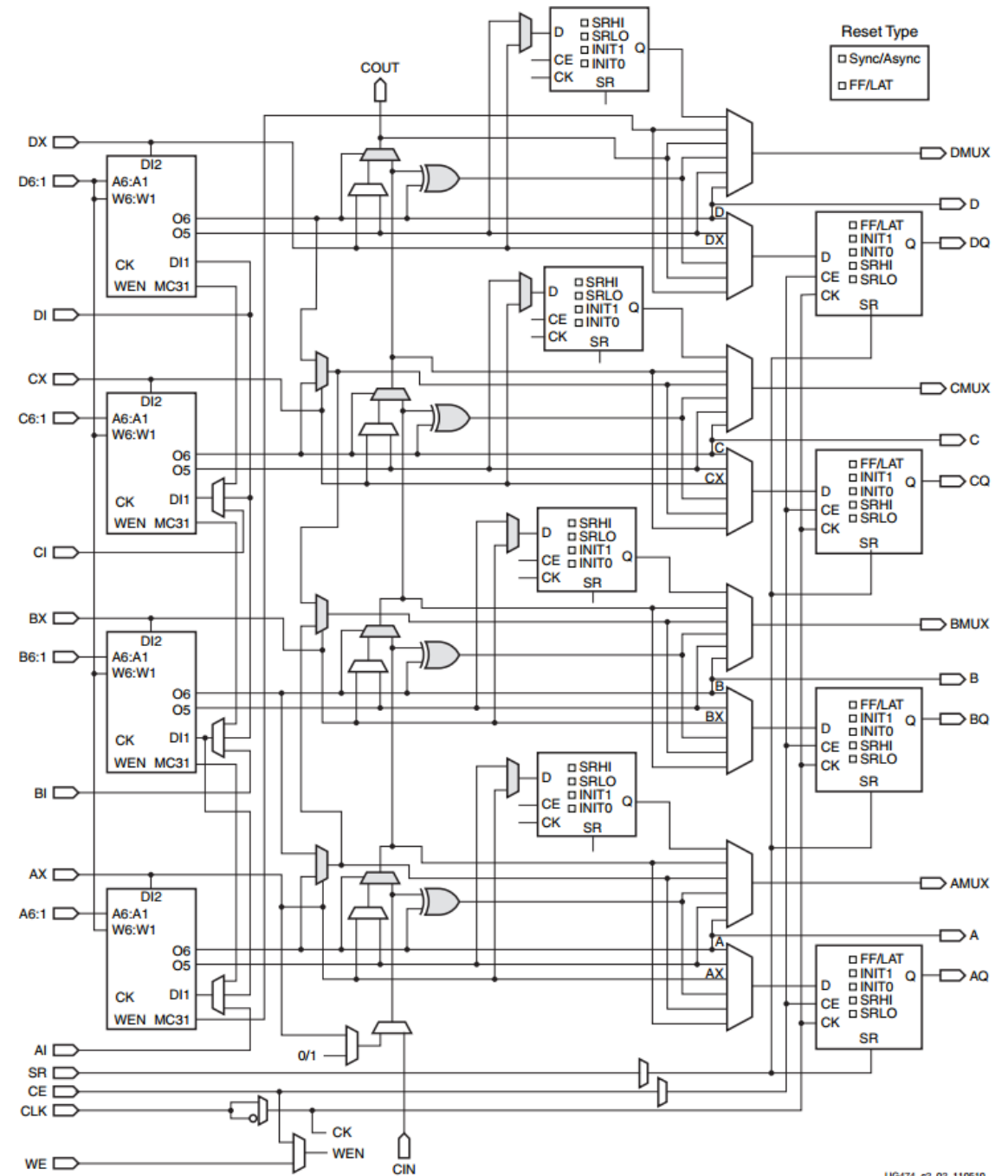

LUT as Shift Registers (only in SLICEM)


- Shift register functions include:
 - **Write operation** (Synchronous with a clock input and an optional clock enable)
 - **Fixed read access to Q31**
 - **Dynamic read access:**
 - Performed through **5-bit address bus** (LSB is unused)
 - Any of the 32 bits can be read out **asynchronously** by controlling the address
 - Useful for **smaller shift registers**
 - Flip-flop can be used for synchronous read with one additional latency
 - **Set/reset is not supported**

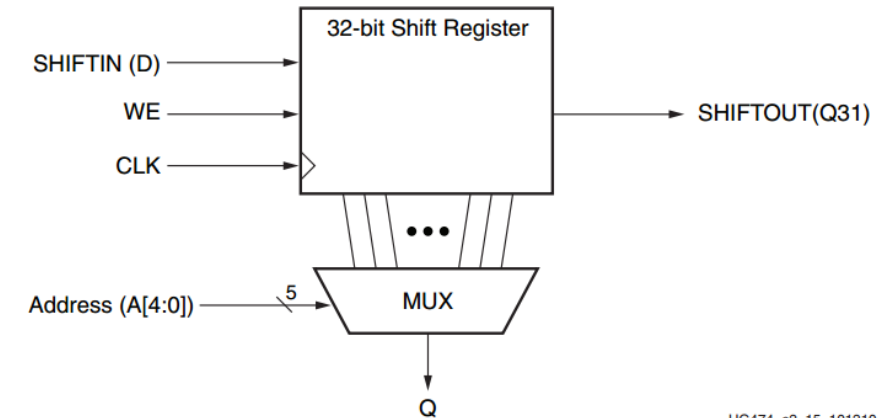



UG474_c2_15_101210

LUT as Shift Registers (only in SLICEM)

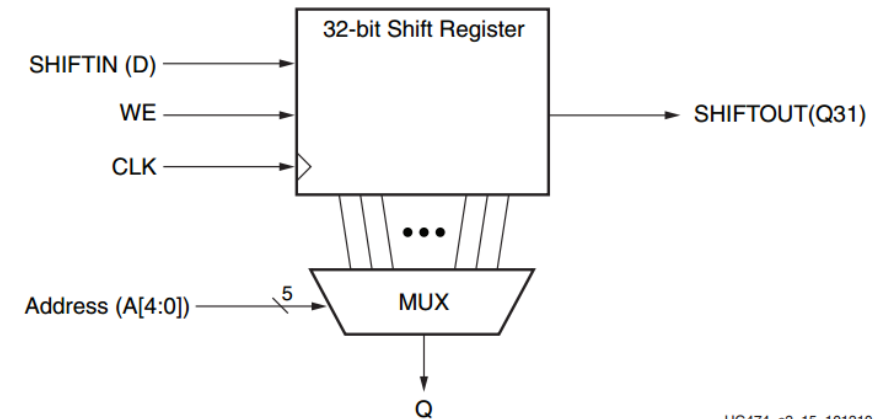- A **SLICEM LUT** can be configured as a **32-bit shift register** without using the flip-flops available in a slice.




UG474_c2_15_101210

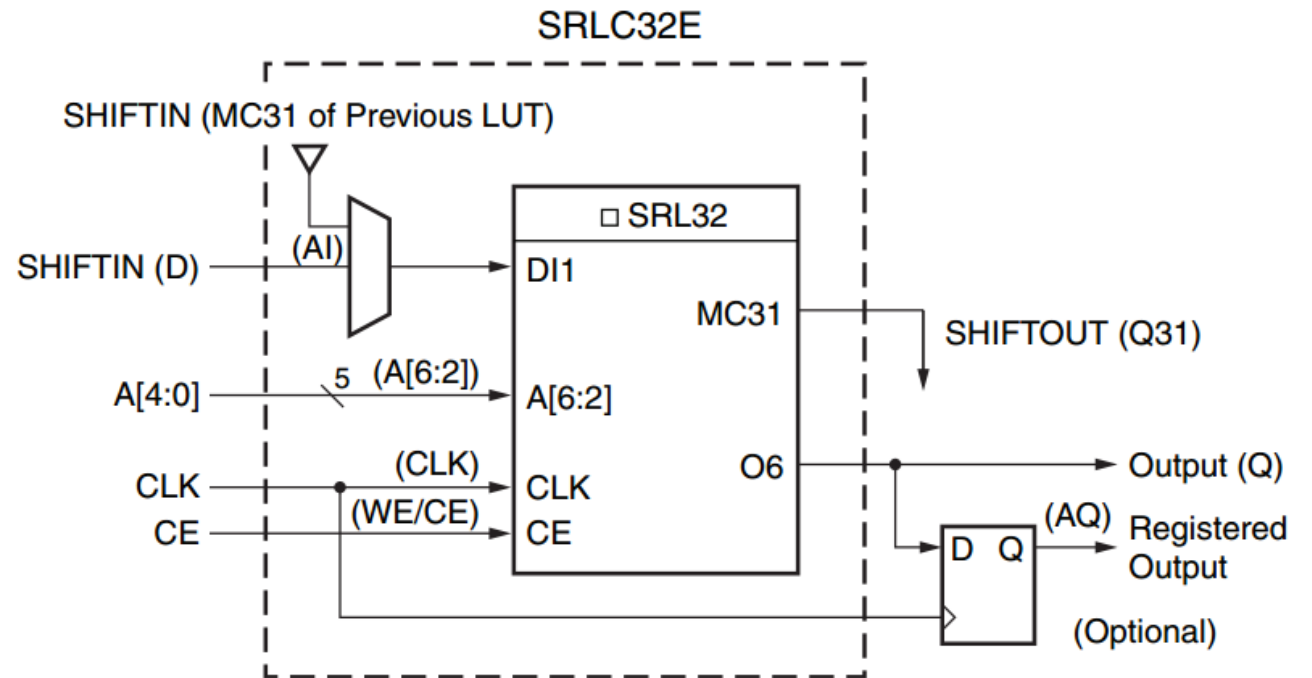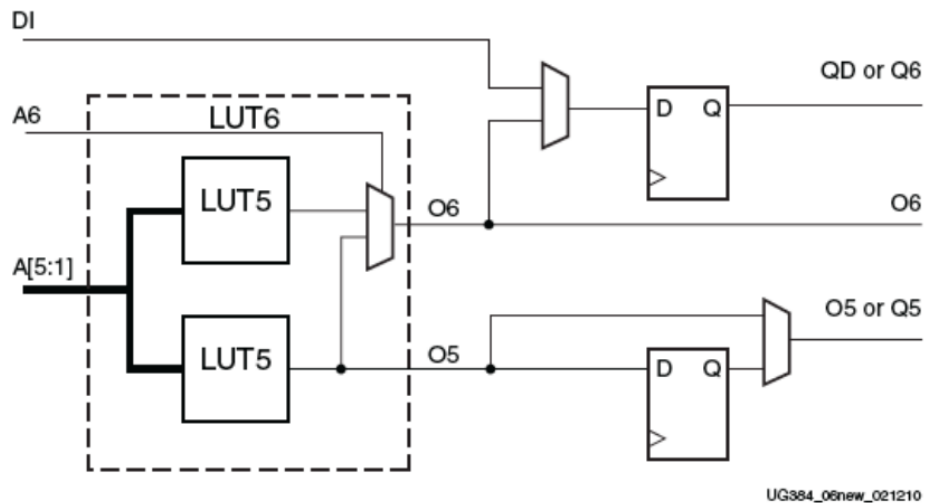

UG474_c2_14_110510


LUT as Shift Registers: 64 Bit

- MC31 output and a dedicated connection between LUTs allows connecting the last bit of one shift register to the first bit of the next, without using the LUT O6 output.
- Longer shift registers can be built with dynamic access to any bit in the chain.
- The shift register chaining and the F7AMUX, F7BMUX, and F8MUX multiplexers allow up to a 128-bit shift register with addressable access to be implemented in one SLICEM

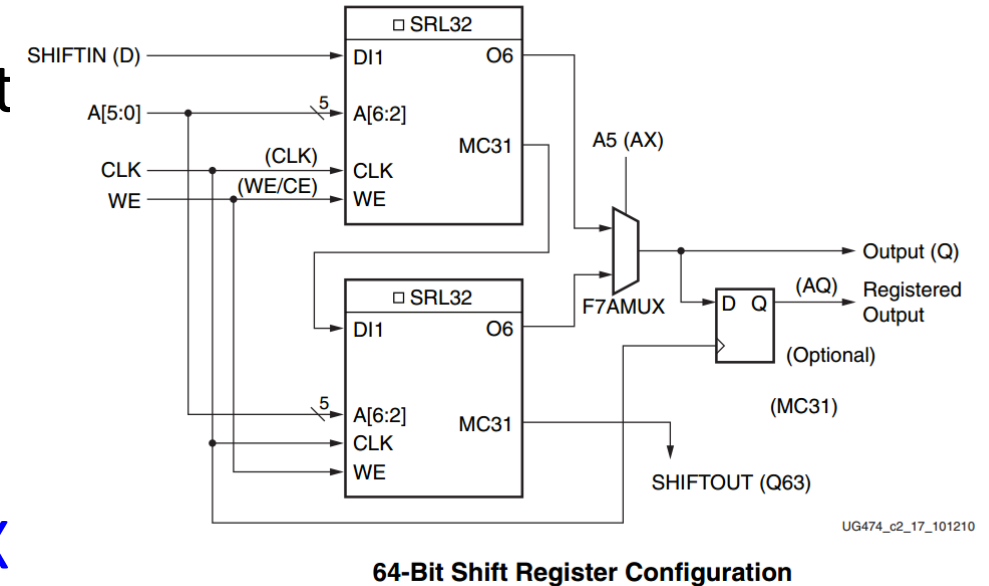

Shift Register

96 Bit

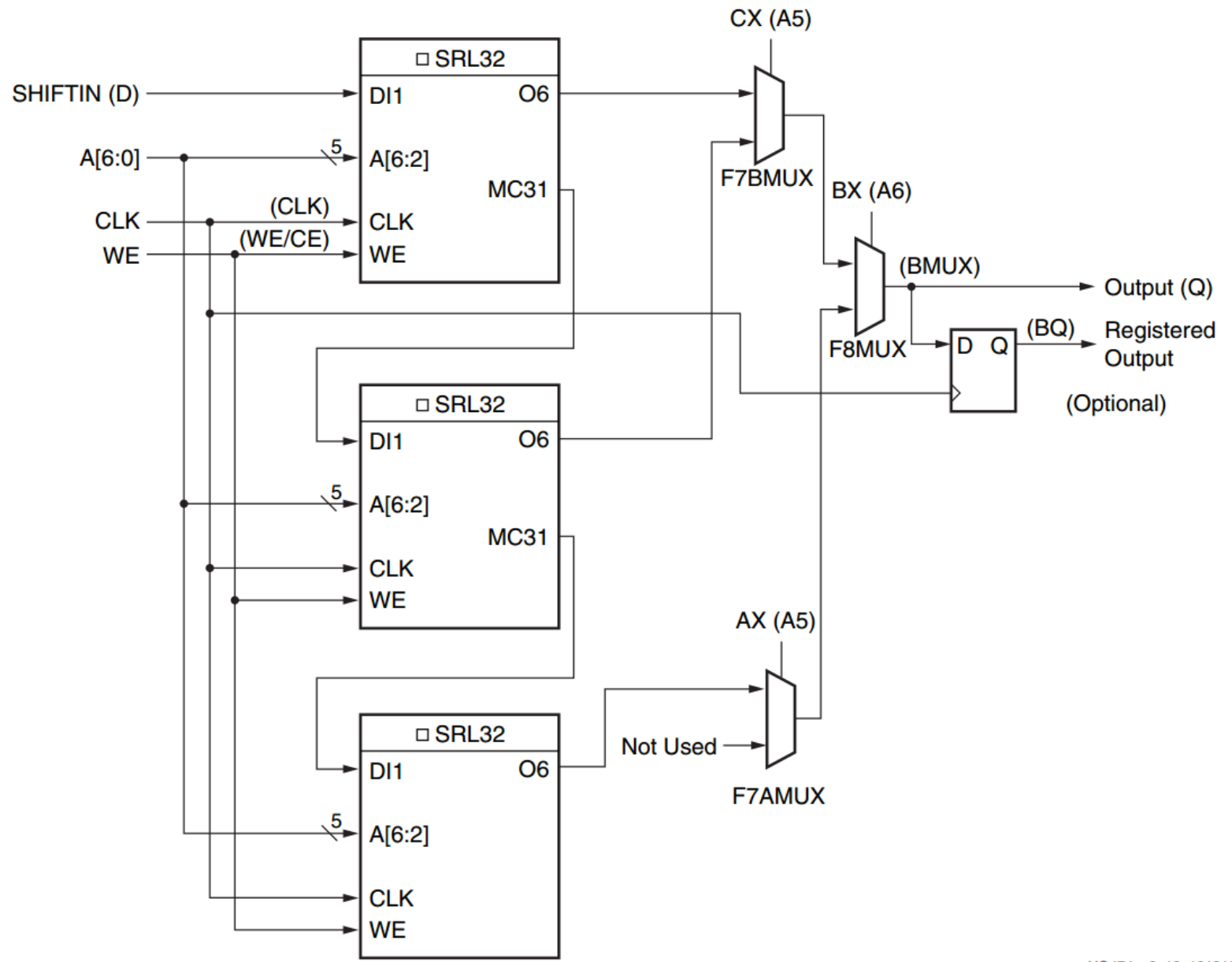


Shift Register

256 Bit


Shift Register

128 Bit

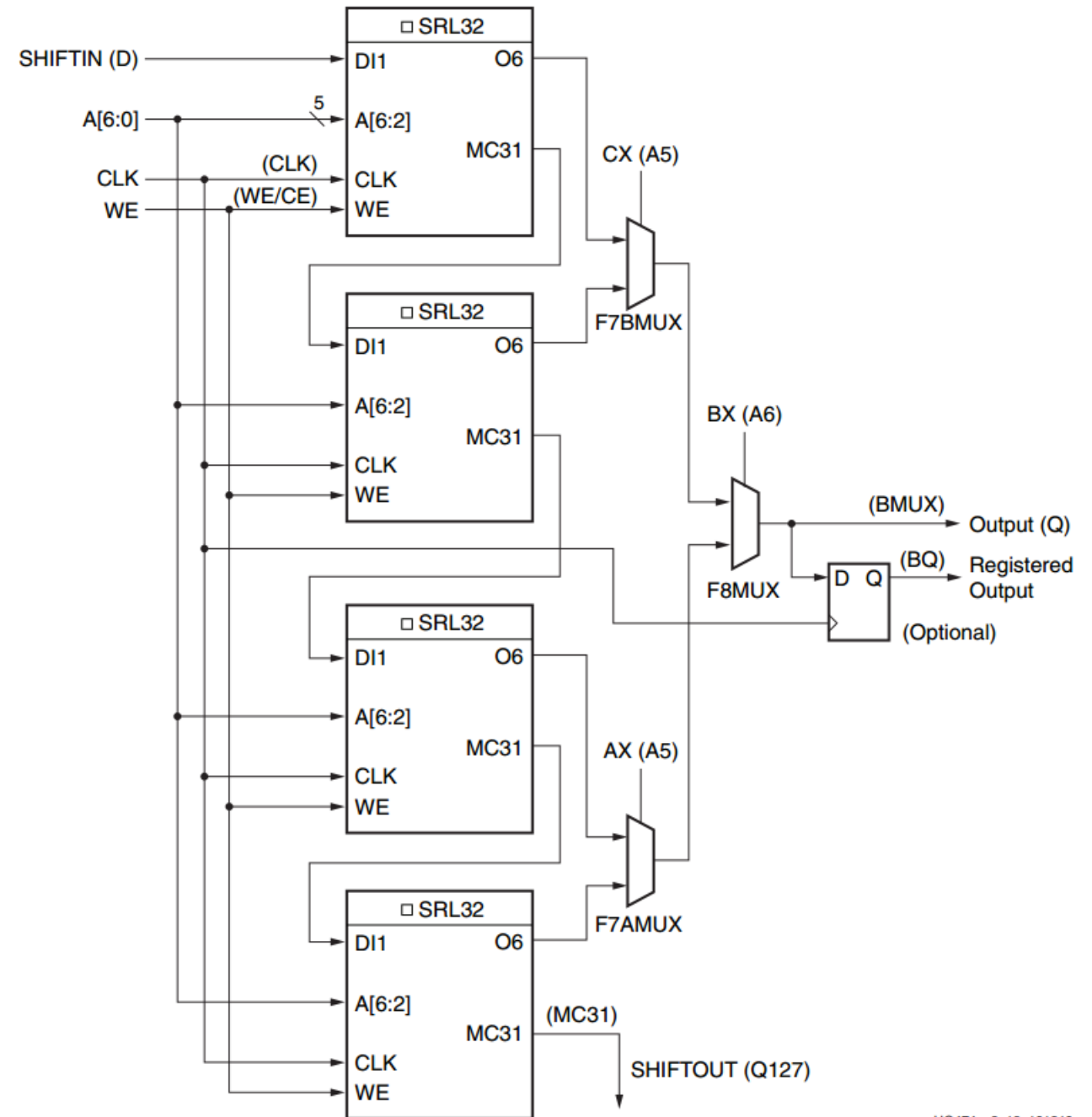

Shift Register LUT Example

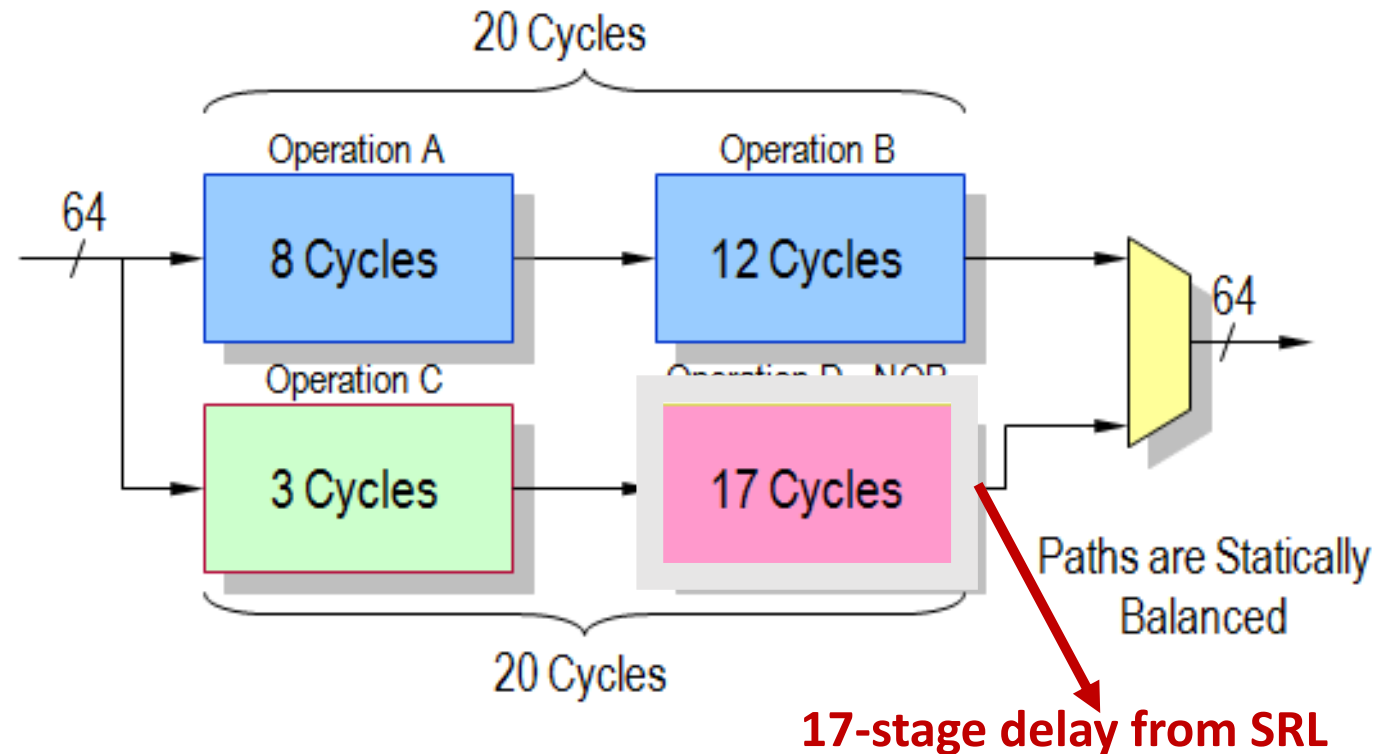- Operation D - NOP must add 17 pipeline stages of 64 bits each
 - 1,088 flip-flops (hence 136 slices) or
 - 64 SRLs (hence 16 slices)



Shift Register LUT Example

The screenshot displays the Vivado IDE interface. On the left, the 'Project Manager' pane shows the project structure with 'top_moo' as the main source. The 'Project Settings' dialog box is open, showing the 'Synthesis' tab. The 'Strategy' is set to 'Vivado Synthesis Defaults (Vivado Synthesis 2015)'. The 'Options' section contains a table of synthesis parameters.

Option	Value
-bufg	12
-fanout_limit	10,000
-directive	Default
-fsm_extraction	auto
-keep_equivalent_registers	<input type="checkbox"/>
-resource_sharing	auto
-control_set_opt_threshold	auto
-no_lc	<input type="checkbox"/>
-shreg_min_size	3
-max_bram	-1
-max_dsp	-1
-cascade_dsp	auto
More Options	


Below the table, the option **-shreg_min_size** is described: Minimum length for chain of registers to be mapped onto SRL.

Types of CLB Slices

Slices	LUTs	Flip-Flops	Arithmetic and Carry Chains	Distributed RAM ⁽¹⁾	Shift Registers ⁽¹⁾
2	8	16	2		

Types of CLB Slices

Slices	LUTs	Flip-Flops	Arithmetic and Carry Chains	Distributed RAM ⁽¹⁾	Shift Registers ⁽¹⁾
2	8	16	2		

 

Types of CLB Slices

Slices	LUTs	Flip-Flops	Arithmetic and Carry Chains	Distributed RAM ⁽¹⁾	Shift Registers ⁽¹⁾
2	8	16	2	256 bits	128 bits

