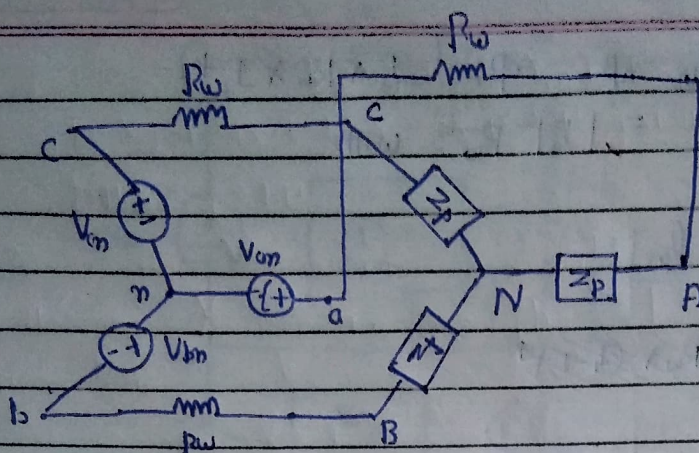


Tutorial 6 Solutions

Date: / /

Page No.

Ans 1)



Given:-

Z_p is parallel combination of:-

$$C = 1 \mu F$$

$$L = 100 mH$$

$$R = 10 \Omega$$

→

Source has positive phase sequence

→

Operating frequency:- 50 Hz

$$V_{ab} = 208 \angle 0^\circ V$$

$$R_w = 0$$

To find:-

a) all phase and voltages

b) all line voltages

c) all three line currents

d) total power drawn by load

⇒

$$\text{Equation of phase voltage: } V_{ob} = \sqrt{3} V_p \angle 30^\circ$$

⇒

$$V_p = \frac{V_{ob}}{\sqrt{3} \angle 30^\circ} = \frac{208 \angle 0^\circ}{\sqrt{3} \angle 30^\circ} = 120.08 \angle -30^\circ V$$

⇒

Now, line phase voltage $V_m = V_p$

$$\Rightarrow V_m \Rightarrow 120.08 \angle -30^\circ V \text{ Ans}$$

Now, the voltage are shifted by 120° since the source has positive phase sequence. Thus

$$V_{bn} = 120.08 \angle -150^\circ \text{ V} \quad \text{Ans.}$$

$$V_{cn} = 120.08 \angle -270^\circ \text{ V} \quad \text{Ans.}$$

(b) The line voltage V_{ab} is:

$$V_{ab} = 208 \angle 0^\circ \text{ V} \quad \text{Ans.}$$

The voltage are shifted by 120° since the source has positive phase sequence. Thus:

$$V_{bc} = 208 \angle -120^\circ \text{ V} \quad \text{Ans.}$$

$$V_{ca} = 208 \angle -240^\circ \text{ V} \quad \text{Ans.}$$

(c) Now, total current needs to be calculated, for that total impedance needs to be calculated first.

$$\begin{aligned} X_L &= j 2\pi f L \\ &= j 2\pi 50 (100 \times 10^{-3}) \\ &= j 31.415 \Omega \end{aligned}$$

$$\begin{aligned} X_C &= 1/j 2\pi f C \\ &= 1/j 2\pi 50 (10^{-3}) \\ &= -j 31.833 \Omega \end{aligned}$$

Now, it is given that R, L, C are in parallel. Hence, the total impedance will be:-

$$Z_p = \frac{R X_L X_C}{R X_L + R X_C + X_L X_C}$$

$$= \frac{10 \times j31.415 \times (-j31.415)}{10 \times j31.415 + 10 \times (-j31.415) + (j31.415)(-j31.415)}$$

$$= 1.115 - j3.147 \Omega$$

→ For the Y connection: the phase and line current are equal;

$$I_{OA} = \frac{V_{om}}{Z_p} = \frac{120.08 \angle -30^\circ}{1.115 - j3.147}$$

$$= 35.97 \angle 40.5^\circ \text{ A}$$

Thus,

$$I_{OA} = 35.97 \angle 40.5^\circ \text{ A} \quad \underline{\text{Ans}}$$

→ Now, the current is shifted by 120° since the source has positive phase sequence. Thus,

$$I_{OB} = 35.97 \angle -79.5^\circ \text{ A} \quad \underline{\text{Ans}}$$

$$I_{OC} = 35.97 \angle -199.5^\circ \text{ A} \quad \underline{\text{Ans}}$$

(d) The equation of power drawn by single phase;

$$P_{AN} = V_{AN} I_{OA} \cos(\phi_v - \phi_i)$$


$$= (120.08)(35.97) \cos(-30^\circ - 40.5^\circ)$$

$$= 1442.5 \text{ W}$$

$$\text{Total power} = 3 \times \text{single phase power} = 3 \times 1442.5$$

$$= 4327.5 \text{ W} \quad \underline{\text{Ans}}$$

Ans 2)

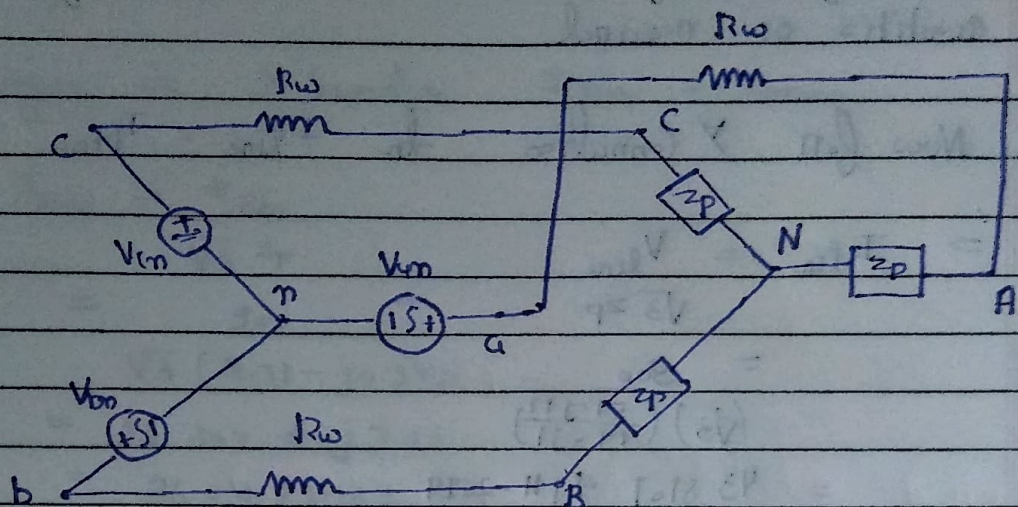Given

Positive phase sequence

line voltage = 300V

 Z_p is parallel combination of

$$C = 5 - j3 \Omega$$

$$L = 9 + j2 \Omega$$

$$R_w = 0$$

To find:

(a) power factor of source

(b) total power supplied by source

(c) find (a) and (b) if $R_w = 1 \Omega$

=

first will calculate the value of Z_p :

$$Z_p = \frac{(5 - j3)(9 + j2)}{(5 - j3) + (9 + j2)}$$

$$= \frac{45 + j10 - j27 + 6}{14 - j1}$$

$$= \frac{51 - j17}{14 - j1}$$

$$= \frac{51 - j17}{14 - j1} \Omega$$

→ Now for the factor, the current and voltage b/w quantities are measured

→ Now for Δ connection, $I_{line} = I_{phase}$

$$I_{line} = \frac{V_{line}}{\sqrt{3} Z_p}$$

$$= \frac{300}{\sqrt{3}}$$

$$\left(\frac{51-j17}{14-j1} \right)$$

$$= 43.8107 + j11.2074$$

$$= 45.22 \angle 14.35^\circ A$$

$$\text{Now, power factor} = \cos(\theta - \phi)$$

$$= \cos(0 - 14.35^\circ)$$

$$= \cos(-14.35^\circ)$$

$$= \boxed{0.968755} \quad \underline{A}$$

(b) Total power supplied by source -

$$\text{Power} = \sqrt{3} V_L I_L \cos(\theta - \phi)$$

$$= \sqrt{3} \times 300 \times 45.22 \cos(-14.35^\circ)$$

$$= 22764 \text{ W} \quad \underline{A}$$

(c) Now, we have $R_{eq} = 12$

So we need to again calculate Z_p

$$Z_p = 1 + \frac{(5-j3)(9+j2)}{(5-j3) + (9+j2)}$$

$$= 1 + \frac{45 + j10 - j27 + 6}{14-j1}$$

$$= 1 + \frac{51-j17}{14-j1}$$

$$= 4.71 - j0.949$$

→ Now, again in Y connection $I_{line} = I_{phase}$

$$\begin{aligned} \Rightarrow I_{line} &= \frac{V_{line}}{\sqrt{3} Z_p} \\ &= \frac{300}{\sqrt{3} (4.71 - j0.949)} \\ &= 35.334 + j7.12 \\ &= 36.04 \angle 11.39^\circ A \end{aligned}$$

$$\begin{aligned} \Rightarrow \text{Power factor} &= \cos(\theta - \phi) \\ &= \cos(0 - 11.39^\circ) \\ &= \cos(-11.39^\circ) \\ &= \boxed{0.980306} \quad A \end{aligned}$$

→ Now, total power supplied by source:

$$\begin{aligned} P_{\text{power}} &= \sqrt{3} V_L I_L \cos(\theta - \phi) \\ &= \sqrt{3} \times 300 \times 36.04 \cos(0 - 11.39^\circ) \\ &= 18358 \text{ W} \quad A \end{aligned}$$