
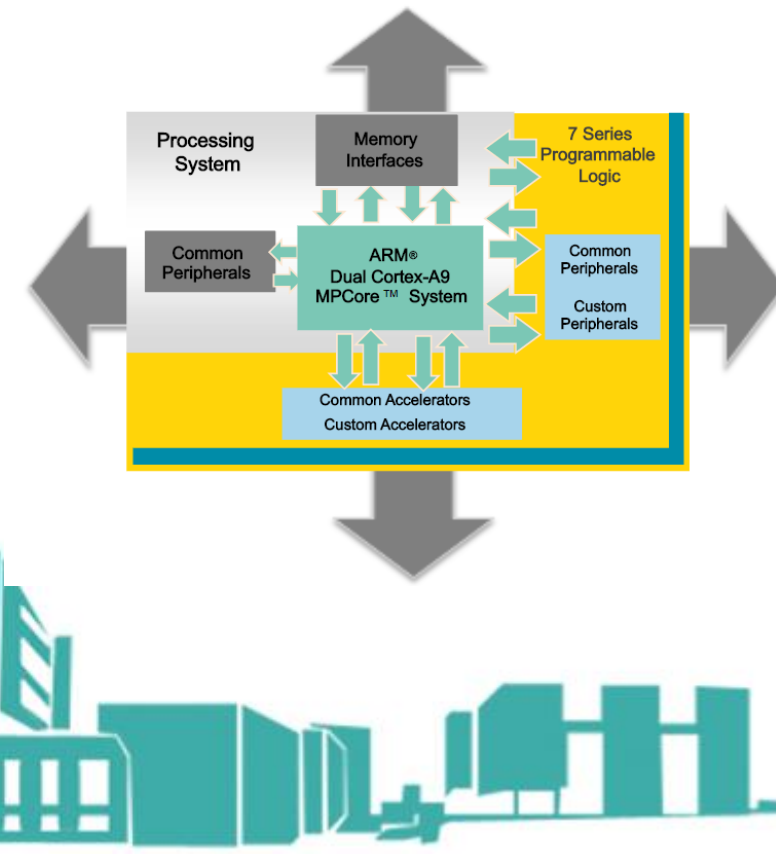


 

ECE 270: Embedded Logic Design



Behavioral Modeling for Combinational Circuits

- While writing Verilog code for synthesis, we need to be aware of how the various language constructs are mapped to hardware.
- **Common errors:**
 1. Variable assigned in **multiple always blocks**
 2. **Incomplete sensitivity** list
 3. **Incomplete branch** and **incomplete output** assignments

Behavioral Modeling: Guidelines

- Variable assigned in multiple always blocks

```
reg y;  
reg a, b, clear;  
...  
always @*  
    if (clear) y = 1'b0;  
  
always @*  
    y = a & b;  
  
always @*  
    if (clear)  
        y = 1'b0;  
    else  
        y = a & b;
```

- LHS code is not synthesizable since output **y** is driven by two blocks (i.e. two different circuits).
- No physical circuit exhibits such behaviour.

Behavioral Modeling: Guidelines

- Incomplete sensitivity list

```
module and_gate (out, in1, in2) ;  
    input  in1, in2 ;  
    output reg out ;  
  
    always @(in1)    // should be (in1 or in2)  
    begin  
        out = in1 & in2 ;  
    end  
endmodule
```

- Leaving out an input trigger usually results in a sequential circuit
- Use **always@*** for combinational circuits

Behavioral Modeling: Guidelines

- Incomplete branch and incomplete output assignment

```
always @*  
    if (a > b)           // eq not assigned in this branch  
        gt = 1'b1;  
    else if (a == b) // gt not assigned in this branch  
        eq = 1'b1;  
                        // final else branch is omitted
```

```
always @*  
begin  
    gt = 1'b0; // default value for gt  
    eq = 1'b0; // default value for eq  
    if (a > b)  
        gt = 1'b1;  
    else if (a == b)  
        eq = 1'b1;  
end
```

```
always @*  
    if (a > b)  
        begin  
            gt = 1'b1;  
            eq = 1'b0;  
        end  
    else if (a == b)  
        begin  
            gt = 1'b0;  
            eq = 1'b1;  
        end  
    else // i.e., a < b  
        begin  
            gt = 1'b0;  
            eq = 1'b0;  
        end  
end
```

Behavioral Modeling: Guidelines

- Incomplete branch and incomplete output assignment

```
reg [1:0] s
. . .
case (s)
    2'b00: y = 1'b1;
    2'b10: y = 1'b0;
    2'b11: y = 1'b1;
endcase

case (s)
    2'b00: y = 1'b1;
    2'b10: y = 1'b0;
    default: y = 1'b1; // y gets 1 for 2'b01
endcase


case (s)
    2'b00: y = 1'b1;
    2'b10: y = 1'b0;
    2'b11: y = 1'b1;
    default: y = 1'bx; // y gets x for 2'b01
endcase

y = 1'b0; // can also use y = 1'bx for don't-care
case (s)
    2'b00: y = 1'b1;
    2'b10: y = 1'b0;
    2'b11: y = 1'b1;
endcase
```


Case Statement: Full and Parallel

- Full Case Statement: all possible outcomes are accounted
- Parallel Case Statement: all stated alternatives are mutually exclusive
 
```
module full_par (sel, a, b, c, d, out);  
input [1:0] sel;  
input      a, b, c, d;  
output     out; reg out;  
always @ (sel or a or b or c or d)  
    case (sel)  
        2'b11: out <= a;  
        2'b10: out <= b;  
        2'b01: out <= c;  
        default: out <= d; // 2'b00  
    endcase  
endmodule
```


 
```
module par_not_full (sel, a, b, c, out);  
input [1:0] sel;  
input      a, b, c;  
output     out; reg out;  
always @ (sel or a or b or c)  
    case (sel)  
        2'b11: out <= a;  
        2'b10: out <= b;  
        2'b01: out <= c;  
    endcase  
endmodule
```




Case Statement: Full and Parallel

- Full Case Statement: all possible outcomes are accounted
- Parallel Case Statement: all stated alternatives are mutually exclusive

```
module full_not_par (sel, a, b, c, out);  
input [1:0] sel;  
input      a, b, c;  
output      out; reg out;  
always @ (sel or a or b or c)  
    case (sel)  
        2'b1?: out <= a; // 2'b10, 2'b11  
        2'b?1: out <= b; // 2'b01, 2'b11  
        default: out <= c; // 2'b00  
    endcase  
endmodule
```

 
// If the case is 2'b11 occurs, the first outcome gets higher priority because it is closer to the output.



Case Statement: Full and Parallel

- Full Case Statement: all possible outcomes are accounted
- Parallel Case Statement: all stated alternatives are mutually exclusive
 
```
module not_full_not_par (sel, a, b, out);  
input [1:0] sel;  
input      a, b;  
output     out; reg out;  
always @ (sel or a or b)  
    case (sel)  
        2'b1?: out <= a; // 2'b10, 2'b11  
        2'b?1: out <= b; // 2'b01, 2'b11  
    endcase  
endmodule
```



Behavioral Modeling for Combinational Circuits

- If an *always* block executes and a variable is **NOT** assigned:
 - Variable keeps its old value
 - *NOT* combinational logic -> latch is inserted (implied memory)
 - This is usually *NOT* what you want
- Any variable assigned in an *always* block **SHOULD** be assigned *for any (and every!) execution of the block*
- **Poorly coded always block** leads to **unnecessarily complex implementation** or can **not be synthesized** at all.

Behavioral Modeling: Summary

- Assign a variable **ONLY in a single always block**
- **Use @*** to include all the **desired** identifiers automatically in the sensitivity list
- Make sure that **all branches** of the *if and case statements* are included
- Make sure that the **outputs are assigned** in **all branches**
- One way to satisfy previous two guidelines is to **assign default values for outputs** in the beginning of the always block
- **Use blocking assignments for combinational circuits**
- **Think hardware**, not C or Python or MATLAB code

Verilog (Three Concepts)

- Difference between Register and Wire (Next two lectures)
- Efficient Behavioral modelling
- **Difference between blocking and non-blocking assignments**

Blocking Vs Non-Blocking Assignments

Behavioral Modeling

- **Blocking assignment** statements are executed in the order they are specified in a sequential block
- A blocking assignment will **NOT** block execution of statements that **follows in a parallel block**
- The **=** operator is used to specify blocking assignments
- **Non-blocking assignments** allow scheduling of assignments **without locking execution** of the statements that follow in a sequential block
- A **<=** operator is used to specify non-blocking assignments

Behavioral Modeling

reg_a = 16'b0 ;

```
reg [15:0] reg_a, reg_b ;
```

```
reg x, y, z ;
```

```
integer count ;
```

```
Initial
```

```
begin
```

```
    x = 0 ; y = 0 ; z = 0 ; count = 0 ;
```

```
    reg_b = reg_a ;
```

```
    #15 reg_a[2] = 1'b1 ;
```

```
    #10 reg_b[15:13] = {x, y, z} ;
```

```
    count = count + 1 ;
```

```
end
```

Behavioral Modeling

reg_a = 16'b0 ;

```
reg [15:0] reg_a, reg_b ;
```

```
reg x, y, z ;
```

```
integer count ;
```

```
Initial
```

```
begin
```

```
  x <= 0 ; y <= 0 ; z <= 0 ; count <= 0 ;
```

```
  reg_b <= reg_a ;
```


```
  #15 reg_a[2] <= 1'b1 ;
```

```
  #10 reg_b[15:13] <= {x, y, z} ;
```

```
  count <= count + 1 ;
```

```
end
```


Behavioral Modeling

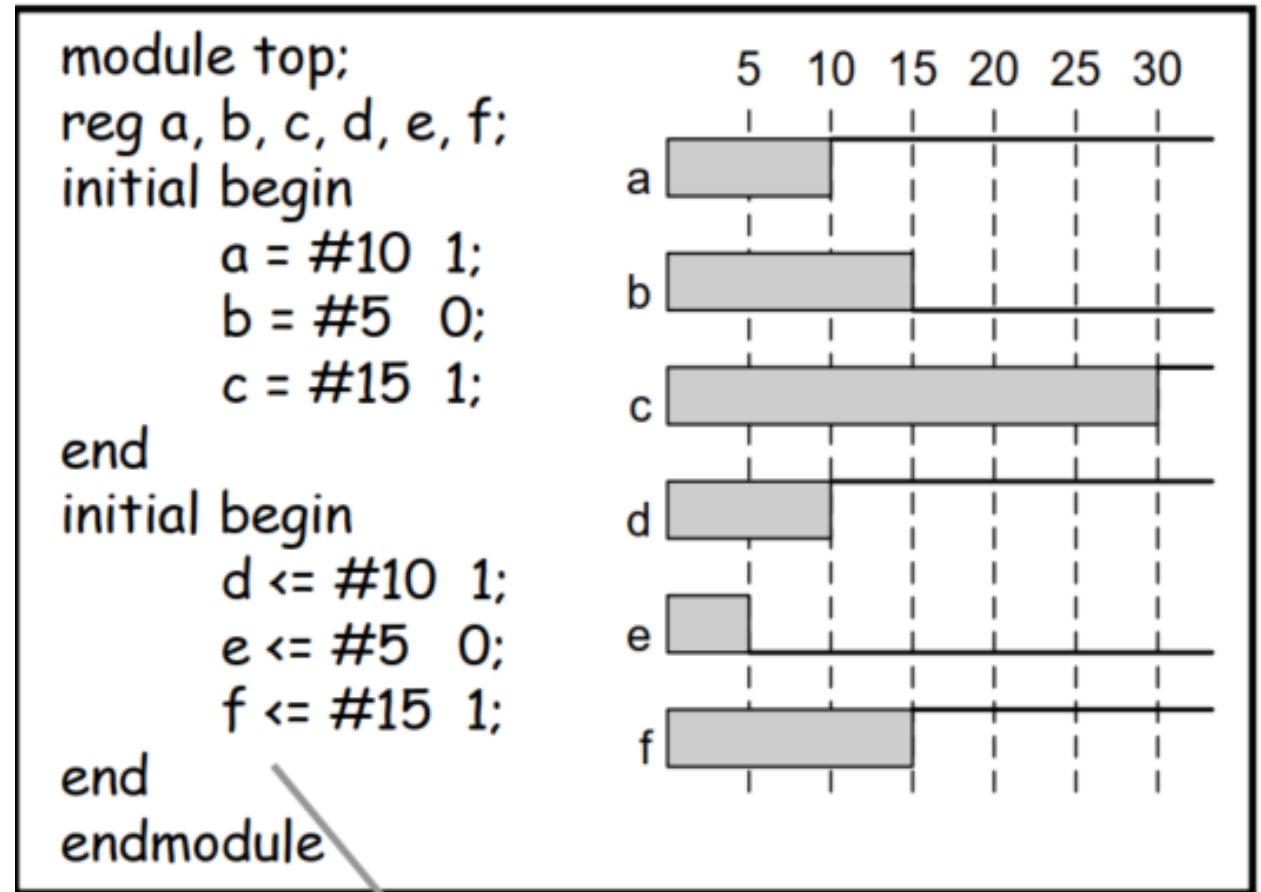

Note that what are different with blocking and non-blocking assignments.

Behavioral Modeling

```
always @(posedge clock)
```

```
begin reg1 <= #1 in1 ;
```

```
    reg2 <= @(negedge clock) in2 ^ in3 ;
```

```
    reg3 <= #1 reg1 ;
```

```
end
```

Behavioral Modeling: Swapping


```
Race Conditions:           // Two concurrent always blocks with blocking
always @(posedge clock)
    a = b ;
always @(posedge clock)
    b = a ;
```

The values of both registers will not be swapped */


```
Race Conditions: /* Two concurrent always blocks with non- blocking
always @(posedge clock)
    a <= b ;
always @(posedge clock)
    b <= a ;
```

Behavioral Modeling

 
```
module blocking (in,clk,out) ;  
  input in, clk ;  
  output reg out ;  
  reg q1, q2 ;  
  always @(posedge clk)  
    begin  
      q1 = in ;  
      q2 = q1 ;  
      out = q2 ;  
    end  
endmodule
```



 “at each rising clock edge, $q1 = in$,
after that, $q2 = q1 = in$
after that, $out = q2 = q1 = in$
Therefore, $out = in$ ”



Behavioral Modeling

 


```
module nonblocking (in,clk,out) ;  
  input in, clk ;  
  output reg out ;  
  reg q1, q2;  
  always @(posedge clk)  
    begin  
      q1 <= in ;  
      q2 <= q1 ;  
      out <= q2 ;  
    end  
endmodule
```

“at each rising clock edge, q1, q2 and out **simultaneously receive the old values** of in, q1 and q2. Therefore, out = q2”


- Blocking assignments do not reflect the intrinsic behaviour of multi-stage sequential logic
- Use non-blocking assignments for sequential always blocks

Behavioral Modeling

 
```
module blocking (in,clk,out) ;  
  input in, clk ;  
  output reg out ;  
  reg q1, q2 ;  
  always @(posedge clk)  
    begin  
      q1 = in ;  
      q2 = q1 ;  
      out = q2 ;  
    end  
endmodule
```



 “at each rising clock edge, $q1 = in$,
after that, $q2 = q1 = in$
after that, $out = q2 = q1 = in$
Therefore, $out = in$ ”



Behavioral Modeling

 


```
module nonblocking (in,clk,out) ;  
  input in, clk ;  
  output reg out ;  
  reg q1, q2;  
  always @(posedge clk)  
    begin  
      q1 <= in ;  
      q2 <= q1 ;  
      out <= q2 ;  
    end  
endmodule
```

“at each rising clock edge, q1, q2 and out **simultaneously receive the old values** of in, q1 and q2. Therefore, out = q2”

- Blocking assignments do not reflect the intrinsic behaviour of multi-stage sequential logic
- Use non-blocking assignments for sequential always blocks


Behavioral Modeling

 

```
module blocking (a, b, c, x, y) ;  
  input a, b, c ;  
  output reg x, y ;  
  always @ (a or b or c)  
  begin  
    x = a & b ;  
    y = x | c ;  
  end  
endmodule
```

```
module nonblocking (a, b, c, x, y) ;  
  input a, b, c ;  
  output reg x, y ;  
  always @ (a or b or c)  
  begin  
    x <= a & b ;  
    y <= x | c ;  
  end  
endmodule
```


Behavioral Modeling

 

- Given initial conditions:
a=1, b=1, c=0, x=1, y=1.
- a changes to 0. always block triggered.
- Blocking behaviour of simulator: 1st calculates $x = a \& b = 0$. Then calculates $y = x \mid c = 0$
- Non-Blocking behavior of simulator: Concurrently calculates $x(\text{new}) = a \& b = 0$. $y = x(\text{old}) \mid c = 1$
- Non-blocking assignment *do not* reflect the intrinsic behavior of multi-stage combinational logic
- While non-blocking assignments can be hacked to simulate correctly (expand sensitivity list), its not elegant
- **Guideline: Use blocking assignments for combinational always blocks**

```
module blocking (a, b, c, x, y);  
  input a, b, c;  
  output reg x, y;  
  always @ (a or b or c)  
  begin  
    x = a & b;  
    y = x | c;  
  end  
endmodule
```

```
module nonblocking (a, b, c, x, y);  
  input a, b, c;  
  output reg x, y;  
  always @ (a or b or c)  
  begin  
    x <= a & b;  
    y <= x | c;  
  end  
endmodule
```


Behavioral Modeling

- When modelling sequential logic, use non-blocking assignments.
- When modelling combinational logic with an always block, use blocking assignments.
- When modelling both sequential and combinational logic within the same always block, use non-blocking assignments.
- Do not mix blocking and non-blocking assignments in the same always block.

Behavioral Modeling (Self Study)


Blocking assignments (1/2)
 
```
always @ (posedge clk) begin
  a = din;
  b = a;
end
```




Non-blocking assignments (1/2)
 
```
always @ (posedge clk) begin
  a <= din;
  b <= a;
end
```



Blocking assignments (2/2)
 
```
always @ (posedge clk) begin
  b = a;
  a = din;
end
```



Non-blocking assignments (2/2)

```
always @ (posedge clk) begin
  b <= a;
  a <= din;
end
```

