
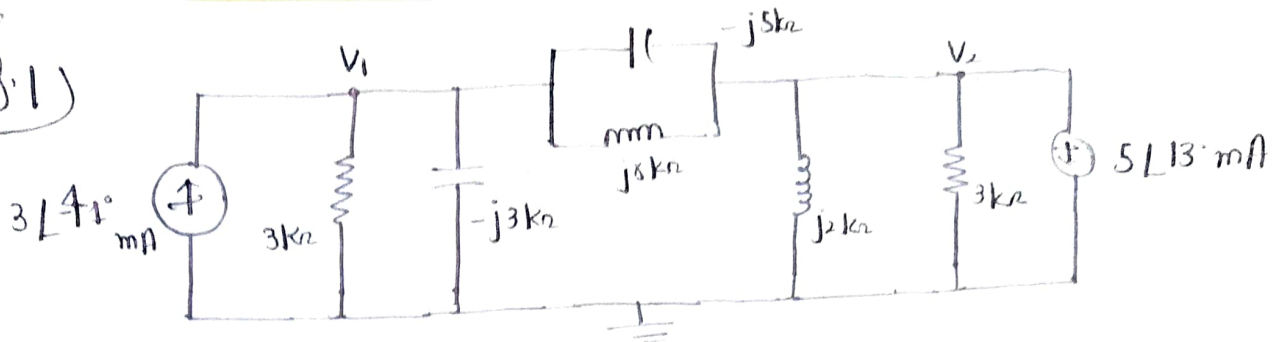


Q.1)

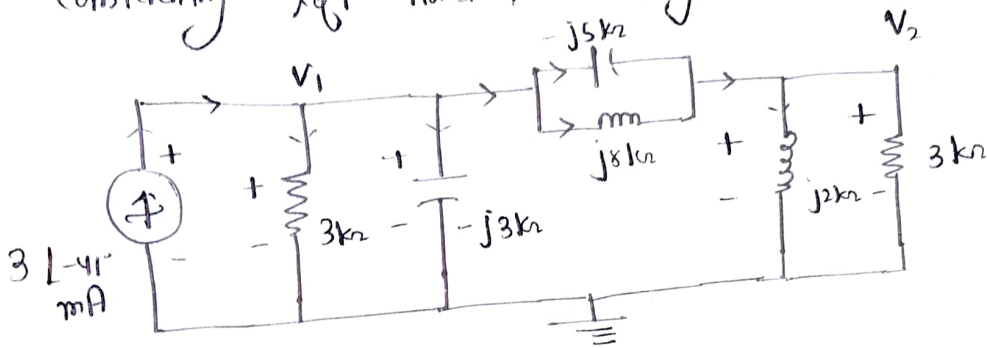

⇒ Considering left hand portion only :-



⇒ Writing KCL equation at node V_1 :-

$$3 \times 10^{-3} \angle -41^\circ = \frac{V_1}{3000} + \frac{V_1}{-j3000} + \frac{V_1 - V_2}{-j5000} + \frac{V_1 - V_2}{j8000}$$

$$\Rightarrow 3 \times 10^{-3} \angle -41^\circ = V_1 \left(\frac{1}{3000} + \frac{1}{-j3000} + \frac{1}{-j5000} + \frac{1}{j8000} \right) + V_2 \left(\frac{1}{j5000} - \frac{1}{j8000} \right)$$

$$\Rightarrow V_1 \left(-\frac{1}{3} + j0.4083 \right) + V_2 \left(-j7.5 \times 10^{-2} \right) = 3 \angle -41^\circ \quad \text{--- (1)}$$

$$A_1 V_1 + A_2 V_2 = C_1$$

⇒ Writing KCL equation at node V_2 :-

$$\Rightarrow \frac{V_1 - V_2}{-j5000} + \frac{V_1 - V_2}{j8000} = \frac{V_2}{j2000} + \frac{V_2}{3000} = 0$$

$$\Rightarrow V_1 \left(\frac{1}{-j5000} + \frac{1}{j8000} \right) + V_2 \left(\frac{1}{j5000} - \frac{1}{j8000} - \frac{1}{j2000} - \frac{1}{3000} \right) = 0$$

$$\Rightarrow V_1 \left(-j7.5 \times 10^{-2} \right) + V_2 \left(\frac{1}{3} - j0.425 \right) = 0 \quad \text{--- (2)}$$

$$A_2 V_1 + B_2 V_2 = C_2$$

$$\begin{aligned} & \because 3 \angle -41^\circ \\ & \Rightarrow 3 (\cos(-41^\circ) + j \sin(-41^\circ)) \\ & = 2.26 + j(-1.96) \end{aligned}$$

⇒ Solving (1) and (2) using Cramer's Rule -

$$V_1 = \frac{\begin{vmatrix} c_1 & B_1 \\ c_2 & B_2 \end{vmatrix}}{\begin{vmatrix} A_1 & B_1 \\ A_2 & B_2 \end{vmatrix}} = \frac{\begin{vmatrix} 2.26 - j1.96 & -j7.5 \times 10^{-2} \\ 0 & \frac{1}{3} - j0.425 \end{vmatrix}}{\begin{vmatrix} \frac{1}{3} + j0.4083 & -j7.5 \times 10^{-2} \\ -j7.5 \times 10^{-2} & \frac{1}{3} - j0.425 \end{vmatrix}}$$

Solving it:-

$$\boxed{V_1 = -0.618 - j5.573 \text{ V}} \quad A$$

$$V_2 = \frac{\begin{vmatrix} A_1 & c_1 \\ A_2 & c_2 \end{vmatrix}}{\begin{vmatrix} A_1 & B_1 \\ A_2 & B_2 \end{vmatrix}} = \frac{\begin{vmatrix} \frac{1}{3} + j0.4083 & 2.26 - j1.96 \\ -j7.5 \times 10^{-2} & 0 \end{vmatrix}}{\begin{vmatrix} \frac{1}{3} + j0.4083 & -j7.5 \times 10^{-2} \\ -j7.5 \times 10^{-2} & \frac{1}{3} - j0.425 \end{vmatrix}}$$


Solving it:-

$$\boxed{V_2 = 0.496 + j0.595 \text{ V}} \quad A$$

Thus, due to left hand source, the nodal voltage V_1 comes out to be $-0.618 - j5.573 \text{ V}$ and the nodal voltage V_2 comes out to be $0.496 + j0.595 \text{ V}$

⇒ Now, the circuit needs to be solved for the contribution of right hand side source.

⇒ Redrawing the circuit:-

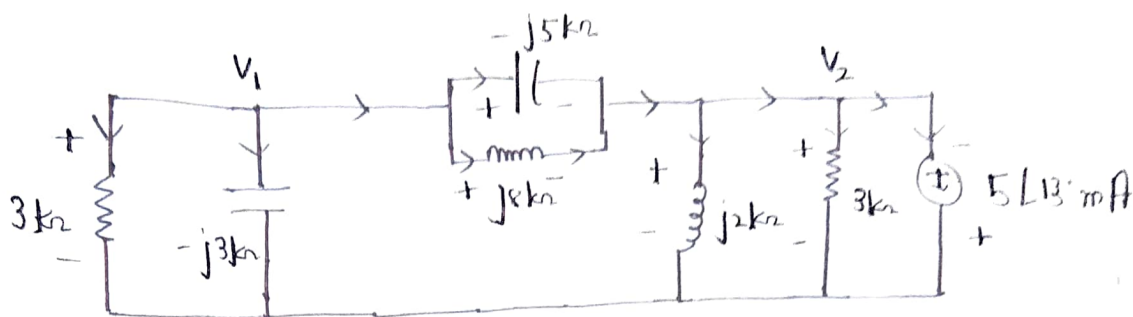

Applying KCL at node V_1 :-

$$\Rightarrow \frac{V_1}{3000} + \frac{V_1}{-j3k} + \frac{V_1 - V_2}{-j5k} + \frac{V_1 - V_2}{j8k} = 0$$

$$\Rightarrow V_1 \left(\frac{1}{3000} + \frac{1}{-j3k} + \frac{1}{-j5k} + \frac{1}{j8k} \right) + V_2 \left(\frac{1}{j5k} - \frac{1}{j8k} \right) = 0$$

$$\Rightarrow V_1 \left(\frac{1}{3} + j0.4083 \right) + V_2 \left(-j0.075 \right) = 0 \quad \text{--- (3)}$$

$$A_3 V_1 + B_3 V_2 = C_3$$

Applying KCL at node V_2 :-

$$\Rightarrow \frac{V_1 - V_2}{-j5k} + \frac{V_1 - V_2}{j8k} = \frac{V_2}{j2k} + \frac{V_2}{3k} + 5\angle 13^\circ$$

$$\Rightarrow \frac{V_1 - V_2}{-j5k} + \frac{V_1 - V_2}{j8k} - \frac{V_2}{j2k} - \frac{V_2}{3k} - 5\angle 13^\circ = 0$$

$$\Rightarrow V_1 \left(\frac{1}{-j5k} + \frac{1}{j8k} \right) + V_2 \left(\frac{1}{j5k} - \frac{1}{j8k} - \frac{1}{j2k} - \frac{1}{3k} \right) = 5\angle 13^\circ$$

$$\Rightarrow V_1 \left(-j0.075 \right) + V_2 \left(\frac{1}{3} - j0.425 \right) = -5\angle 13^\circ \quad \text{--- (4)}$$

$$A_4 V_1 + B_4 V_2 = C_4$$

⇒ Solving (3) and (4) using Cramer's Rule:-

$$5 \angle 13^\circ = 5 \cos(13^\circ) + 5j \sin(13^\circ)$$

$$= 4.87 + j1.12$$

$$V_1 = \frac{\begin{vmatrix} C_3 & B_3 \\ C_4 & B_4 \end{vmatrix}}{\begin{vmatrix} A_3 & B_3 \\ A_4 & B_4 \end{vmatrix}}} = \frac{\begin{vmatrix} 0 & -j0.075 \\ -4.87 - j1.12 & \frac{1}{3} - j0.425 \end{vmatrix}}{\begin{vmatrix} \frac{1}{3} + j0.4083 & -j0.075 \\ -j0.075 & \frac{1}{3} - j0.425 \end{vmatrix}}}$$

Solving it:-

$$\boxed{V_1 = -0.315 - j1.253 \text{ V}} \quad \text{A}$$

$$V_2 = \frac{\begin{vmatrix} A_3 & C_3 \\ A_4 & C_4 \end{vmatrix}}{\begin{vmatrix} A_1 & B_1 \\ A_2 & B_2 \end{vmatrix}}} = \frac{\begin{vmatrix} \frac{1}{3} + j0.4083 & 0 \\ -j0.075 & -4.87 - j1.12 \end{vmatrix}}{\begin{vmatrix} \frac{1}{3} + j0.4083 & -j0.075 \\ -j0.075 & \frac{1}{3} - j0.425 \end{vmatrix}}}$$


Solving it:-

$$\boxed{V_2 = -3.85 - j8.22 \text{ V}} \quad \text{A}$$

Thus, due to right hand source, the node voltage V_1 comes out to be $-0.315 - j1.253 \text{ V}$ and the node voltage V_2 comes out to be $-3.85 - j8.22 \text{ V}$

Determine the average power supplied by dependent source.

Q5)

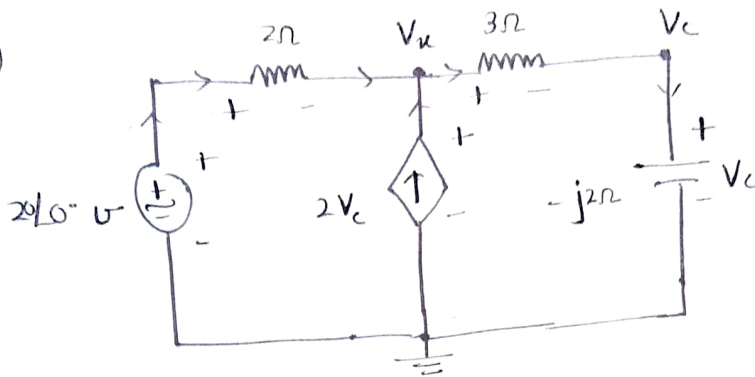

Average power supplied by dependent source = ?

→ Identify nodes: V_x , V_c , ground.

⇒ Apply KCL at node V_x :-

$$\Rightarrow \frac{20 - V_x}{2} + 2V_c = \frac{V_x - V_c}{3}$$

$$\Rightarrow \frac{20}{2} - \frac{V_x}{2} + 2V_c + \frac{V_c}{3} - \frac{V_x}{3} = 0$$

$$\Rightarrow 10 - \frac{V_x}{2} + 2V_c + \frac{V_c}{3} - \frac{V_x}{3} = 0$$

$$\Rightarrow V_c \left(2 + \frac{1}{3} \right) + V_x \left(-\frac{1}{2} - \frac{1}{3} \right) = -10$$

$$\Rightarrow V_x \left(-\frac{5}{6} \right) + V_c \left(\frac{7}{3} \right) = -10$$

multiply by -6 on both sides.

$$\Rightarrow \underline{5V_x - 14V_c = 60} \quad \text{--- (1)}$$

⇒ Apply KCL at node V_c :-

$$\Rightarrow \frac{V_c}{-j2} = \frac{V_x - V_c}{3}$$

$$\Rightarrow V_c \left(-\frac{1}{j2} \right) + \frac{V_c}{3} - \frac{V_x}{3} = 0$$

$$A_1 V_x + B_1 V_c = C_1$$

$$\left[\begin{array}{l} \because A_1 = 5 \\ B_1 = -14 \\ C_1 = 60 \end{array} \right]$$

$$\Rightarrow V_c \left(-\frac{1}{j^2} + \frac{1}{3} \right) + V_n \left(-\frac{1}{3} \right) = 0$$

$$\Rightarrow V_c \left(\frac{3 - j^2}{-j^6} \right) + V_n \left(-\frac{1}{3} \right) = 0$$

$$\Rightarrow \text{multiply by } -j^6 \text{ on both side}$$

$$\Rightarrow V_c (3 - j^2) + V_n (j^2) = 0$$

$$\Rightarrow \underline{V_n (j^2) + (3 - j^2) V_c = 0} \quad \text{--- (2)}$$

$$A_2 V_n + B_2 V_c = C_2$$

$$\begin{bmatrix} \therefore A_2 = j^2 \\ B_2 = 3 - j^2 \\ C_2 = 0 \end{bmatrix}$$

now, $V_n =$ $\frac{\begin{vmatrix} C_1 & B_1 \\ C_2 & B_2 \end{vmatrix}}{\begin{vmatrix} A_1 & B_1 \\ A_2 & B_2 \end{vmatrix}} \Rightarrow \frac{\begin{vmatrix} 60 & -14 \\ 0 & 3 - j^2 \end{vmatrix}}{\begin{vmatrix} 5 & -14 \\ j^2 & 3 - j^2 \end{vmatrix}}$

solving by Cramer's rule

$$\Rightarrow \frac{60(3 - j^2) - 0}{5(3 - j^2) - (j^2)(-14)} = \frac{180 - 120j}{(15 - 10j) - (-28j)}$$

$$\Rightarrow \frac{180 - 120j}{15 - 10j + 28j} = \frac{180 - 120j}{15 + 18j}$$

$$\Rightarrow \frac{180 - 120j}{15 + 18j} \times \frac{15 - 18j}{15 - 18j} \quad (\text{By Rationalizing \& solving})$$

$$\Rightarrow 0.983 - j 9.17$$

Convert into polar form:-

$$\text{magnitude} = \sqrt{(0.983)^2 + (-9.17)^2}$$
$$= 9.223$$

$$\text{Angle} = \tan^{-1} \left(\frac{-9.17}{0.983} \right) = -83.88^\circ$$

$$\Rightarrow 9.223 \angle -83.88^\circ \text{ V} \equiv 9.223 \cos(\omega t - 83.88^\circ) \text{ V}$$

↓
Equivalent to

now, solving for V_c :-

$$V_c = \frac{\begin{vmatrix} A_1 & C_1 \\ A_2 & C_2 \end{vmatrix}}{\begin{vmatrix} A_1 & B_1 \\ A_2 & B_2 \end{vmatrix}}} = \frac{\begin{vmatrix} 5 & 60 \\ j^2 & 0 \end{vmatrix}}{\begin{vmatrix} 5 & -14 \\ j^2 & 3-j^2 \end{vmatrix}}}$$

$$\Rightarrow \frac{0 - 60(j^2)}{5(3-j^2) - (j^2)(-14)} = \frac{-j120}{15 + 18j}$$

$$= \frac{j120}{15 + 18j} \times \frac{15 - 18j}{15 - 18j} \Rightarrow -3.93 - j3.27$$

Convert into polar form

$$\text{magnitude} = \sqrt{(-3.93)^2 + (-3.27)^2} = 5.122$$

$$\text{angle} = \tan^{-1} \left(\frac{3.27}{3.93} \right) = -140.2^\circ$$

$$\Rightarrow 5.122 \angle -140.2^\circ = 5.122 \cos(\omega t - 140.2^\circ) \text{ V}$$

⇒ Power associated with dependent source:-


$$P_{2V_c} = -\frac{1}{2} (9.223) (2 \times 5.122) \cos(-83.88^\circ + 146.2^\circ)$$
$$= -26.22 \text{ W}$$

⇒ power supplied by dependent source = $\boxed{26.22 \text{ W}}$ A

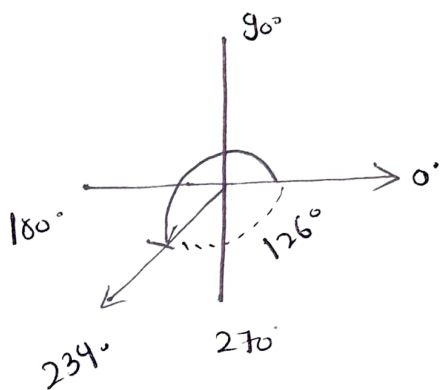Q.6) (a) $V = 240 \angle 243^\circ \text{ V rms}$
 $I = 3 \angle 9^\circ \text{ A rms}$

Phase angle difference between voltage and current = ?

$$\Rightarrow 243^\circ - 9^\circ = 234^\circ$$



$$= -360^\circ + 234^\circ \text{ (OR)} -126^\circ$$

$$= \boxed{-126^\circ}$$

⇒ Voltage lags current by

$$\boxed{126^\circ} \text{ A}$$

(b) power factor of load is 0.55 lagging.

$$\text{Power factor} = \cos(\theta - \phi)$$

↓
phase angle difference b/w voltage and current

if $\theta > \phi$ (voltage lead)

$\theta < \phi$ (voltage lag).

$$\Rightarrow \cos(\theta - \phi) = 0.55$$

$$\Rightarrow \theta - \phi = \cos^{-1}(0.55) \\ = 56.6^\circ$$

\Rightarrow Voltage leads current by $\boxed{56.6^\circ}$ A

(c) power factor of load is 0.685 leading

$$\Rightarrow \cos(\theta - \phi) = -0.685$$

$$\theta - \phi = \cos^{-1}(0.685) \\ = -46.76^\circ$$

\Rightarrow Voltage lags current by $\boxed{46.76^\circ}$ A

(d) Capacitive load

$\frac{\text{Draws } 100 \text{ W average power}}{500 \text{ VA apparent power}}$

$$\Rightarrow \theta - \phi = \cos^{-1} \left(\frac{\text{Average power}}{\text{Apparent power}} \right)$$

$$\Rightarrow \theta - \phi = \cos^{-1} \left(\frac{-100}{500} \right) = -78.46^\circ$$

\Rightarrow Voltage lags current by $\boxed{78.46^\circ}$ A