
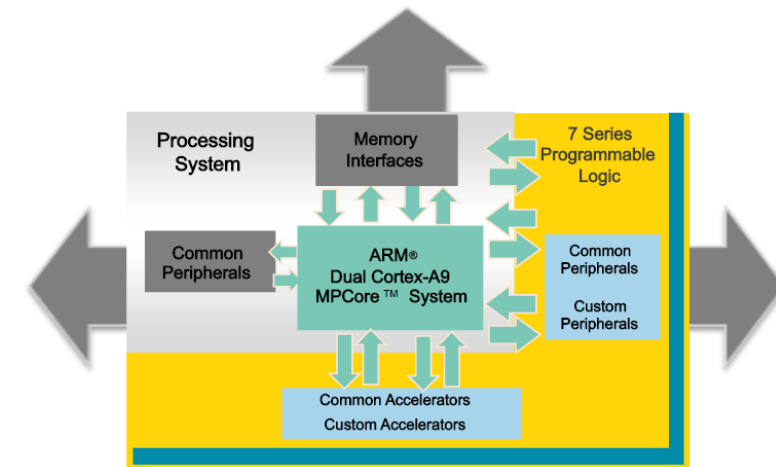


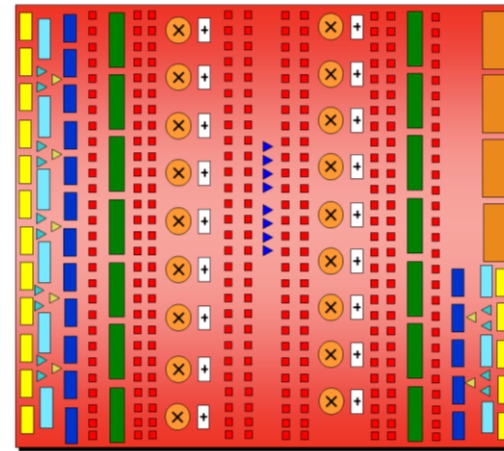

# ECE 270: Embedded Logic Design




# Verilog

# Few words of wisdom

- One of the common mistakes for beginners is to **think of HDL as a computer program** rather than as a shorthand for describing digital hardware.
- If you do not know approximately what hardware your HDL should synthesize into, you probably won't like what you get.
- You might create far more hardware than is necessary or you might write non-synthesizable code
- **THINK** of your system in terms of blocks of combinational logic, registers and FSMs. **SKETCH** these blocks on paper and show how they are connected **BEFORE** you start writing code.
- Describing hardware with a language is similar, however, to **writing a parallel program**

# Verilog: Module (Examples)

 

```
module AND (out, in1, in2) ; // <module name> <ports list>
    input in1, in2 ;
    output wire out ;
    assign out = in1 & in2 ; // data flow - continuous Assignment
endmodule
```

```
module AND (out, in1, in2) ; // <module name> <ports list>
    input in1, in2 ;
    output reg out ;
    // must be reg type when used as LHS in an always block
    always @( in1 or in2) // always block (sensitivity list) - behavioral
        out = in1 & in2 ; /* statements inside always block are
executed only when one or more signals in the list changes value */
endmodule
```

# Verilog

```
module exam_1 (o1,in1,in2,in3); //module
    output o1;
    input in1,in2,in3;
        and a1 (Q, in1, in3); //and instantiation
        not n1 (P,in3);      // not instantiation
        and a2 (R, in2, P); // and instantiation
        or   o1 (o1, Q, R); // or instantiation
Endmodule
```

# HDL Bits (Lab Homework 1: Due on Thursday)

## Submit Report from My Stats Page



1. <https://hdlbits.01xz.net/wiki/Wire>
2. <https://hdlbits.01xz.net/wiki/Wire4>
3. <https://hdlbits.01xz.net/wiki/Notgate>
4. <https://hdlbits.01xz.net/wiki/Andgate>
5. <https://hdlbits.01xz.net/wiki/Norgate>
6. <https://hdlbits.01xz.net/wiki/Xnorgate>
7. [https://hdlbits.01xz.net/wiki/Wire\\_decl](https://hdlbits.01xz.net/wiki/Wire_decl)
8. <https://hdlbits.01xz.net/wiki/7458>
9. <https://hdlbits.01xz.net/wiki/7420>
10. [https://hdlbits.01xz.net/wiki/Mt2015\\_q4a](https://hdlbits.01xz.net/wiki/Mt2015_q4a)
11. [https://hdlbits.01xz.net/wiki/Mt2015\\_q4b](https://hdlbits.01xz.net/wiki/Mt2015_q4b)
12. <https://hdlbits.01xz.net/wiki/Mux9to1v>

# Verilog

```
module test_1(  
  input in_1,  
  input in_2,  
  input in_3,  
  output out_1  
);
```


```
  wire Q, P, R;  
  and a1(Q, in_1, in_3); //and instantiation  
  not n1(P,in_3);        // not instantiation  
  and a2(R, in_2, P);    // and instantiation  
  or  o1(out_1, Q, R);   // or instantiation
```

```
endmodule
```

 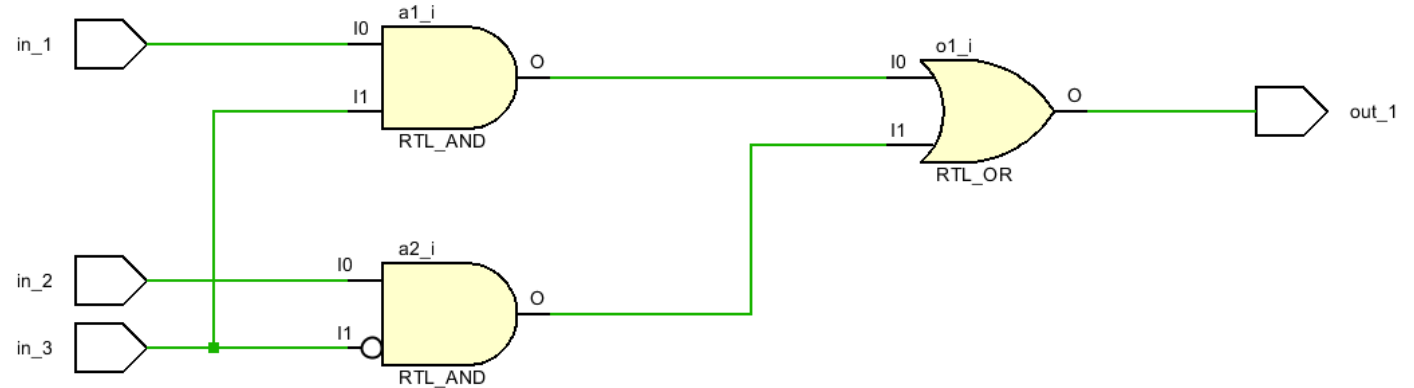
 
# Verilog

```
module test_1(  
  input in_1,  
  input in_2,  
  input en,  
  output out_0,out_1,out_2,out_3  
);  
  
  assign out_0 =(en & ~in_2 & ~in_1);  
  assign out_1 =(en & ~in_2 & in_1);  
  assign out_2 =(en & in_2 & ~in_1);  
  assign out_3 =(en & in_2 & in_1);  
  
endmodule
```



en	in_1	in_2	o <sub>0</sub>	o <sub>1</sub>	o <sub>2</sub>	o <sub>3</sub>
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	X	X	0	0	0	0



# Verilog

```
module ex1
    // I/O ports
    (
        input wire i0, i1,
        output wire eq
    );

    // signal declaration
    wire p0, p1;

    // body
    // sum of two product terms
    assign eq = p0 | p1;
    // product terms
    assign p0 = ~i0 & ~i1;
    assign p1 = i0 & i1;

endmodule
```

# Verilog: Module (Examples)

```
module module_name (port_list) ;
```

*declarations:*

port declaration (input, output, inout, ...)

data type declaration (reg, wire, parameter, ...)

task and function declaration

*statements:*

initial block

always block

module instantiation

gate instantiation

UDP instantiation


continuous assignment

```
endmodule
```

} Behavioral

} Structural

} Data-flow

 

```
module ModF ( input wire A
              , input wire [7:0] B
              , output wire [7:0] C);
    // declarations
    // description of 'f'
endmodule
```

```
module ModF (A, B, C);
    input      A;
    inout [7:0] B;
    output [7:0] C;
    // declarations
    // description of 'f'
endmodule
```

# Verilog

```
module test_1(  
    input clk,  
    input clr,  
    input D_in,  
    output reg Q_out  
);  
  
always@(*) begin  
    if(clr)  
        Q_out=1'b0;  
    else if (clk)  
        Q_out=D_in;  
end  
  
endmodule
```

always@(\*) — comb.

always@(posedge clk  
negedge clk



Mem

always@ (clr, clk, D-in)



active high clr

# Verilog:

```
module test_1(  
  input [2:0] in_1,  
  input [2:0] in_2,  
  input sel,  
  output reg [2:0] out_1  
);
```

```
  always@(*) begin  
    if(sel == 1'b0)  
      out_1 = in_1;  
    else  
      out_1 = in_2;  
  end
```


```
endmodule
```

  

```
always@(*) begin  
  if(sel == 1'b0)  
    out_1 = in_1;  
end
```

 
# Verilog: Module (Examples)

```
module D_FF(clk, nrst, d, q) ;  
    input clk, nrst, d ;  
    output reg q ;  
    always @(posedge clk or negedge nrst)  
        // Event-based Timing Control  
        // reset state  
        if (!nrst)  
            q <= 0 ;  
        else  
            // normal operation  
            q <= d ;  
endmodule
```


 
# Verilog: Register

```
module test_1(  
    input [7:0] d_in,  
    input ce,  
    input clk,  
    input clr,  
    output [7:0] d_out  
);  
  
    reg [7:0] d_reg;  
    always@(posedge clk)  
    begin  
        if(clr)  
            d_reg <= 8'b00000000;  
        else if (ce)  
            d_reg <= d_in;  
    end  
    assign d_out = d_reg;  
endmodule
```



# Self Study

- Using module for 2:1 mux (**data flow level** approach), design 8:1 mux via module interconnections
- Design comparator for 2-bit inputs using **data flow level** approach.
- Using comparator for 1-bit inputs, design comparator for 2-bit inputs via module interconnections