

Tutorial 9

Q1. You are to design and simulate a MOSFET differential amplifier.

Instructions:

- 1) Draw the circuit schematics in LTSpice with the given circuit parameters
- 2) Add this command to model the MOSFET's ".model nmos1 nmos(Vto=1 KP=100e-6)
- 3) For input voltages take a sine signal with an amplitude 10mV and the phase difference between these two voltages should be 180 degrees.
- 4) Connect the substrate of both the MOSFET's to Vss.
- 5) Add the output labels on the out+ and out- side to log all necessary values for each MOSFET.
- 6) Compare all the values with theoretical values and calculate the theoretical and practical CMRR.

