
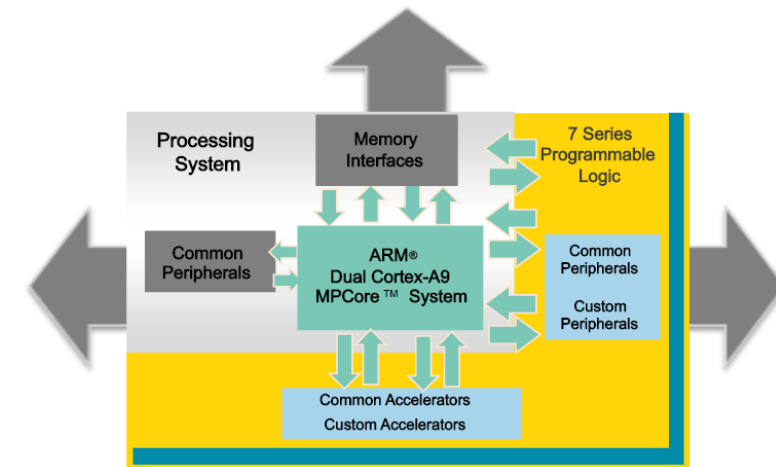


 

ECE 270: Embedded Logic Design




Opine Feedback


- **No of feedback:** 19% (lost opportunity and can be easily ignored)
- **We all need people who will give us feedback. That's how we improve: Bill Gates**
- **Feedback often tells you more about the person who is giving it than about you: Stephen Covey**
- **Couple of suggestions:** TA office hour slots and Lab homework deadline (Done)
- **Reminder:** Below 30 marks get F grade and 3 plagiarism cases reported so far

Behavioral Modeling

 
```
module blocking (in,clk,out) ;  
  input in, clk ;  
  output reg out ;  
  reg q1, q2 ;  
  always @(posedge clk)  
    begin  
      q1 = in ;  
      q2 = q1 ;  
      out = q2 ;  
    end  
endmodule
```



 “at each rising clock edge, $q1 = in$,
after that, $q2 = q1 = in$
after that, $out = q2 = q1 = in$
Therefore, $out = in$ ”



Behavioral Modeling

 


```
module nonblocking (in,clk,out) ;  
  input in, clk ;  
  output reg out ;  
  reg q1, q2;  
  always @(posedge clk)  
    begin  
      q1 <= in ;  
      q2 <= q1 ;  
      out <= q2 ;  
    end  
endmodule
```

“at each rising clock edge, q1, q2 and out **simultaneously receive the old values** of in, q1 and q2. Therefore, out = q2”

- Blocking assignments do not reflect the intrinsic behaviour of multi-stage sequential logic
- Use non-blocking assignments for sequential always blocks


Behavioral Modeling

 

```
module blocking (a, b, c, x, y) ;  
  input a, b, c ;  
  output reg x, y ;  
  always @ (a or b or c)  
  begin  
    x = a & b ;  
    y = x | c ;  
  end  
endmodule
```

```
module nonblocking (a, b, c, x, y) ;  
  input a, b, c ;  
  output reg x, y ;  
  always @ (a or b or c)  
  begin  
    x <= a & b ;  
    y <= x | c ;  
  end  
endmodule
```

Behavioral Modeling

 

- Given initial conditions:
a=1, b=1, c=0, x=1, y=1.
- a changes to 0. always block triggered.
- Blocking behaviour of simulator: 1st calculates $x = a \& b = 0$. Then calculates $y = x \mid c = 0$
- Non-Blocking behavior of simulator: Concurrently calculates $x(\text{new}) = a \& b = 0$. $y = x(\text{old}) \mid c = 1$
- Non-blocking assignment *do not* reflect the intrinsic behavior of multi-stage combinational logic
- While non-blocking assignments can be hacked to simulate correctly (expand sensitivity list), its not elegant
- **Guideline: Use blocking assignments for combinational always blocks**

```
module blocking (a, b, c, x, y);  
  input a, b, c;  
  output reg x, y;  
  always @ (a or b or c)  
  begin  
    x = a & b;  
    y = x | c;  
  end  
endmodule
```

```
module nonblocking (a, b, c, x, y);  
  input a, b, c;  
  output reg x, y;  
  always @ (a or b or c)  
  begin  
    x <= a & b;  
    y <= x | c;  
  end  
endmodule
```


Behavioral Modeling

- When modelling sequential logic, use non-blocking assignments.
- When modelling combinational logic with an always block, use blocking assignments.
- When modelling both sequential and combinational logic within the same always block, use non-blocking assignments.
- Do not mix blocking and non-blocking assignments in the same always block.



FPGA Architecture

Configurable Logic Block (CLB)

 - Primary resource for design in Xilinx FPGAs
- **CLB** contains more than one **slice**
- Connected to **switch matrix** for routing to other FPGA resources
- **Carry chain** runs vertically in a column from one slice to the one above



Configurable Logic Block (CLB)

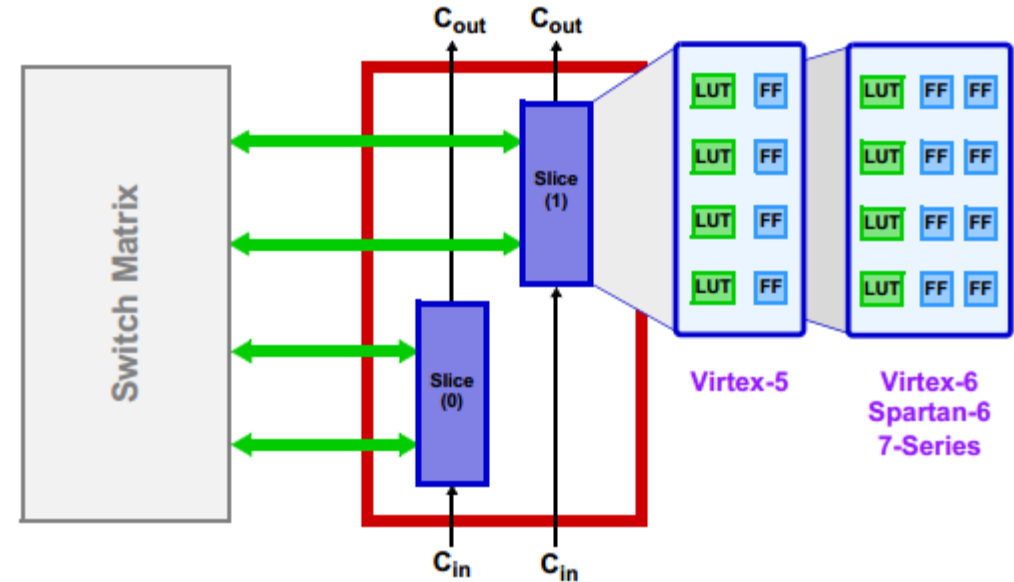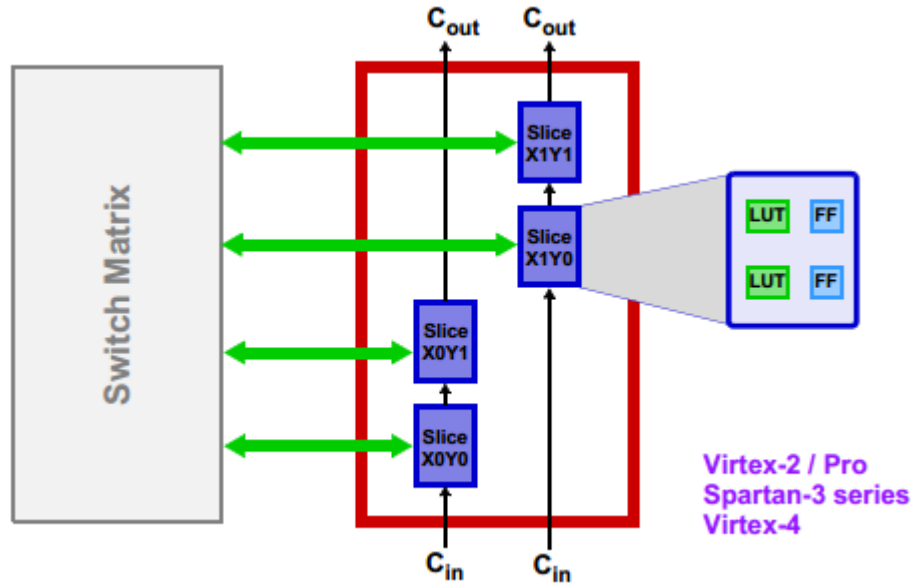

Slices	LUTs	Flip-Flops	Arithmetic and Carry Chains
2	8	16	2


Types of CLB Slices

- **SLICEM: Full slice**
 - LUT can be used for logic and memory/SRL
- **SLICEL: Logic and arithmetic only**
 - LUT can only be used for logic (not memory/SRL)
- Each CLB can contain **two SLICEL** or **a SLICEL and a SLICEM**.
- In the 7-series FPGAs, **approximately ¼ of slices** are SLICEM, the remainder are SLICEL.





Slice Resource

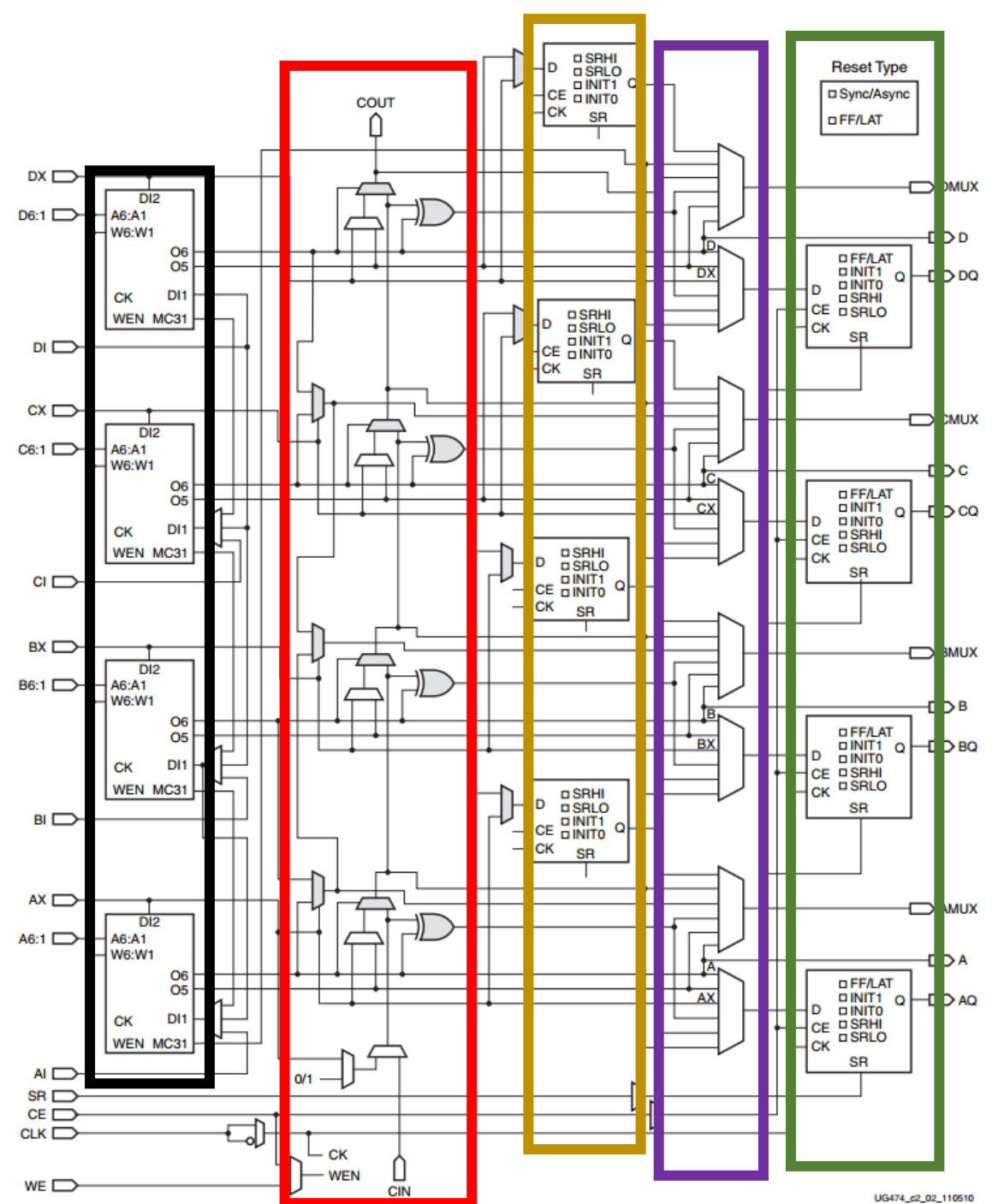- Four six-input Look-Up Tables (LUT)
- Multiplexers
- Carry chains
- Four flip-flops/latches
- Four additional flip-flops
- Four 6-input LUTs and their eight flip-flops as well as multiplexers and arithmetic carry logic form a slice, and two slices form a CLB.




SLICEM Vs SLICEL

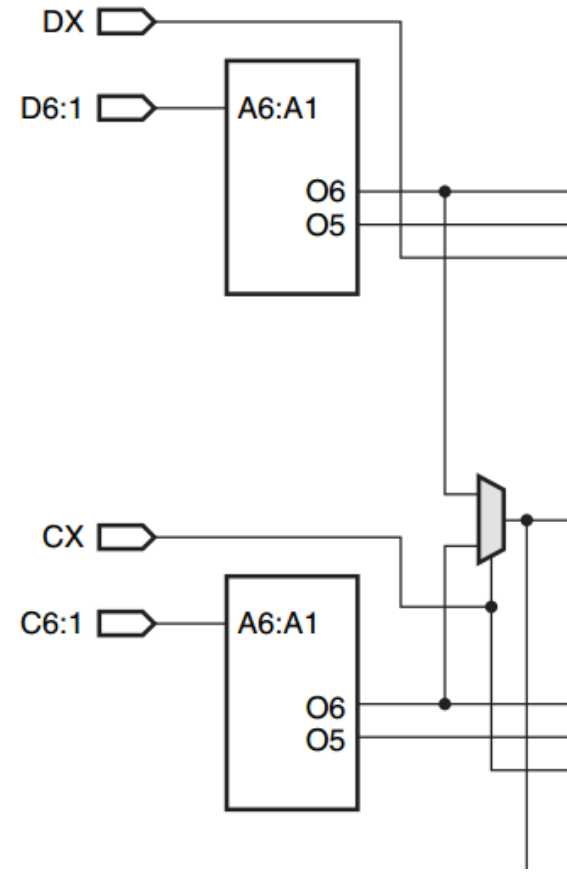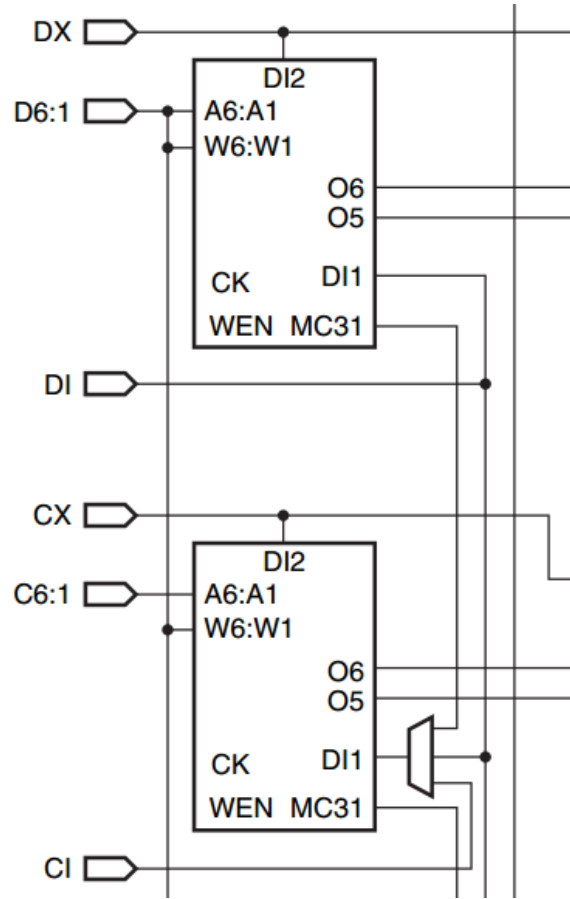


LUT

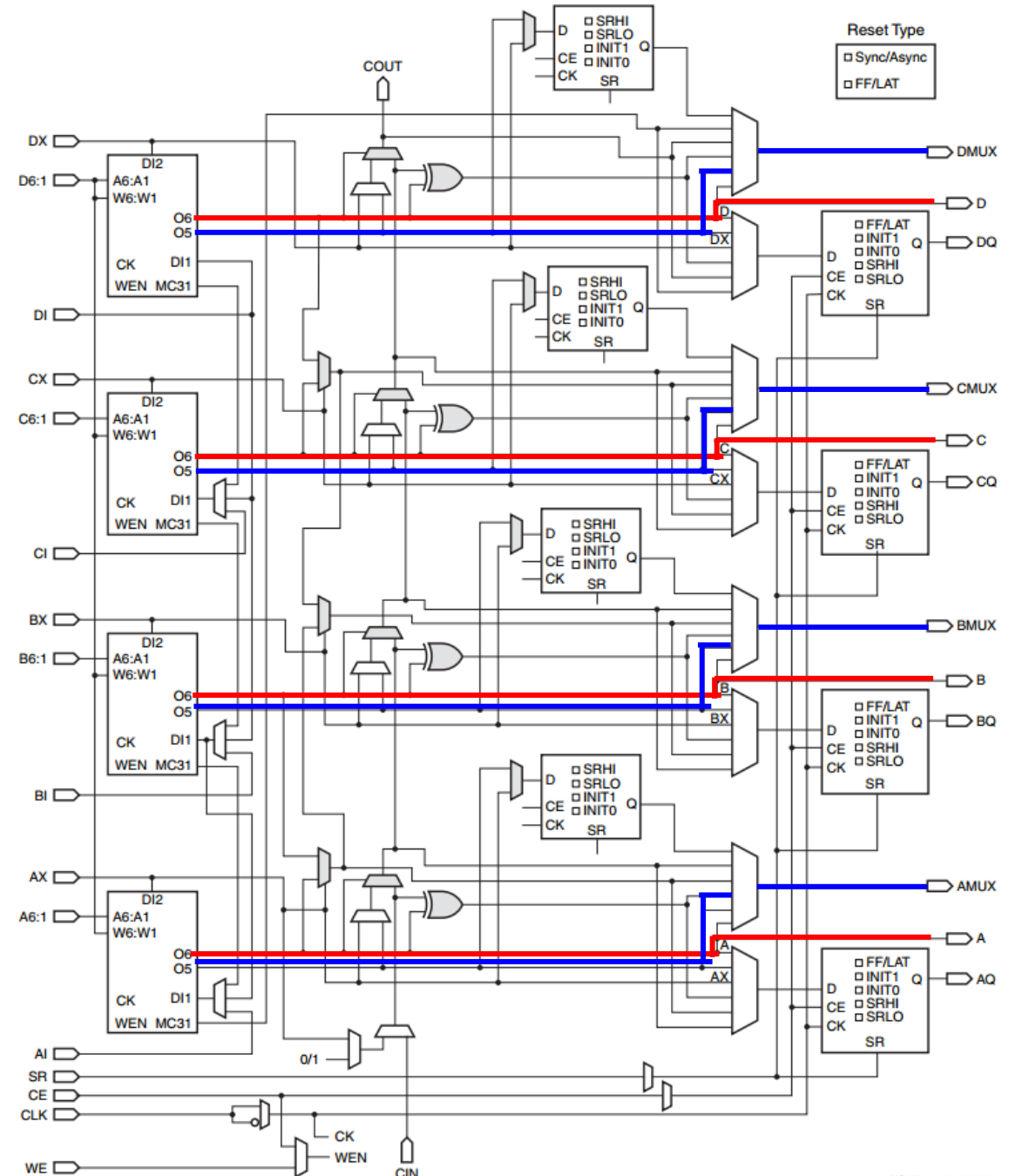- Signals from the LUT can:
 - Exit the slice (through A, B, C, D output for O6 or AMUX, BMUX, CMUX, DMUX output for O5)




LUT

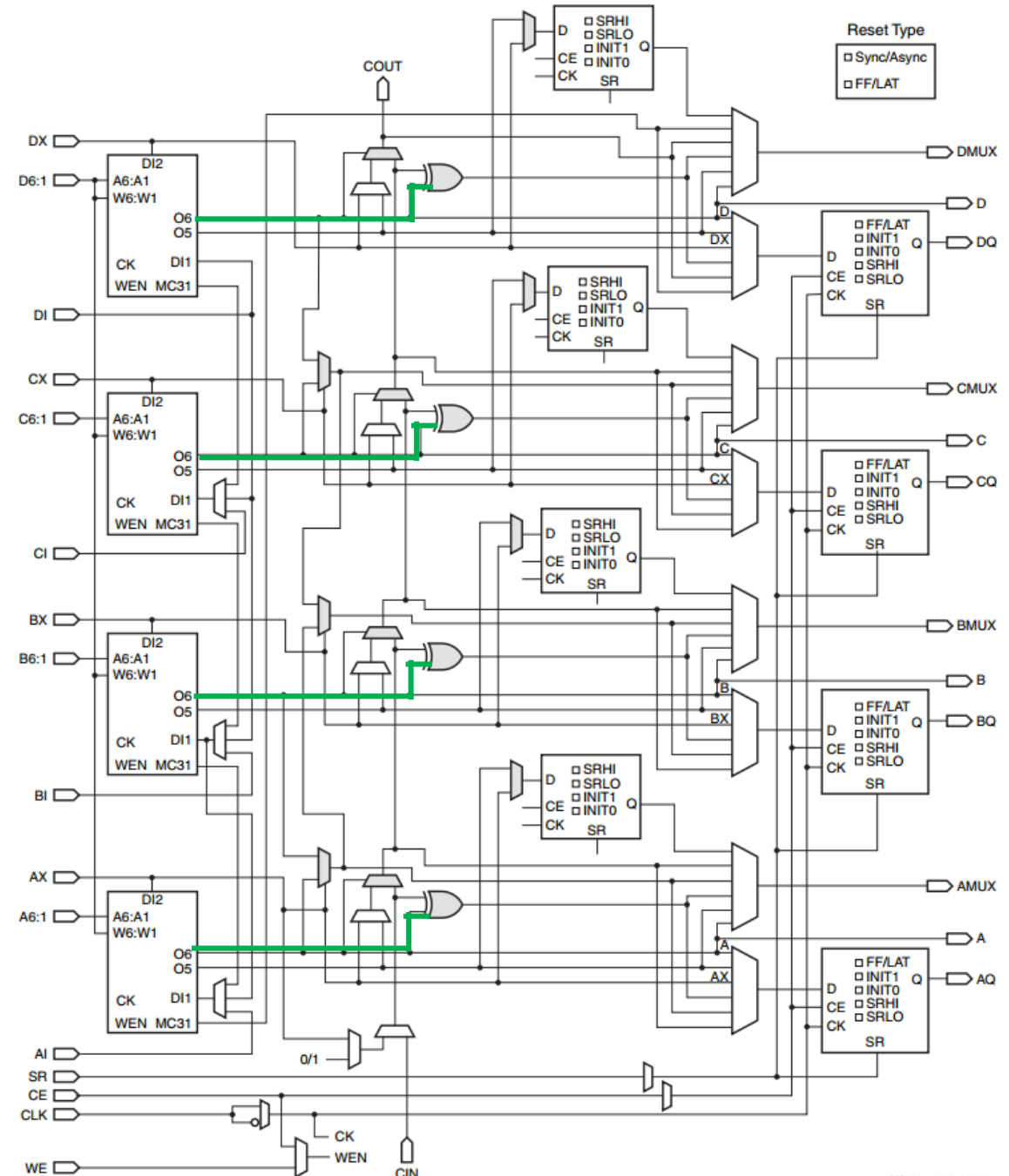- Signals from the LUT can:
 - Exit the slice (through A, B, C, D output for O6 or AMUX, BMUX, CMUX, DMUX output for O5)
 - Enter the XOR dedicated gate from an O6 output




LUT

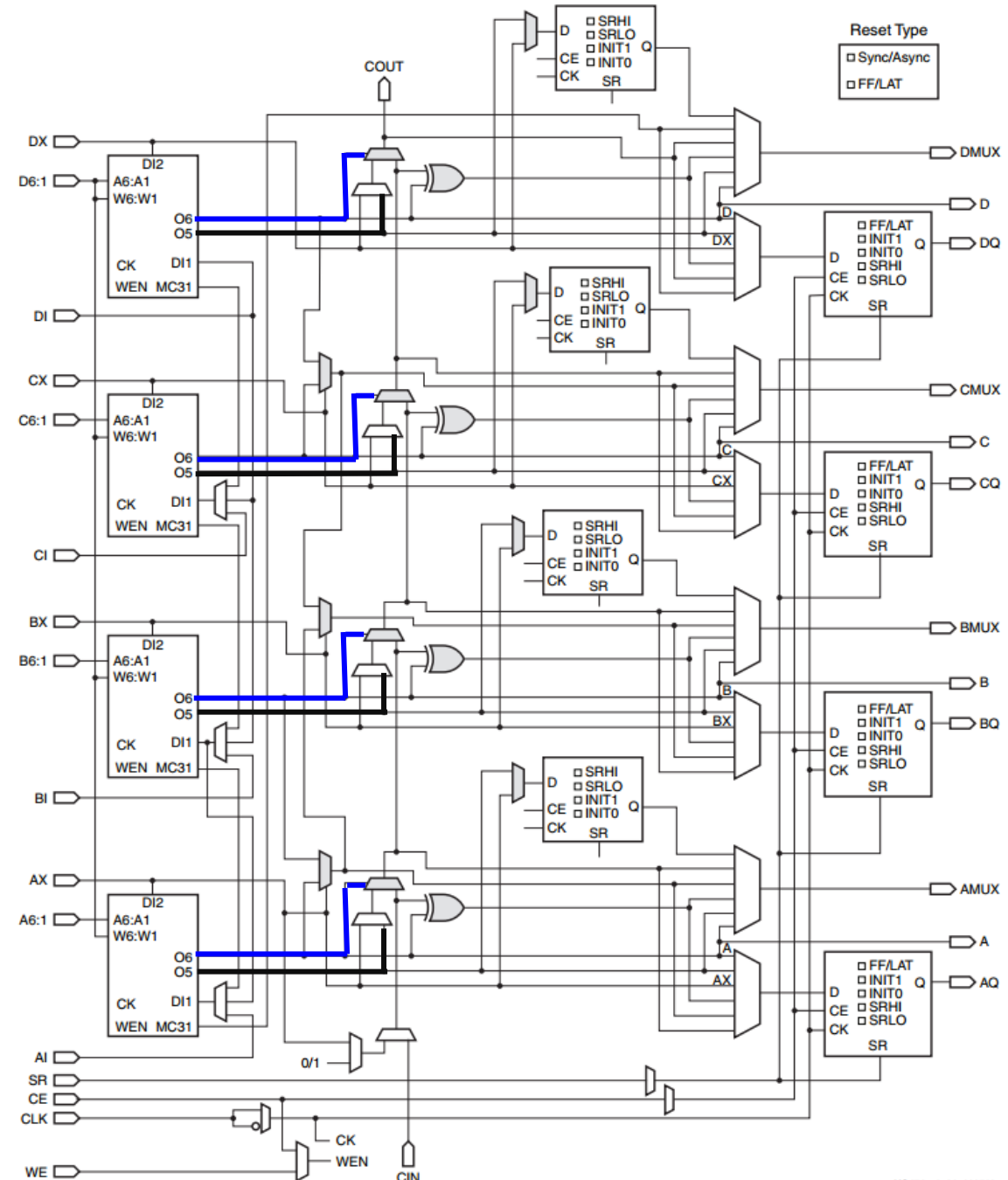- Signals from the LUT can:
 - Exit the slice (through A, B, C, D output for O6 or AMUX, BMUX, CMUX, DMUX output for O5)
 - Enter the XOR dedicated gate from an O6 output
- **Enter the carry-logic chain from an O5 output**
- Enter the select line of the carry-logic multiplexer from O6 output




LUT

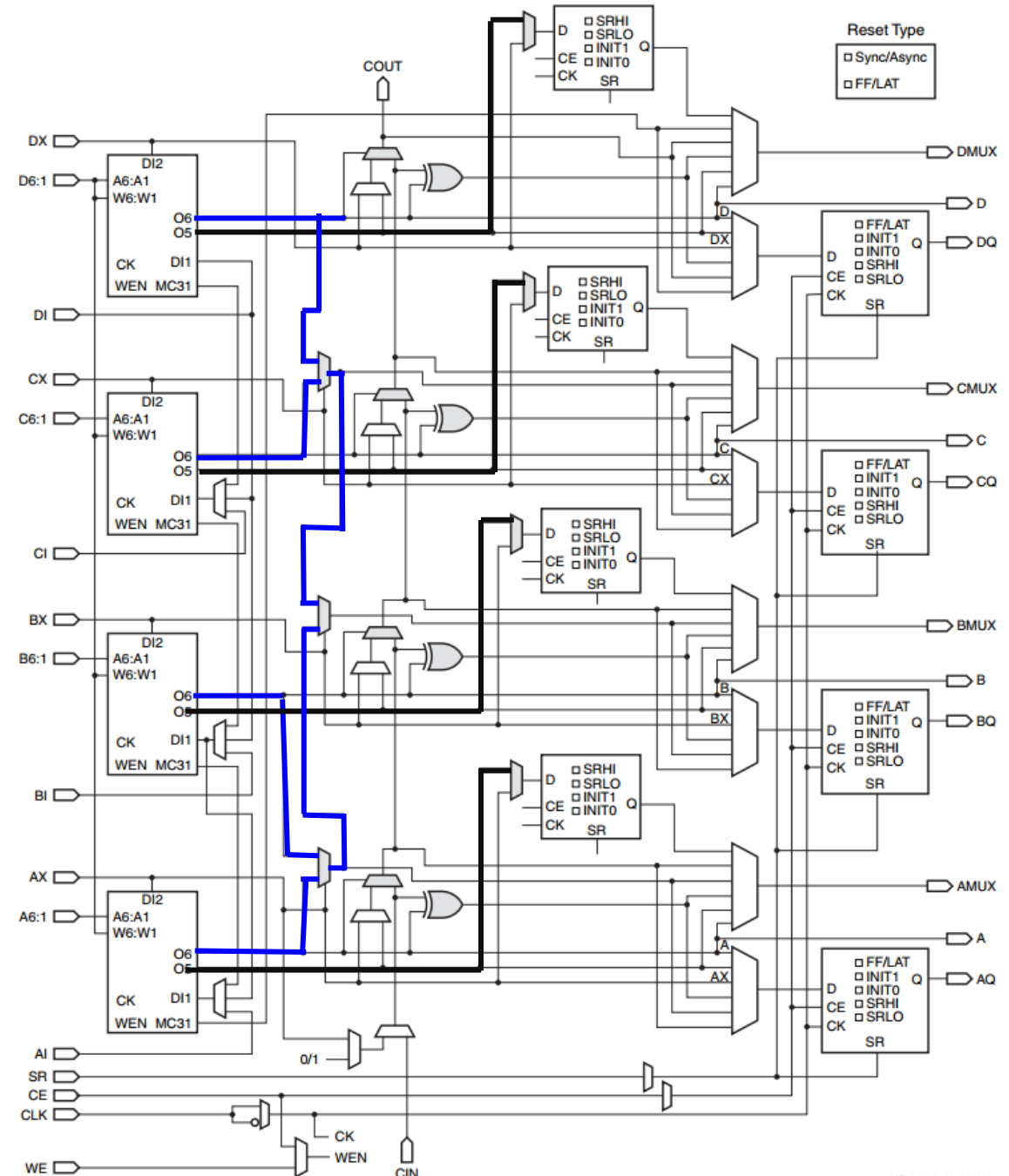- Signals from the LUT can:
- Exit the slice (through A, B, C, D output for O6 or AMUX, BMUX, CMUX, DMUX output for O5)
- Enter the XOR dedicated gate from an O6 output
- Enter the carry-logic chain from an O5 output
- Enter the select line of the carry-logic multiplexer from O6 output
- **Feed the D input of the storage element**
- Go to F7AMUX/F7BMUX wide multiplexers from O6 output




Slice Resource

 - Four six-input Look-Up Tables (LUT)
- Multiplexers
- Carry chains
- Four flip-flops/latches
- Four additional flip-flops
- Four 6-input LUTs and their eight flip-flops as well as multiplexers and arithmetic carry logic form a slice, and two slices form a CLB.





3 Input LUT

C	B	A	F1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


3 Input LUT

  

LUT

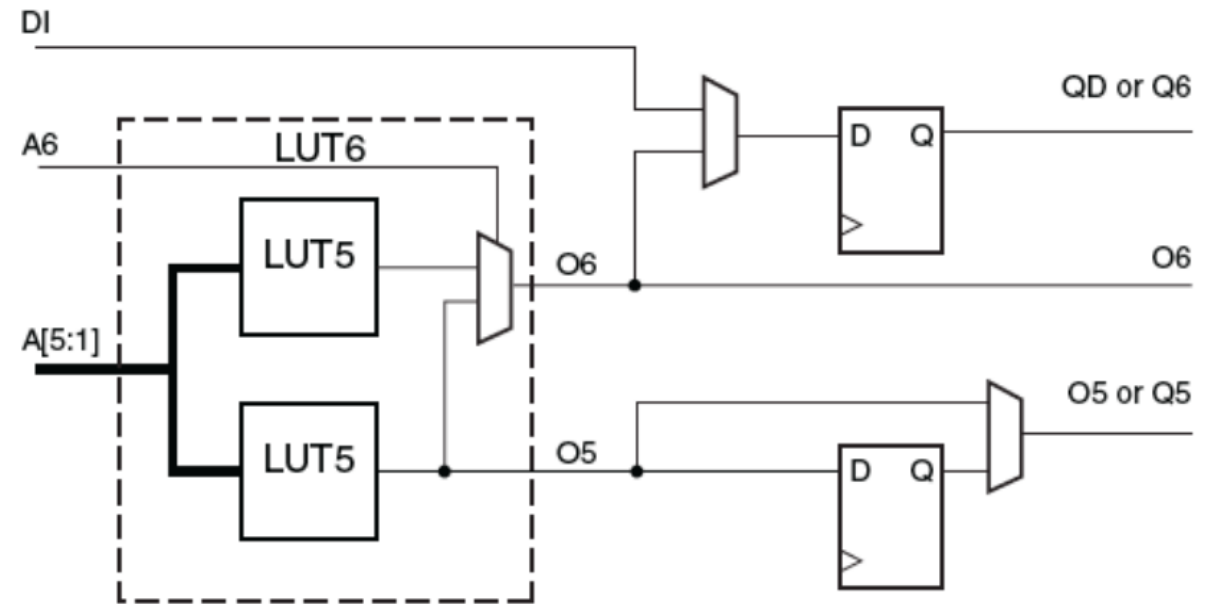
- There are six independent inputs (A inputs - A1 to A6) and two independent outputs (O5 and O6)



3-Input LUT for Logic

- Any single arbitrarily defined 3-input Boolean function
- A 3-input function uses: A1-A3 inputs and O3 output
- Two arbitrarily defined 2-input Boolean functions, as long as these two functions share common inputs
- Two 2-input or less functions use: A1–A2 inputs, A3 driven High, O2 and O3 outputs
- Two arbitrarily defined Boolean functions of 1 input

6-Input LUT for Logic

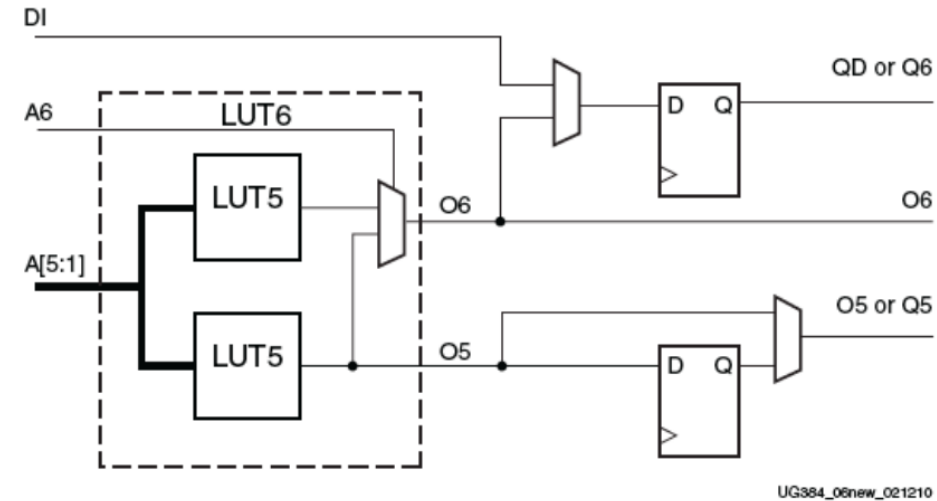

- Any arbitrarily defined six-input Boolean function
- A six-input function uses: A1-A6 inputs and O6 output
- Two arbitrarily defined five-input Boolean functions, as long as these two functions share common inputs
- Two five-input or less functions use: A1–A5 inputs, A6 driven High, O5 and O6 outputs
- Two arbitrarily defined Boolean functions of 3 and 2 inputs or less