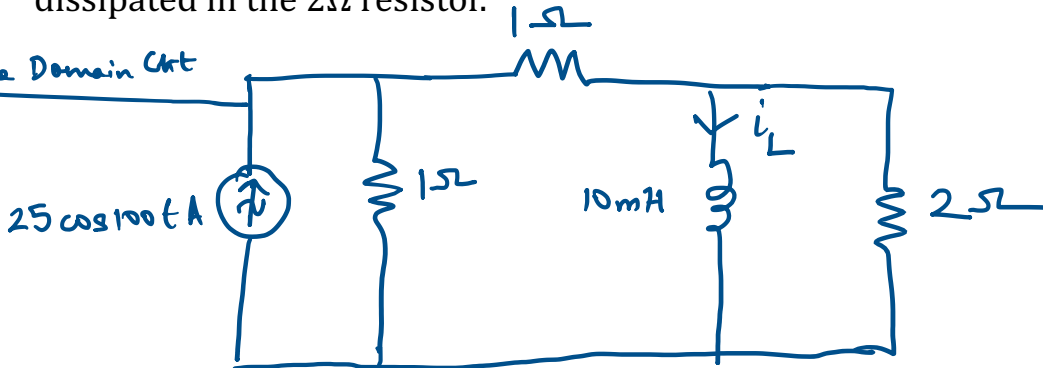


Mesh Analysis

①


- Assuming there are no longer any transients present, determine the current labeled i_L in the following circuit. Also calculate the power dissipated in the 2Ω resistor.

Time Domain Ckt



|||

Phasor/Freq Domain Ckt

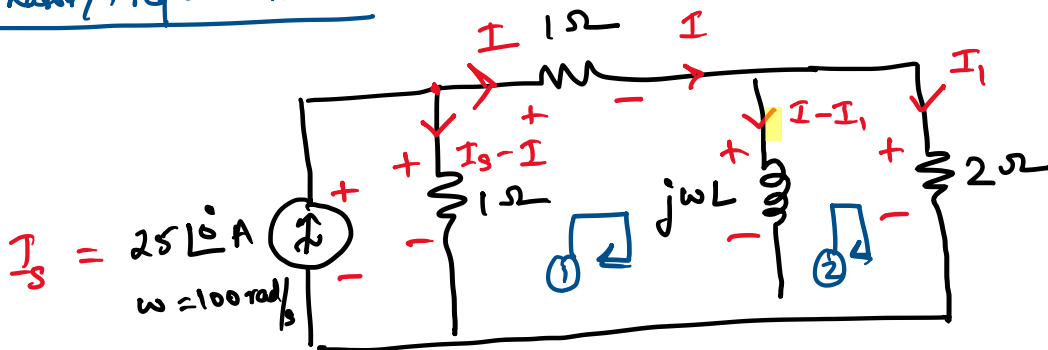

Mesh ①

$$+ (\vec{I}_s - \vec{I})(1) - \vec{I}(1) - (\vec{I} - \vec{I}_1)(j\omega L) = 0$$

$$\Rightarrow \vec{I}(-1 - 1 - j\omega L) + \vec{I}_1(+j\omega L) = -\vec{I}_s$$

$$\Rightarrow \vec{I}(2 + j\omega L) + \vec{I}_1(-j\omega L) = +\vec{I}_s \quad \text{--- (1)}$$

Mesh ②

$$+ (\vec{I} - \vec{I}_1)(j\omega L) - (\vec{I}_1)(2) = 0$$

$$\Rightarrow \vec{I}(j\omega L) + \vec{I}_1(-2 - j\omega L) = 0 \quad \text{--- (2)}$$

$$\Rightarrow \begin{bmatrix} 2+j & -j \\ j & -2-j \end{bmatrix} \begin{bmatrix} \vec{I} \\ \vec{I}_1 \end{bmatrix} = \begin{bmatrix} 25 \\ 0 \end{bmatrix}$$

$$\Rightarrow \vec{I}_1 = 4.419 \angle 45^\circ \text{ A}, \quad P_{avg} = \frac{1}{2} |\vec{I}_1|^2 R = 19.53 \text{ W}$$


Thevenin's Theorem

(2)

I Independent Sources

II Independent + Dependent Sources


III Only Dependent sources

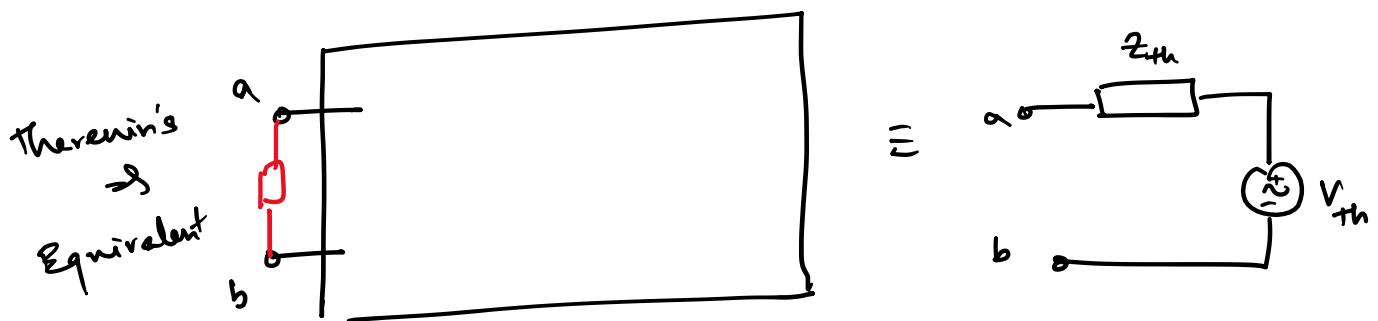


Step.1 Find V_{th} . \rightarrow Open terminals ab & find V_{oc}

③

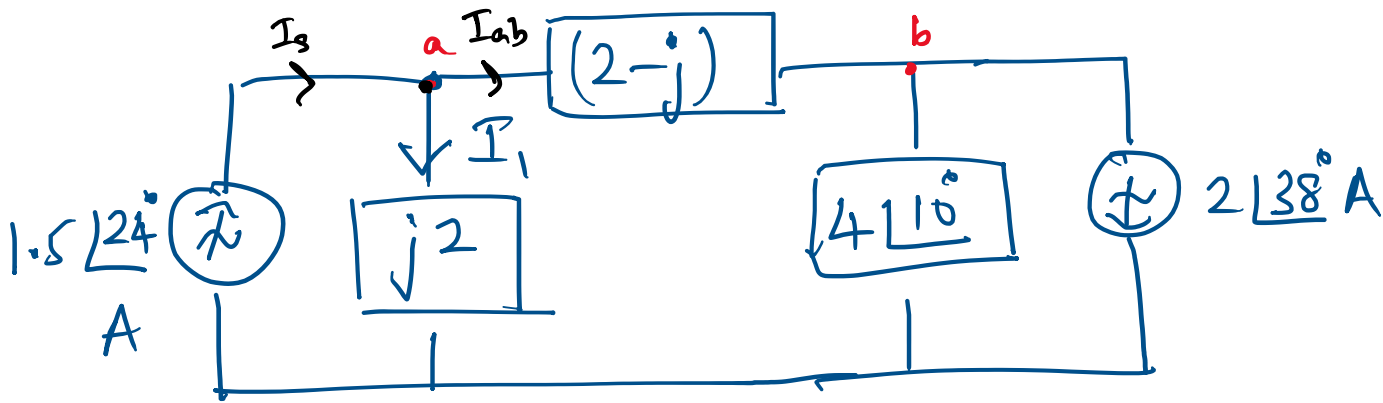- Obtain the Thevenin equivalent seen by the $(2 - j)\Omega$ impedance and employ it to determine the current I_1 .




I Find V_{th}

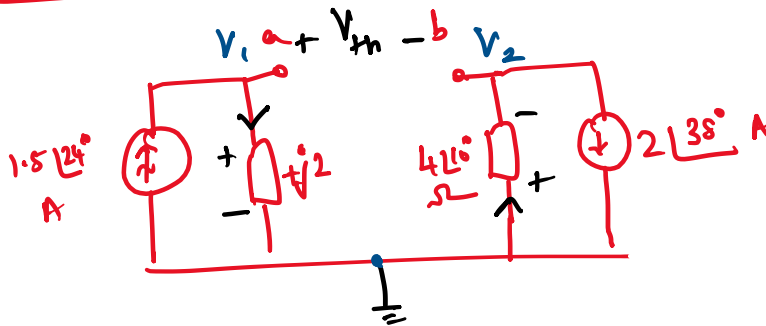

$$\frac{V_1}{j2} = 1.5 \angle 24^\circ \text{ A} \Rightarrow V_1 = j2 \times 1.5 \angle 24^\circ = 3 \angle 114^\circ \text{ V}$$

$$\frac{0 - V_2}{4 \angle 10^\circ} = 2 \angle 38^\circ \text{ A} \Rightarrow V_2 = -2 \times 4 \angle 38^\circ + 10^\circ = 8 \angle 180^\circ + 38^\circ = 8 \angle 228^\circ \text{ V}$$

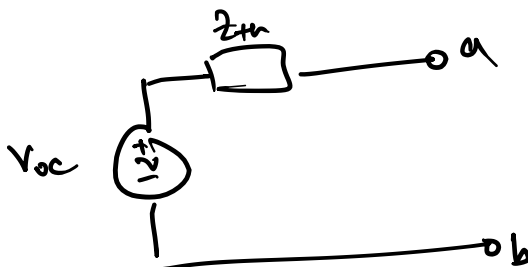
$$V_{oc} = V_1 - V_2 = 9.62 \angle 64.5^\circ \text{ V}$$



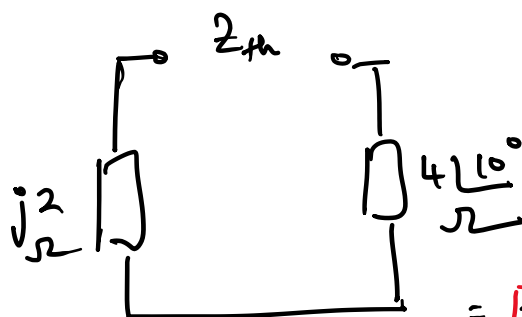(4)

II Find z_{th}


Turn off sources - $V_s \rightarrow$ short
 $I_s \rightarrow$ open



$$z_{th} = j2 + 4 \angle 10^\circ \Omega$$


$$= 1 + j2 + 4 \cos(10^\circ) + j4 \sin(10^\circ)$$

$$= \boxed{3.94 + j2.69 \Omega}$$

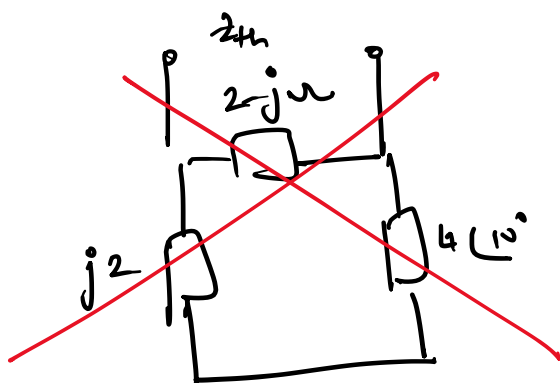

$$z_{th} = (2-j) \parallel (j2 + 4 \angle 10^\circ) \Omega$$
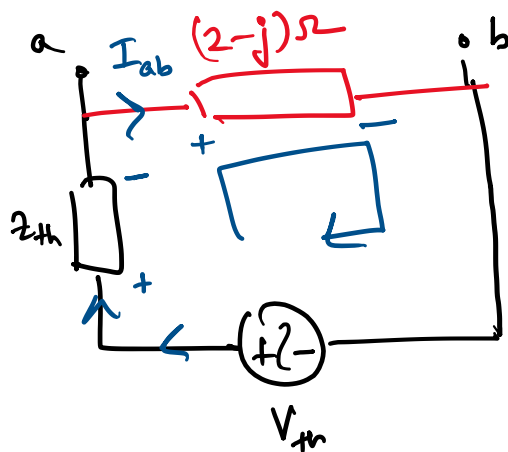
$$j2 + 4 \angle 10^\circ = 6 \angle 100^\circ \Omega$$





$$-I_{ab} z_{th} - I_{ab} (2-j) + V_{th} = 0$$

$$I_{ab} = \frac{V_{th}}{z_{th} + (2-j)}$$

$$I_1 = I_s - I_{ab} = 0.65 \angle -58.6^\circ \text{ A}$$

Theremin's Equivalent

⑤

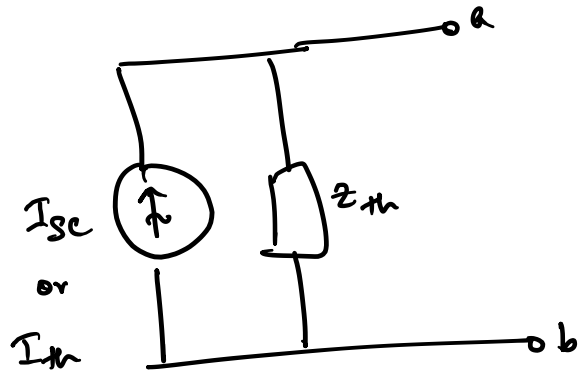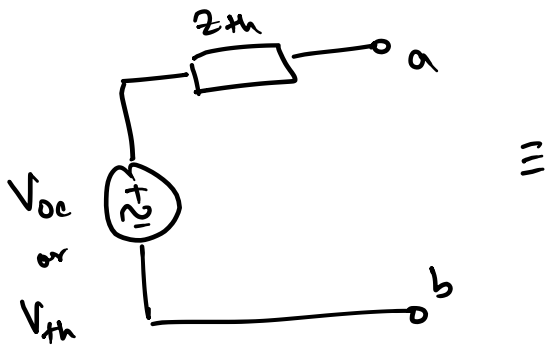

Cases

Independent Sources

V_{oc}

✓

I_{sc}

✓

Z_{th}

✓


Dummy source

Independent + Dependent source

✓


✓

only Dependent source

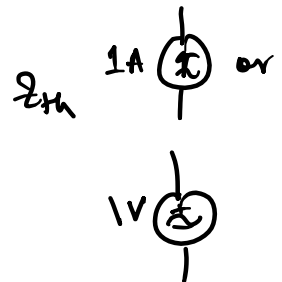

6

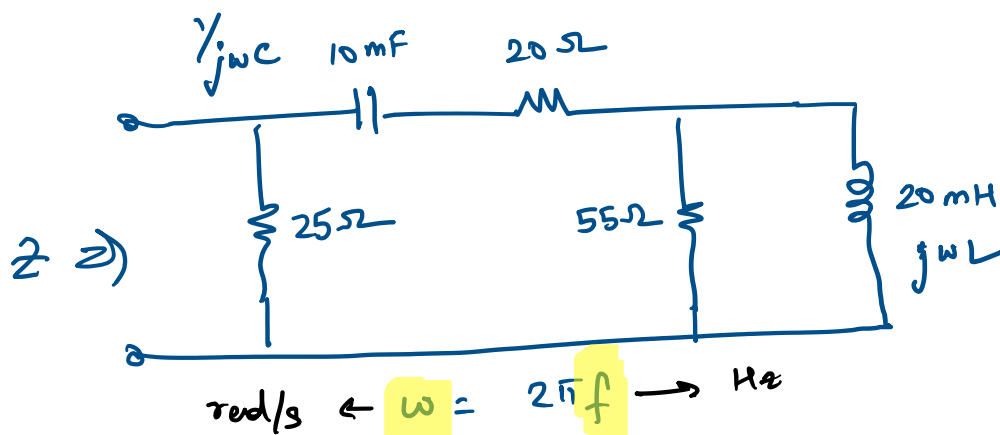- Consider the network depicted in the figure, and determine the equivalent impedance seen looking into the open terminals if the angular frequency is 1 rad/s.



pico	-	p	-	10^{-12}		Peta (?)	
nano	-	n	-	10^{-9}		Giga - G	10^9
micro	-	μ	-	10^{-6}		mega - M	10^6
milli	-	m	-	10^{-3}		kilo - k	10^3

$$Z = \left[(j\omega L \parallel 55) + \left(20 + \frac{1}{j\omega C} \right) \right] \parallel 25$$

$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{Z_2 + Z_1}{Z_1 Z_2}$$

$$\Rightarrow Z_p = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z = 11.13 + j0.16 \Omega$$

Theremins

