
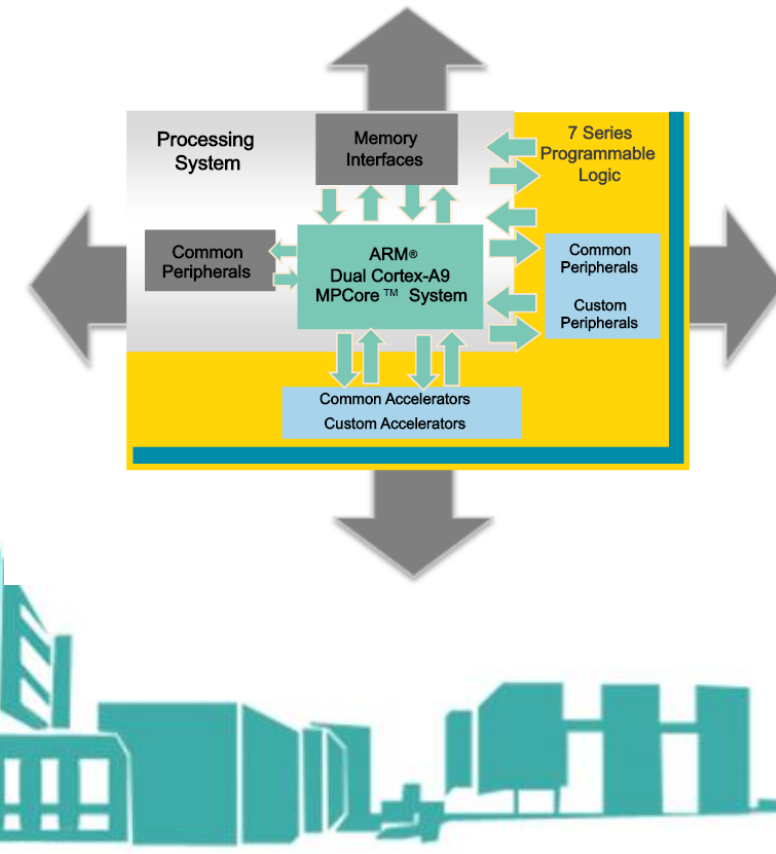


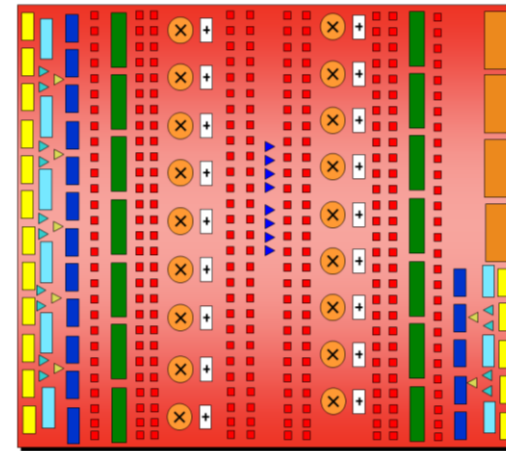

ECE 270: Embedded Logic Design





Pipelining

Why Pipelining?



	Cycle														
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Fetch	A					B					C				
Decode		A					B					C			
Execute			A					B					C		
Memory				A					B					C	
Write					A					B					C

	Cycle						
	1	2	3	4	5	6	7
Fetch	A	B	C				
Decode		A	B	C			
Execute			A	B	C		
Memory				A	B	C	
Write					A	B	C

Pipelining Combinational Circuits

  



Pipelining

 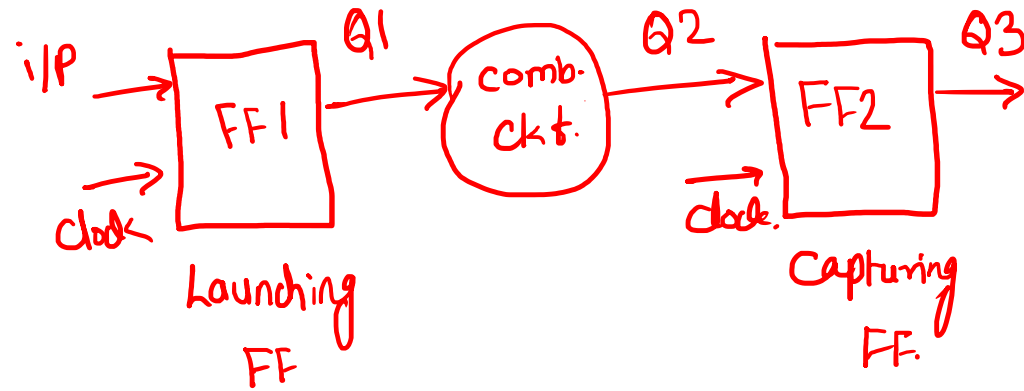



→ Data launched by launching FF at t_k^{th} clock cycle & corresponding output is captured by capturing FF at t_{k+1}^{th} clock cycle.

— clock period should be sufficiently large so that correct data is captured.
($t_2 - t_1$)


FF Timing Constraints

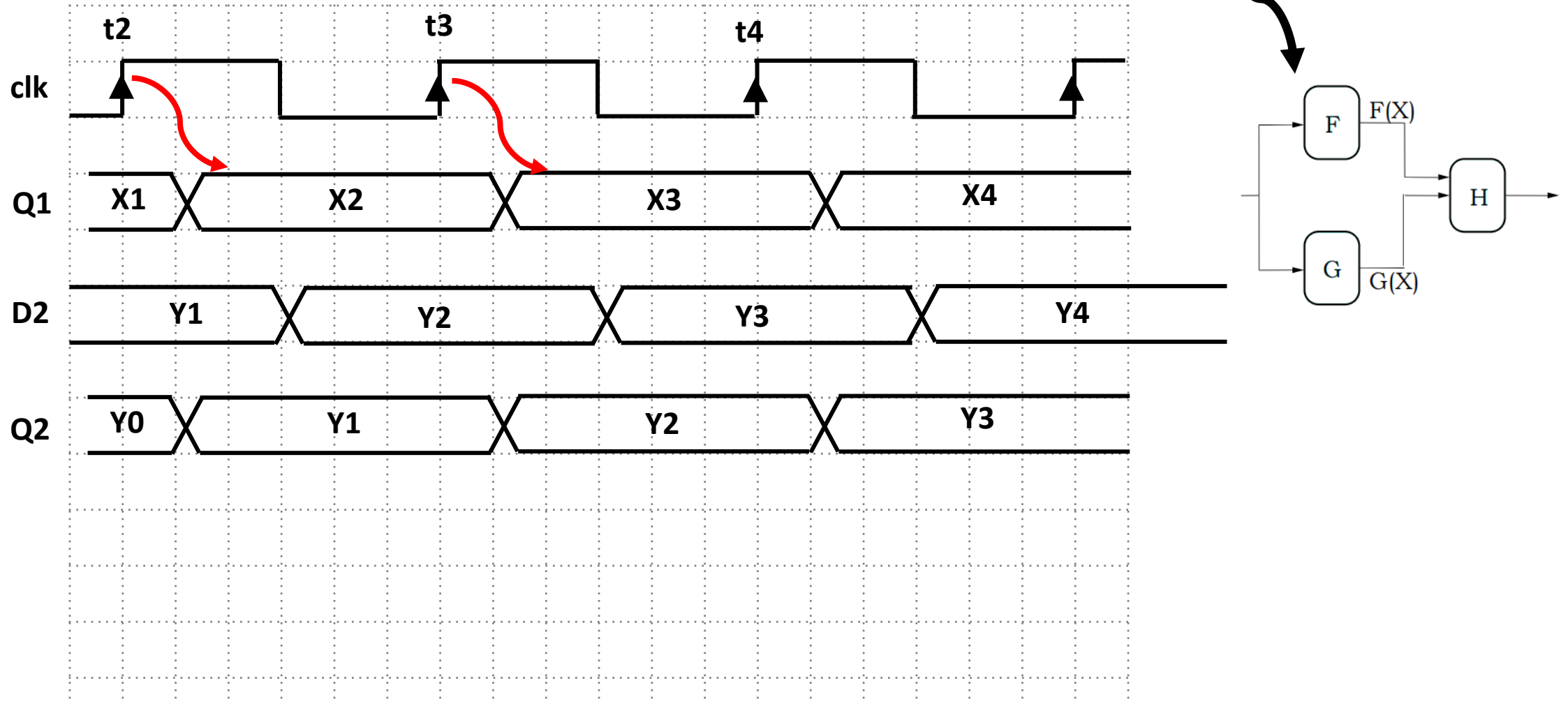 

FF Timing Constraints

  


FF Timing Constraints

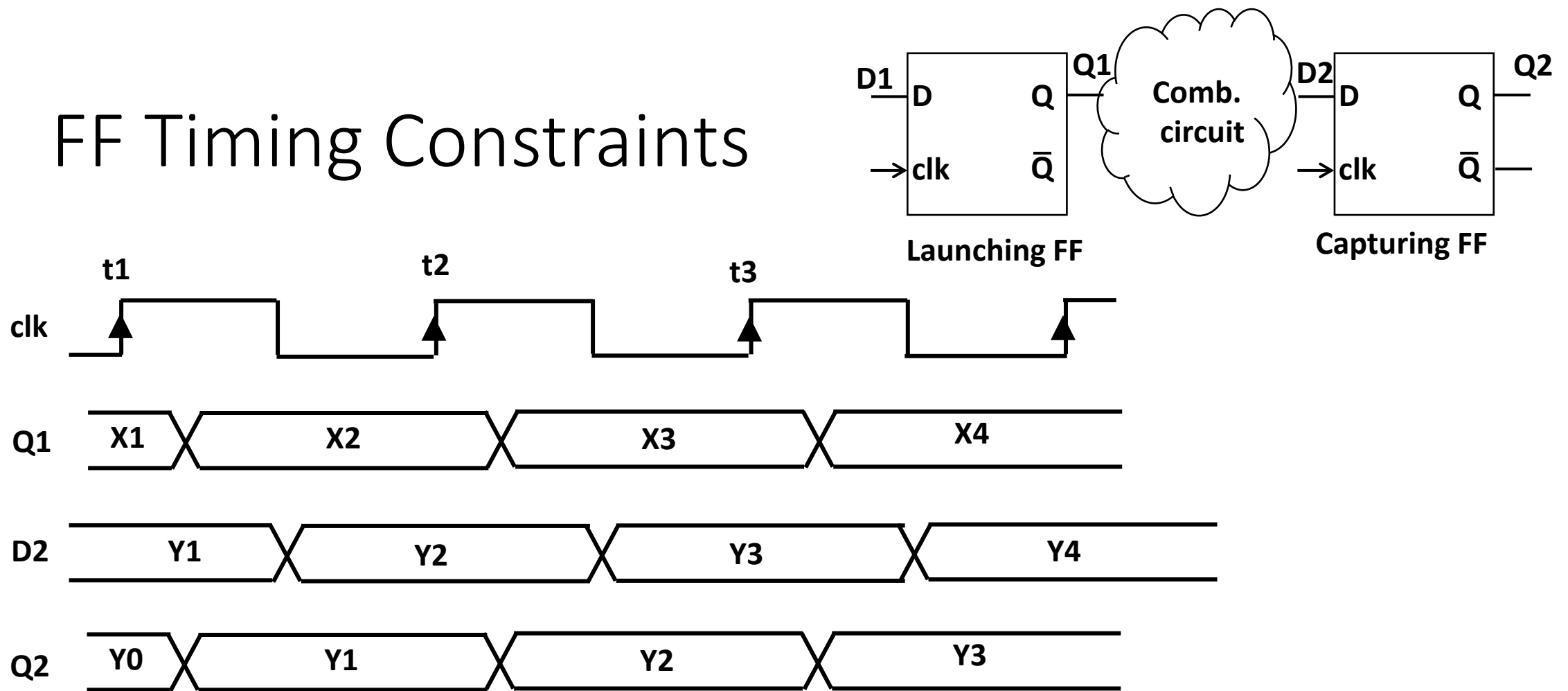

$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$


- This equation ensures that if the output of launching FF changes, this will make it to capturing FF before its set-up time.

FF Timing Constraints

 


$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$

 
- This is very important equation since it puts **limit on the minimum value of clock period** and hence, **maximum value of clock frequency**.
- Limit on maximum value of clock frequency means **limit on the speed at which the circuit can operates**.



- How to increase the clock frequency or reduce the clock period?
 
$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$




 

$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$

- Consider a travel from A-> C where there is vehicle changeover at B (A->B->C)
- The time from A->B is **30 minutes** and from B->C is **60 minutes**.
- Since there is a separate vehicle is used from each travel, we have two options:
 - 1) **Trip duration is 90 minutes** where **only one vehicle** is active at a time. For N trips, total time required is **90N minutes**.
 - 2) **Two vehicles are active simultaneously**. Here, for N trips, the time required is **60N+30 minutes**. The second term is very small for large N and hence, ignored.


Pipelining

 


$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$

- Which approach is better???
- Lets discuss two more definitions:
- **Latency:** Delay when an input is established until the output associated with that input becomes valid
- Approach 1: 90 mins and Approach 2: 120 mins
- **Throughput:** The rate at which the new output is produced
- Approach 1: 1/90 mins and Approach 2: 1/60 mins
- Approach must be selected based on the application requirements.


Pipelining

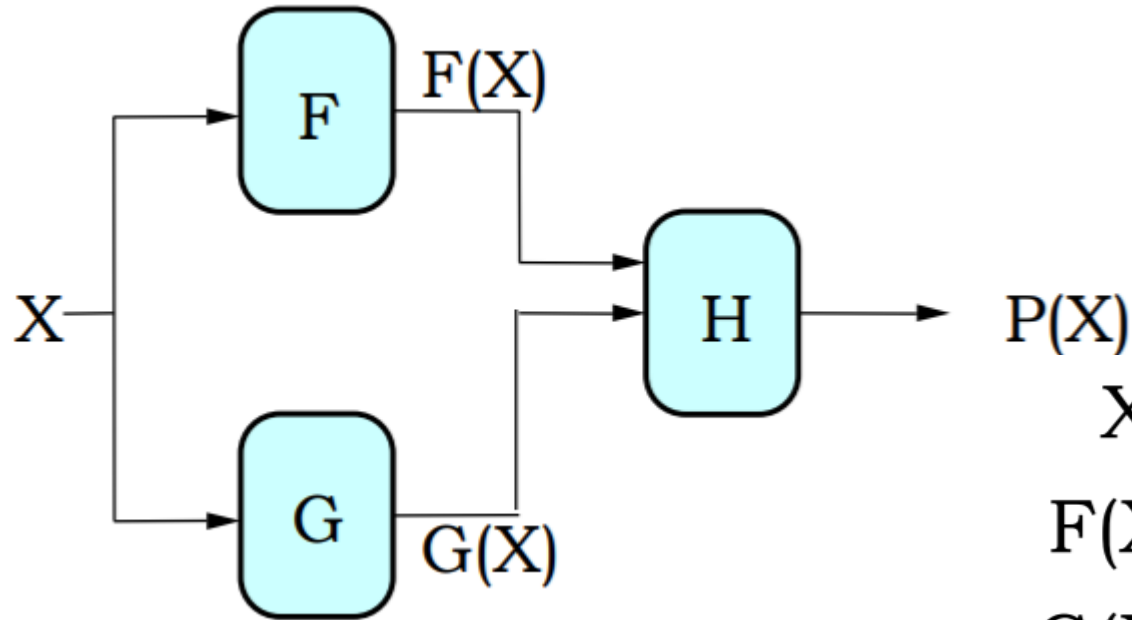

 - How to make F and G work concurrently with H ?




 
$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$




F & G are "idle", just holding their outputs stable while H performs its computation

Pipelining

  
 
$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$





F & G are "idle", just holding their outputs stable while H performs its computation

- We need something which is good at holding or remembering the values of F and G outputs when H needs it as well it should free up F and G to do other computations.

Pipelining

  
- Now, **F and G** can be working on input X_{i+1} while **H** is performing its computations on X_i .
- This is **2-stage pipeline** i.e. if we have valid input X during clock cycle j , $P(X)$ is valid during clock cycle $j+2$.
- Assuming F , G and H have propagation delay of 15, 20 and 25 ns, and ideal registers i.e. FFs, then



	<u>latency</u>	<u>throughput</u>
unpipelined	45	1/45
2-stage pipeline	50	1/25

Pipelining

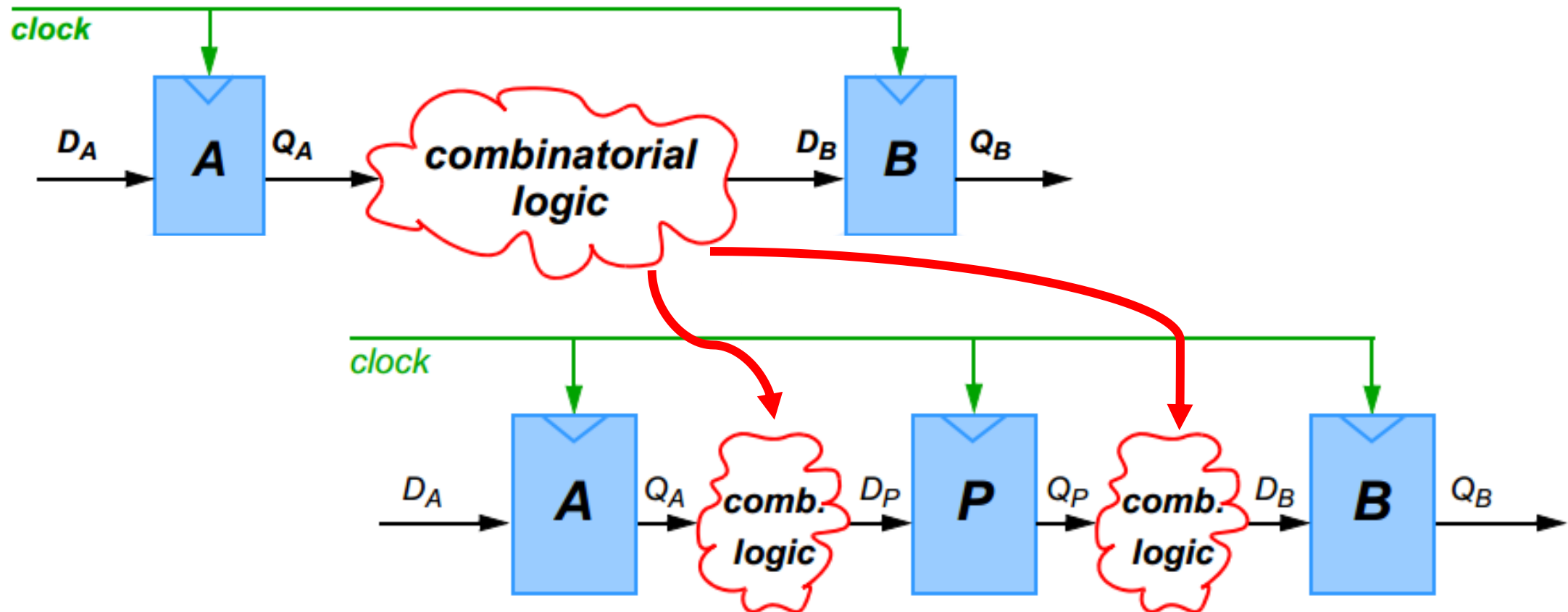- ❖ Pipelining: Breaking of comb. Circuit by inserting additional registers



Pipelining (Summary)

- A **well-formed K-Stage Pipeline** (“K-pipeline”) circuit have exactly K registers **on every path** from an input to an output.
- A **COMBINATIONAL CIRCUIT** is thus a **0-stage pipeline**.
- Every pipeline stage, hence every K-Stage pipeline, has a register on its OUTPUT (not on its input).
- The CLOCK common to all registers must have a period sufficient to cover propagation delay of combinational circuit, clock-to-output delay of launching FF, setup time of capturing FF and clock skew.
- The **LATENCY** of a K-stage pipeline is K times the period of the system’s clock. The **THROUGHPUT** of a K-stage pipeline is the frequency of the clock.

$$T_{clk} \geq \cancel{T_{clk-out}} + T_{pmax} + \cancel{T_{setup}} + \cancel{T_{skew}}$$