


## Tutorial 4

**Q.1.**

Compute  $Q_0$  and  $\zeta$  for a simple parallel  $RLC$  network if (a)  $R = 1 \text{ k}\Omega$ ,  $C = 10 \text{ mF}$ , and  $L = 1 \text{ H}$ ; (b)  $R = 1 \text{ }\Omega$ ,  $C = 10 \text{ mF}$ , and  $L = 1 \text{ H}$ ; (c)  $R = 1 \text{ k}\Omega$ ,  $C = 1 \text{ F}$ , and  $L = 1 \text{ H}$ ; (d)  $R = 1 \text{ }\Omega$ ,  $C = 1 \text{ F}$ , and  $L = 1 \text{ H}$ .

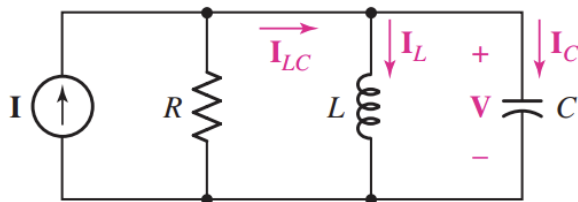**Q.2.**

The circuit of Fig. 16.1 is built using component values  $L = 1 \text{ mH}$  and  $C = 100 \text{ }\mu\text{F}$ . If  $Q_0 = 15$ , determine the bandwidth and estimate the magnitude and angle of the input impedance for operation at (a)  $3162 \text{ rad/s}$ ; (b)  $3000 \text{ rad/s}$ ; (c)  $3200 \text{ rad/s}$ ; (d)  $2000 \text{ rad/s}$ . (e) Verify your estimates using an exact expression for  $\mathbf{Y}(j\omega)$ .




■ **FIGURE 16.1**

**Q.3.**

A series  $RLC$  circuit is constructed employing component values  $R = 100 \text{ }\Omega$  and  $L = 1.5 \text{ mH}$  along with a sinusoidal voltage source  $v_s$ . If  $Q_0 = 7$ , determine (a) the magnitude of the impedance at  $500 \text{ Mrad/s}$ ; (b) the current which flows in response to a voltage  $v_s = 2.5 \cos(425 \times 10^6 t) \text{ V}$ .

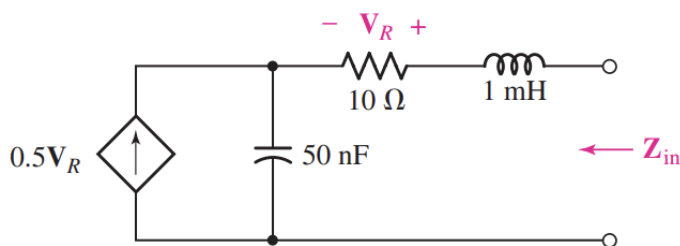**Q.4.**


After deriving  $\mathbf{Z}_{in}(s)$  in Fig. 16.54, find (a)  $\omega_0$ ; (b)  $Q_0$ .



■ **FIGURE 16.54**

**Q.5.**

For the network represented in Fig. 16.55, determine the resonant frequency and the corresponding value of  $|Z_{in}|$ .

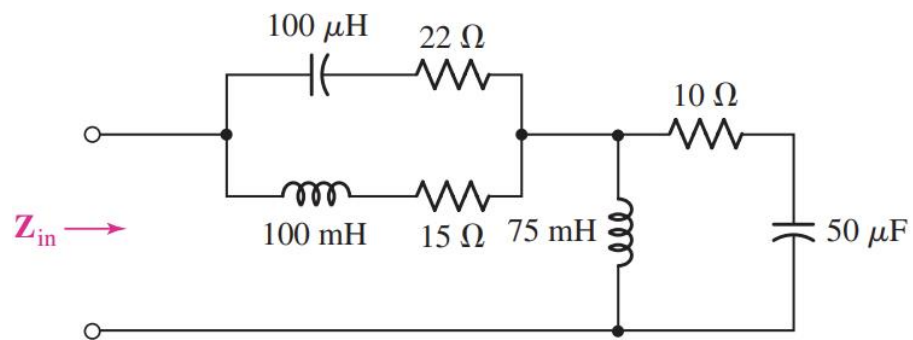

■ **FIGURE 16.55**