


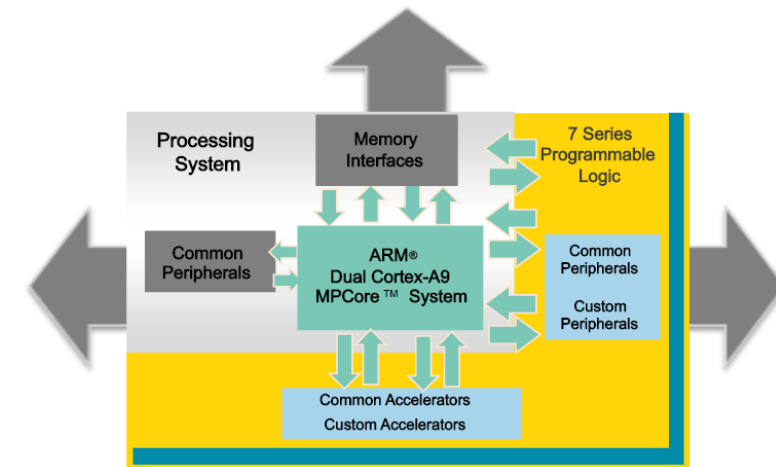


 

ECE 270: Embedded Logic Design

 


Block RAM

 


Block RAM

 - All members of the **7-series families** have **dual-port 36 Kb block RAM** with port widths of **up to 72**
- Fully **synchronous** operation
- Multiple configuration options: **True dual port, simple dual port, single port**




Block RAM

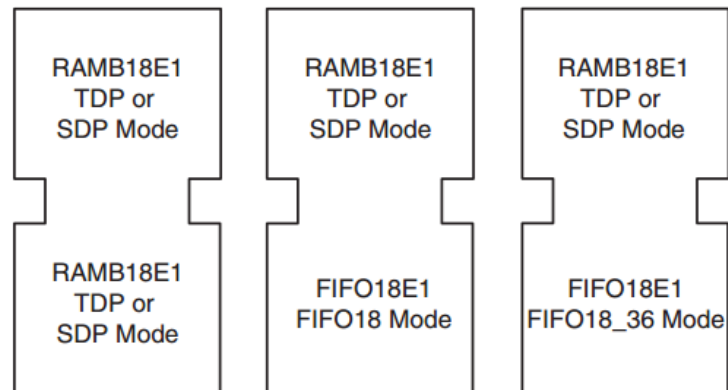- Each BRAM can be segmented as:
 - 36 Kb BRAM
 - 36 Kb FIFO
 - Independent 18 Kb BRAMs
 - 18 Kb FIFO and 18 Kb BRAM




UG473_c2_13_052610

Legal Block RAM and FIFO Combinations

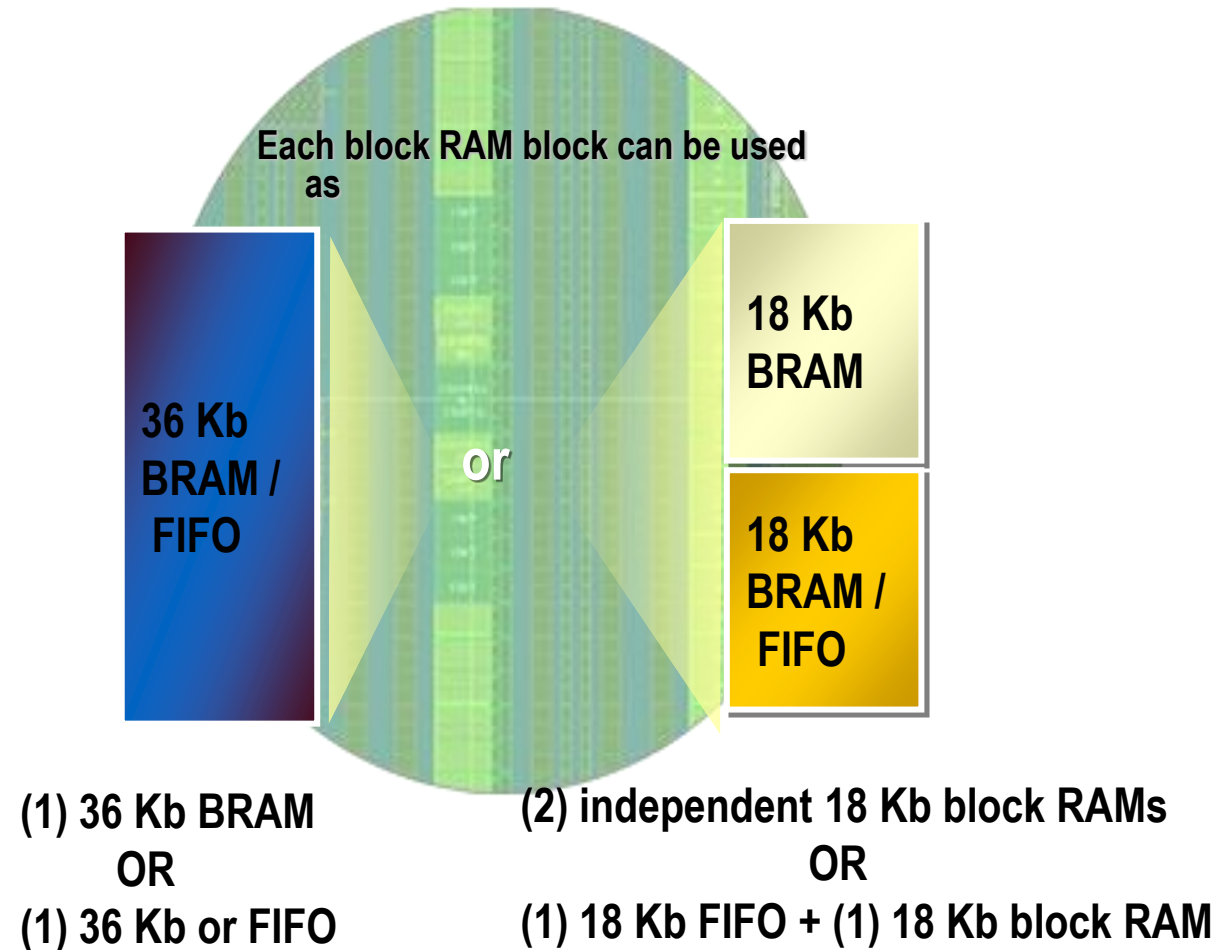

Block RAM

 
- Each BRAM can be segmented as:
 - 36 Kb BRAM
 - 36 Kb FIFO
 - Independent 18 Kb BRAMs
 - 18 Kb FIFO and 18 Kb BRAM
- Dedicated hardware to convert BRAM in to FIFO
- Integrated cascade logic to build larger memories
- Integrated error correction logic to fix bit errors*



Dual Port Block RAM


Dual-Port Block RAM

Port Function	Description
DI[A B]	Data input bus.
DIP[A B] ⁽¹⁾	Data input parity bus. Can be used for additional data inputs.
ADDR[A B]	Address bus.
WE[A B]	Byte-wide write enable.
EN[A B]	When inactive no data is written to the block RAM and the output bus remains in its previous state.
RSTREG[A B]	Synchronous Set/Reset the output registers (DO_REG = 1). The RSTREG_PRIORITY attribute determines the priority over REGCE.
RSTRAM[A B]	Synchronous Set/Reset the output data latches.
CLK[A B]	Clock input.
DO[A B]	Data output bus.
DOP[A B] ⁽¹⁾	Data output parity bus. Can be used for additional data outputs.
REGCE[A B]	Output Register clock enable.
CASCADEIN[A B]	Cascade input for 64K x 1 mode.
CASCADEOUT[A B]	Cascade output for 64K x 1 mode.

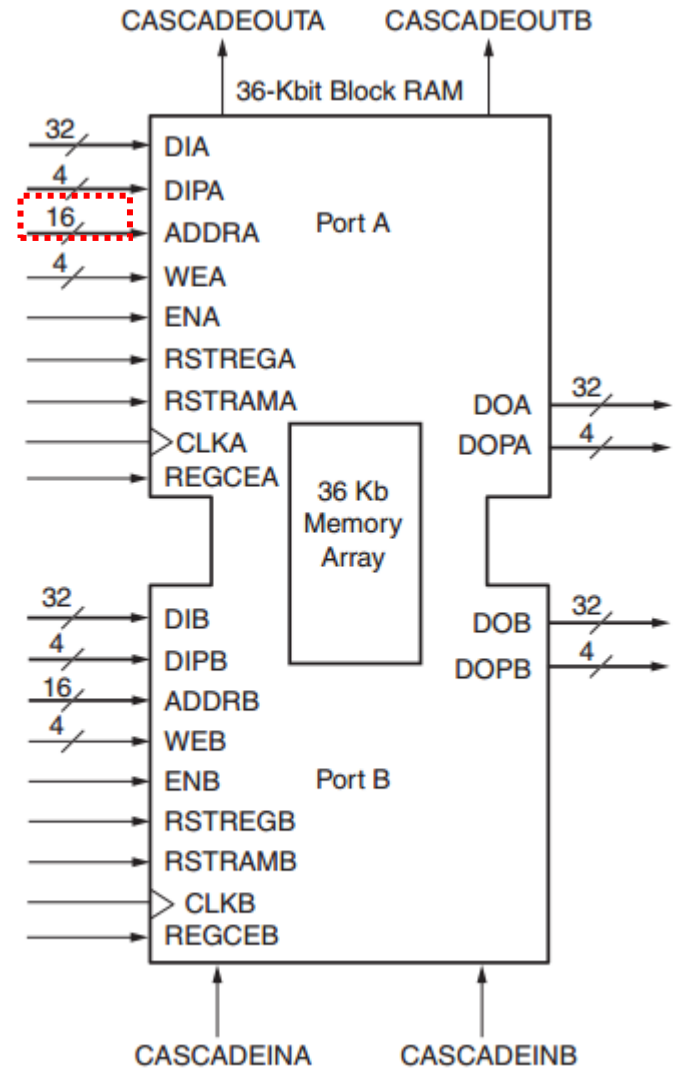

Dual-Port Block RAM

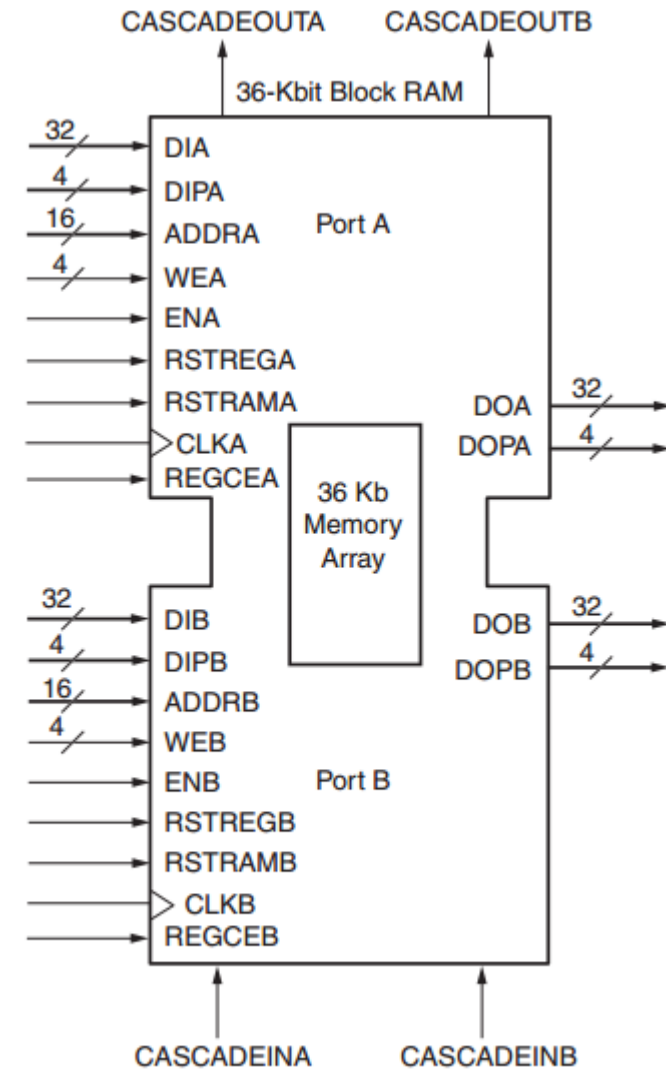- **Two separate read/write ports**
 - Each port has **separate clock, address, data in, data out, write enable...**
 - Clocks can be **asynchronous** to each other
 - The two ports can have **different widths**
 - The two ports can have **different write modes**
- Each block RAM can be divided into two completely independent 18 Kb block RAMs



Dual-Port Block RAM


Configurations
32K x 1
16K x 2
8K x 4
4K x 8(or 9)
2K x 16(or 18)
1K x 32(or 36)

Primitive	Port A Width	Port B Width
RAMB16_S1_S1	1	1
RAMB16_S1_S2		2
RAMB16_S1_S4		4
RAMB16_S1_S9		(8+1)
RAMB16_S1_S18		(16+2)
RAMB16_S1_S36		(32+4)
RAMB16_S2_S2	2	2
RAMB16_S2_S4		4
RAMB16_S2_S9		(8+1)
RAMB16_S2_S18		(16+2)
RAMB16_S2_S36		(32+4)
RAMB16_S4_S4	4	4
RAMB16_S4_S9		(8+1)
RAMB16_S4_S18		(16+2)
RAMB16_S4_S36		(32+4)
RAMB16_S9_S9	(8+1)	(8+1)
RAMB16_S9_S18		(16+2)
RAMB16_S9_S36		(32+4)
RAMB16_S18_S18	(16+2)	(16+2)
RAMB16_S18_S36		(32+4)
RAMB16_S36_S36	(32+4)	(32+4)


Block RAM Cascading

- Built-in cascade logic for 64Kx1
 - Cascade *two* vertically adjacent 32Kx1 block RAMs without using external CLB logic or compromising performance

Block RAM Cascading

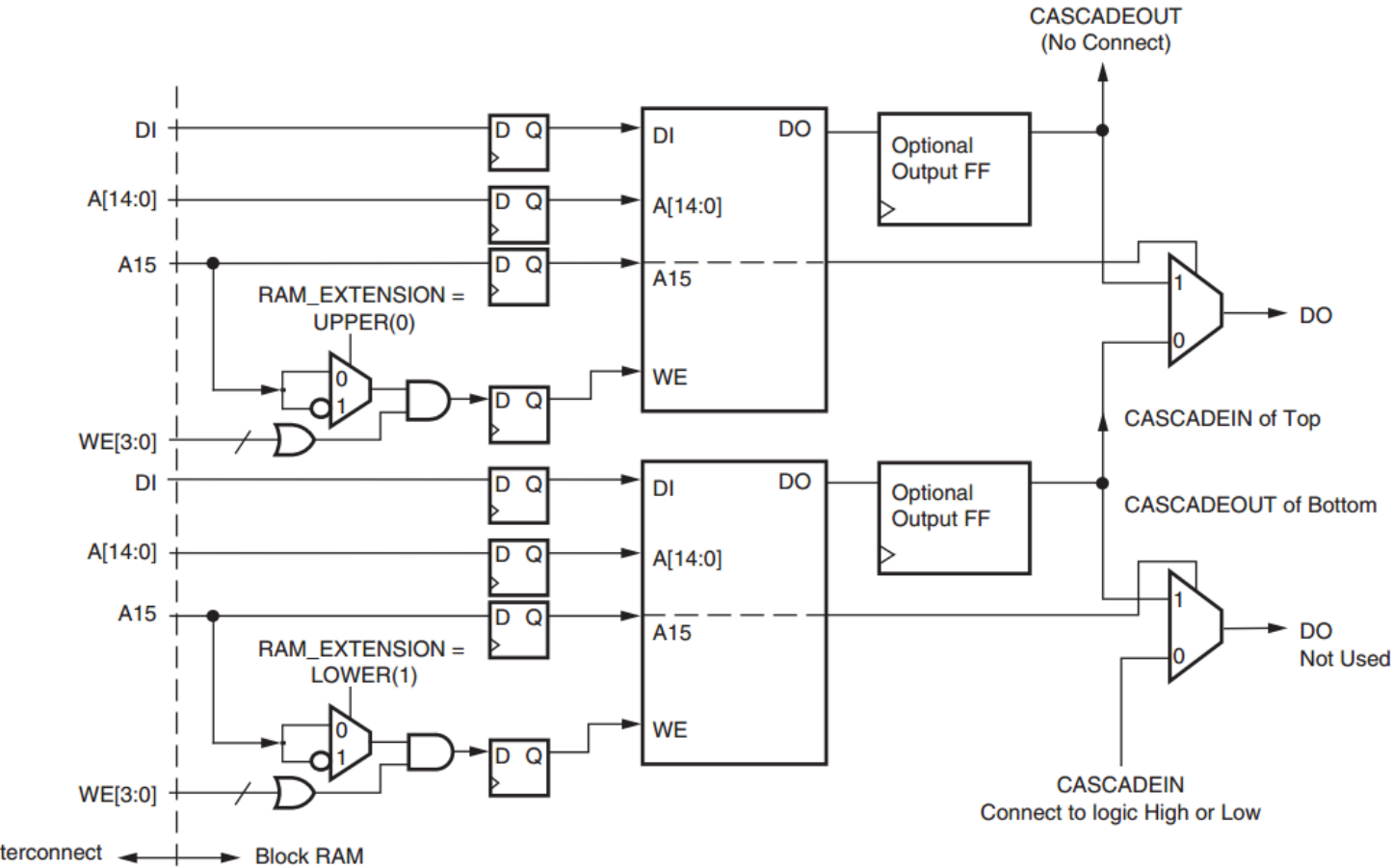


UG473_c1_07_040411

 

 Example: Cascade 8 block RAMs to build 256-Kb memory

Block RAM Cascading

- Built-in cascade logic for 64Kx1
 - Cascade *two* vertically adjacent 32Kx1 block RAMs without using external CLB logic or compromising performance
 - Saves resources and improves speed of larger memories
- Cascade option for larger arrays
 - 128Kb, 256Kb, 512Kb, 1 Mb, ...
 - Using external CLB logic for depth expansion
 - Not quite as fast as cascaded block RAMs
 - Width expansion uses parallel block RAMs



Example: Cascade 8 block RAMs to build 256-Kb memory

Verilog Codes for Memory

- Dual-Port RAM with Asynchronous Read (Distributed RAM)

```
module rams_dist (clk, we, a, dpra, di, spo, dpo);
```

```
input clk;
```

```
input we;
```

```
input [5:0] a;
```

```
input [5:0] dpra;
```

```
input [15:0] di;
```

```
output [15:0] spo;
```

```
output [15:0] dpo;
```

```
reg [15:0] ram [63:0];
```

```
always @(posedge clk)
```

```
begin
```

```
if (we)
```

```
    ram[a] <= di;
```

```
end
```

```
assign spo = ram[a];
```

```
assign dpo = ram[dpra];
```

```
endmodule
```


128x2 Dual Port LUT

reg[1:0] LUT[127:0];